
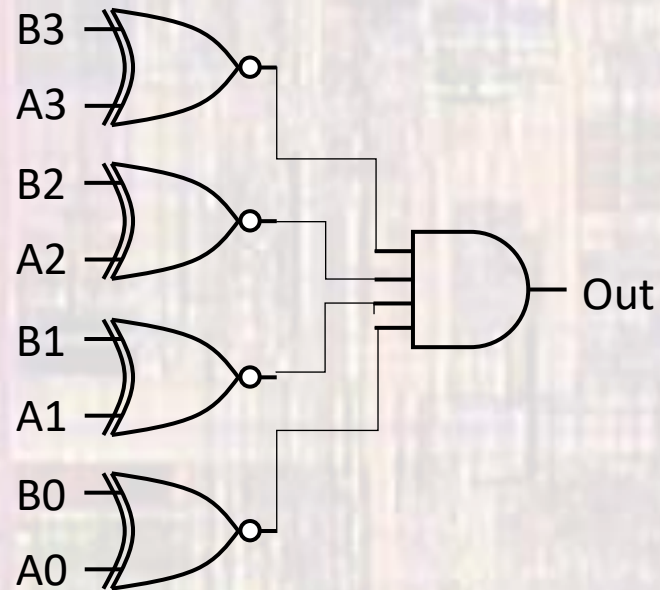


Comparators

Last updated 10/31/24

Comparators

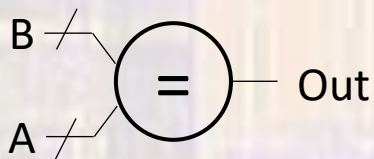- Equality Comparator
 - All bits match between 2 inputs



Comparators

- Magnitude Comparator
 - Unsigned numbers
 - 1 bit comparison

A	B	A < B	A = B	A > B
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

$$A < B = \overline{A} B$$

$$A = B = A \odot B$$

$$A > B = A \overline{B}$$

Comparators

- Magnitude Comparator
 - Unsigned numbers
 - 2 bit comparison

$$A < B = (A1 < B1) \text{ or } (A1 = B1 \text{ and } A0 < B0)$$

$$A = B = (A1 = B1) \text{ and } (A0 = B0)$$

$$A > B = (A1 > B1) \text{ or } (A1 = B1 \text{ and } A0 > B0)$$

- Expanding and putting into SOP form



$$A < B = \overline{A}1B1 + \overline{A}0B1B0 + \overline{A}1\overline{A}0\overline{B}0$$

$$A = B = (A1 \odot B1)(A0 \odot B0)$$

$$A > B = A1\overline{B}1 + A0\overline{B}1\overline{B}0 + A1A0\overline{B}0$$

Comparators

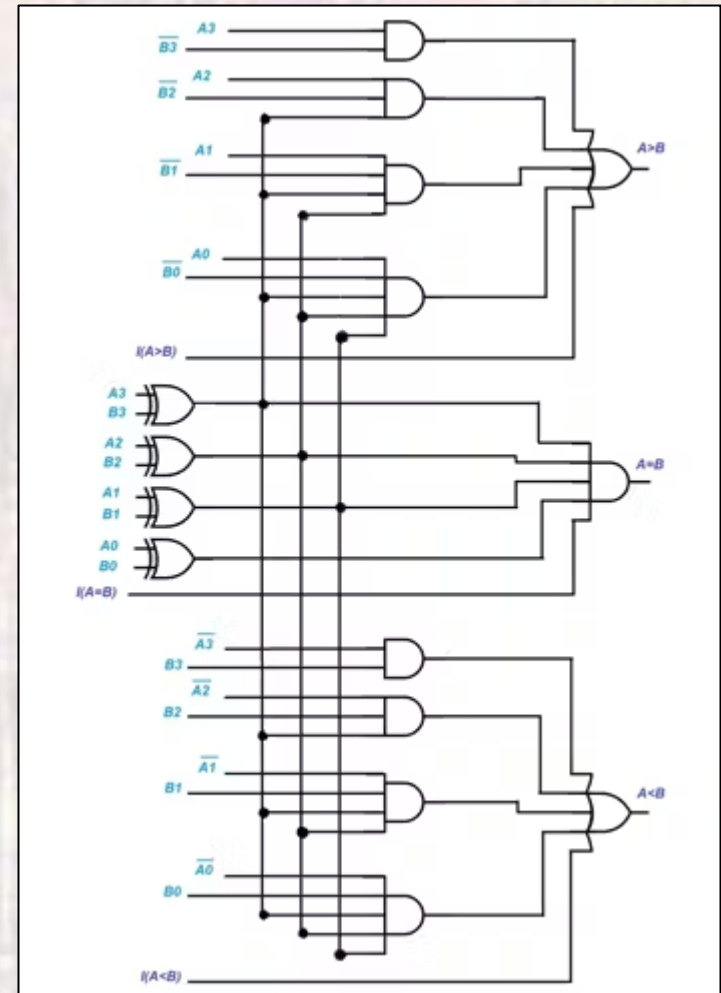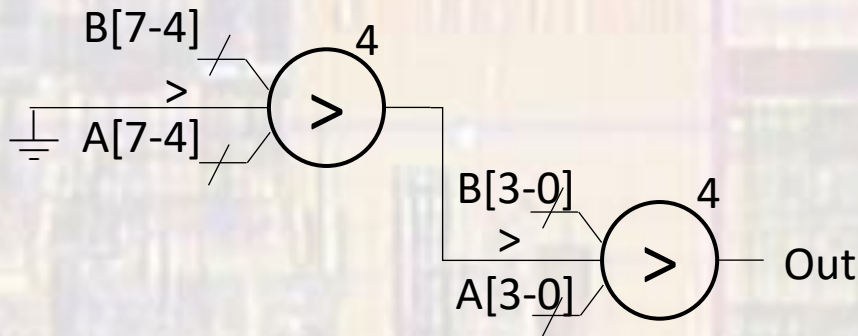- Magnitude Comparator
 - Unsigned numbers
 - 4 bit comparison with chain input
 - n-bit comparison
 - Chain 4 bit comparators



src: Electronic Design

Comparators

- Magnitude Comparator
 - Signed numbers
 - Subtract and check the sign bit (n bit)
 - $Z = A - B$
 - $Z[n-1] = 0 \rightarrow A \geq B$
 - $Z[n-1] = 1 \rightarrow A < B$
 - Fails if there is overflow
 - Overflow: $(A[n-1] \neq B[n-1]) \text{ AND } (Z[n-1] \neq A[n-1])$
 - If there is overflow – flip the result of the comparison