

Decoders


Last updated 10/31/24

Decoders

- A decoder sets one of many outputs to 1 based on the inputs
 - N data outputs – typically a power of 2
 - D data inputs – $\log_2(N)$
 - D:N Decoder


$N = 8$

$D = 3$

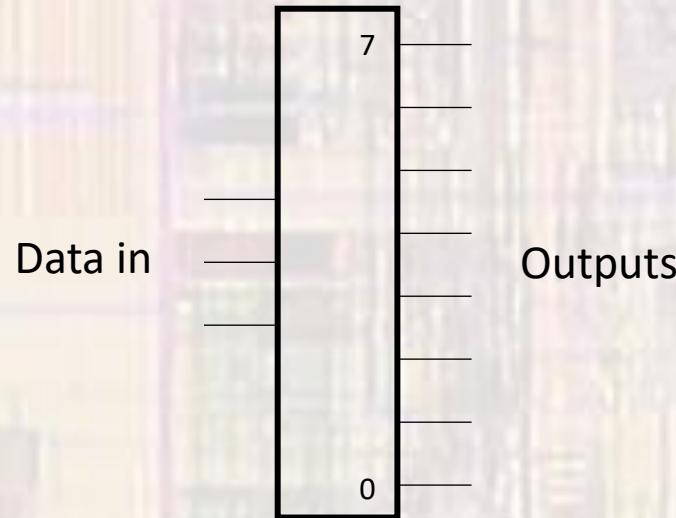



Decoders

- A closer look

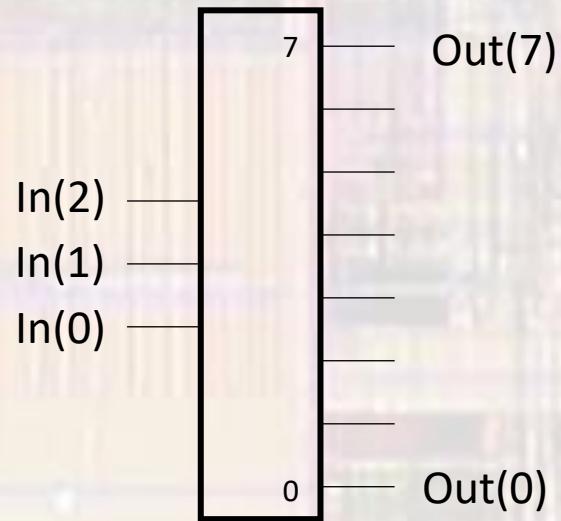

Decoders


- A closer look

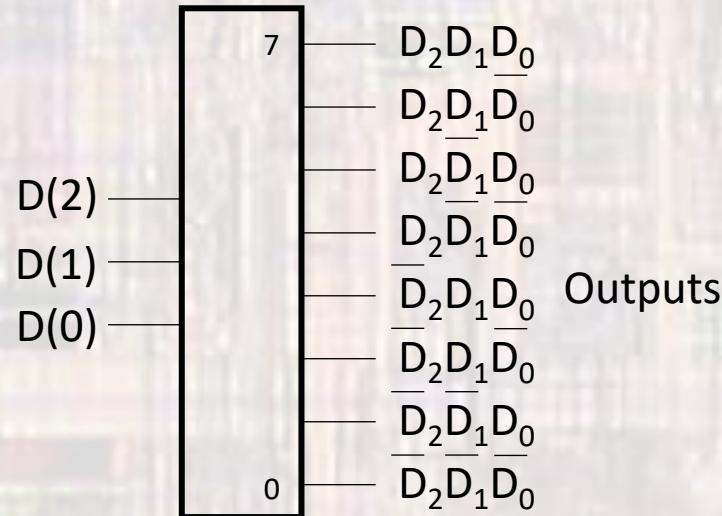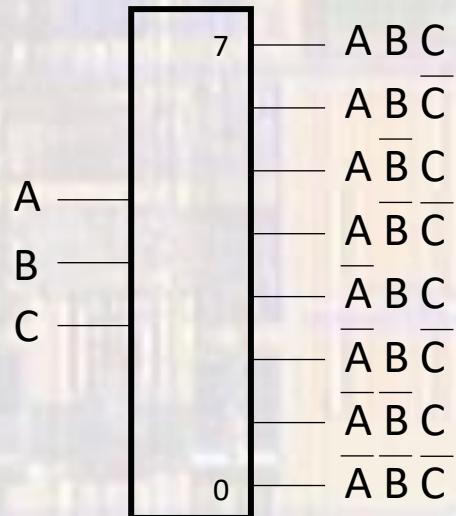

Only one output high

Decoders

- Implementation
 - Direct Synthesis

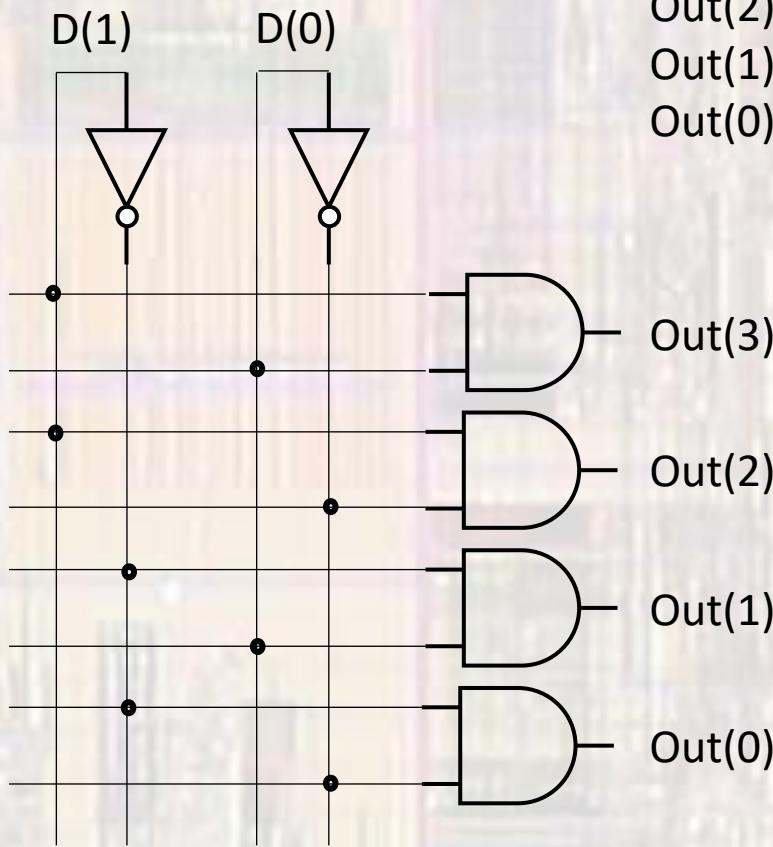

$$\begin{aligned}Out(3) &= D1 \ D0 \\Out(2) &= D1 \ \overline{D0} \\Out(1) &= \overline{D1} \ D0 \\Out(0) &= \overline{D1} \ \overline{D0}\end{aligned}$$

Only one output high