

# Digital Logic Basics

Last updated 10/10/24

These slides introduce digital logic concepts

# Digital Logic Basics

- Digital Logic
  - Defining an expression(operand) as **True** or **False**
  - Logical
    - In the digital world we indicate **T** with a **logical** value **1**
    - In the digital world we indicate **F** with the **logical** value **0**
  - Physical
    - These are signals – voltages on a wire
    - **1** is defined as the positive voltage supply value ( $V_{DD}$ )
      - 5V, 3.3V, 2.5V, ...
    - **0** is defined as Gnd (0V)

# Digital Logic Basics

- Digital Logic
  - Logic Expression
    - Operation Operand  $\rightarrow$  1(T) or 0(F)
    - Operand Operation Operand  $\rightarrow$  1(T) or 0(F)
  - More complex expressions are built out of these two basic operations

((Operand Operation Operand) Operation (Operand Operation Operand ))

((((Operand Operation Operand) Operation Operand ) Operation Operand )

Always remember, 1 and 0 are abstractions  
The actual values on the wires are  $V_{DD}$  and Gnd

# Digital Logic Basics

- **NOT** – flips (negates) the value of the input
  - **1** → **0** or **0** → **1**
  - **not** operand
  - **~** operand
  - operand

A = 1

B = 0

not A → 0

~ B → 1

not (not A) → 1

~ A → 1

NOT	
A	Not A
0	1
1	0

Always remember, 1 and 0 are abstractions  
The actual values on the wires are  $V_{DD}$  and Gnd

# Digital Logic Basics

- **OR** – evaluates as 1(T) if **either** input is 1 (T)
  - op1 or op2
  - op1 | op1
  - op1 + op2

A = 1

B = 0

C = 1

A or B → 1

A | C → 1

B + C → 1

(not A) | B → 0

OR		
A	B	A or B
0	0	0
0	1	1
1	0	1
1	1	1

Always remember, 1 and 0 are abstractions  
The actual values on the wires are  $V_{DD}$  and Gnd

# Digital Logic Basics

- **NOR** – evaluates as 0(T) if **either** input is 1 (T)
  - This is the NOT of an OR
  - $op1 \text{ nor } op2$
  - $\overline{op1 | op2}$
  - $\overline{op1 + op2}$

A = 1

B = 0

C = 0

$A \text{ nor } B \rightarrow 0$

$\overline{A | C} \rightarrow 0$

$\overline{B + C} \rightarrow 1$

$\overline{(\text{not } A) | B} \rightarrow 1$

NOR		
A	B	$\overline{A \text{ or } B}$
0	0	1
0	1	0
1	0	0
1	1	0

Always remember, 1 and 0 are abstractions  
The actual values on the wires are  $V_{DD}$  and Gnd

# Digital Logic Basics

- **AND** – evaluates as 1(T) if **both** inputs are 1(T)
  - op1 and op2
  - op1 & op2
  - op1op2, (op1)(op2)

A = 1

B = 0

C = 1

A and B → 0

A & C → 1

BC → 0

A & (not B) → 1

AND		
A	B	A and B
0	0	0
0	1	0
1	0	0
1	1	1

Always remember, 1 and 0 are abstractions  
The actual values on the wires are  $V_{DD}$  and Gnd

# Digital Logic Basics

- **NAND** – evaluates as 0(F) if **both** inputs are 1(T)
  - This is the NOT of an AND
  - $op1 \text{ nand } op2$
  - $\overline{op1 \ \& \ op2}$
  - $\overline{op1}op2, (op1)\overline{(op2)}$

A = 1

B = 0

C = 1

$A \text{ nand } B \rightarrow 1$

$\overline{A \ \& \ C} \rightarrow 0$

$\overline{BC} \rightarrow 1$

$\overline{A \ \& \ (\text{not } B)} \rightarrow 0$

NAND		
A	B	$\overline{A \ \& \ B}$
0	0	1
0	1	1
1	0	1
1	1	0

Always remember, 1 and 0 are abstractions  
The actual values on the wires are  $V_{DD}$  and Gnd



# Digital Logic Basics

- **XOR** – evaluates as 1(T) if an **odd number** of inputs are 1(T)
  - $op1 \text{ xor } op2$
  - $op1 \otimes op2$

$$A = 1$$

$$B = 0$$

$$C = 1$$

$$A \text{ xor } B \rightarrow 1$$

$$A \otimes C \rightarrow 0$$

$$A \otimes (\text{not } B) \rightarrow 0$$

XOR		
A	B	A xor B
0	0	0
0	1	1
1	0	1
1	1	0

Always remember, 1 and 0 are abstractions  
The actual values on the wires are  $V_{DD}$  and Gnd

# Digital Logic Basics

- **XNOR** – evaluates as 0(F) if an **odd number** of inputs are 1(T)
  - This is the NOT of an XOR
  - $op1 \text{ xnor } op2$
  - $op1 \odot op2$

$$A = 1$$

$$B = 0$$

$$C = 1$$

$$A \text{ xnor } B \rightarrow 0$$

$$A \odot C \rightarrow 1$$

$$\overline{A \otimes C} \rightarrow 1$$

$$A \odot (\text{not } B) \rightarrow 1$$

XNOR		
A	B	$\overline{A \text{ xor } B}$
0	0	1
0	1	0
1	0	0
1	1	1

Always remember, 1 and 0 are abstractions  
The actual values on the wires are  $V_{DD}$  and Gnd