


# Digital Logic Evaluation Gates

Last updated 10/10/24


These slides show how to evaluate digital logic circuits via truth tables
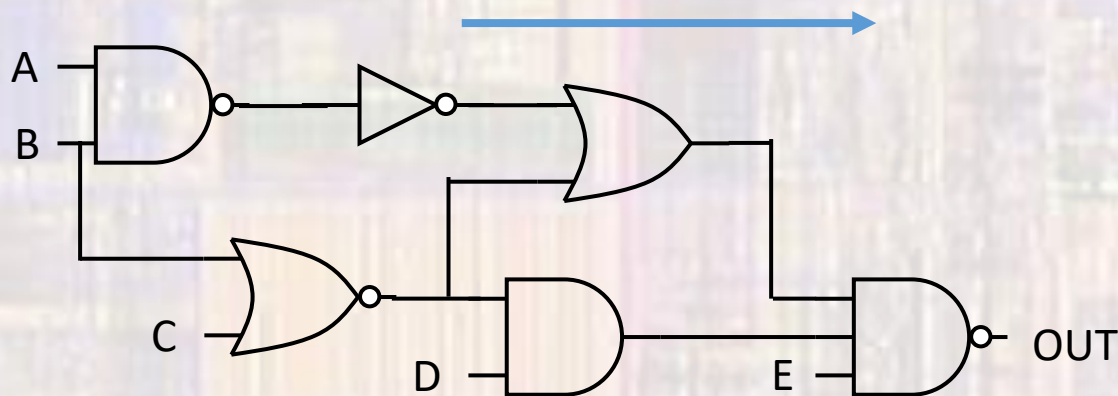
# Digital Logic Evaluation – Gates

- Circuits are evaluated from input to output when creating truth tables



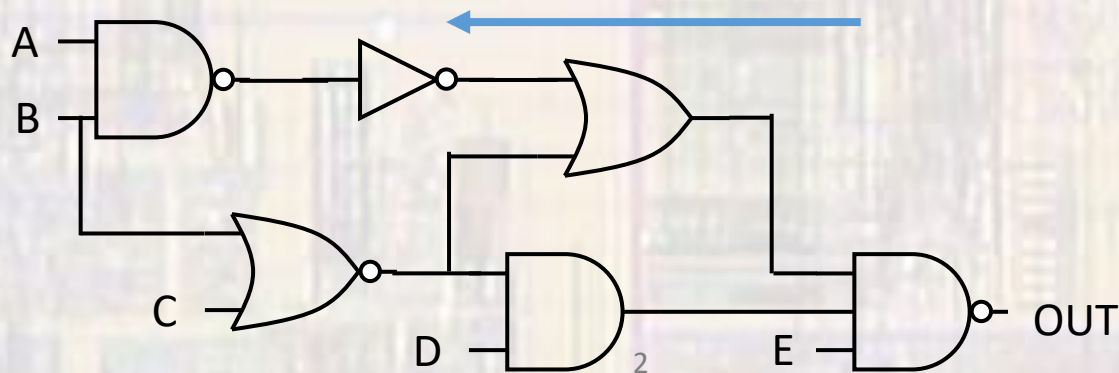- Circuits are evaluated from output to input when creating logic expressions




# Digital Logic Evaluation – Gates

- Logic Evaluation – Gates

- Truth Table** Process

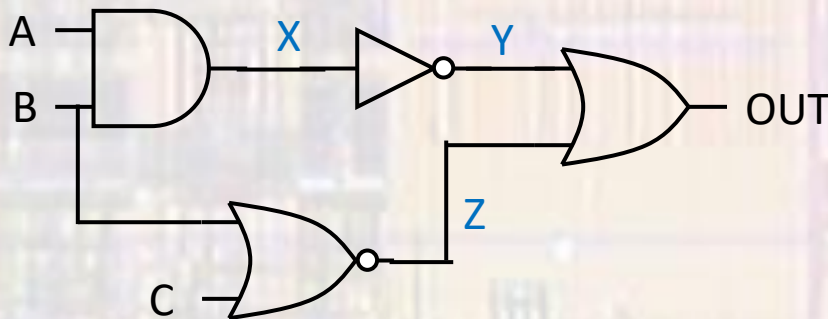1. Label all intermediate nodes
2. Create a truth table that includes all inputs, intermediate nodes and the output – working from input to output
3. Fill in the table 1 step at a time – working from inputs to output




C	B	A	X (AB)	Y ( $\overline{X}$ )	Z (B + C)	OUT (Y+Z)
0	0	0	0	1	1	1
0	0	1	0	1	1	1
0	1	0	0	1	0	1
0	1	1	1	0	0	0
1	0	0	0	1	0	1
1	0	1	0	1	0	1
1	1	0	0	1	0	1
1	1	1	1	0	0	0

# Digital Logic Evaluation – Gates

- Logic Evaluation – Gates

- Logic Expression Process

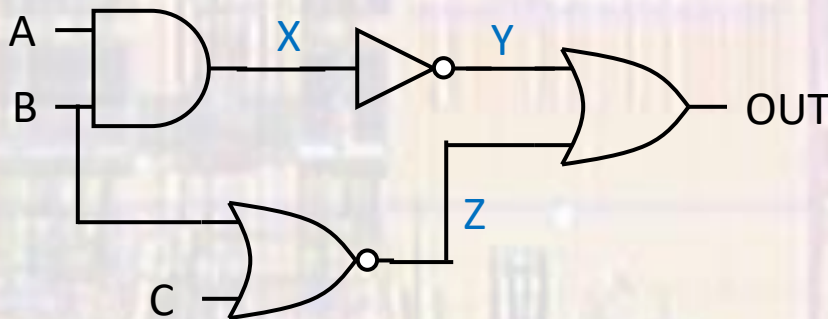1. Label all intermediate nodes
2. Starting at the output – write the single gate logic expression
3. Working from output toward input – substitute each new level's logic gate expression
4. Reduce as desired



$$\text{Out} = Y + Z$$

$$\text{Out} = (\overline{X}) + (C + B)$$

$$\text{Out} = (\overline{AB}) + (\overline{C + B})$$

Reduction (covered elsewhere)

$$\text{Out} = \overline{A} + \overline{B} + \overline{BC}$$

$$\text{OUT} = \overline{A} + \overline{B}$$