

Digital Logic Gates

Last updated 10/8/24

These slides introduce digital logic gates

Digital Logic Gates


- Digital Logic
 - Defining signal as **True** or **False**
 - Logical
 - In the digital world we indicate **T** with a **logical value 1**
 - In the digital world we indicate **F** with the **logical value 0**
 - Physical
 - These are signals – voltages on a wire
 - **1** is defined as the positive voltage supply value (V_{DD})
 - 5V, 3.3V, 2.5V, ...
 - **0** is defined as Gnd (0V)

Digital Logic Gates


- NOT – flips the value of the input

- Logic Gate - Inverter

- Circuit Symbol

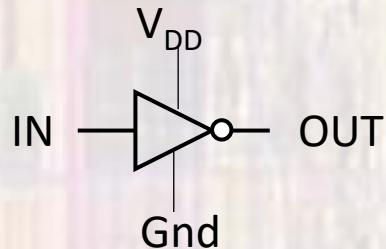

- Logic Symbol

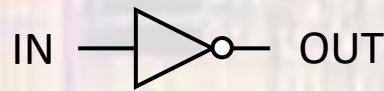

- Truth Table (logic)


IN	OUT
0	1
1	0

Always remember, 1 and 0 are abstractions
The actual values on the wires are V_{DD} and Gnd


Digital Logic Gates

- **Buffer** – replicates the value of the input
 - Logic Gate - Buffer

- Circuit Symbol

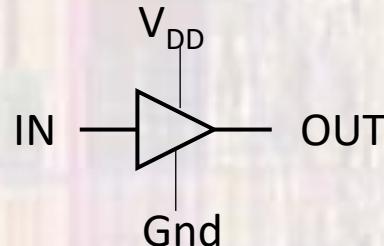

- Logic Symbol

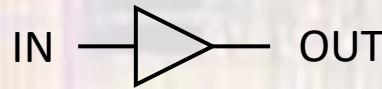

- Truth Table (logic)

IN	OUT
0	0
1	1


Always remember, 1 and 0 are abstractions
The actual values on the wires are V_{DD} and Gnd

Digital Logic Gates


- OR – outputs 1(F) if either input is 1(T)

- Logic Gate - OR

- Circuit Symbol

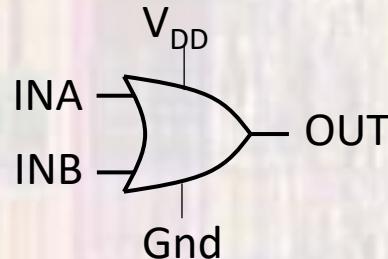

- Logic Symbol

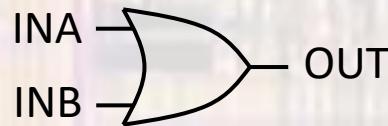


- Truth Table (logic)

INB	INA	OUT
0	0	0
0	1	1
1	0	1
1	1	1


Digital Logic Gates

- NOR – outputs 0(F) if **either** input is 1(T)
 - Logic Gate - NOR

- Circuit Symbol

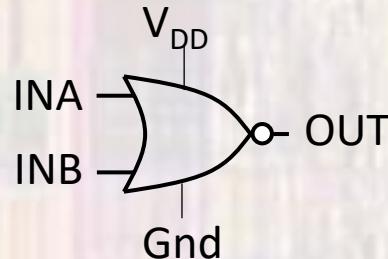

- Logic Symbol

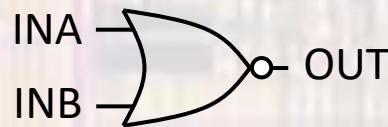

- Truth Table (logic)


INB	INA	OUT
0	0	1
0	1	0
1	0	0
1	1	0

Digital Logic Gates


- AND – outputs 1(F) if **both** inputs are 1(T)

- Logic Gate - NAND

- Circuit Symbol

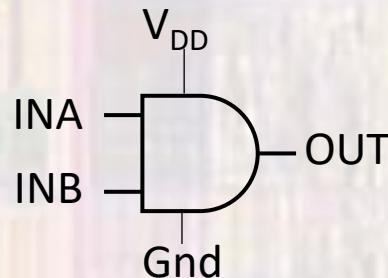

- Logic Symbol

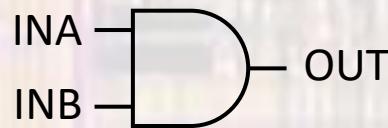

- Truth Table (logic)


INB	INA	OUT
0	0	0
0	1	0
1	0	0
1	1	1

Digital Logic Gates


- **NAND** – outputs 0(F) if **both** inputs are 1(T)

- Logic Gate - NAND

- Circuit Symbol

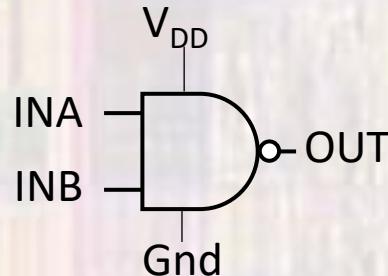

- Logic Symbol

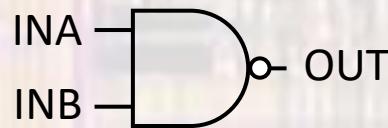

- Truth Table (logic)


INB	INA	OUT
0	0	1
0	1	1
1	0	1
1	1	0

Digital Logic Gates


- **XOR** – outputs 1(T) if **only** 1 input is 1(T)

- Logic Gate - XOR

- Circuit Symbol

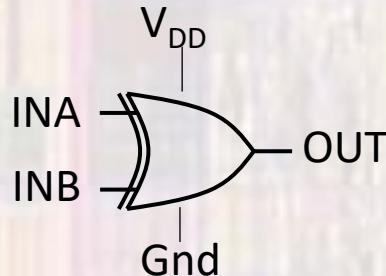

- Logic Symbol

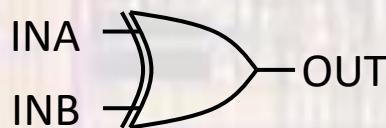

- Truth Table (logic)

INB	INA	OUT
0	0	0
0	1	1
1	0	1
1	1	0


Sometimes called the
In-equality Gate

Digital Logic Gates


- **XNOR** – outputs 0(F) if **only** 1 input is 1(T)

- Logic Gate - XNOR

- Circuit Symbol

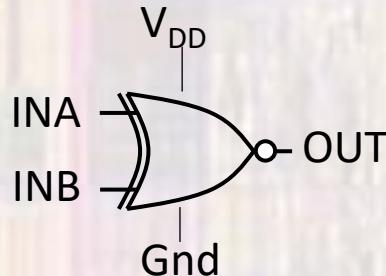

- Logic Symbol

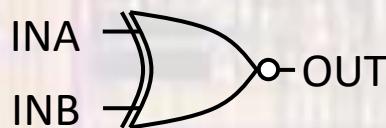

- Truth Table (logic)


INB	INA	OUT
0	0	1
0	1	0
1	0	0
1	1	1

Sometimes called the
Equality Gate


Digital Logic Gates

- Multi-input gates

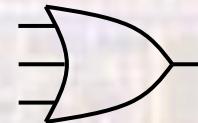
- OR – outputs $1(T)$ if **any** inputs are $1(T)$



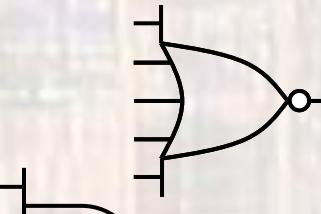
- NOR – outputs $0(F)$ if **any** inputs are $1(T)$



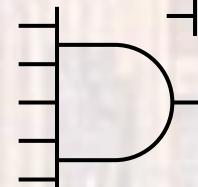
- AND – outputs $1(T)$ if **all** inputs are $1(T)$



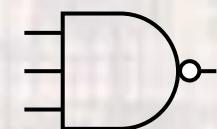- NAND – outputs $0(T)$ if **all** inputs are $1(T)$



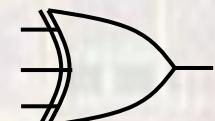- XOR – outputs $1(T)$ if an **odd number** of inputs are $1(T)$



- XNOR – outputs $0(T)$ if an **odd number** of inputs are $1(T)$

