

# Digital Logic Reduction

## Bubble Pushing

Last updated 1/7/25




# Digital Logic Reduction – bubble pushing

- CMOS NAND and NOR gates are preferred over AND and OR gates
  - Faster
  - Smaller
  - Less Power

# Digital Logic Reduction – bubble pushing


- Use De Morgan's theorem to switch between AND/OR/NAND/NOR
- Flip the inputs and outputs and swap the gate

T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots} = \overline{B_0} + \overline{B_1} + \overline{B_2} \dots$	$\overline{B_0 + B_1 + B_2 \dots} = \overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots$	DeMorgan's
-----	---	---	------------

   


# Digital Logic Reduction – bubble pushing

- Bubble Destruction

 


- Bubble Creation

 

# Digital Logic Reduction – bubble pushing

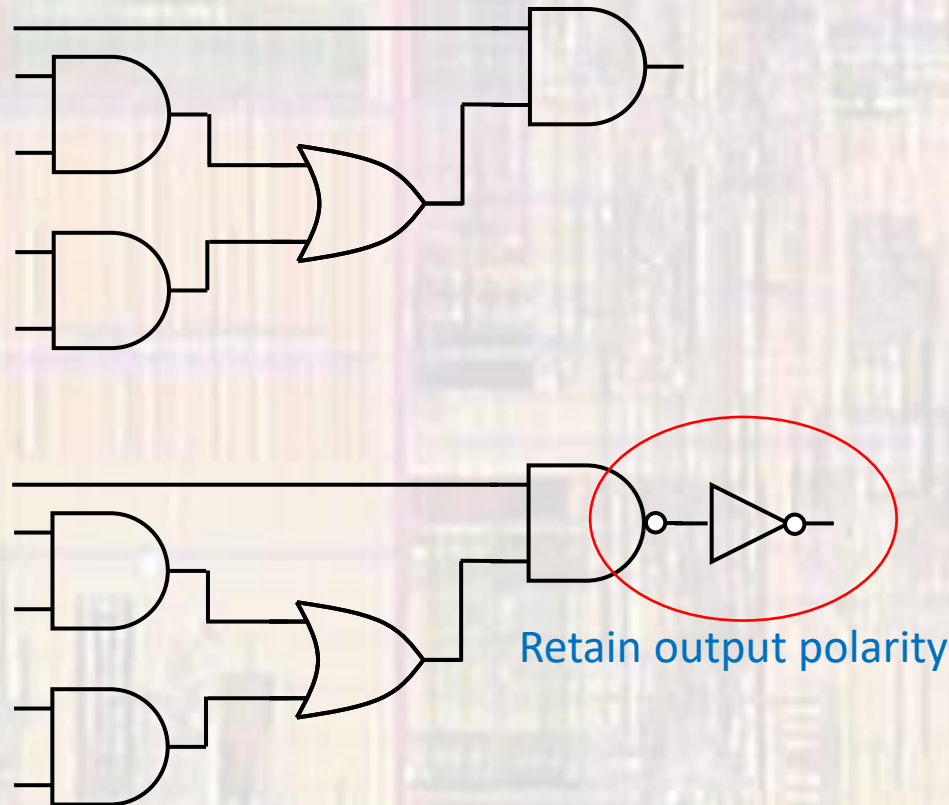- Example – step 1
  - Convert to NANDs and NORs where possible



# Digital Logic Reduction – bubble pushing

- Example – step 2/3

