

Enumerate States

Last updated 12/12/24

Enumerated States

- Enumerated States
 - Similar to enumerated types in C
 - Define a new TYPE with a fixed set of recognized values

```
type STATE_TYPE is (A, B, C, D, E, F, G, H, I, J);
```

- Each state can be identified by its position (integer)
 - A – 0
 - B – 1
 - ...
 - J – 9
- STATE_TYPE'pos(D) → 3

Enumerated States


- Enumerated States
 - Create signals of the enumerated type

```
signal state:      STATE_TYPE;  
signal state_next: STATE_TYPE;
```

- Synthesis is done using the enumerated states with the corresponding encoding
 - Binary
 - One Hot
 - Gray
 - Johnson
 - Auto

Enumerated States

Mod 10 Counter using Enumerated States

 

Enumerated States

- Mod 10 Counter – Enumerated States

```
-- counter_mod10_fsmc.vhdl
-- created 3/30/18
-- tj
-- rev 0
-- mod 10 up-counter - state machine with case statement
--           enumerated states
-- Inputs: i_rstb, i_clk
-- Outputs: o_cnt[3:0]
-- 

library ieee;
use ieee.std_logic_1164.all;

entity counter_mod10_fsmc is
  port (
    i_clk : in std_logic;
    i_rstb : in std_logic;
    o_cnt : out std_logic_vector(3 downto 0)
  );
end entity;
```

```
architecture behavioral of counter_mod10_fsmc is
  -- internal signals
  --
  type STATE_TYPE is (A, B, C, D, E, F, G, H, I, J);
  signal state: STATE_TYPE;
  signal state_next: STATE_TYPE;
begin
  -- next state logic
  process(state)
  begin
    case state is
      when A => state_next <= B;
      when B => state_next <= C;
      when C => state_next <= D;
      when D => state_next <= E;
      when E => state_next <= F;
      when F => state_next <= G;
      when G => state_next <= H;
      when H => state_next <= I;
      when I => state_next <= J;
      when J => state_next <= A;
      when others => state_next <= A;
    end case;
  end process;
```

Enumerated state declaration

Next state logic


```
-- Register logic
process(i_clk, i_rstb)
begin
  -- reset
  if (i_rstb = '0') then
    state <= A;
  -- rising i_clk edge
  elsif (rising_edge(i_clk)) then
    state <= state_next;
  end if;
end process;

-- Output logic
process(state)
begin
  case state is
    when A => o_cnt <= "0000";
    when B => o_cnt <= "0001";
    when C => o_cnt <= "0010";
    when D => o_cnt <= "0011";
    when E => o_cnt <= "0100";
    when F => o_cnt <= "0101";
    when G => o_cnt <= "0110";
    when H => o_cnt <= "0111";
    when I => o_cnt <= "1000";
    when J => o_cnt <= "1001";
    when others => o_cnt <= "0000";
  end case;
end process;
```

State initialization and update (register logic)

Enumerated States



- Mod 10 Counter – Enumerated States

 

Quartus recognized part of the code
as a state machine


Enumerated States

- Mod 10 Counter – Enumerated States

  

Enumerated States

- Mod 10 Counter – Enumerated States

 


	Source State	Destination State	Condition
1	A	B	
2	B	C	
3	C	D	
4	D	E	
5	E	F	
6	F	G	
7	G	H	
8	H	I	
9	I	J	
10	J	A	

Transitions / Encoding /

Enumerated States

- Mod 10 Counter – Enumerated States

 

Default encoding is a modified 1-hot

Enumerated States

- Mod 10 Counter – Enumerated States
 - Add the states and re-run the simulation

