

# Flip-Flop Basics





Last updated 10/24/24

# Flip-Flop Basics

- D Latch (data)
   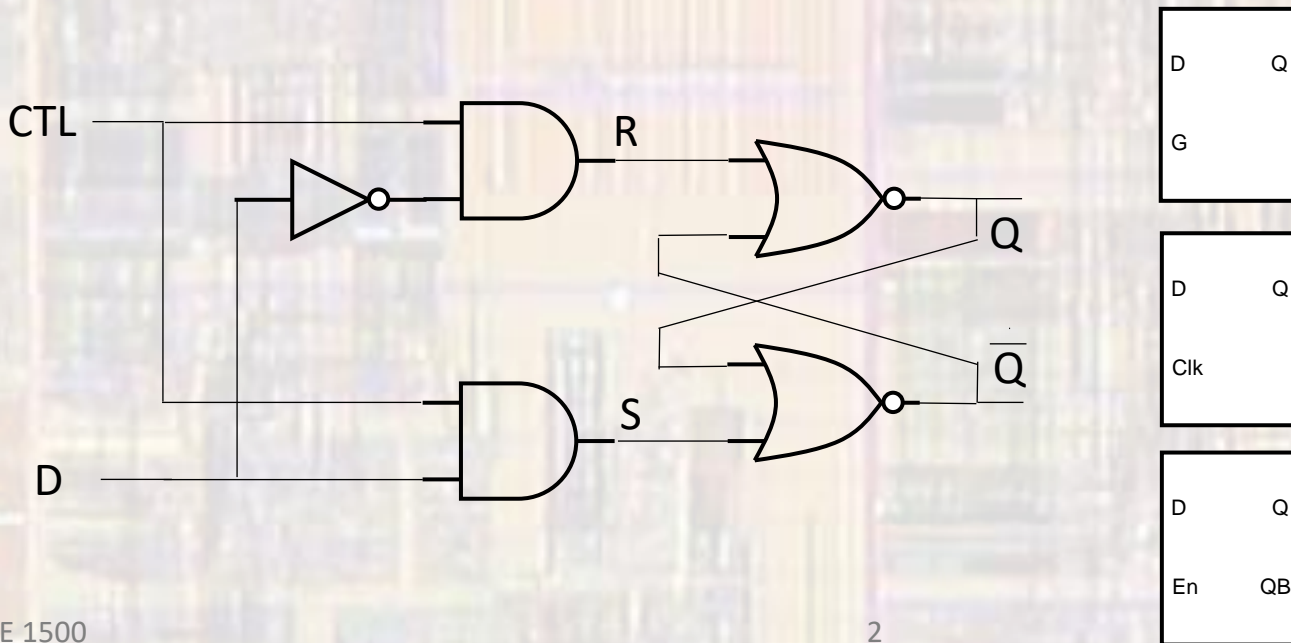
## Level Sensitive Latch


CTL = low  $\rightarrow$  latched  
CTL = high  $\rightarrow$  Transfer



CTL	D	Q
0	x	$Q_{old}$
1	D	D

# Flip-Flop Basics


- D Latch - Abstraction

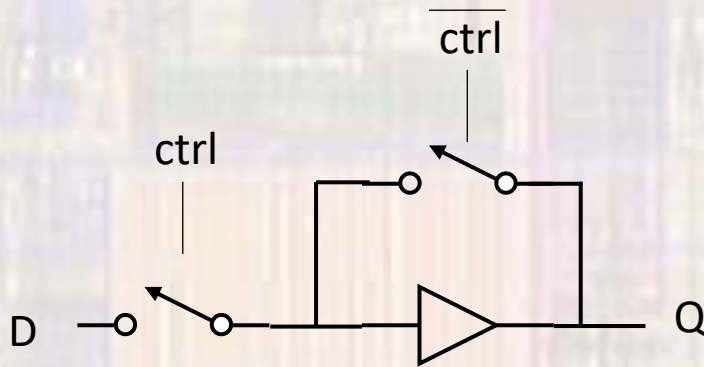

CTRL	D	Q
0	x	$Q_{old}$
1	D	D

 
# Flip-Flop Basics

- D Flip-Flop – Abstraction
  - 2 series D-Latches with opposite control polarity
  - Synchronous Sequential Circuit
    - Sequential - Output depends on inputs and 1 state variable  $Q$  ( $Q_{old}$ )
    - Synchronous – output changes limited to specific input conditions
      - Typically, on a (rising) clk edge
    - Memory is in the bi-stable latch



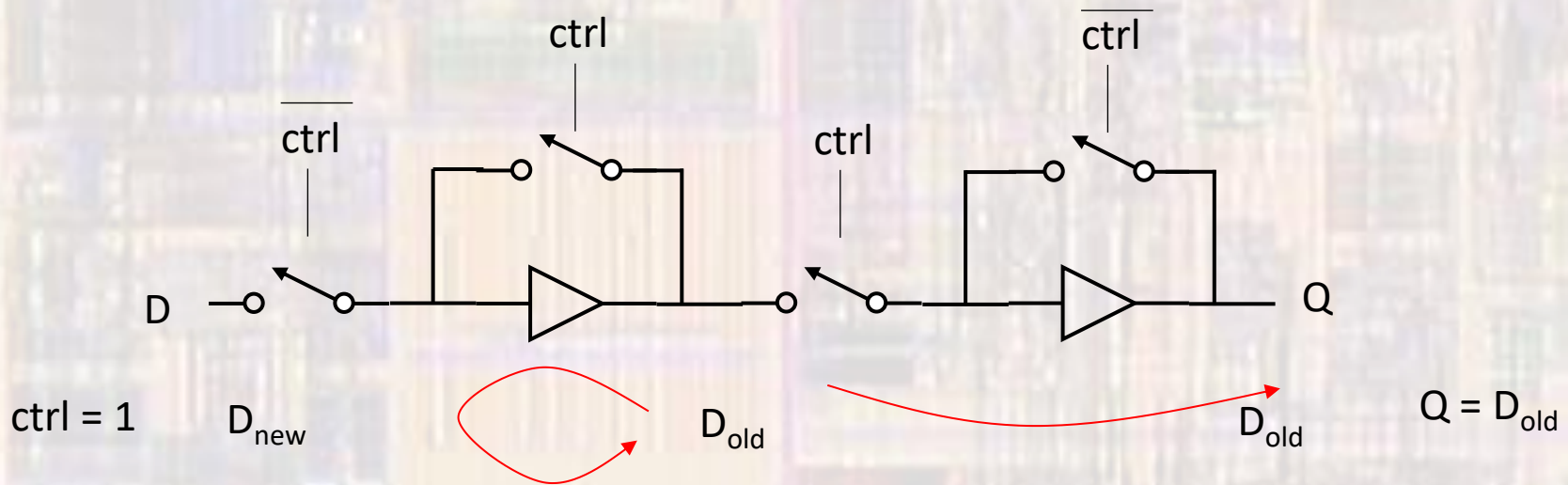
# Flip-Flop Basics

- D Flip-Flop – Abstraction
  - 2 series D-Latches with opposite control polarity



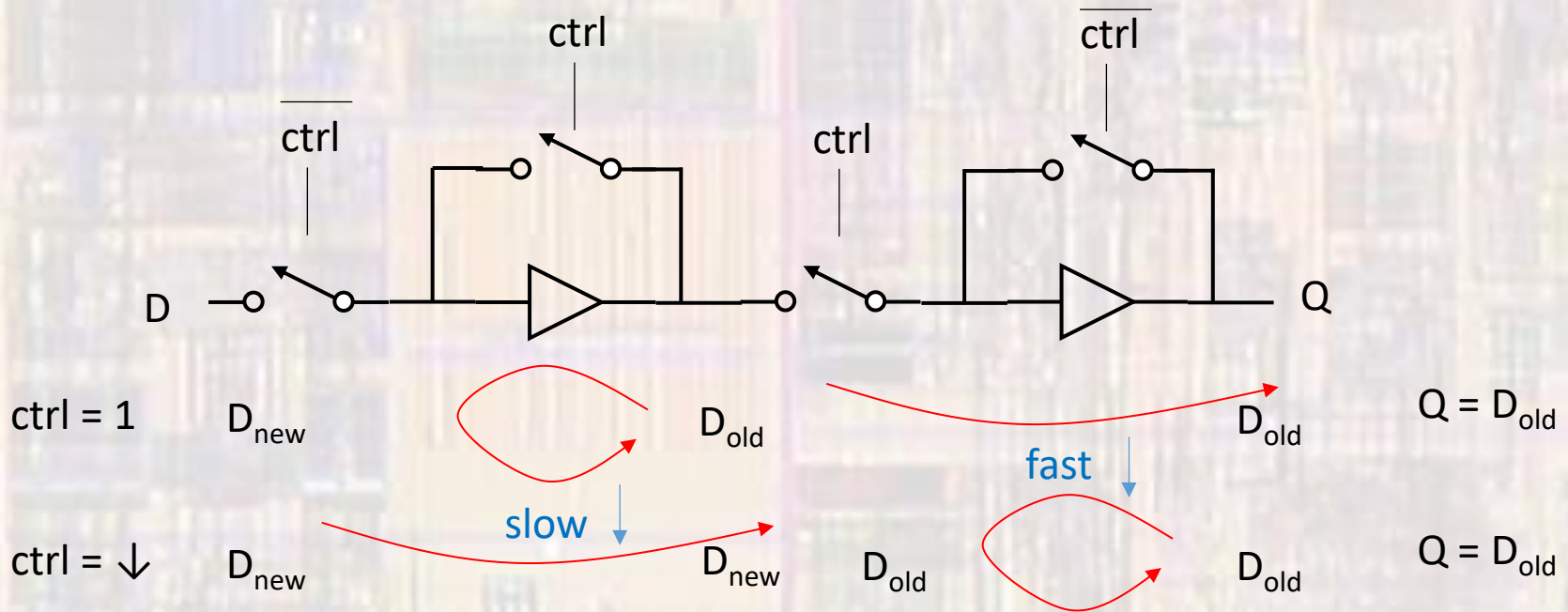
# Flip-Flop Basics

- D Flip-Flop – Abstraction
  - 2 series D-Latches with opposite control polarity



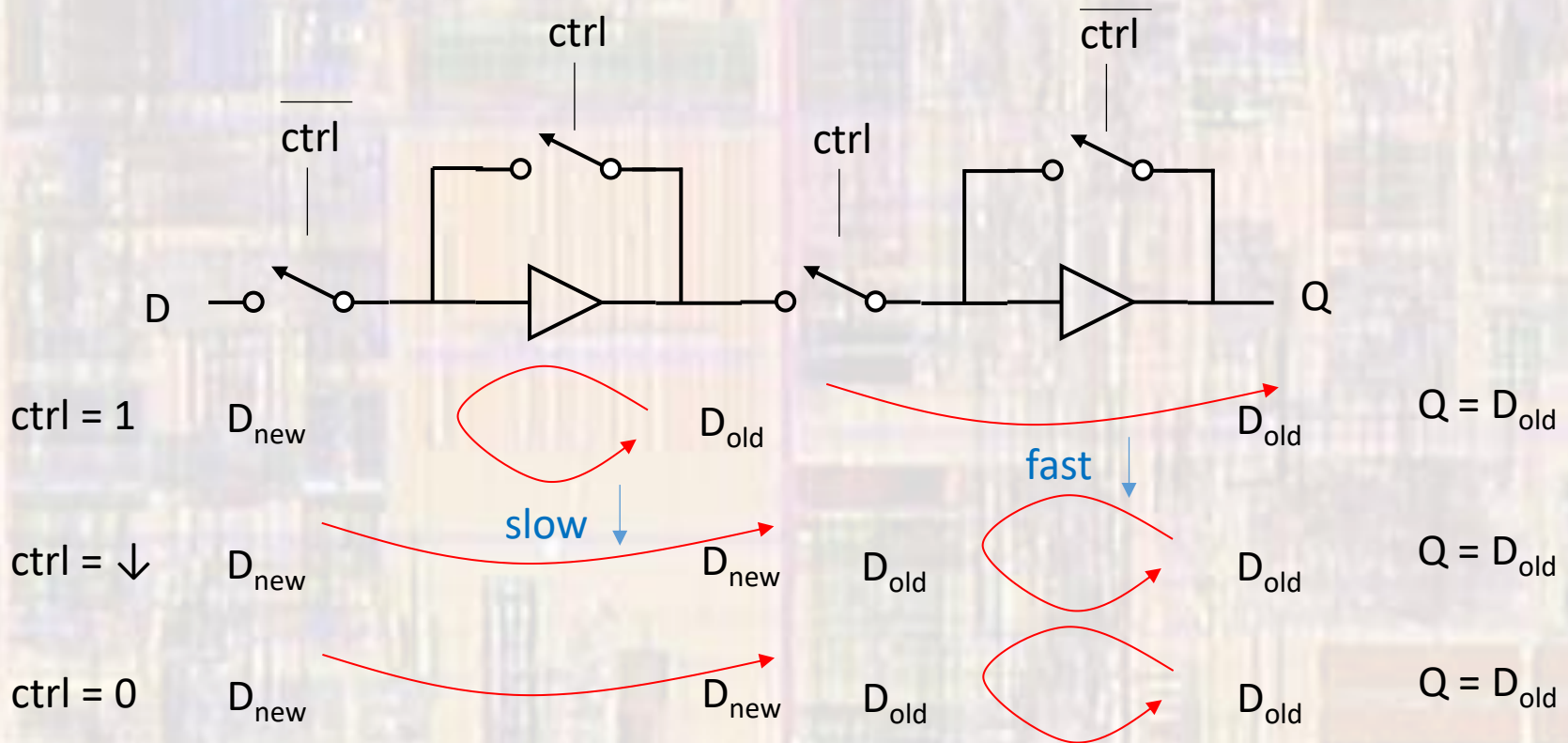
# Flip-Flop Basics

- D Flip-Flop – Abstraction
  - 2 series D-Latches with opposite control polarity


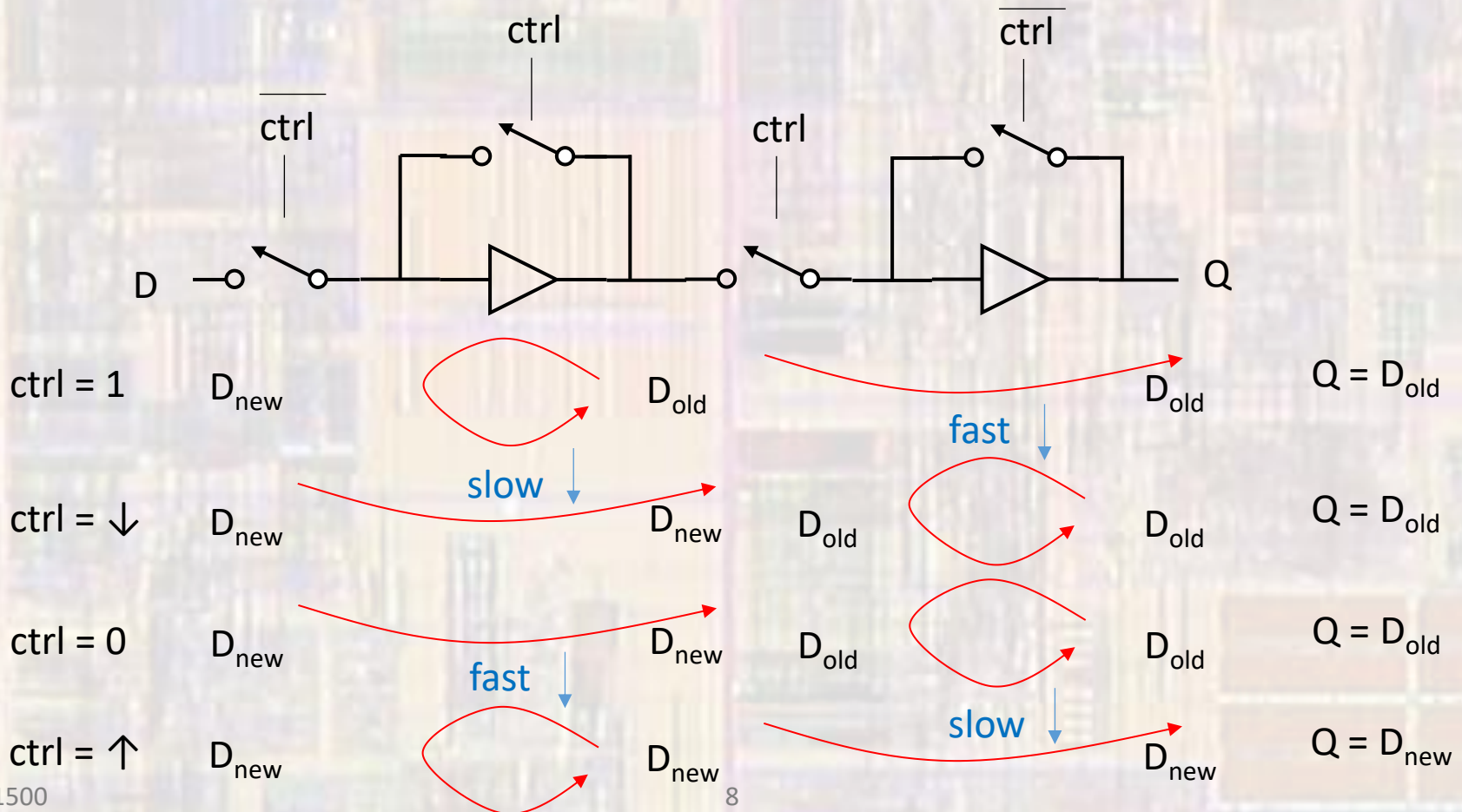
# Flip-Flop Basics


- D Flip-Flop – Abstraction
  - 2 series D-Latches with opposite control polarity




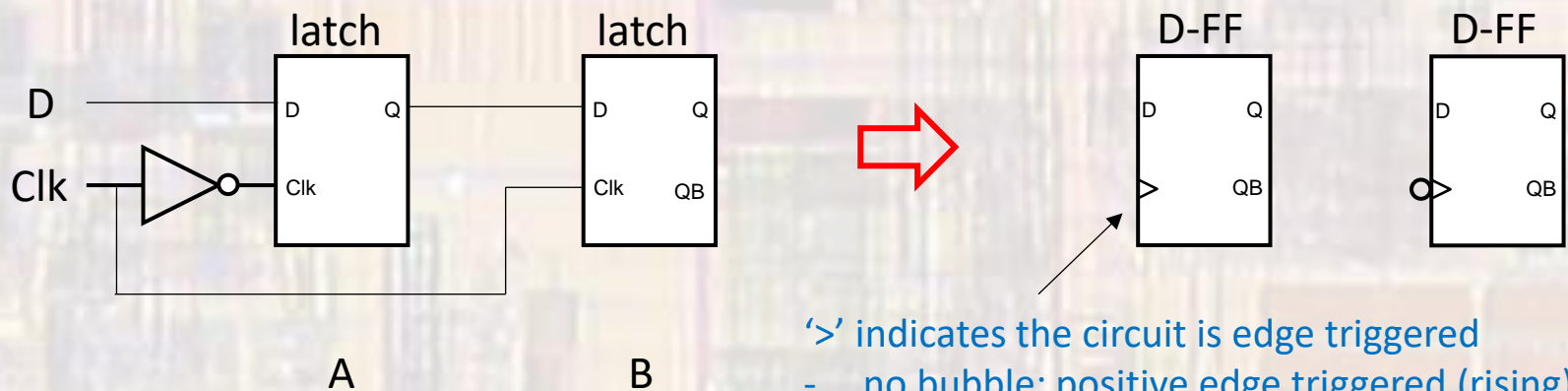
# Flip-Flop Basics

- D Flip-Flop (data)
  - Synchronous Sequential Circuit
    - Sequential - Output depends on inputs and 1 state variable  $Q$  ( $Q_{old}$ )
    - Synchronous – output changes limited to specific input conditions
      - Typically, on a (rising) clk edge
    - Memory is in the bi-stable latch




- '>' indicates the circuit is edge triggered
- no bubble: positive edge triggered (rising)
  - bubble: negative edge triggered (falling)

# Flip-Flop Basics

## D-Latch

CTL CLK	D	Q
0	x	$Q_{old}$
1	D	D

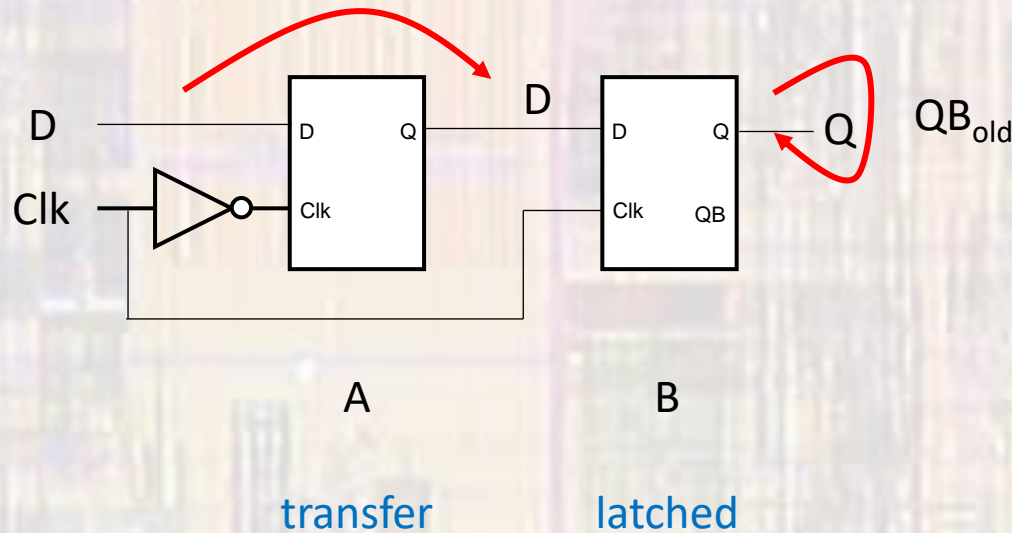- D Flip-Flop (data)
  - Clock low – after a short time
    - A is enabled and passes D to it's Q output
    - B is in latch mode and retains it's state -  $QB_{old}$




D	Clk	Q
x	0	$QB_{old}$

# Flip-Flop Basics

- D Flip-Flop (data)

- Clock high – after a short time

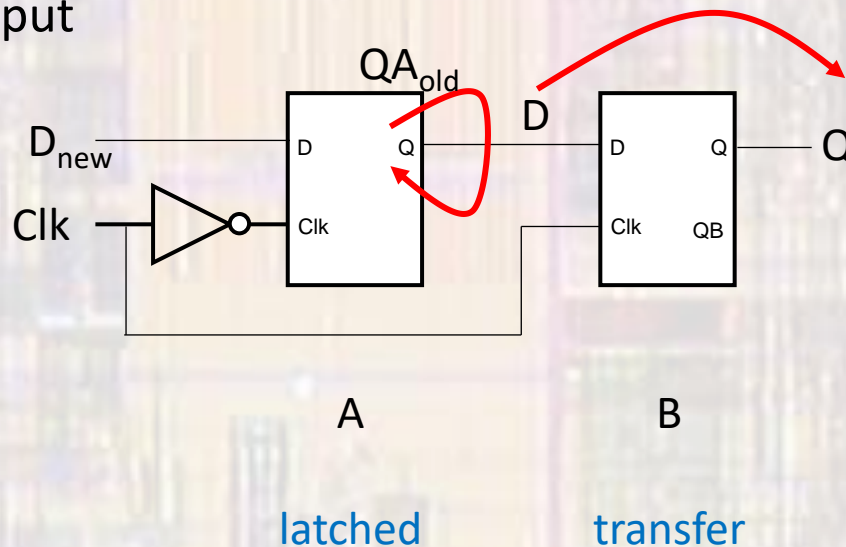- A is latched and retains it's state –  $QA_{old}$  (original value of D)
- B is in transfer mode and would have already passed D to it's Q output




D	Clk	Q
x	0	$QB_{old}$
x	1	$QA_{old}$ ( $D_{old}$ )

# Flip-Flop Basics

- D Flip-Flop (data)

- Clock **Low**  $\rightarrow$  **High**

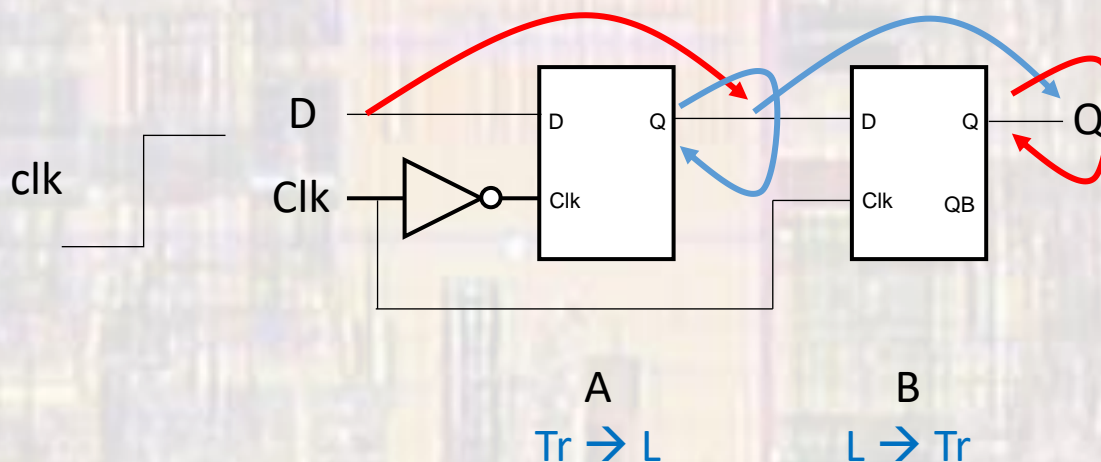- D has previously been passed to the intermediate node
- When clk transitions high, the intermediate value (D) is passed to the output while simultaneously the A becomes latched
- Further changes of the D input are blocked by the latched A




D	Clk	Q
x	0	QB <sub>old</sub>
x	1	QA <sub>old</sub>
D	$\uparrow$	<b>D</b>

# Flip-Flop Basics

- D Flip-Flop (data)

- Clock **High** → **Low**

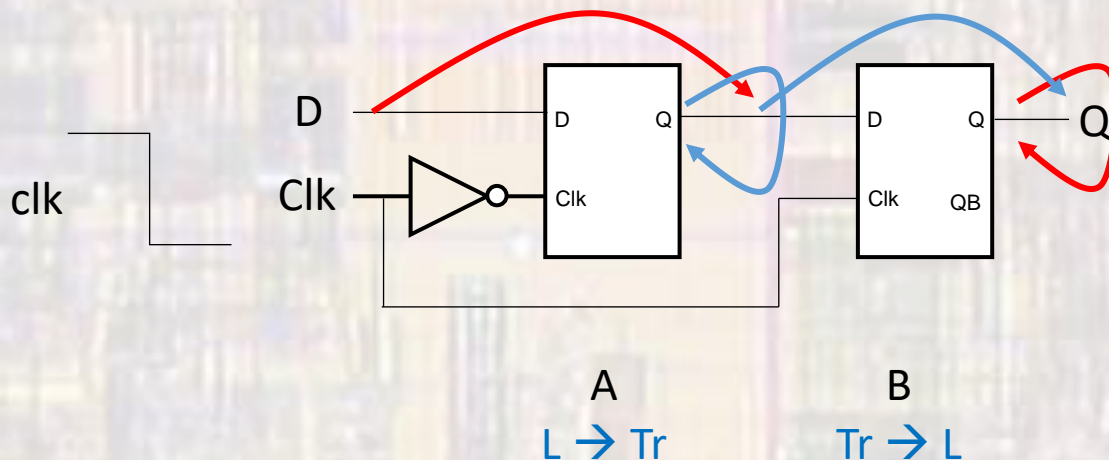- The output is latched by the B
- The new D input is allowed to transfer to the intermediate node but no further





D	Clk	Q
x	0	QB <sub>old</sub>
x	1	QA <sub>old</sub>
D	↑	D
x	↓	QA <sub>old</sub>

# Flip-Flop Basics

- D Flip-Flop (data)

- Truth Table

  - Positive Edge Triggered D Flip-Flop
  - (typically, just called a D Flip-flop)



D	Clk	Q
x	0	$Q_{old}$
x	1	$Q_{old}$
D	↑	D
x	↓	$Q_{old}$