 


Flip-Flop Circuit Analysis

Last updated 11/12/24


Flip-Flop Circuit Analysis

- Flip-Flops - Example



Flip-Flop Circuit Analysis

- ## • Flip-Flops - Example

 


Initial State

	D	J	K	Q1	Q1B	Q2	Q2B
Initial	0	0	0	0	0	0	0
After clk1	1	1	1	1	1	0	0
After clk2	0	0	0	0	0	1	0
After clk3	0	0	0	0	0	0	1

You must know these to analyze the circuit

Flip-Flop Circuit Analysis

- Flip-Flops - Example

 


Initial State

	D	J	K	Q1	Q1B	Q2	Q2B
Initial							
After clk1				1	0	1	0
After clk2							
After clk3							

known

Flip-Flop Circuit Analysis

- Flip-Flops - Example

 

Initial State




Flip-Flop Circuit Analysis

- Flip-Flops - Example

Clk


Synchronous
Propagation

 

D	J	K	Q1	Q1B	Q2	Q2B
Initial						
0	0	1	1	0	1	0
After clk1				0	1	0
After clk2						
After clk3						

Flip-Flop Circuit Analysis

- Flip-Flops - Example

 

Asynchronous
Propagation


D	J	K	Q1	Q1B	Q2	Q2B
Initial						
0	0	1	1	0	1	0
After clk1						
			0	1	0	1
1	1	0				
After clk2						
After clk3						

Flip-Flop Circuit Analysis

- Flip-Flops - Example

Clk


Synchronous
Propagation

 

D	J	K	Q1	Q1B	Q2	Q2B
Initial						
0	0	1	1	0	1	0
After clk1						
			0	1	0	1
After clk2	1	1	0		1	0
				1	0	1
After clk3						

Flip-Flop Circuit Analysis

- Flip-Flops - Example

 

Asynchronous
Propagation


D	J	K	Q1	Q1B	Q2	Q2B
Initial						
0	0	1	1	0	1	0
After clk1				0	1	0
1	1	0				
After clk2				0	1	0
0	0	1				
After clk3						

Flip-Flop Circuit Analysis

- Flip-Flops - Example

Clk


Synchronous
Propagation

 

D	J	K	Q1	Q1B	Q2	Q2B
Initial						
0	0	1	1	0	1	0
After clk1				0	1	0
1	1	0				
After clk2				1	0	1
0	0	1				
After clk3				0	1	0

Flip-Flop Circuit Analysis

- Flip-Flops - Example

 


Asynchronous
Propagation

D	J	K	Q1	Q1B	Q2	Q2B
Initial						
0	0	1	1	0	1	0
After clk1				0	1	0
1	1	0				
After clk2				1	0	1
0	0	1				
After clk3				0	1	0
1	1	0				

Flip-Flop Circuit Analysis

 
- Example – 2
 - Assume all Flip-Flops have been reset



	D1	D2	Q1	Q2	OUT
Initial			0	0	0
async	1	0			
After Clk 1		1	1	0	0
async	1	1			
After Clk 2		1	1	1	1
async	0	1			
After Clk 3		0	0	1	1
async	0	0			
After Clk 4		0	0	0	0
async	1	0			
After Clk 5		1	1	0	0
async	1	1			
After Clk 6		1	1	1	1
async	0	1			

Flip-Flop Circuit Analysis

- Example – 3
 - Assume all reset

 

	D1	D2	D3	Q1	Q1B	Q2	OUT
Initial				0	1	0	0
async	1	1	0	0	1	0	0
After Clk 1				1	0	1	0
async	0	0	1	0	1	0	1
After Clk 2				0	1	0	1
async	1	1	0	1	0	1	0
After Clk 3				0	1	1	0
async	0	0	1	1	0	1	1
After Clk 4				0	1	0	1
async	1	1	0	0	1	0	1
After Clk 5				1	0	1	0
async	0	0	1	1	0	1	0
After Clk 6				0	1	0	1
async	1	1	0	0	1	0	1