 


# Flip-Flop Timing

Last updated 10/24/24


# Flip-Flop Timing

- D Flip-Flop (data)
  - Edge triggered



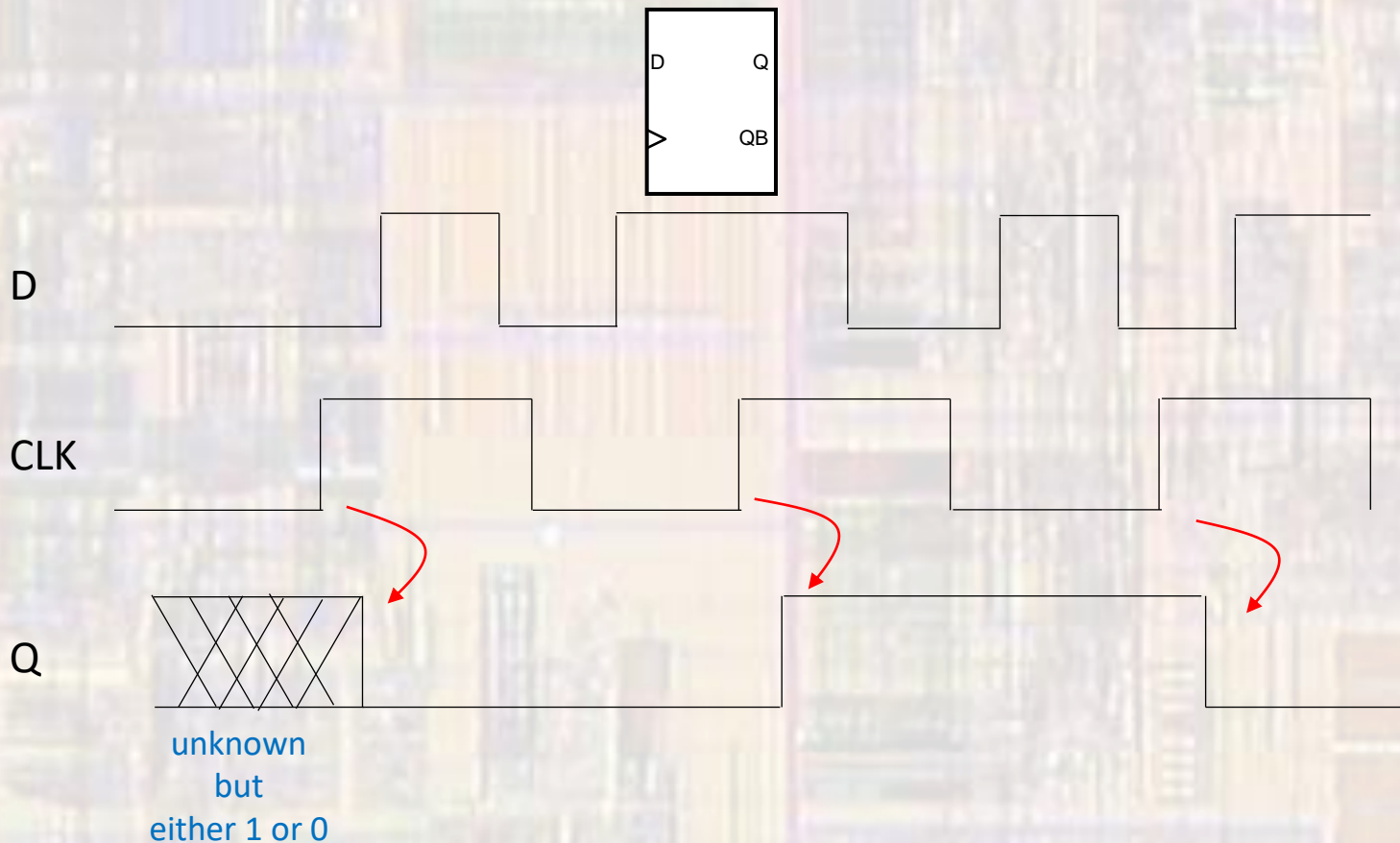
# Flip-Flop Timing

- D Flip-Flop (data)
  - Edge triggered
  - Delay from clk to output change




 
# Flip-Flop Timing

- D Flip-Flop (data)
  - $t_{cq}$  – time from clk to Q valid





# Flip-Flop Timing

- D Flip-Flop –  $T_{cQ}$

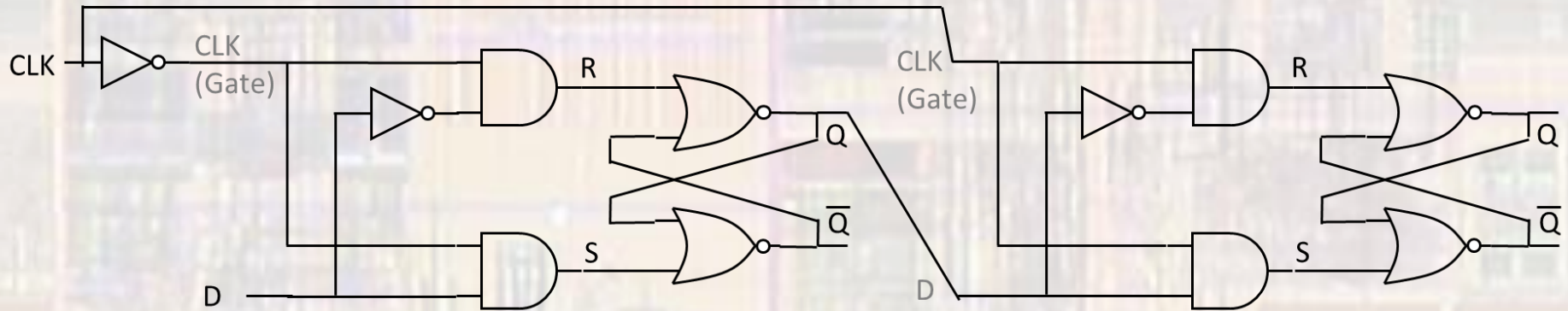 


# Flip-Flop Timing

- D Flip-Flop -  $T_{CQ}$

  


# Flip-Flop Timing

- D Flip-Flop -  $T_{CQ}$

 


clk low – DC state

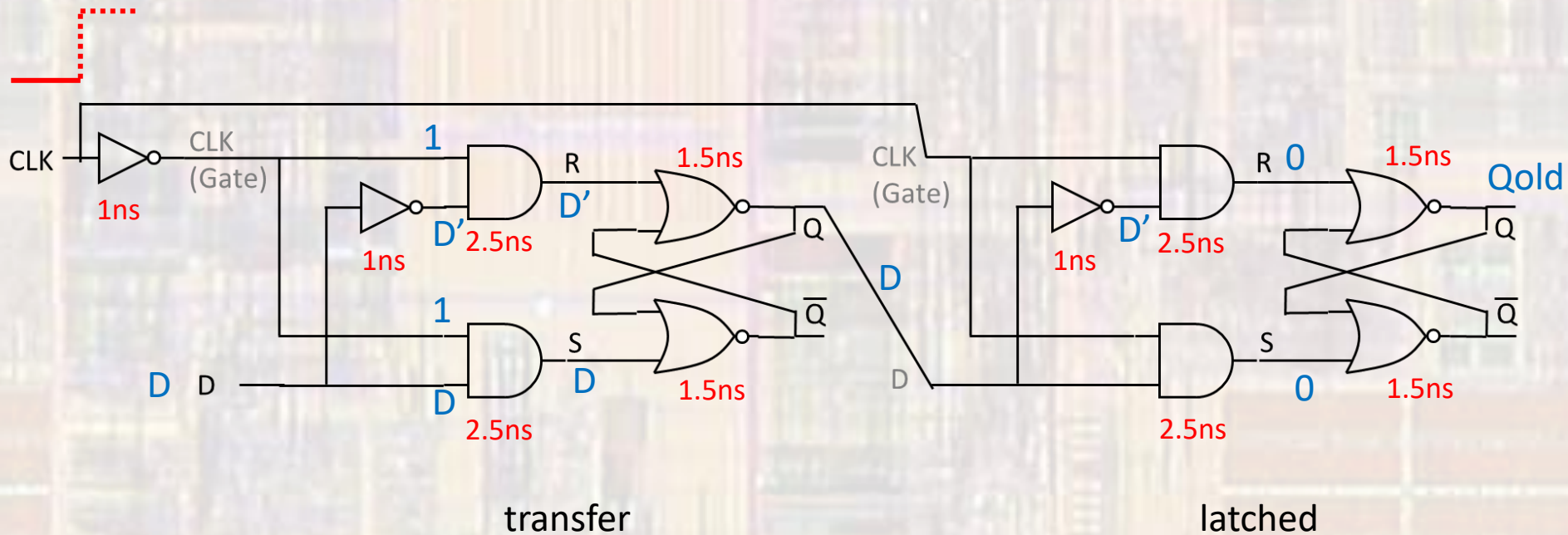


# Flip-Flop Timing

- D Flip-Flop -  $T_{CQ}$

 


$t = 0$  at clock edge

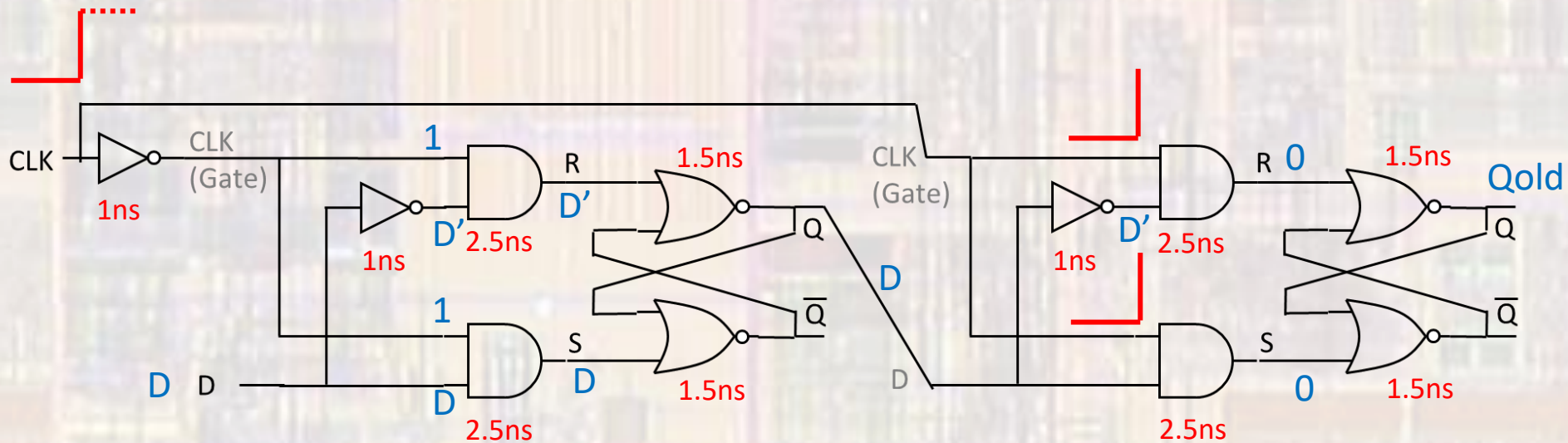




# Flip-Flop Timing

- D Flip-Flop -  $T_{CQ}$

 


After 1 ns

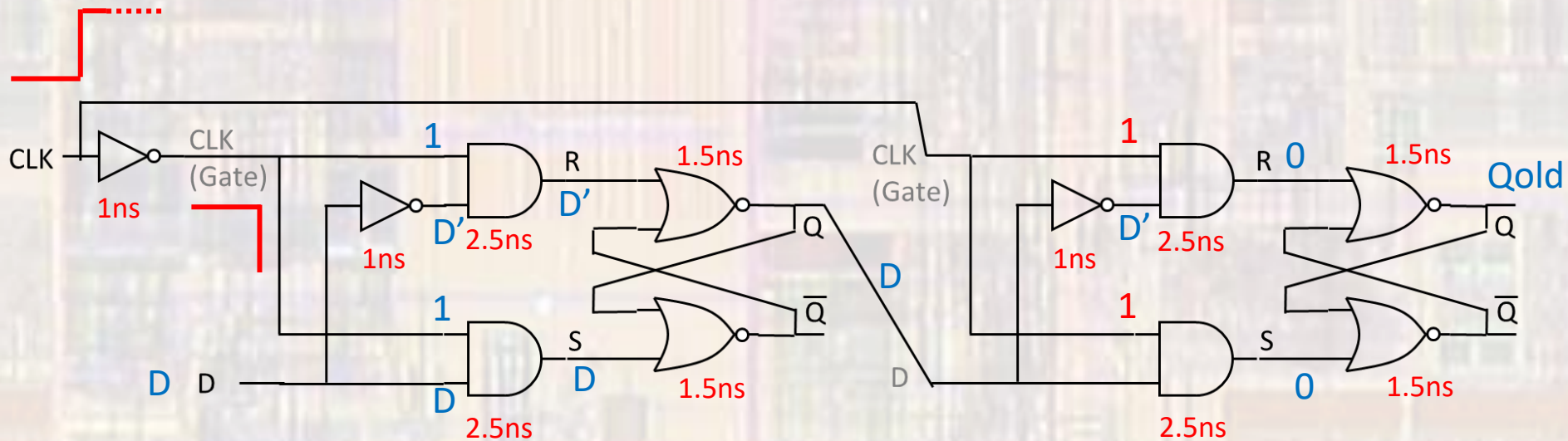


# Flip-Flop Timing

- D Flip-Flop -  $T_{CQ}$

 


After 2.5 ns

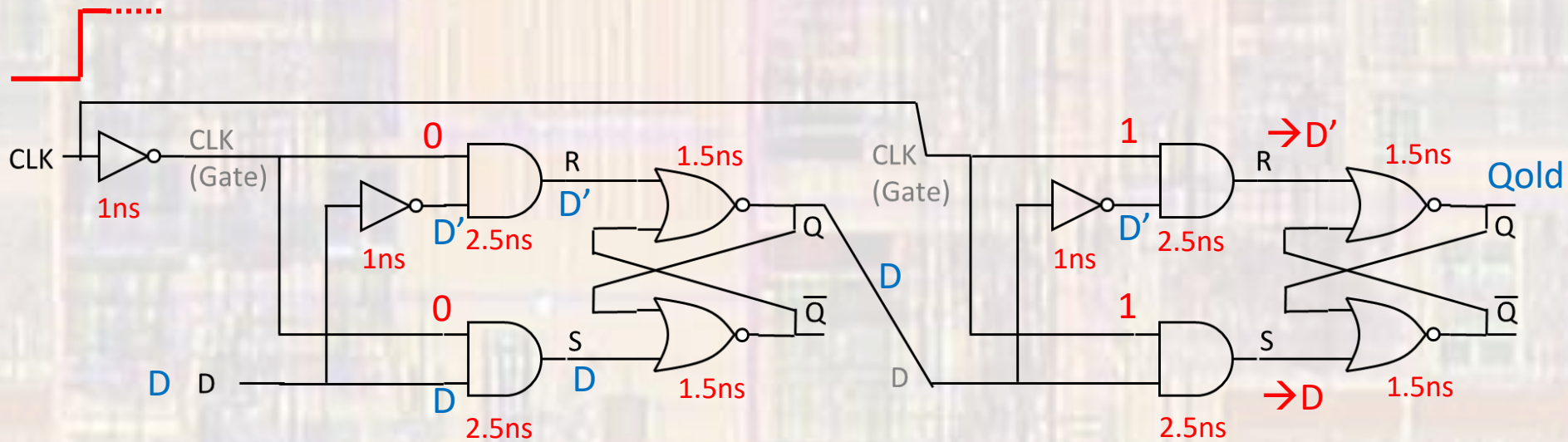


# Flip-Flop Timing

- D Flip-Flop -  $T_{CQ}$

 


After 3.5 ns

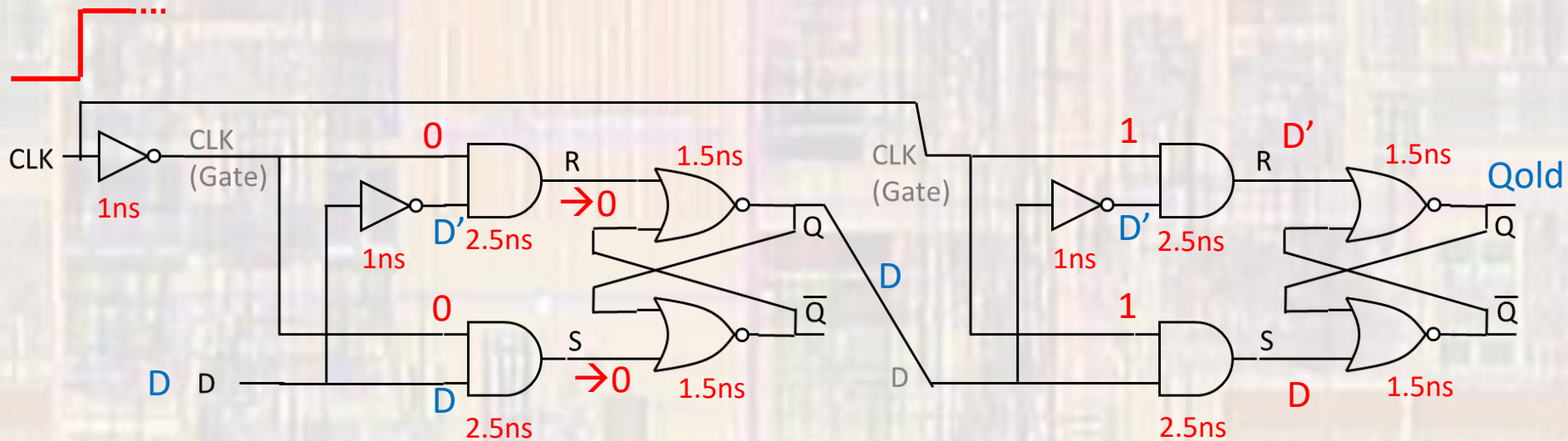


# Flip-Flop Timing

- D Flip-Flop -  $T_{CQ}$

 


$T_{CQ} = 4\text{ns}$   
 Q changes here  
 but A is not latched yet

After 4 ns

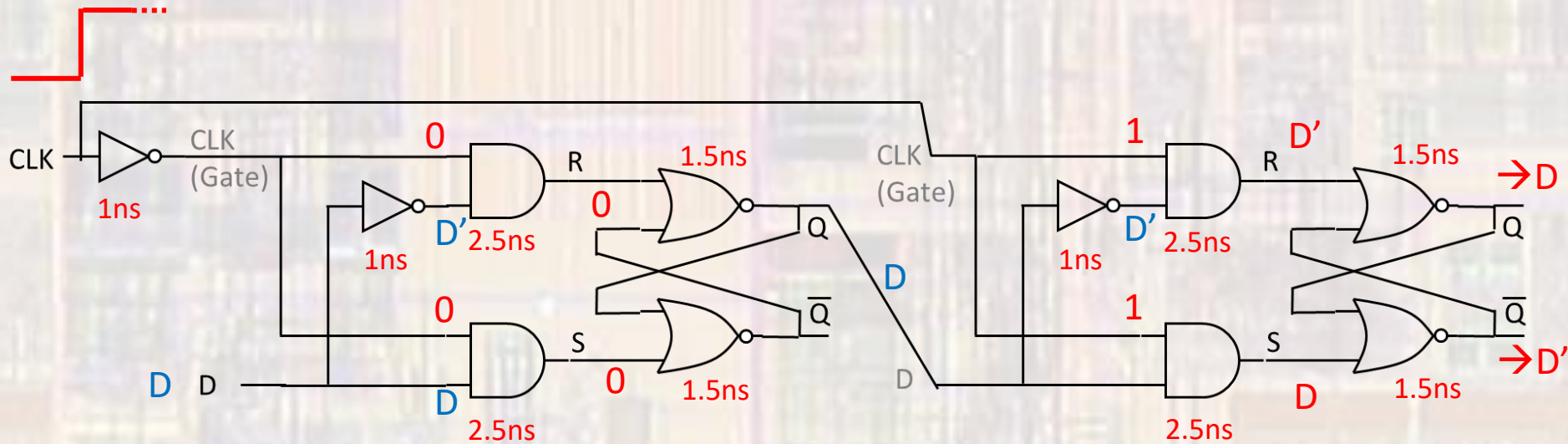


# Flip-Flop Timing

- D Flip-Flop -  $T_{CQ}$

 


After 5 ns

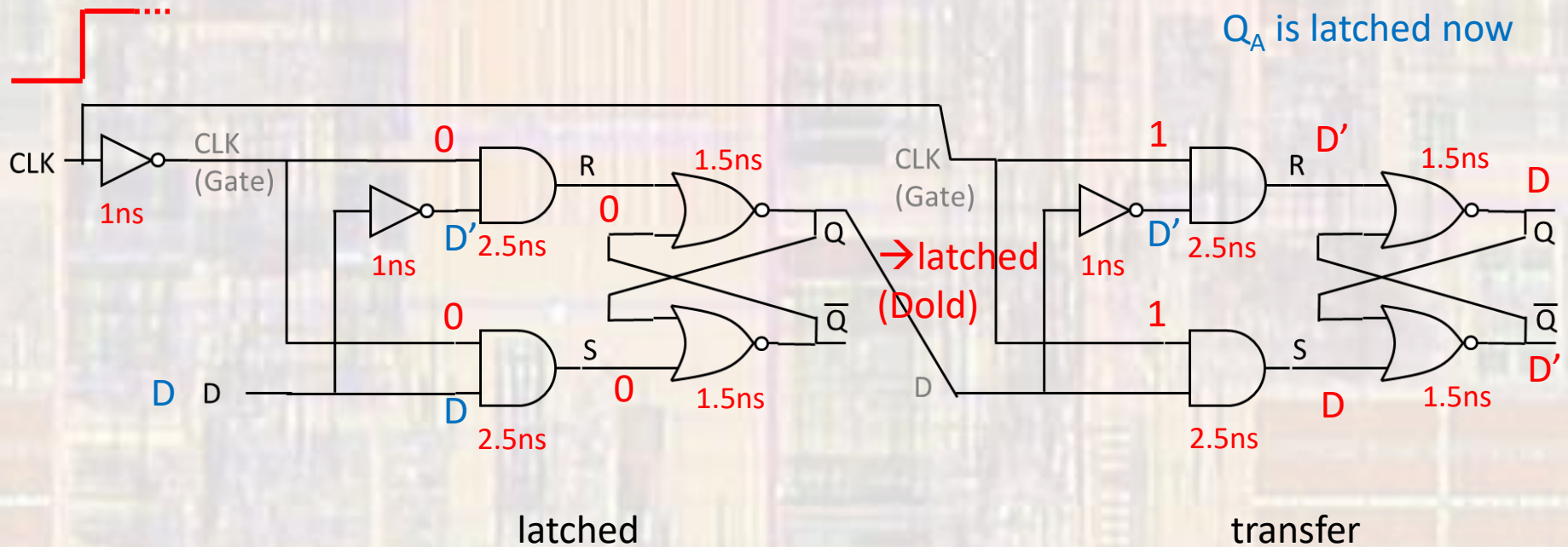

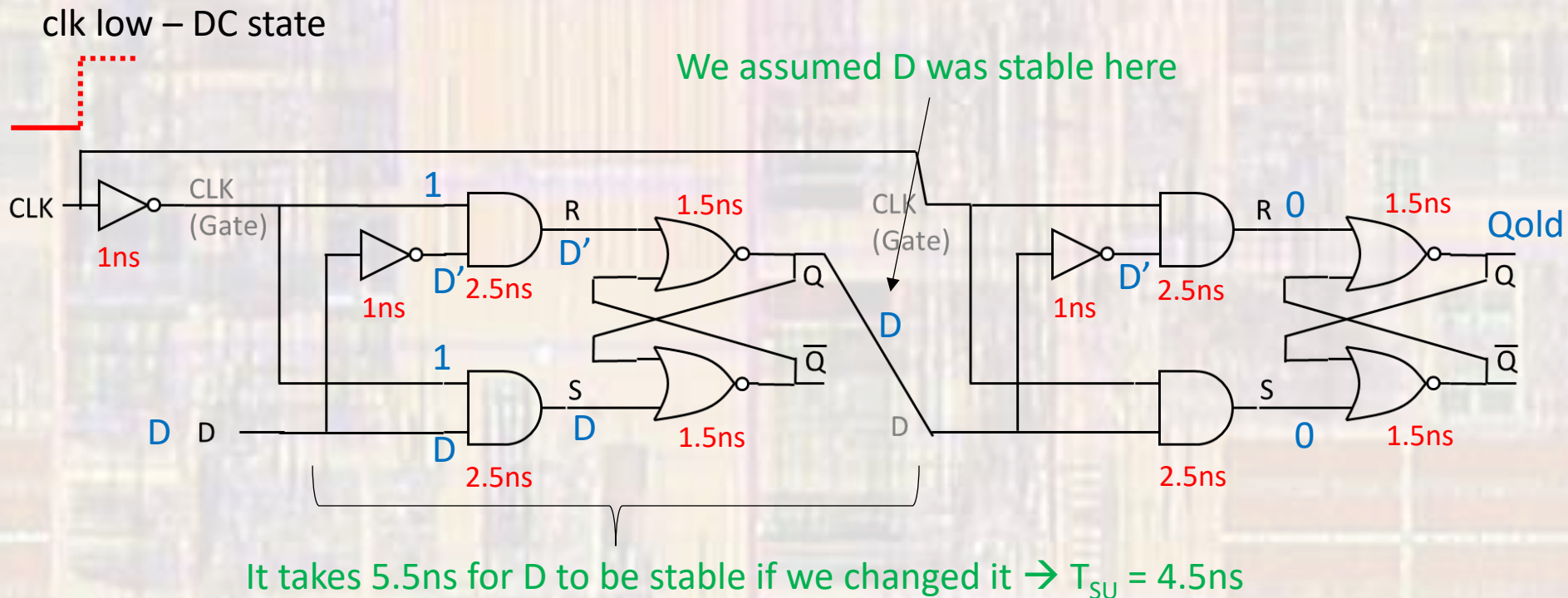
# Flip-Flop Timing

- D Flip-Flop –  $T_{SU}$ 
  - Time D must be stable before the clock edge
  - Not as bad as this would indicate (more analysis required)
    - Typically,  $T_{SU}$  is small compared to  $T_{CQ}$




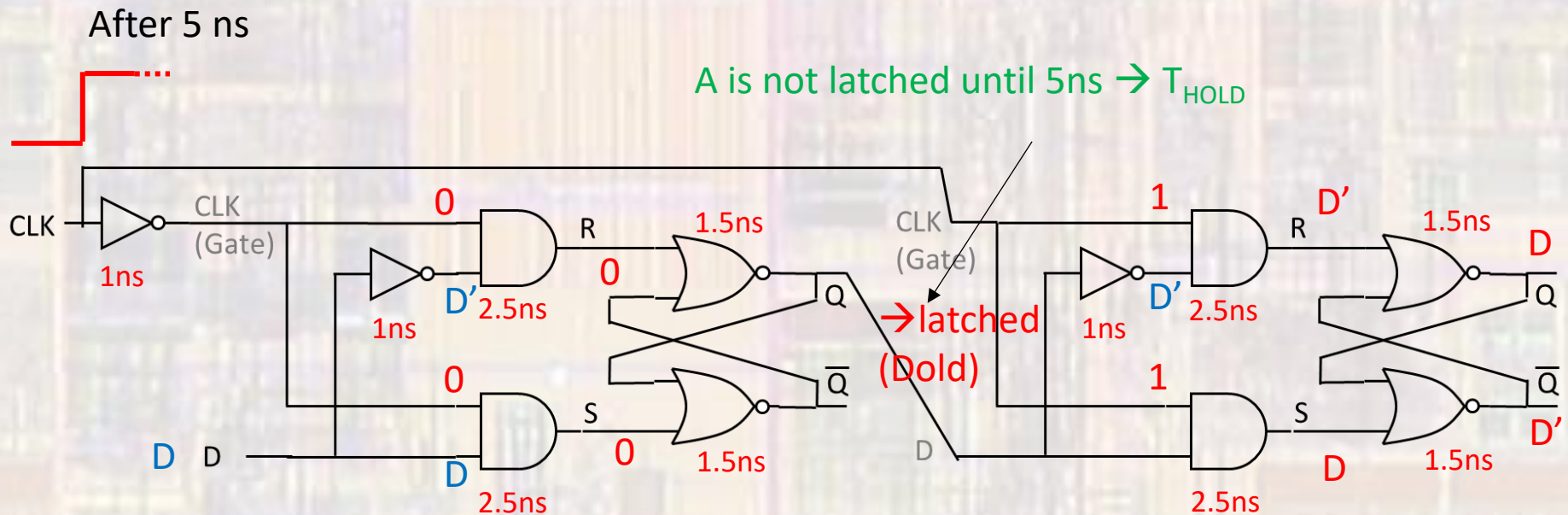
# Flip-Flop Timing

- D Flip-Flop –  $T_{\text{HOLD}}$ 
  - Time D must remain stable after the clock edge
  - Not as bad as this would indicate (more analysis required)
    - Typically,  $T_{\text{HOLD}}$  is designed to be 0ns



# Flip-Flop Timing


- D Flip-Flop –  $T_{cQ}$

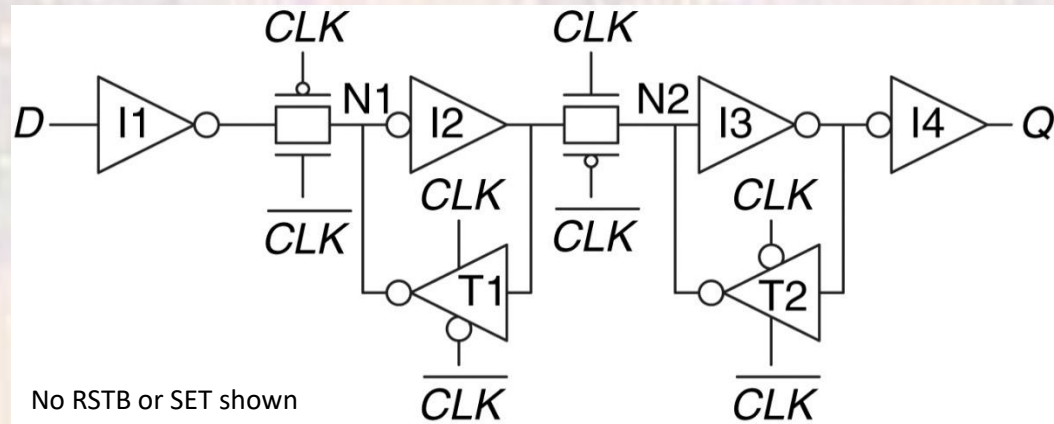 

- Propagation Delays

- Clk to Q
- Clk to QB
- RSTB to Q
- SET to Q



...

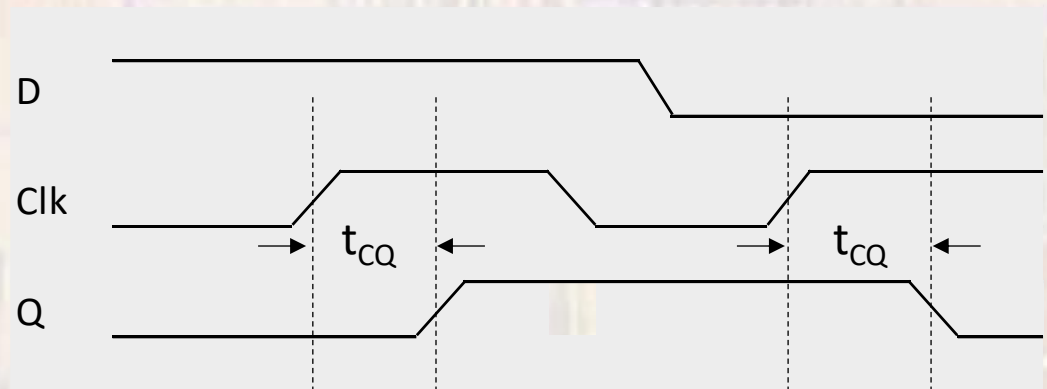



# Flip-Flop Timing

- D Flip-Flop –  $T_{SU}$
- Data changes before Clk  $\uparrow$

  

case 1





Proper operation requires the data to be stable for some amount of time before the clock rises  $\rightarrow$  SETUP TIME

Input is ready for second latch


Input is supported by feedback

# Flip-Flop Timing

- D Flip-Flop –  $T_{SU}$
- Data changes before Clk  $\uparrow$

 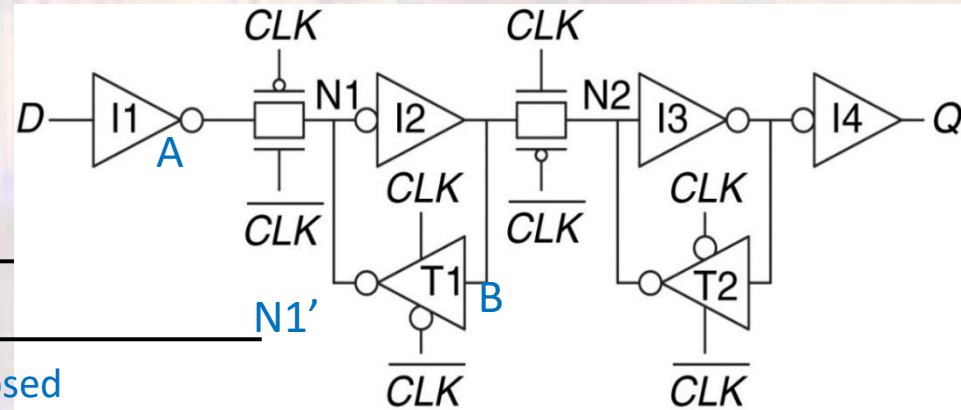

case 2


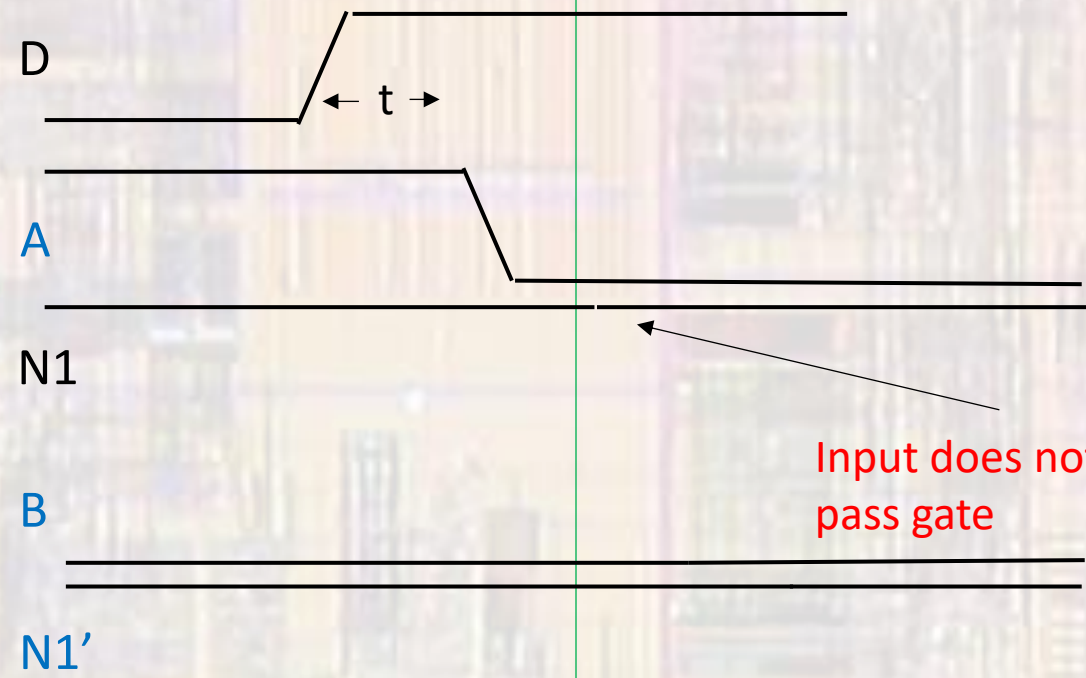


Proper operation requires the data to be stable for some amount of time before the clock rises  $\rightarrow$  SETUP TIME

Input does not make it through the pass gate

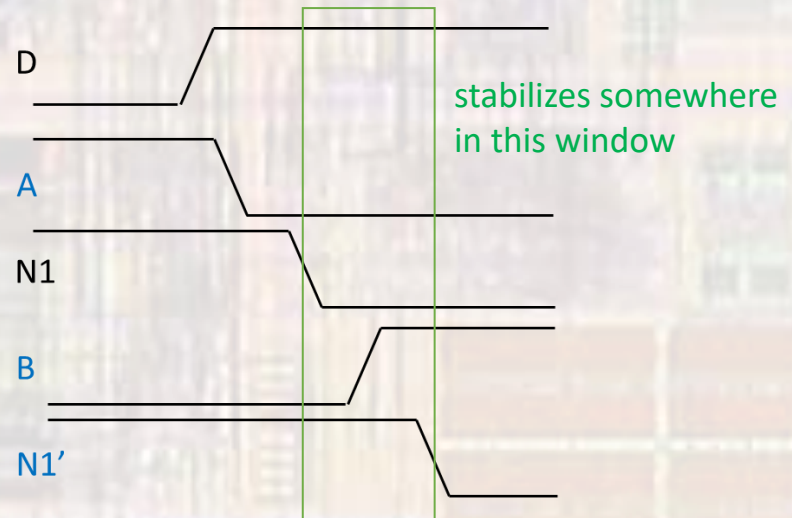
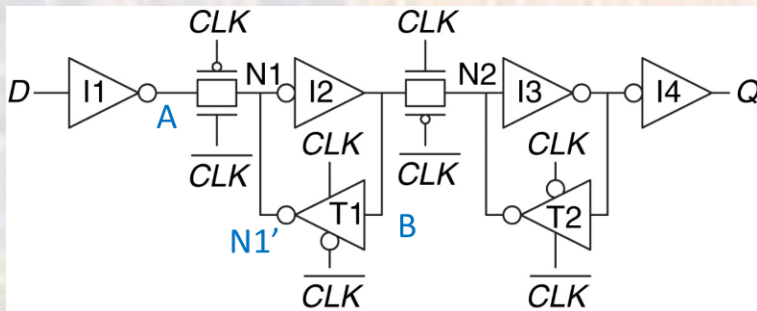
# Flip-Flop Timing

- D Flip-Flop –  $T_{SU}$ 
  - Setup
  - Consider changing D just **before** the rising edge of clock
    - At a minimum requires the new value to get to N1 before the first pass-gate closes
    - May require as long as it takes for N1' to transition
    - → minimum **SETUP** time (data stable before rising clock edge)
    - Established by detailed analysis or characterization



# Flip-Flop Timing

- D Flip-Flop –  $T_{\text{HOLD}}$
- Data changes after Clk  $\uparrow$

 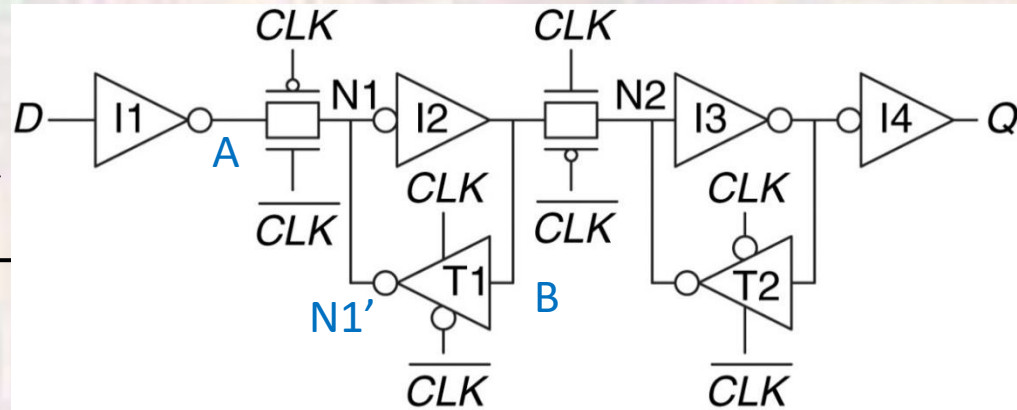


case 1



New data gets through even though it changed after the clock

case 2


 


New data is blocked

Proper operation requires the data to stay stable for some amount of time after the clock rises  $\rightarrow$  HOLD TIME

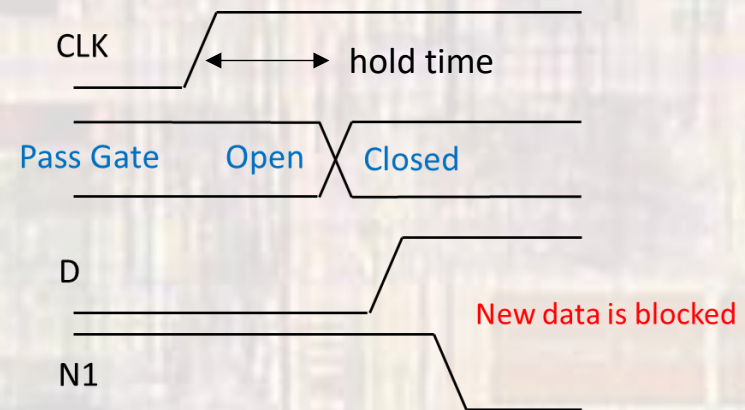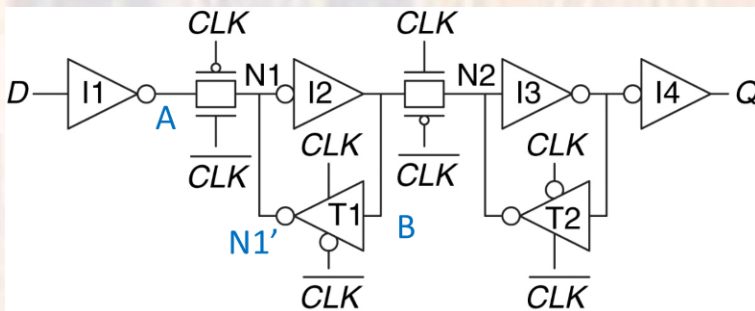
# Flip-Flop Timing

- D Flip-Flop –  $T_{\text{HOLD}}$ 
  - Hold
  - Consider changing D just **after** the rising edge of clock
    - Data must stay constant until the pass gate closes
    - → minimum **HOLD** time (data stable after rising clock edge)
    - Note – front end inverter delay complicates this analysis
      - $T_{\text{inv}} > T_{\text{pass gate}} \rightarrow T_{\text{hold}} < 0$
    - Established by detailed analysis or characterization



# Flip-Flop Timing

- D Flip-Flop

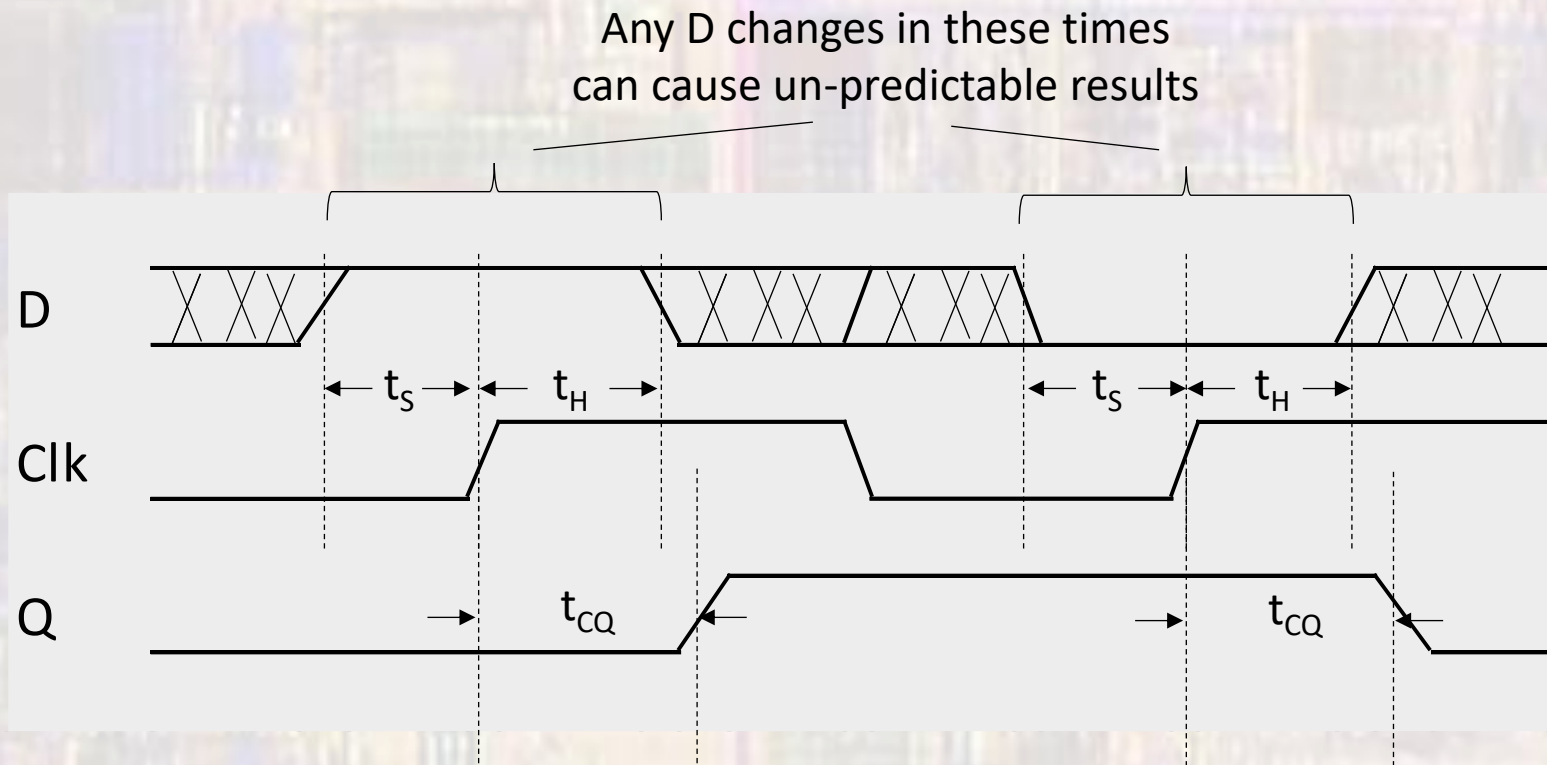

# Flip-Flop Timing

- Flip-Flop Timing
  - Other topologies may require different analysis for setup and hold requirements
  - Most designs have a positive setup time and a 0 or negative hold time
    - This allows synchronous system design

# Flip-Flop Timing

- CD4013B – CMOS D-FF

## 6.6 Electrical Characteristics: Dynamic

at  $T_A = 25^\circ\text{C}$ , input  $t_r, t_f = 20\text{ ns}$ ,  $C_L = 50\text{ pF}$ ,  $R_L = 20\text{ k}\Omega$  (unless otherwise noted)

| PARAMETER                |  | TEST CONDITIONS      | MIN | TYP | MAX | UNIT |
|--------------------------|--|----------------------|-----|-----|-----|------|
| $t_{PHL}$ ,<br>$t_{PLH}$ | Propagation delay time,<br>clock to Q or $\bar{Q}$ outputs | $V_{DD} = 5$         |     | 150 | 300 | ns   |
|                          |  | $V_{DD} = 10$        |     | 65  | 130 |      |
|                          |  | $V_{DD} = 15$        |     | 45  | 90  |      |
| $t_{PLH}$                | Set to Q or reset to $\bar{Q}$                             | $V_{DD} = 5$         |     | 150 | 300 | ns   |
|                          |  | $V_{DD} = 10$        |     | 65  | 130 |      |
|                          |  | $V_{DD} = 15$        |     | 45  | 90  |      |
| $t_{PHL}$                | Set to $\bar{Q}$ or reset to Q                             | $V_{DD} = 5$         |     | 200 | 400 | ns   |
|                          |  | $V_{DD} = 10$        |     | 85  | 170 |      |
|                          |  | $V_{DD} = 15$        |     | 60  | 120 |      |
| $t_{THL}$ ,<br>$t_{TLH}$ | Transition time  | $V_{DD} = 5$         |     | 100 | 200 | ns   |
|                          |  | $V_{DD} = 10$        |     | 50  | 100 |      |
|                          |  | $V_{DD} = 15$        |     | 40  | 80  |      |
| $f_{CL}$                 | Maximum clock input frequency <sup>(1)</sup>               | $V_{DD} = 5$         | 3.5 | 7   |     | MHz  |
|                          |  | $V_{DD} = 10$        | 8   | 16  |     |      |
|                          |  | $V_{DD} = 15$        | 12  | 24  |     |      |
| $t_w$                    | Minimum clock pulse width                                  | $V_{DD} = 5$         |     | 70  | 140 | ns   |
|                          |  | $V_{DD} = 10$        |     | 30  | 60  |      |
|                          |  | $V_{DD} = 15$        |     | 20  | 40  |      |
|                          | Minimum set or reset pulse width                           | $V_{DD} = 5$         |     | 90  | 180 | ns   |
|                          |  | $V_{DD} = 10$        |     | 40  | 80  |      |
|                          |  | $V_{DD} = 15$        |     | 25  | 50  |      |
| $t_S$                    | Minimum data setup time                                    | $V_{DD} = 5$         |     | 20  | 40  | ns   |
|                          |  | $V_{DD} = 10$        |     | 10  | 20  |      |
|                          |  | $V_{DD} = 15$        |     | 7   | 15  |      |
| $t_H$                    | Minimum data hold time                                     | $V_{DD} = 5, 10, 15$ |     | 2   | 5   | ns   |



# Flip-Flop Timing

- D Flip-Flop

