


Gate Level Signal Diagrams

Last updated 10/16/24

These slides show how to draw signal diagrams from gate schematics


Gate Level Signal Diagrams

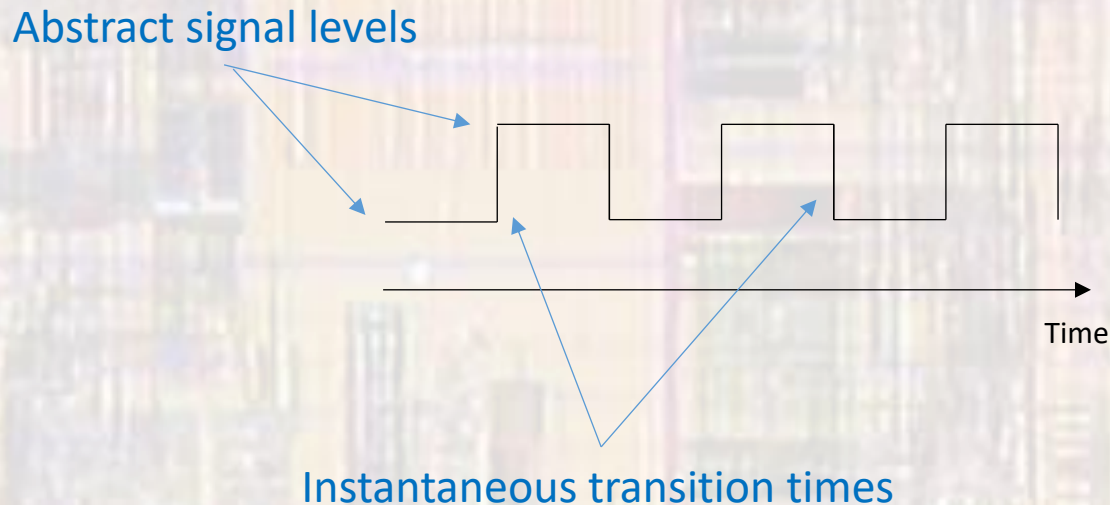- Signal Diagram
 - A simplified drawing of time domain signal changes
 - Abstract signal levels – 0 or 1
 - Could represent any VDD
 - Instantaneous transition times
 - t_{0s} , t_{0us} , t_{0ns} , t_{0ps}



Gate Level Signal Diagrams

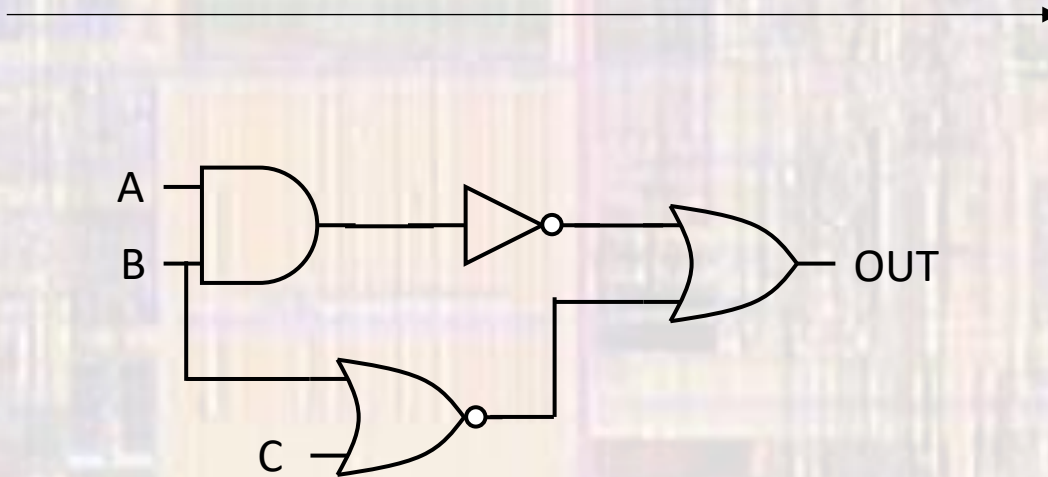- Circuits are evaluated from input to output when creating signal diagrams





Gate Level Signal Diagrams

- Signal Diagram Creation

- Process

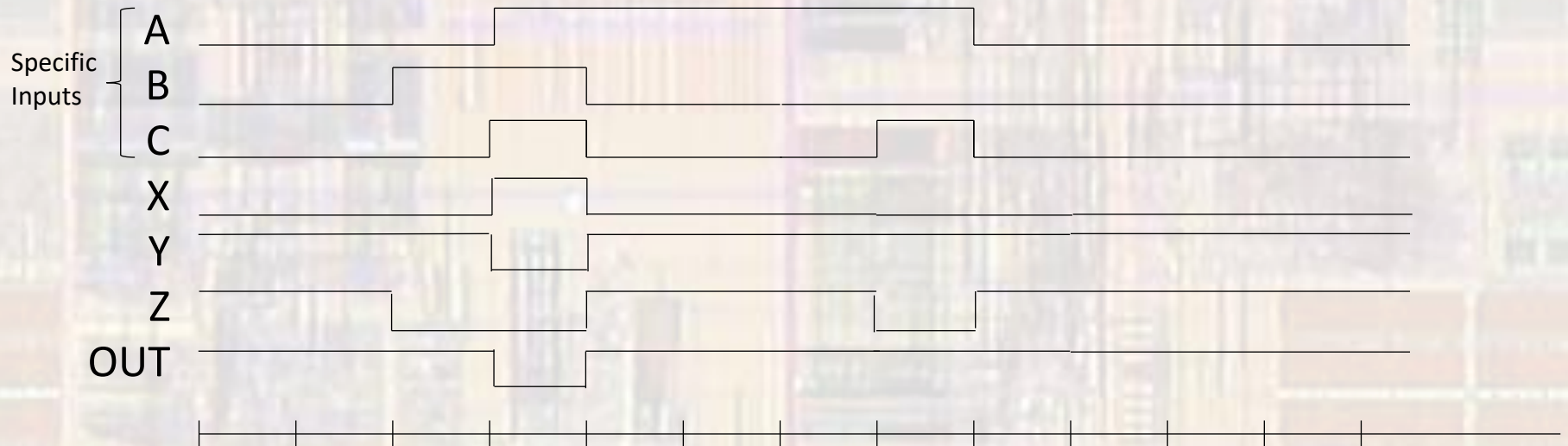 1. Label all intermediate nodes
2. Create a horizontal section for each signal on the diagram
3. Create a time scale at the bottom of the diagram
4. Fill in the input signals
5. Fill in each intermediate signal until the output signal is complete



Gate Level Signal Diagrams

- Signal Diagram Creation

- Process

1. Label all intermediate nodes
2. Create a horizontal section for each signal on the diagram
3. Create a time scale at the bottom of the diagram
4. Fill in the input signals
5. Fill in each intermediate signal until the output signal is complete

