


Wire VinA, VinB, and VinC directly to 0V or 5V

Make a table for each combination of VinA, VinB, VinC and indicate if the diode is on or off

VinA	VinB	VinC	LED(on or off)
0	0	0	
0	0	5	
0	5	0	
0	5	5	
5	0	0	
5	0	5	
5	5	0	
5	5	5	

	Title: Lab1_LED_Or	
	Desc.: LED Or gate circuit for use with AD2 in Lab1 - P3	
	Designed by: tj	Revision:
	Date: 12/16/2024	Size: A
	Sheet 1 of 1	