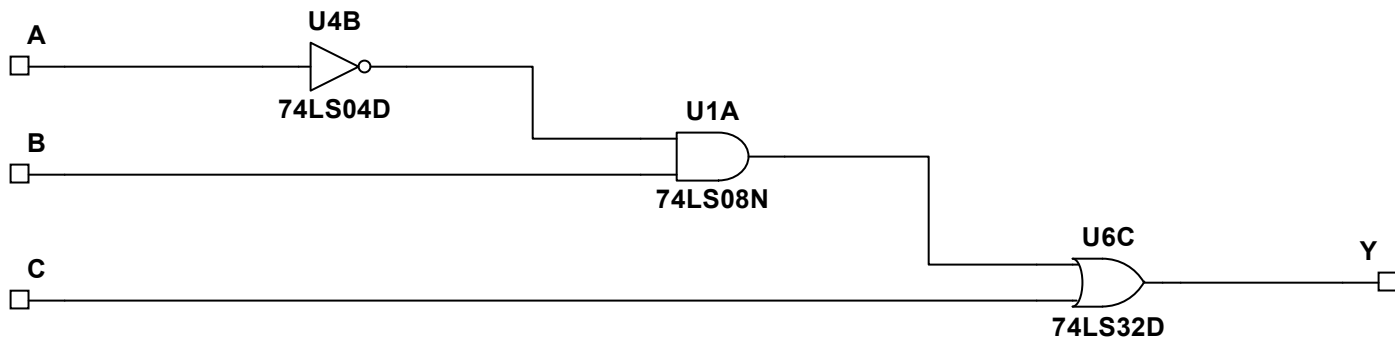


A

A

MSB



B

B




C

C

LSB

D

D

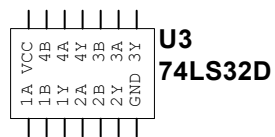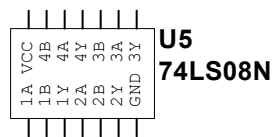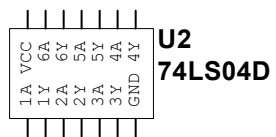

E

E


VCC and all signals are 0V - 5V

F

F

G

G

	Title: Lab3_Prime	
	Desc.: Prime number detector for Lab3_P2	
	Designed by: tj	Revision:
	Date: 12/17/2024	Size: A
Sheet 1 of 1		