

CPE 1500 Lab 1: Tool Setup and AD2 Usage

1 dedicated lab period, 1 lab period to complete

Objectives

- Setup Quartus software
- Setup AD2 Software
- Practice using the AD2 and a breadboard

Prelab

Seek help before the lab if you have any problems with these

- Quartus Download and Installation
- AD2 Waveforms installation
- Prewire your breadboard power/gnd crossover

student
check off

Assignment

Part 1: **Build the Resistor divider circuit from the [Lab1 Resistor Divider](#) schematic**

Use the AD2 to power the circuit at 0.5V increments from 1V to 3.5V

Measure the output voltage

Create a table of your results

Part 2: **Build the Resistor-Capacitor circuit from the [Lab1 Resistor Capacitor](#) schematic**

Use the AD2 to create a 20ms, 50% duty cycle, 0 - 3.3V square wave for v_{in}

Measure the output voltage using the oscilloscope on the AD2

Plot (print) V_{out} for 2 full periods

Part 3: **Build the LED Or circuit from the [Lab1 LED Or](#) schematic**

Hand wire the inputs to GND or 5V according to the table on the schematic

Complete the table with the LED On/Off results

Check Off

- Pework Checkoff 20%

You must demonstrate parts 1, 2, and 3 prior to submission of your report

- Demo part 1 results and informal report 25%
- Demo part 2 results and informal report 25%
- Demo part 3 results and informal report 30%

Due at 3:00pm on Tuesday following the lab period – in the box