

# CPE 1500 Lab 4: Integrated Circuits Parametrics

1 dedicated lab period, 1 lab period to complete

## Objectives

- Measure VOL, VOH
- Measure delays,  $t_{pdr}$  and  $t_{pdf}$
- Measure VIL, VIH

## Prelab

- Review the [Common Waveform Measurements](#) slides

student  
check off

## Assignment

Common Settings:  $V_{DD} = V_{CC} = 5V$

### Part 1: $V_{OH}$ , $V_{OL}$ measurements

#### A. Wire up a 74LS08 AND gate

Tie both inputs to Gnd

Using the AD2 – measure the output voltage

Tie both inputs to  $V_{CC}$

Using the AD2 – measure the output voltage

#### B. Repeat part A with a CD4081 AND gate

### Part 2: Delay measurements

#### A. Wire up 2, 74LS08 AND gates in series

Tie one input of each to  $V_{CC}$

Using the AD2 – measure the gate delay through the 2 gates

Be sure to measure  $t_{pdr}$  and  $t_{pdf}$

#### B. Repeat part A with a CD4081 AND gate

### Part 3: $V_{IL}$ , $V_{IH}$

#### A. Wire up a single 74LS08 AND gate

Tie both inputs together

Keep the supply set to 5V

Raise the input low value until the AND gate fails

Lower the input high value until the AND gate fails

#### B. Repeat with a single CD4081 AND gate

For all 3 parts: Document your results and compare them to the specifications

## Check Off

You must demonstrate **part 2B** prior to submission of your report

- Part 1B results and full part 1 informal report 30%
- Demo part 2B results and full part 2 informal report 40%
- Part 3 results and full part 3 informal report 30%

**Due at 3:00pm on Tuesday following the lab period – in the box**