
 
 


Latches


Last updated 11/12/24

Latches



- Shortcuts

 

0


 


1

  

Latches

 
 
- Bi-stable circuit
 - Sequential Circuit ?
 - Circuit with 2 stable operating points
 - Holds 1 element of memory
 - 1 state variable
 - 2 values for the state variable
 - 1 bit – 0 or 1



state variable	
State	A
0	0
1	1
state variable	
State	Q
0	0
1	1
	\bar{Q}
0	1
1	0

Latches

  - Bi-stable circuit
 - Sequential Circuit ?
 - Circuit with 2 stable operating points
 - Holds 1 element of memory
 - 1 state variable
 - 2 values for the state variable
 - 1 bit – 0 or 1




What's wrong with this circuit

state variable	
State	A
0	0
1	1

state variable	
State	Q
0	0
1	1

Latches

 - SR Latch (set/reset)
 - Asynchronous Sequential Circuit
 - Sequential - Output depends on Inputs and 1 state variable Q (Q_{old})
 - Asynchronous – output changes occur when inputs change
 - Memory is in the bi-stable latch




R : Reset

S : Set

Latches

- SR Latch (set/reset)
 - 0,0 Inputs

 


S	R	Q
0	0	Q_{old}

Latch

Latches

- SR Latch (set/reset)

- 0,1 Inputs

 


S	R	Q
0	0	Q_{old}
0	1	0

Reset

Latches

- SR Latch (set/reset)

- 1,0 Inputs

 


Set

S	R	Q
0	0	Q_{old}
0	1	0
1	0	1

Latches

- SR Latch (set/reset)

- 1,1 Inputs


 


S	R	Q
0	0	Q_{old}
0	1	0
1	0	1
1	1	0

Fault?

Latches


- SR Latch (set/reset)

  

S	R	Q
0	0	Q_{old}
0	1	0
1	0	1
1	1	0

Latches

 
- D Latch (data)
 - Asynchronous Sequential Circuit
 - Sequential - Output depends on Inputs and 1 state variable Q (Q_{old})
 - Asynchronous – output changes occur when inputs change
 - Memory is in the bi-stable latch




Latches

- D Latch (data)

- 0,0 inputs – control (CTRL), data (D)

 


CTRL	D	Q
0	0	Q_{old}

 


Latches

- D Latch (data)

- 0,1 inputs – control, data

 


CTRL	D	Q
0	0	Q_{old}
0	1	\bar{Q}_{old}

 


Latches

- D Latch (data)

- 1,0 inputs – control, data

 


CTRL	D	Q
0	0	Q_{old}
0	1	Q_{old}
1	0	0 (D)

 


Latches

- D Latch (data)

- 1,1 inputs – control, data

 

CTRL	D	Q
0	0	Q_{old}
0	1	Q_{old}
1	0	0 (D)
1	1	1 (D)




 


Latches

- D Latch (data)

Level Sensitive Latch

 
 
 
 
CTRL = low \rightarrow latched
CTRL = high \rightarrow Transfer



CTRL	D	Q
0	x	Q_{old}
1	D	D

Latches

    
- D Latch (data)
 - Control input: Clk(clock), G (gate), En (enable)



CTRL	D	Q
0	x	Q_{old}
1	D	D

Latches

- D Latch - Abstraction

 

CTRL	D	Q
0	x	Q_{old}
1	D	D