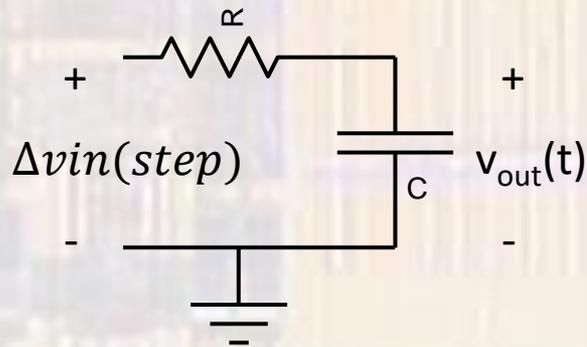


RC Circuits

Last updated 1/6/25

RC Circuits

- RC Configuration
 - Step inputs - transient
 - $R \cdot C \equiv RC$ product \equiv time constant $\equiv \tau$ (tau)




$$v_{out}(t) = v_{final} + (v_{initial} - v_{final})e^{\frac{-t}{RC}}$$


$$v_{out}(t) = v_{final} + (v_{initial} - v_{final})e^{\frac{-t}{\tau}}$$

RC Circuits

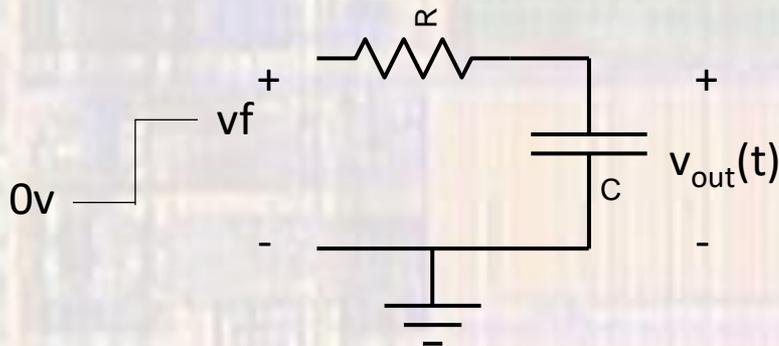- RC Response
 - Step up in voltage - charging



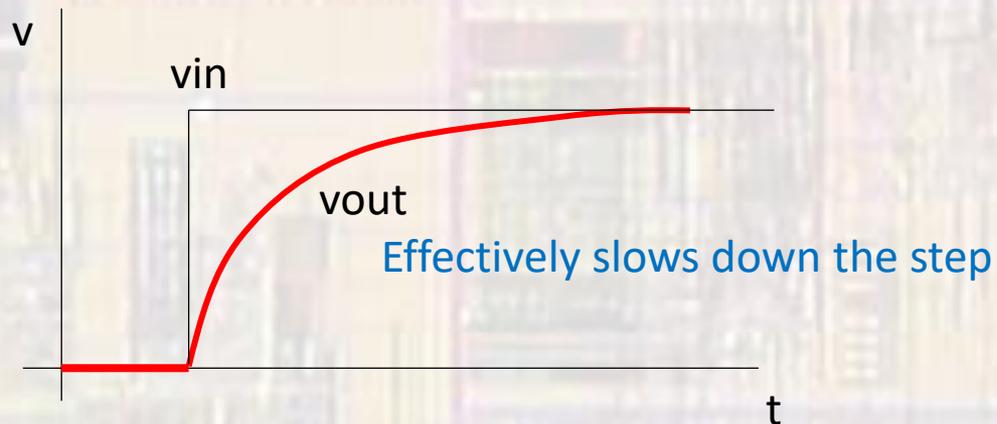
$$v_{out}(t) = v_f(1 - e^{\frac{-t}{RC}})$$




RC Circuits

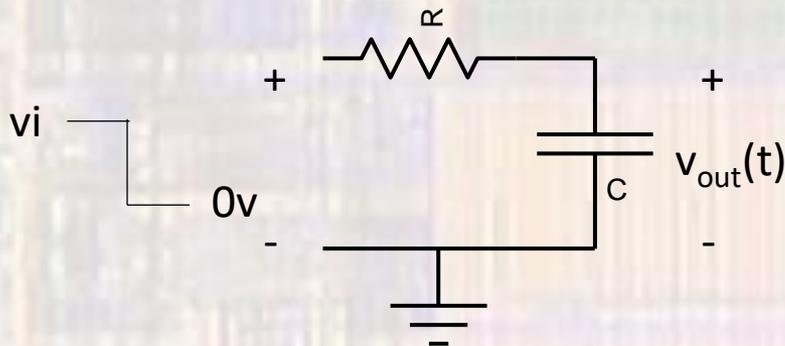- RC Response
 - Step down in voltage - discharging




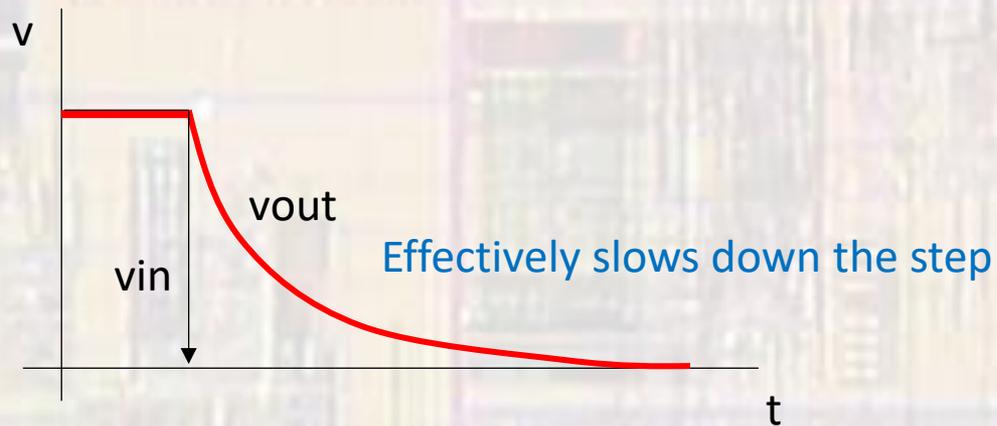
$$v_{out}(t) = v_i e^{\left(\frac{-t}{RC}\right)}$$





RC Circuits

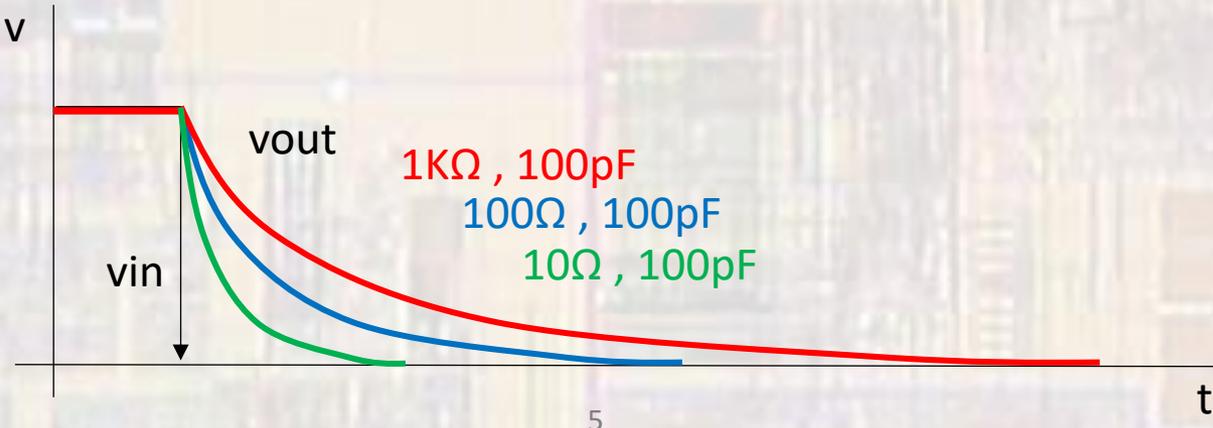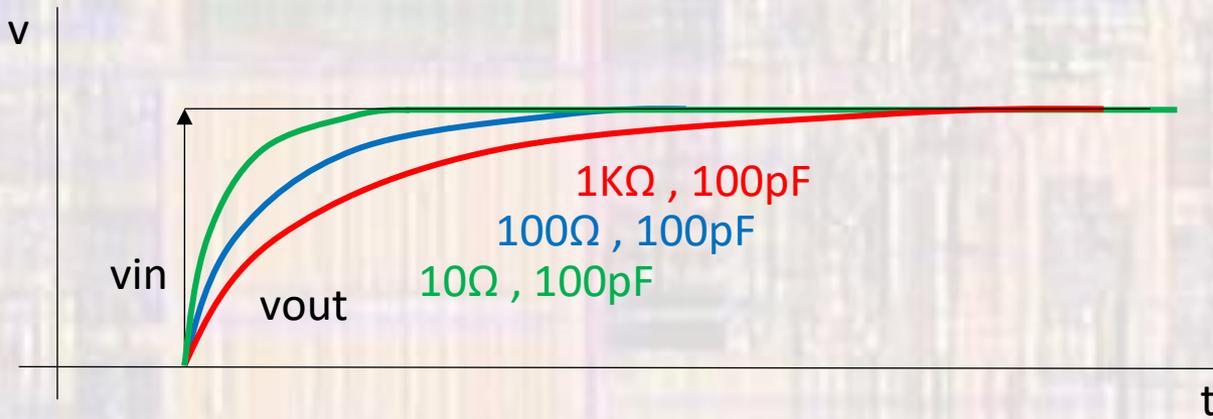- RC Response
 - RC time-constant impact
 - Increasing R, for a given C \rightarrow slower response



RC Circuits

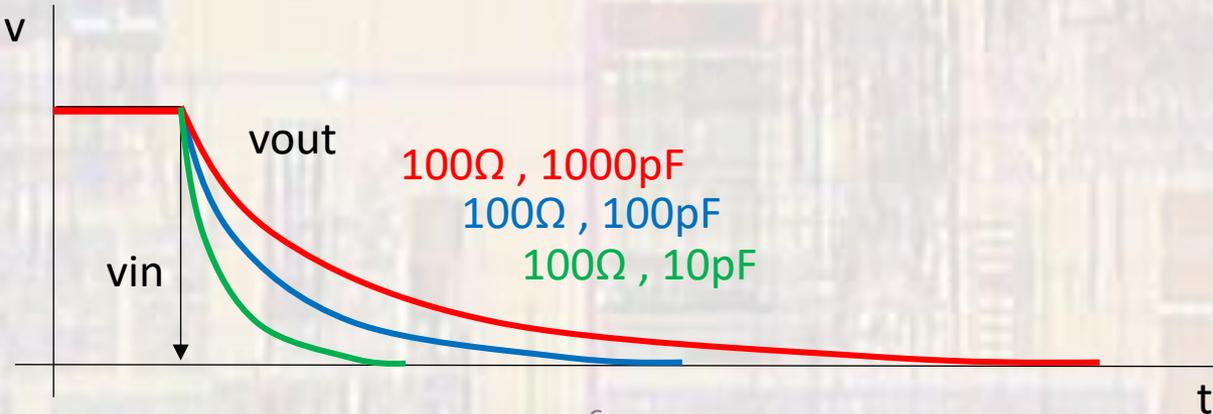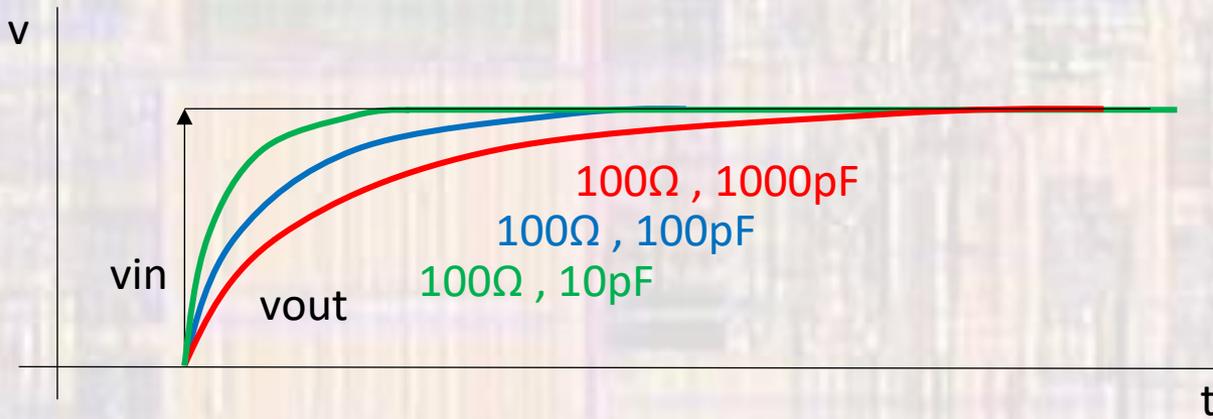- RC Response
 - RC time-constant impact
 - Increasing C , for a given $R \rightarrow$ slower response



RC Circuits

- RC Response
 - This was one of our digital signal abstractions

