


Registers

Last updated 1/9/25


Registers

- Data Register
 - Collection of n Flip-Flops
 - Configured in parallel
 - Common clock, set/reset, enable
 - Stores an n-bit state variable


n-bit register

 

n bit wide bus

 

signal indices n-1 down to 0

 

Registers


- Shift Register
 - Shift a series of bits within a register
 - Left/right
 - N bit shift
 - Wrapping (rotate)
 - Load register with load signal
 - Direction
- Non-wrapping
 - Data input – both sides
 - Direction

DATA	dir	load	Din	result
XXXXX	X	1	00100	00101
00101	R	0	XXXXX	10010
00101	L	0	XXXXX	01010

Din	DATA	dir	result
1	00100	R	10010
0	10010	R	01001
1	01001	L	10011

Registers

 - Shift Register
 - Non-wrapping, Data in (from both ends)
 - sel[0]: dir : right(1) / left(0)
 - sel[1]: shift: shift(1) / no-shift(0)



Registers

- Rotate Register
 - Wrapping, needs a load signal
 - SEL: 0 0 load
 - SEL: 0 1 Idle
 - SEL: 1 0 Shift left
 - SEL: 1 1 Shift right

