

# Resistor Circuits

Last updated 10/3/24

These slides review basic resistor circuits


# Resistor Circuits

- Resistor
  - Resists the flow of electrical current
  - Units: Ohms ( $\Omega$ )

Schematic Symbol



Physical

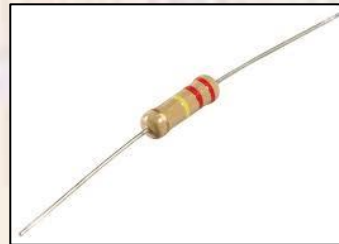

Leaded



Chip





# Resistor Circuits

- DC Circuit Characteristics

$$I = V / R$$

Amps = Volts / Ohms

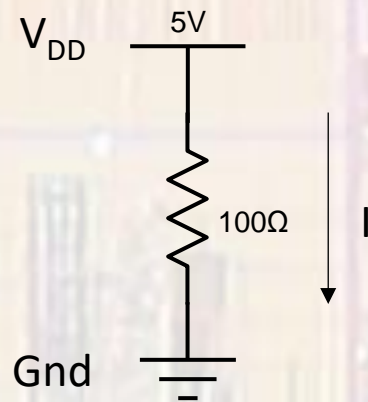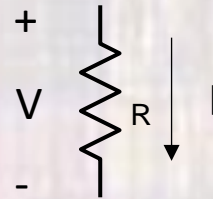

$$I = 5V / 100\Omega$$
$$I = 50\text{mA}$$

# Resistor Circuits


- Resistor Configurations

Series



$$R_{eq} = R1 + R2$$


Parallel

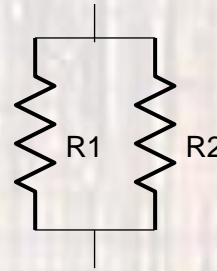

$$R_{eq} = 1/(1/R1 + 1/R2)$$

# Resistor Circuits

- Resistor Divider

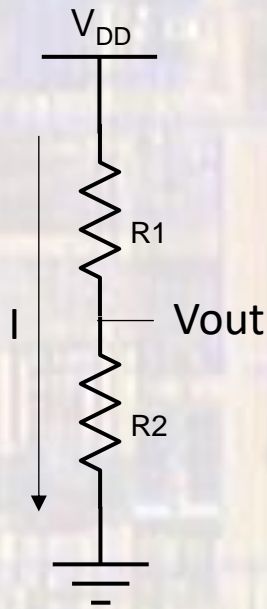


$$I = V_{DD} / (R1 + R2)$$

$$V_{out} = I * R2$$


$$V_{out} = V_{DD} \left( \frac{R2}{R1 + R2} \right)$$

# Resistor Circuits


- Pull-up / Pull-down Circuits

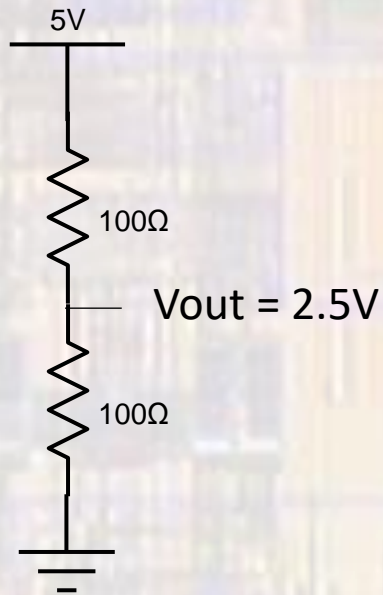

Divider

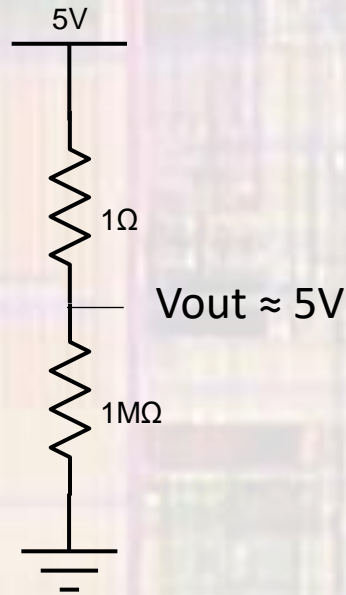

Pull-up

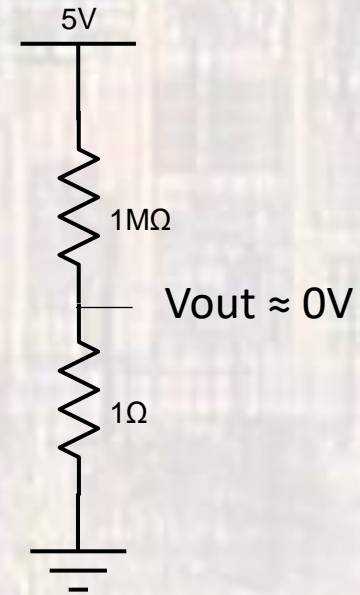

Pull-down