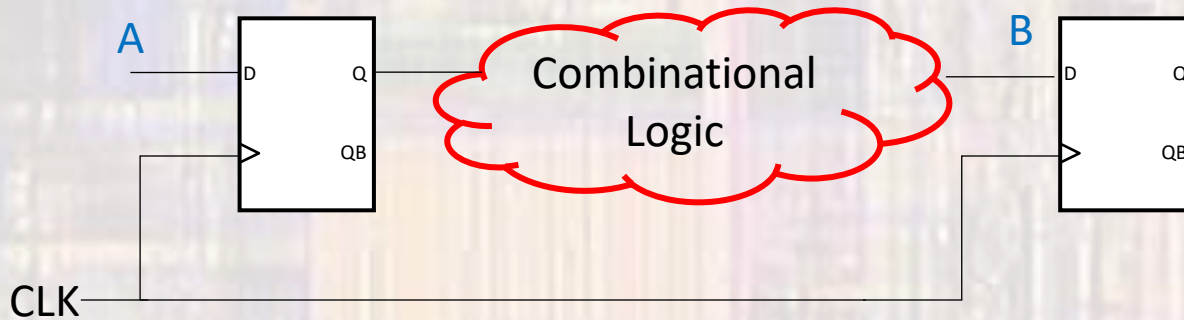


RTL Timing Analysis

Last updated 12/12/24

RTL Timing Analysis

- Typical Flip-Flop Circuit




- Need the data to get from point **A** to point **B** before the next clock edge occurs

RTL Timing Analysis

- Flip-Flop Example

- $t_{PD\ INV} = 10ps$
- $t_{CQ} = 22ps$
- $t_{setup} = 4ps$
- $t_{hold} = 2ps$

All values already account for loading

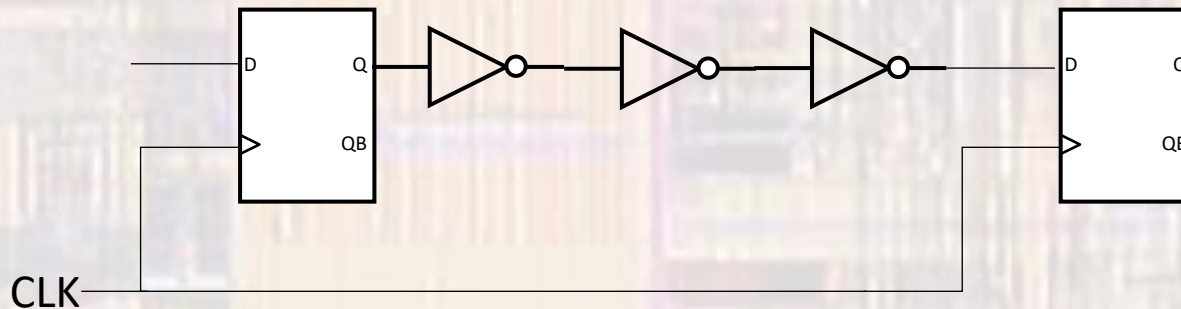


Shortest clock period = $t_{CQ} + t_{INV} + t_{INV} + t_{INV} + t_{setup} = 56ps$

Fastest clock speed = 17.857GHz

RTL Timing Analysis

- RTL Example

All values already account for loading

 

src: Harris & Harris

$$t_{CQ_min} = 30ps$$

$$t_{CQ_max} = 80ps$$

$$t_{setup} = 50ps$$

$$t_{hold} = 60ps$$



$$t_{pd_min} \text{ Logic} = 25ps$$

$$t_{pd_max} \text{ Logic} = 40ps$$

RTL Timing Analysis

- RTL Example – Critical Path

All values already account for loading

 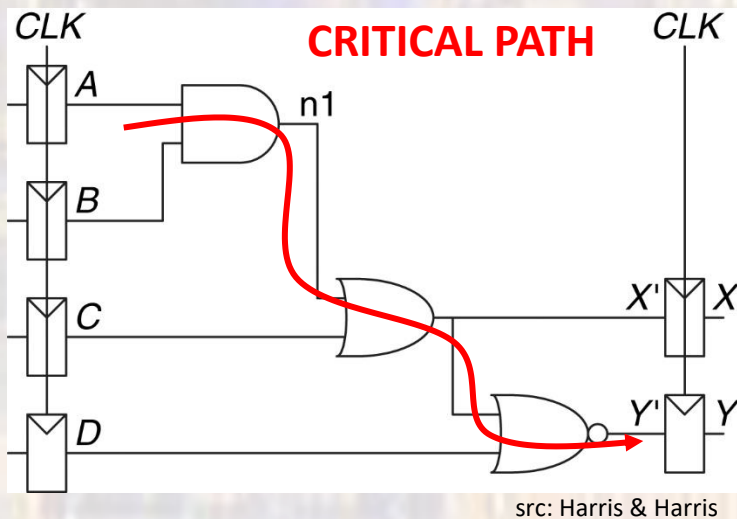

$$t_{CQ_min} = 30ps$$

$$t_{CQ_max} = 80ps$$

$$t_{setup} = 50ps$$

$$t_{hold} = 60ps$$

$$t_{pd_min} \text{ Logic} = 25ps$$

$$t_{pd_max} \text{ Logic} = 40ps$$

$$t_{crit} = t_{CQ_max} + 3 * t_{pd_max} + t_{setup}$$



$$t_{crit} = 80ps + 3 * 40ps + 50ps = 250ps$$

$$F_{max} = 1/250ps = 4GHz$$

RTL Timing Analysis

- RTL Example – Fast Path

All values already account for loading

 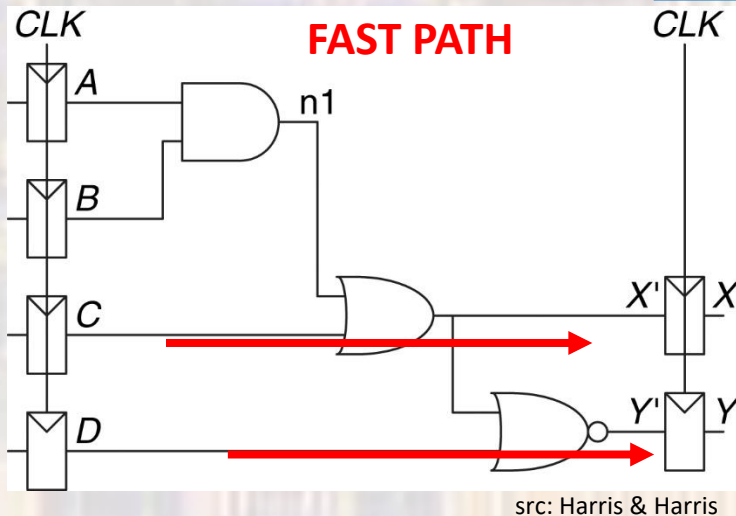

$$t_{CQ_min} = 30ps$$

$$t_{CQ_max} = 80ps$$

$$t_{setup} = 50ps$$

$$t_{hold} = 60ps$$

$$t_{pd_min} \text{ Logic} = 25ps$$

$$t_{pd_max} \text{ Logic} = 40ps$$

$$t'_{fast} = t_{CQ_min} + t_{pd_min}$$


$$t'_{fast} = 30ps + 25ps = 55ps$$

$$t'_{fast} < \text{hold time} \rightarrow \text{unpredictable output}$$


RTL Timing Analysis

- RTL Example – Fast Path - corrected

All values already account for loading

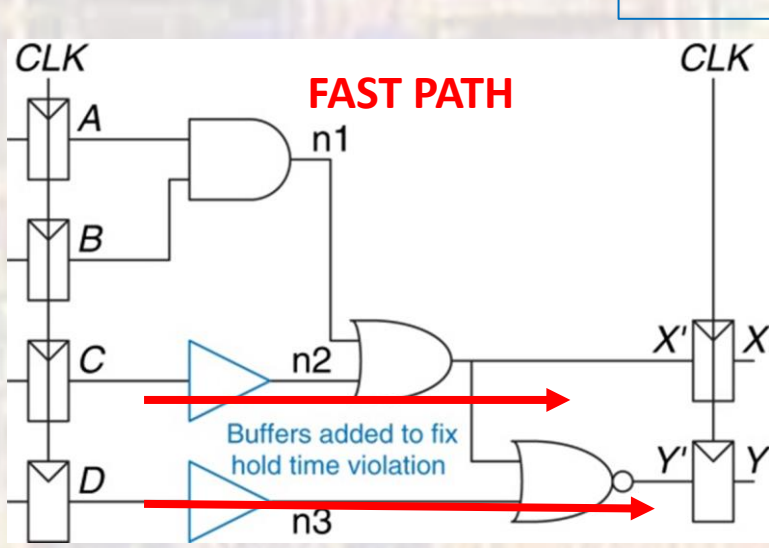

src: Harris & Harris

 

$t_{CQ_min} = 30ps$
 $t_{CQ_max} = 80ps$
 $t_{setup} = 50ps$
 $t_{hold} = 60ps$

$t_{pd_min} \text{ Logic} = 25ps$
 $t_{pd_max} \text{ Logic} = 40ps$

$$t'_{fast} = t_{CQ_min} + 2 * t_{pd_min}$$

$$t'_{fast} = 30ps + 2 * 25ps = 80ps$$

$t'_{fast} > \text{hold time} \rightarrow \text{predictable output}$

RTL Timing Analysis

- HOLD time reality
 - In almost all modern systems, $T_{\text{HOLD}} \ll T_{\text{CQ}}$ so Hold requirements rarely are a concern
 - In most integrated circuit systems, $T_{\text{HOLD}} = 0$

RTL Timing Analysis

- Additional Timing Issues
 - Clock skew
 - Variation in clock edge arrival time
 - Due to path variations (capacitances)
 - Reduces maximum clock frequency
 - Can create hold time issues
 - Clock Gating
 - Creates clock skew