


State Diagrams

Last updated 12/12/24

State Diagrams

- State Diagram – Moore

- State name

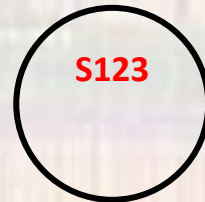

- Outputs



- Inputs

- Conditions




State Diagrams


- State Transition Diagram – Moore

- Transitions ONLY occur on clock edges (rising)
- Transitions occur on EVERY clock edge (rising)
- Priority stop light – Inputs: Reset, Traffic N/S, Traffic E/W

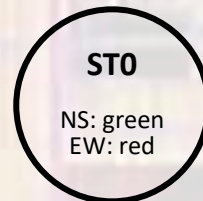- State 0 : NS light state variable (memory) holds code for green
 EW light state variable (memory) holds the code for red



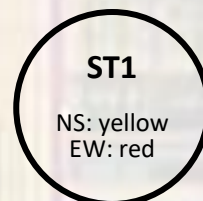- State 1 : NS light state variable (memory) holds code for yellow
 EW light state variable (memory) holds the code for red




State Diagrams

- State Transition Diagram – Moore
 - Transitions ONLY occur on clock edges (rising)
 - Transitions occur on EVERY clock edge (rising)
 - Priority stop light – Inputs: Reset, Traffic N/S, Traffic E/W



State Diagrams

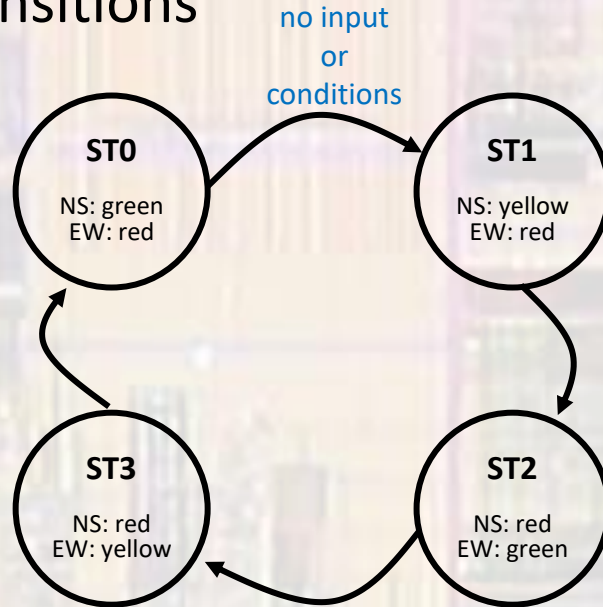
- State Transition Diagram – Moore
 - Transitions ONLY occur on clock edges (rising)
 - Transitions occur on EVERY clock edge (rising)
 - Priority stop light – Inputs: Reset, Traffic N/S, Traffic E/W
- Basic transitions



If we did not sense for traffic – this would be complete

State Diagrams

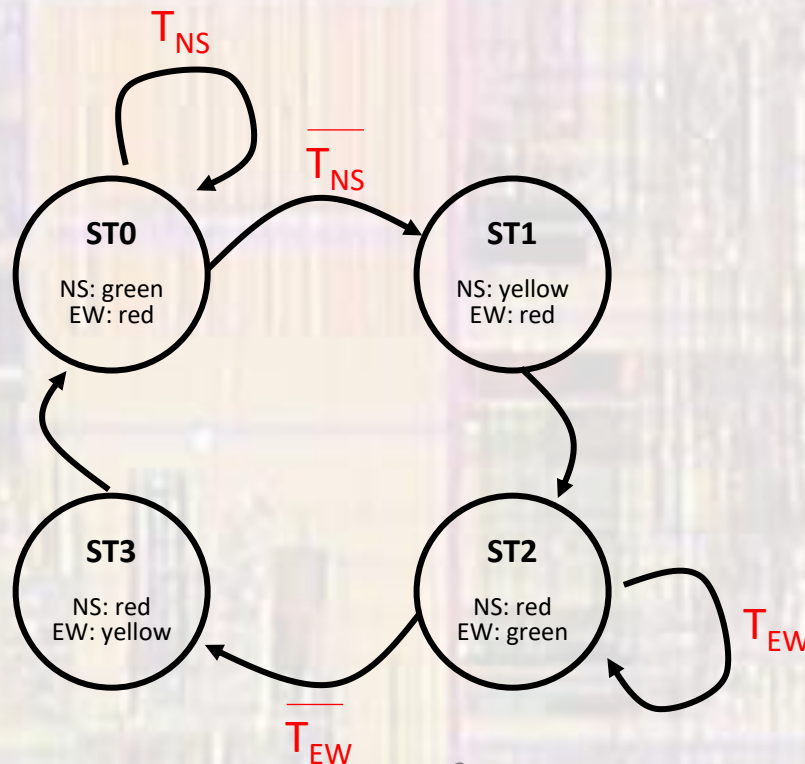- State Transition Diagram – Moore
 - Transitions ONLY occur on clock edges (rising)
 - Transitions occur on EVERY clock edge (rising)
 - Priority stop light – **Inputs:** Reset, Traffic N/S, Traffic E/W



State Diagrams

- State Transition Diagram – Moore
 - Transitions ONLY occur on clock edges (rising)
 - Transitions occur on EVERY clock edge (rising)
 - Priority stop light – **Inputs:** Reset, Traffic N/S, Traffic E/W

