

VHDL

Adders / Subtractors

Last updated 1/7/25

VHDL Adders/Subtractors

- Unsigned Addition
 - Overflow – Interpretation

4 bit unsigned binary


$$\begin{array}{r} 1010 \\ + 1001 \\ \hline \cancel{1}0011 \end{array}$$

10
9
19

Overflow

19 does not fit in 4 bit unsigned

Result in 4 bits is 3

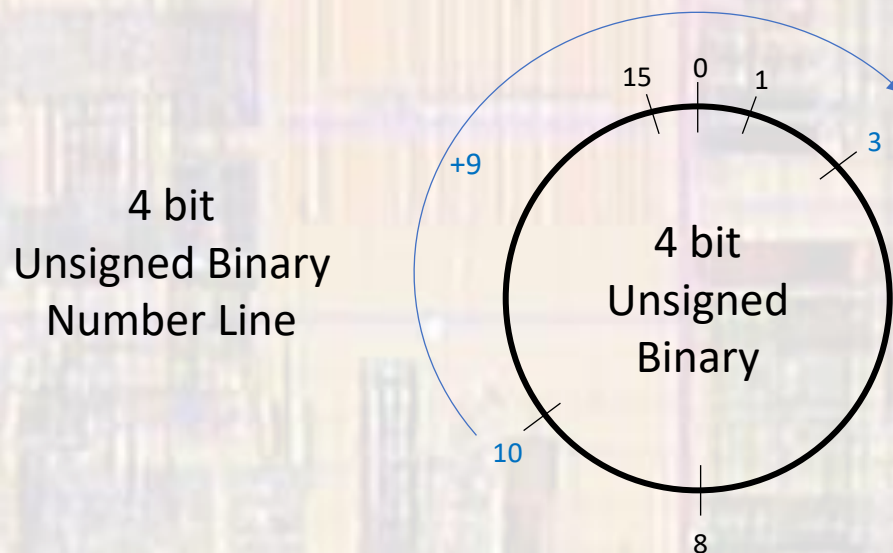

VHDL Adders/Subtractors


- Unsigned Addition
 - I/Os must be converted to/from unsigned to allow addition

```
-----  
-- adder_4bit_unsigned.vhdl  
-- by: johnsontimoj  
-- created: 12/31/24  
-- version: 0.0  
-----  
-- 4bit unsigned adder  
-- inputs: a, b  
-- outputs: sum  
-----  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity adder_4bit_unsigned is  
  port( i_a:      in std_logic_vector(3 downto 0);  
        i_b:      in std_logic_vector(3 downto 0);  
        o_sum:    out std_logic_vector(3 downto 0)  
  );  
end entity;
```


```
architecture behavioral of adder_4bit_unsigned is  
  signal a_sig:  unsigned(3 downto 0);  
  signal b_sig:  unsigned(3 downto 0);  
  signal sum_sig: unsigned(3 downto 0);  
  
begin  
  a_sig <= unsigned(i_a);  
  b_sig <= unsigned(i_b);  
  
  sum_sig <= a_sig + b_sig;  
  
  o_sum <= std_logic_vector(sum_sig);  
  
end architecture;
```

VHDL Adders/Subtractors

- Unsigned Addition



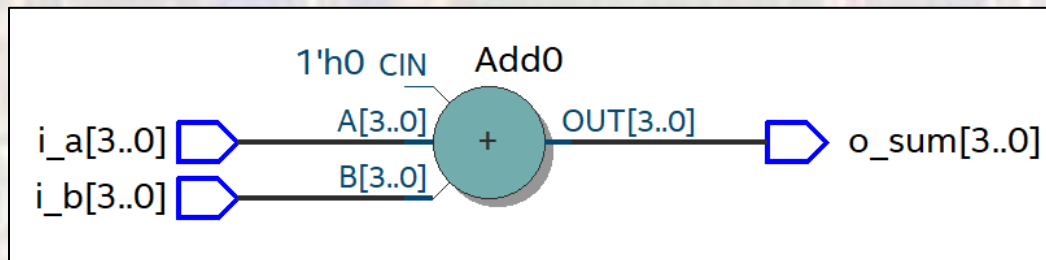


Flow Summary	
Search: <<Filter>>	
Flow Status	Successful - Tue Jan 07 17:16:56 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	adder_4bit_unsigned
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	4
Total registers	0
Total pins	12
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

 

VHDL Adders/Subtractors

   - Unsigned Addition
 - Wrapping on overflow



VHDL Adders/Subtractors

- Signed Addition
 - Overflow – Interpretation

4 bit signed binary


$$\begin{array}{r}
 1011 \quad - \quad 5 \\
 + \quad 1011 \quad - \quad 5 \\
 \hline
 \cancel{1}0110 \quad - \quad 10
 \end{array}$$

Overflow

MSB Carry-out \neq carry-in

Result in 4 bits is 6

4 bit
Signed Binary
Number Line

 

VHDL Adders/Subtractors


- Signed Addition
 - I/Os must be converted to/from signed to allow addition

```
-----  
-- adder_4bit_signed.vhdl  
-- by: johnsontimoj  
-- created: 12/31/24  
-- version: 0.0  
-----  
-- 4bit signed adder  
-- inputs: a, b  
-- outputs: sum  
-----  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity adder_4bit_signed is  
    port( i_a:      in std_logic_vector(3 downto 0);  
          i_b:      in std_logic_vector(3 downto 0);  
          o_sum:    out std_logic_vector(3 downto 0)  
    );  
end entity;
```


```
architecture behavioral of adder_4bit_signed is  
  
    signal a_sig: signed(3 downto 0);  
    signal b_sig: signed(3 downto 0);  
    signal sum_sig: signed(3 downto 0);  
  
begin  
  
    a_sig <= signed(i_a);  
    b_sig <= signed(i_b);  
  
    sum_sig <= a_sig + b_sig;  
  
    o_sum <= std_logic_vector(sum_sig);  
  
end architecture;
```

VHDL Adders/Subtractors

- Signed Addition

 

Flow Summary	
Filter	
Flow Status	Successful - Tue Jan 07 17:44:19 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	adder_4bit_signed
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	4
Total registers	0
Total pins	12
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

 

VHDL Adders/Subtractors

- Unsigned Subtraction
 - Wrapping – Interpretation

4 bit unsigned binary


$$\begin{array}{r} 0111 \quad 7 \\ - 1011 \quad 11 \\ \hline \cancel{0}1100 \quad -4 \end{array}$$

Wrap

-4 does not exist in 4 bit unsigned

Result in 4 bits is 12

4 bit
Unsigned Binary
Number Line

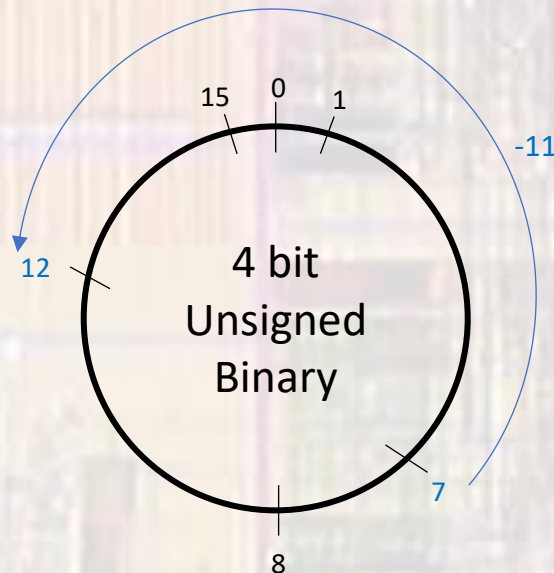

VHDL Adders/Subtractors


- Unsigned Subtraction
 - I/Os must be converted to/from unsigned to allow subtraction

```
-----  
-- subtractor_4bit_unsigned.vhdl  
-- by: johnsontimoj  
-- created: 12/31/24  
-- version: 0.0  
-----  
-- 4bit unsigned subtractor  
-- inputs: minuend, subtrahend  
-- outputs: difference  
-----  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity subtractor_4bit_unsigned is  
    port( i_minuend:      in std_logic_vector(3 downto 0);  
          i_subtrahend:  in std_logic_vector(3 downto 0);  
          o_difference:  out std_logic_vector(3 downto 0)  
    );  
end entity;
```

```
architecture behavioral of subtractor_4bit_unsigned is  
  
    signal minuend_sig:      unsigned(3 downto 0);  
    signal subtrahend_sig:   unsigned(3 downto 0);  
    signal difference_sig:   unsigned(3 downto 0);  
  
begin  
  
    minuend_sig <= unsigned(i_minuend);  
    subtrahend_sig <= unsigned(i_subtrahend);  
  
    difference_sig <= minuend_sig - subtrahend_sig;  
  
    o_difference <= std_logic_vector(difference_sig);  
end architecture;
```


VHDL Adders/Subtractors

- Unsigned Subtraction

 

Note – this is not an obvious model
more info in ELE3510

Flow Summary	
Search <<Filter>>	
Flow Status	Successful - Wed Jan 08 07:12:38 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	subtractor_4bit_unsigned
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	4
Total registers	0
Total pins	12
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

 

VHDL Adders/Subtractors

- Unsigned Subtraction
 - Wrapping

