

VHDL Generic Adders / Subtractors

Last updated 1/8/25


VHDL Generic Adders/Subtractors

- Make our VHDL more versatile using generics

```
-----  
-- adder_nbit_signed.vhdl  
-- by: johnsontimoj  
-- created: 12/31/24  
-- version: 0.0  
-----  
-- nbit signed adder  
-- inputs: a, b  
-- outputs: sum  
-----  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity adder_nbit_signed is  
    generic( N: positive := 8  
    );  
    port( i_a: in std_logic_vector((N-1) downto 0);  
          i_b: in std_logic_vector((N-1) downto 0);  
          o_sum: out std_logic_vector((N-1) downto 0)  
    );  
end entity;
```

default value
 
```
architecture behavioral of adder_nbit_signed is  
    signal a_sig: signed((N-1) downto 0);  
    signal b_sig: signed((N-1) downto 0);  
    signal sum_sig: signed((N-1) downto 0);  
begin  
    a_sig <= signed(i_a);  
    b_sig <= signed(i_b);  
    sum_sig <= a_sig + b_sig;  
    o_sum <= std_logic_vector(sum_sig);  
end architecture;
```



VHDL Generic Adders/Subtractors

- Using generics in structural VHDL

```
-----  
-- adder_nbit_signed_3x.vhdl  
-- by: johnsontimoj  
-- created: 12/31/24  
-- version: 0.0  
-----  
-- nbit signed adder instantiated 3x  
-- inputs: a, b  
-- outputs: sum  
-----  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity adder_nbit_signed_3x is  
  generic(  
    X: positive := 4;  
    Y: positive := 8;  
    Z: positive := 12;  
  );  
  port(  
    i_a1: in std_logic_vector((X-1) downto 0);  
    i_b1: in std_logic_vector((X-1) downto 0);  
    o_sum1: out std_logic_vector((X-1) downto 0);  
  
    i_a2: in std_logic_vector((Y-1) downto 0);  
    i_b2: in std_logic_vector((Y-1) downto 0);  
    o_sum2: out std_logic_vector((Y-1) downto 0);  
  
    i_a3: in std_logic_vector((Z-1) downto 0);  
    i_b3: in std_logic_vector((Z-1) downto 0);  
    o_sum3: out std_logic_vector((Z-1) downto 0);  
  );  
end entity;
```

```
architecture behavioral of adder_nbit_signed_3x is  
  component adder_nbit_signed is  
    generic(  
      N: positive := 8  
    );  
    port(  
      i_a: in std_logic_vector((N-1) downto 0);  
      i_b: in std_logic_vector((N-1) downto 0);  
      o_sum: out std_logic_vector((N-1) downto 0);  
    );  
  end component;  
  
begin  
  add4: adder_nbit_signed  
    generic map(  
      N => X  
    )  
    port map (  
      i_a => i_a1,  
      i_b => i_b1,  
      o_sum => o_sum1  
    );  
  
  add8: adder_nbit_signed  
    generic map(  
      N => Y  
    )  
    port map (  
      i_a => i_a2,  
      i_b => i_b2,  
      o_sum => o_sum2  
    );  
  
  add12: adder_nbit_signed  
    generic map(  
      N => Z  
    )  
    port map (  
      i_a => i_a3,  
      i_b => i_b3,  
      o_sum => o_sum3  
    );  
end architecture;
```

generic adder
instantiated 3 times
with different sizes

