

# VHDL

## Best Practices – CPE1500

Last updated 1/21/25

# VHDL Best Practices – CPE1500

- Best Practices ???
  - Best practices are often defined by company, toolset or device
  - In our case – Dr. Johnson is setting the “best practices”
  - These rules are for Class/Lab purposes. Industry best practices would include a much more extensive list
    - I/O synchronization
    - Clock domains
    - Revision control
    - Test coverage
    - ...
  - These rules have been reduced from the ELE3510 rules

# VHDL Best Practices – page 1/2

- Use meaningful names for blocks, signals and programs
- Use i\_xyz for block input signal names and o\_xyz for block output signal names
- Use \_tb and \_de10 name extensions for testbenches and hardware implementations
- 1 design file, instantiate it in the testbench and hardware implementation files
- No latches
- Use explicit port mapping when instantiating components
- No signal initialization in declarations

# VHDL Best Practices – page 2/2

- No variables as signals
- I/O signals are SLV, internal signals are signed/unsigned as appropriate
- Use rising edge()
- Reset bar for general (control) synchronous logic
- Clock divider OK for slowing to human speeds
- Break FSM designs into separate Next State, Register, and Output Logic(Mealy) sections

# Use meaningful names ...

- Use meaningful names for blocks, signals and programs

## Stoptlight with emergency detection for lab 22

~~lab22.vhdl~~

~~testbench.vhdl~~

~~board.vhdl~~

stoptlight\_w\_emergency.vhdl

stoptlight\_w\_emergency\_tb.vhdl

stoptlight\_w\_emergency\_de10.vhdl

Note: primary function followed by  
secondary functions

# Use i\_xyz ...

- Use i\_xyz for block input names and o\_xyz for block output names


```
port(i_A:      in    std_logic_vector(3 downto 0);
     i_B:      in    std_logic_vector(3 downto 0);
     i_CIN:    in    std_logic;
     o_SUM:    out   std_logic_vector(3 downto 0);
     o_COUT:   out   std_logic
);
```

**Exception:** When using the pin-names from the QSF file for DE10 implementations, the names must match exactly



```
entity lab_4_de10 is
port(
  CLOCK_50 : in    std_logic;
  SW:      in    std_logic_vector(9 downto 0);
  HEX0:    out   std_logic_vector(7 downto 0);
  HEX1:    out   std_logic_vector(7 downto 0);
  HEX2:    out   std_logic_vector(7 downto 0);
  HEX3:    out   std_logic_vector(7 downto 0)
);
end entity;
```
 
# 1 design file, instantiate ...

- 1 design file, instantiate it in the testbench and HW implementation files



No Changes to the design

 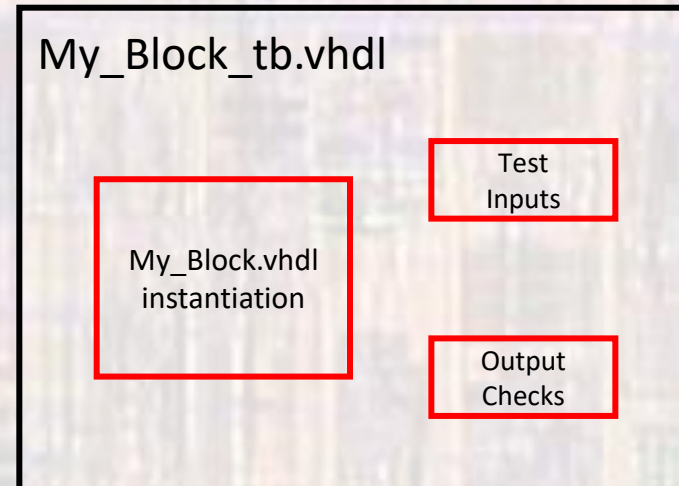

# No Latches


- No Latches

```
library ieee;
use ieee.std_logic_1164.all;

entity latches is
  port(
    i_clk:  in std_logic;
    i_d:    in std_logic;

    o_q:   out std_logic
  );
end entity latches;

 architecture behavioral of latches is
begin
  process(i_clk, i_d)
  begin
    if(i_clk = '1') then
      o_q <= i_d;
    end if;
  end process;
end architecture;
```



Type	ID	Message
Warning	10631	VHDL Process Statement warning at latches.vhdl(26): inferring latch(es) for signal or variable "q", which holds its previous value in one or
Info	10041	Inferred latch for "q" at latches.vhdl(26)




# Use Explicit Port Mapping

- Always use explicit port mapping on component instantiation

```
library ieee;
use ieee.std_logic_1164.all;

entity dff_instantiation is
  port (
    CLOCK_50 : in std_logic;
    SW       : in std_logic_vector(1 downto 0);
    LEDR     : out std_logic_vector(0 downto 0)
  );
end entity;
```

port map

 

architecture structural of dff\_instantiation is

```
component d_ff
  port(
    i_D : in std_logic;
    i_clk : in std_logic;
    i_rstb: in std_logic;

    o_Q: out std_logic
  );
end component;

begin
  reg_0: d_ff
    port map(i_D => SW(1),
             i_clk => CLOCK_50,
             i_rstb => SW(0),
             o_Q => LEDR(0)
    );
end architecture;
```

component prototype

explicit port mapping  
component pin => my signal

# No Signal Initialization



- No signal initialization in declarations
  - It is not possible to implement signal initialization in hardware
  - Rely on reset for any required initialization in hardware

```
signal foo: std_logic := '1';
```

```
signal foo: std_logic := '1';
begin
-- sections to show initialization fails
process(i_clk)
begin
  if(rising_edge(i_clk)) then
    foo <= '0';
    y <= '1';
  end if;
end process;
x <= foo;
```

x = foo

Sim says it works  
HW fails !!!

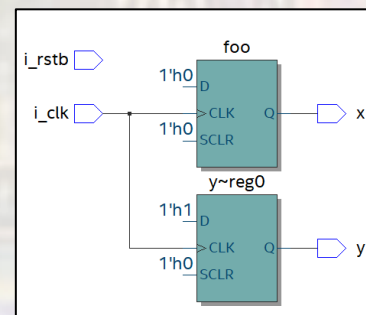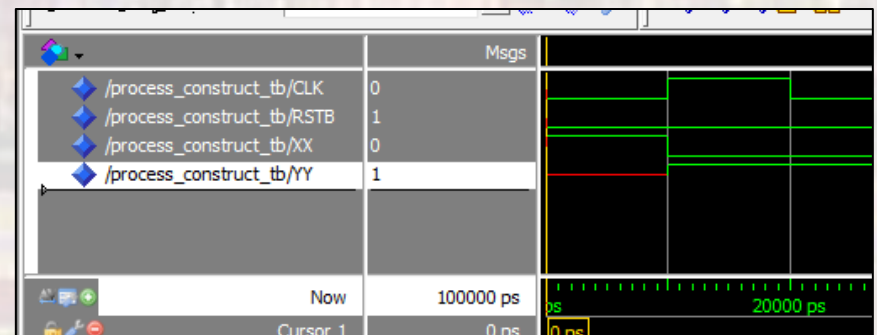

Sim shows x (foo) starts at '1'

Hardware has nothing to make x (foo) start at 1

# No Variables as Signals

- No variables as signals
  - We are using HDL code to represent HARDWARE
  - Variables do not have a HARDWARE analog
- Variables are treated differently than signals
  - Variables are updated immediately in a process
  - Signals are only updated at the end of a process
- Variable are appropriate for compile time calculations
  - Generate
  - Test Benches

# I/O signals are ...

- I/O signals are SLV, internal signals are signed/unsigned as appropriate
  - We are using HDL code to represent HARDWARE
- I/O ports are represented by `std_logic` or `std_logic_vectors`
  - They are interpreted as connections
- Internal signals
  - Use `std_logic` to represent single wires
  - Use `unsigned` to represent unsigned bus signals and structural buses (memory addresses, ...)
  - Use `signed` to represent signed bus signals

# Use Rising\_Edge()

- Use Rising\_Edge()
  - (rising\_edge(clk)) instead of (clk'event and clk = '1') in register (FF designs)
  - Also use (falling\_edge(clk))
- These do better multi-state checking in simulation

clk'event includes things like

Z → 1

U → 1

rising\_edge only includes 0 → 1

```
process(i_clk, i_rstb)
begin
  if (i_rstb = '0') then
    o_Q <= '0';
  elsif (rising_edge(i_clk)) then
    o_Q <= i_D;
  end if;
end process;
```

# Reset\_bar for general ...

- Reset\_bar for general (control) synchronous logic
  - All non-data path registers will have a rstb signal

```
library ieee;
use ieee.std_logic_1164.all;

entity d_ff is
  port (
    i_clk : in std_logic;
    i_rstb:in std_logic;
    i_D :   in std_logic;

    o_Q:   out std_logic
  );
end entity;

architecture behavioral of d_ff is
begin
  process(i_clk, i_rstb)
  begin
    if (i_rstb = '0') then
      o_Q <= '0';
    elsif (rising_edge(i_clk)) then
      o_Q <= i_D;
    end if;
  end process;
end behavioral;
```

```
library ieee;
use ieee.std_logic_1164.all;

entity registers is
  generic(
    N: integer := 8
  );
  port (
    i_clk : in std_logic;
    i_rstb: in std_logic;
    i_D :   in std_logic_vector((N - 1) downto 0);

    o_Q:   out std_logic_vector((N - 1) downto 0)
  );
end entity;

architecture behavioral of registers is
begin
  process(i_clk, i_rstb)
  begin
    if (i_rstb = '0') then
      o_Q <= (others => '0');
    elsif (rising_edge(i_clk)) then
      o_Q <= i_D;
    end if;
  end process;
end behavioral;
```