


# VHDL Data Registers

Last updated 1/9/25


# VHDL Data Registers

- Register
  - Collection of n Flip-Flops
  - Configured in parallel
  - Common clock, set/reset, enable
  - Stores an n-bit state variable


n-bit register

 

n bit wide bus

 

signal indices n-1 down to 0

 

# VHDL Data Registers

- Registers are collections of Flip-Flops
- Registers are created by creating code that conforms to the Flip-Flop synthesis template

```
process (clock signal)
begin
    if(clock edge detection) then
        actions
    end if;
end process;
```

note:

- here the else is not required because the synthesizer recognizes the edge detection
- you can include an else for clarity

# VHDL Data Registers


- 4 bit data register

```
--  
-- reg_4bit.vhdl  
-- by: johnsontimoj  
-- created: 12/31/24  
-- version: 0.0  
--  
--  
-- standard 4 bit register  
-- inputs: clk, rstb, d  
-- outputs: q  
--  
--  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity reg_4bit is  
    port(  
        i_clk:    in std_logic;  
        i_rstb:   in std_logic;  
        i_D :     in std_logic_vector(3 downto 0);  
        o_Q :     out std_logic_vector(3 downto 0)  
    );  
end entity;
```

```
architecture behavioral of reg_4bit is  
begin  
    process (i_clk, i_rstb)  
    begin  
        if (i_rstb = '0') then  
            o_Q <= "0000";  
        elsif (rising_edge(i_clk)) then  
            o_Q <= i_D;  
        end if;  
    end process;  
end architecture;
```

# VHDL Data Registers

- 4 bit data register

 

| Flow Summary                       |                                             |
|------------------------------------|---------------------------------------------|
| <<Filter>>                         |                                             |
| Flow Status                        | Successful - Thu Jan 09 11:52:16 2025       |
| Quartus Prime Version              | 18.1.0 Build 625 09/12/2018 SJ Lite Edition |
| Revision Name                      | general                                     |
| Top-level Entity Name              | reg_4bit                                    |
| Family                             | MAX 10                                      |
| Device                             | 10M50DAF484C7G                              |
| Timing Models                      | Final                                       |
| Total logic elements               | 4                                           |
| Total registers                    | 4                                           |
| Total pins                         | 10                                          |
| Total virtual pins                 | 0                                           |
| Total memory bits                  | 0                                           |
| Embedded Multiplier 9-bit elements | 0                                           |
| Total PLLs                         | 0                                           |
| UFM blocks                         | 0                                           |
| ADC blocks                         | 0                                           |



# VHDL Data Registers

- 4 bit data register - testbench


```
-- reg_4bit_tb.vhd1
-- by: johnsontimoj
-- created: 12/31/24
-- version: 0.0
--
-- testbench for standard 4 bit register
-- inputs: clk, rstb, d
-- outputs: q
--
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity reg_4bit_tb is
  -- no ports in TB
end entity;
```

```
architecture testbench of reg_4bit_tb is
  signal CLK:      std_logic;
  signal RSTB:     std_logic;
  signal D:        std_logic_vector(3 downto 0);
  signal Q:        std_logic_vector(3 downto 0);

  constant PER:    time := 20 ns;

   component reg_4bit is
    port(
      i_clk:  in std_logic;
      i_rstb: in std_logic;
      i_d:    in std_logic_vector(3 downto 0);
      o_q:    out std_logic_vector(3 downto 0)
    );
  end component;
```



```
-- Device under test (DUT)
DUT: reg_4bit
port map(
  i_clk      => CLK,
  i_rstb     => RSTB,
  i_d        => D,
  o_q        => Q
);
--
-- Test processes
--
-- Clock process
clock: process
begin
  CLK <= '0';
  wait for PER/2;
  infinite: loop
    CLK <= not CLK;
    wait for PER/2;
  end loop;
end process clock;

-- Reset process
reset: process
begin
  RSTB <= '0'; wait for 2*PER;
  RSTB <= '1'; wait;
end process reset;

-- Run process
data: process
begin
  -- initialize D
  D <= std_logic_vector(to_unsigned(0, 4));


  -- wait for reset
  wait for 3 * PER;

  -- loop exhaustive inputs
  binary_cnt: for i in 0 to 15 loop
    D <= std_logic_vector(to_unsigned(i, 4));
    wait for 2 * PER;
  end loop;
end process;

end architecture;
```

# VHDL Data Registers

- 4 bit data register - testbench

 

# VHDL Data Registers

- N bit data register

```
-- reg_nbit.vhdl
-- by: johnsontimoj
-- created: 12/31/24
-- version: 0.0
--
-- standard N bit register
-- inputs: clk, rstb, d
-- outputs: q
--
library ieee;
use ieee.std_logic_1164.all;
entity reg_nbit is
  generic(
    N: positive := 8
  );
  port(
    i_clk: in std_logic;
    i_rstb: in std_logic;
    i_D : in std_logic_vector((N - 1) downto 0);
    o_Q : out std_logic_vector((N - 1) downto 0)
  );
end entity;
```

generic section

- defines N
- defaults N to 8
- can be overwritten when instantiated

(others => '0') used since N can change


```
architecture behavioral of reg_nbit is
begin
  process (i_clk, i_rstb)
  begin
    if (i_rstb = '0') then
      o_Q <= (others => '0');
    elsif (rising_edge(i_clk)) then
      o_Q <= i_D;
    end if;
  end process;
end architecture;
```

Vector sizes now defined with N



# VHDL Data Registers

- N bit data register

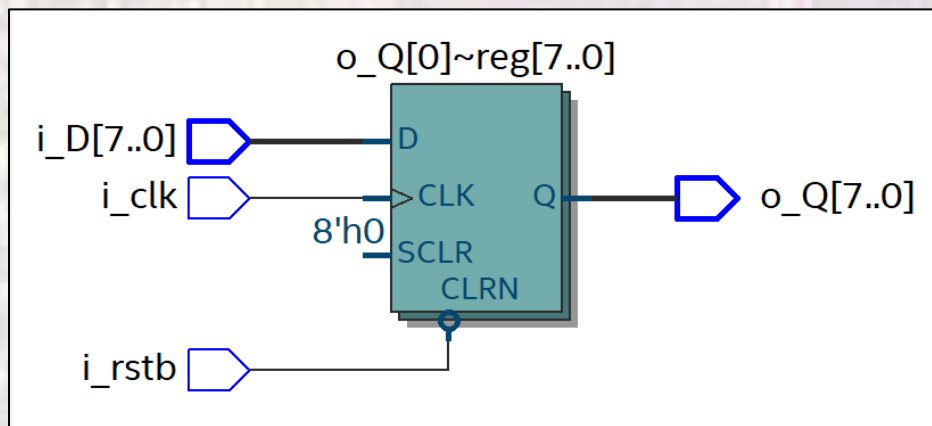


| Flow Summary                       |                                             |
|------------------------------------|---------------------------------------------|
| <<Filter>>                         |                                             |
| Flow Status                        | Successful - Thu Jan 09 12:06:01 2025       |
| Quartus Prime Version              | 18.1.0 Build 625 09/12/2018 SJ Lite Edition |
| Revision Name                      | general                                     |
| Top-level Entity Name              | reg_nbit                                    |
| Family                             | MAX 10                                      |
| Device                             | 10M50DAF484C7G                              |
| Timing Models                      | Final                                       |
| Total logic elements               | 8                                           |
| Total registers                    | 8                                           |
| Total pins                         | 18                                          |
| Total virtual pins                 | 0                                           |
| Total memory bits                  | 0                                           |
| Embedded Multiplier 9-bit elements | 0                                           |
| Total PLLs                         | 0                                           |
| UFM blocks                         | 0                                           |
| ADC blocks                         | 0                                           |

# VHDL Data Registers

- n bit data register - testbench

```
-----  
-- reg_nbit_tb.vhd1  
-- by: johnsontimmoj  
-- created: 12/31/24  
-- version: 0.0  
-----  
-- testbench for standard n bit register  
-- inputs: clk, rstb, d  
-- outputs: q  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity reg_nbit_tb is  
    generic(  
        NN: positive := 4  
    );  
    -- no ports in TB  
end entity;
```


```
architecture testbench of reg_nbit_tb is  
    signal CLK: std_logic;  
    signal RSTB: std_logic;  
    signal D: std_logic_vector((NN - 1) downto 0);  
    signal Q: std_logic_vector((NN - 1) downto 0);  
    constant PER: time := 20 ns;  
    component reg_nbit is  
        generic(  
            N: positive := 8  
        );  
        port(  
            i_clk: in std_logic;  
            i_rstb: in std_logic;  
            i_d: in std_logic_vector((N - 1) downto 0);  
            o_q: out std_logic_vector((N - 1) downto 0)  
        );  
    end component;
```

 

```
begin  
    -----  
    -- Device under test (DUT)  
    -----  
    DUT: reg_nbit  
    generic map(  
        N => NN  
    )  
    port map(  
        i_clk => CLK,  
        i_rstb => RSTB,  
        i_d => D,  
        o_q => Q  
    );  
    -----  
    -- Test processes  
    -----  
    -- clock process  
    clock: process  
    begin  
        CLK <= '0';  
        wait for PER/2;  
        infinite: loop  
            CLK <= not CLK;  
            wait for PER/2;  
        end loop;  
    end process clock;  
    -- Reset process  
    reset: process  
    begin  
        RSTB <= '0'; wait for 2*PER;  
        RSTB <= '1'; wait;  
    end process reset;  
    -- Run process  
    data: process  
    begin  
        -- initialize D  
        D <= std_logic_vector(to_unsigned(0, NN));  
        -- wait for reset  
        wait for 3 * PER;  
        -- loop exhaustive inputs  
        binary_cnt: for i in 0 to (2*NN - 1) loop  
            D <= std_logic_vector(to_unsigned(i, NN));  
            wait for 2 * PER;  
        end loop;  
    end process;  
end architecture;
```
 
# VHDL Data Registers

- n bit data register – testbench
  - Default for the nbit register is 8 bits
  - Instantiated a 4 bit version



# VHDL Data Registers

- Data Register Enhancements
  - Asynch/synch reset, set
  - Clear
  - Load
  - Preload
  - Enable