

# VHDL Decoders


Last updated 1/1/25

# VHDL Decoders

- A decoder sets one of many outputs to 1 based on the inputs
  - N data outputs – typically a power of 2
  - D data inputs –  $\log_2(N)$
  - **D:N Decoder**


D = 3

N = 8

 

# VHDL Decoders

 - 3-8 Example
  - Description
  - Libraries
  - Entity



```
-----  
--  
-- decoder_1.vhd1  
--  
-- created 7/5/2018  
-- tj  
--  
-- rev 0  
-----  
--  
-- vhd1 encoder example 1 - brute-force  
--  
-----  
--  
-- Inputs: in(2-0)  
-- Outputs: out(7-0)  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity decoder_1 is  
    port (  
        i_in:    in std_logic_vector(2 downto 0);  
        o_out:   out std_logic_vector(7 downto 0)  
    );  
end entity;
```

# VHDL Decoders


- 3-8 Example
  - Architecture

```
architecture behavioral of decoder_1 is
begin
    with i_in select o_out <=
        "00000001" when "000",
        "00000010" when "001",
        "00000100" when "010",
        "00001000" when "011",
        "00010000" when "100",
        "00100000" when "101",
        "01000000" when "110",
        "10000000" when "111",
        "00000000" when others;
end behavioral;
```

exhaustive list

# VHDL Decoders

- 3-8 Example

 

Flow Summary	
Flow Status	Successful - Thu Jan 02 11:48:21 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	decoder_1
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	8
Total registers	0
Total pins	11
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0