

# VHDL Flip-Flop Examples

Last updated 1/8/25

# VHDL Flip-Flop Examples


- Base D-FF with reset

```
--  
-- ff_d.vhdl  
--  
-- by: johnsontimoj  
--  
-- created: 12/31/24  
--  
-- version: 0.0  
--  
-----  
--  
-- standard d-ff with rstb  
-- inputs: clk, rstb, d  
--  
-- outputs: q  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity ff_d is  
  port(  
    i_clk:   in std_logic;  
    i_rstb:  in std_logic;  
    i_D :    in std_logic;  
  
    o_Q :    out std_logic  
  );  
end entity;
```


```
architecture behavioral of ff_d is  
begin  
  
  process (i_clk, i_rstb)  
  begin  
    if (i_rstb = '0') then  
      o_Q <= '0';  
    elsif (rising_edge(i_clk)) then  
      o_Q <= i_D;  
    end if;  
  end process;  
  
end architecture;
```

# VHDL Flip-Flop Examples

- Base D-FF with reset

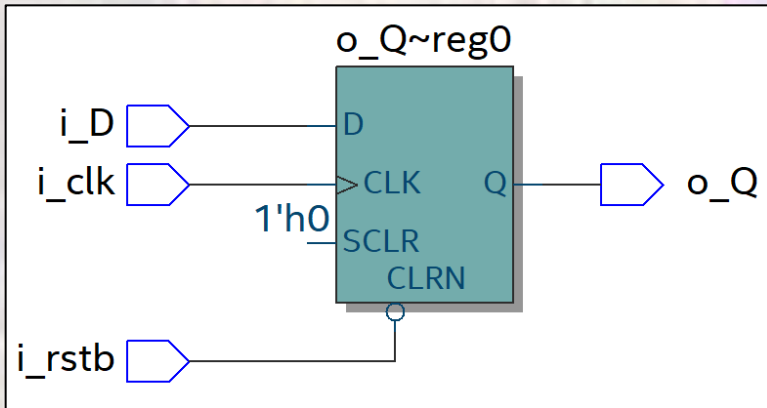

Flow Summary	
<<Filter>>	
Flow Status	Successful - Wed Jan 08 15:34:59 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	ff_d
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	1
Total registers	1
Total pins	4
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

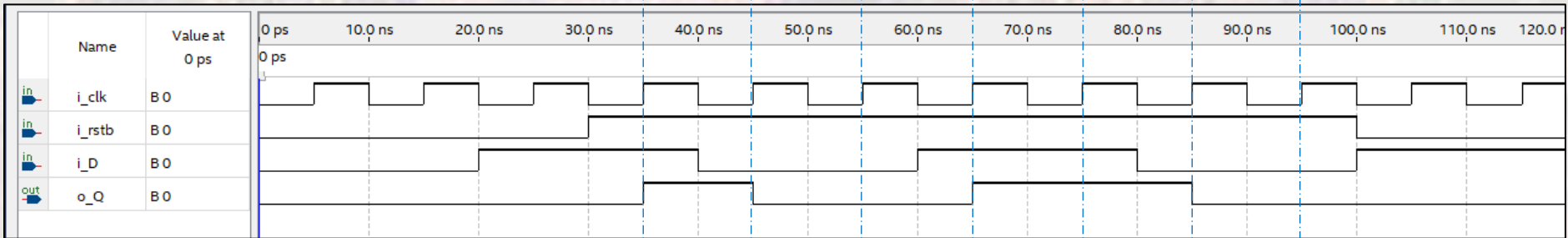

reset enabled (active low)  
Q is reset – nothing happening

edge captures

reset enabled (active low)  
Q is reset – nothing happening

# VHDL Flip-Flop Examples

- d-ff w/asy en, sync set

```
-----  
-- ff_d_asy_en_syn_set.vhdl  
-- by: johnsontimoj  
-- created: 12/31/24  
-- version: 0.0  
-----  
-- standard d-ff with rstb  
-- inputs: clk, rstb, d  
-- outputs: q  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity ff_d_asy_en_syn_set is  
  port(  
    i_clk: in std_logic;  
    i_rstb: in std_logic;  
    i_en: in std_logic;  
    i_set: in std_logic;  
    i_d : in std_logic;  
  
    o_q : out std_logic  
  );  
end entity;
```

```
architecture behavioral of ff_d_asy_en_syn_set is  
begin  
  process (i_clk, i_rstb, i_en)  
  begin  
    if (i_rstb = '0') then  
      o_q <= '0';  
    elsif (i_en = '0') then  
      o_q <= o_q;  
    elsif (rising_edge(i_clk)) then  
      if (i_set = '1') then  
        o_q <= '1';  
      else  
        o_q <= i_d;  
      end if;  
    end if;  
  end process;  
end architecture;
```


set an explicit priority

$\text{rstb} > \text{en}$


$\text{set} > \text{d}$

# VHDL Flip-Flop Examples

- d\_ff w/asy en, sync set

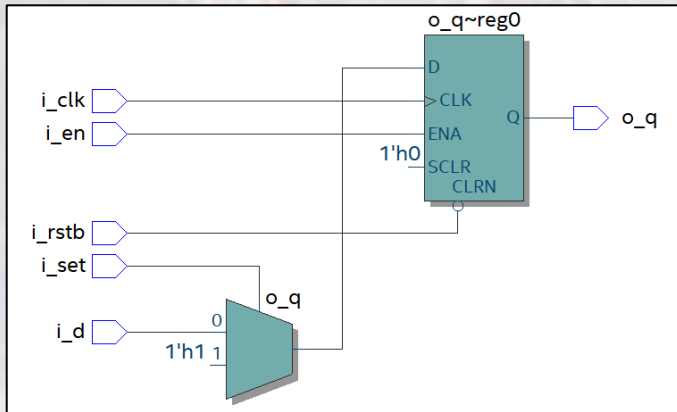

Flow Summary	
<<Filter>>	
Flow Status	Successful - Wed Jan 08 16:08:16 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	ff_d_asy_en_syn_set
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	1
Total registers	1
Total pins	6
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

 

# VHDL Flip-Flop Examples

- **Warning – Warning – Warning**
  - The FF template is an exception to the **if/else** and **case** rules for creating latches
  - Outside the FF construct:
    - If you do not complete an **if-else** with an **else**, a latch will be created
    - If you do not cover all cases in a **case** statement, a latch will be created
    - All paths/cases must be covered
    - The compiler will always warn you it created a latch

**We do not want latches - EVER**

I can see a latch in an RTL diagram from a mile away