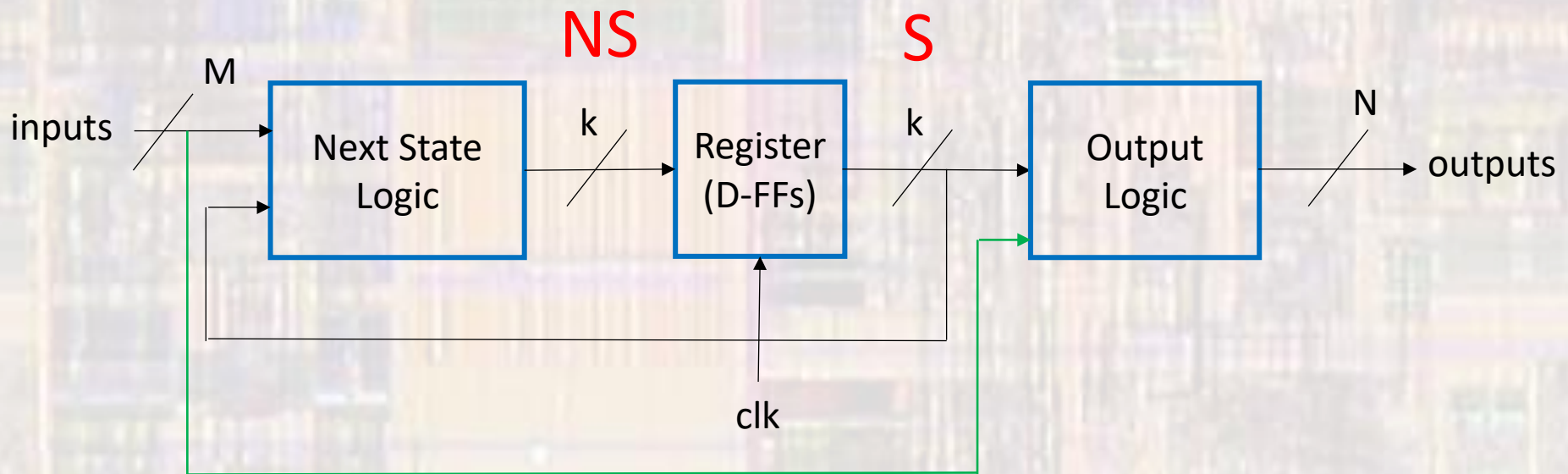


Advanced VHDL FSMs

Last updated 4/23/26

Advanced VHDL FSMs


- Finite State Machine
 - Moore Machine
 - Outputs depend only on the current state(S)



- Mealy Machine
 - Outputs depend on the current state(S) and the inputs

Advanced VHDL FSMs

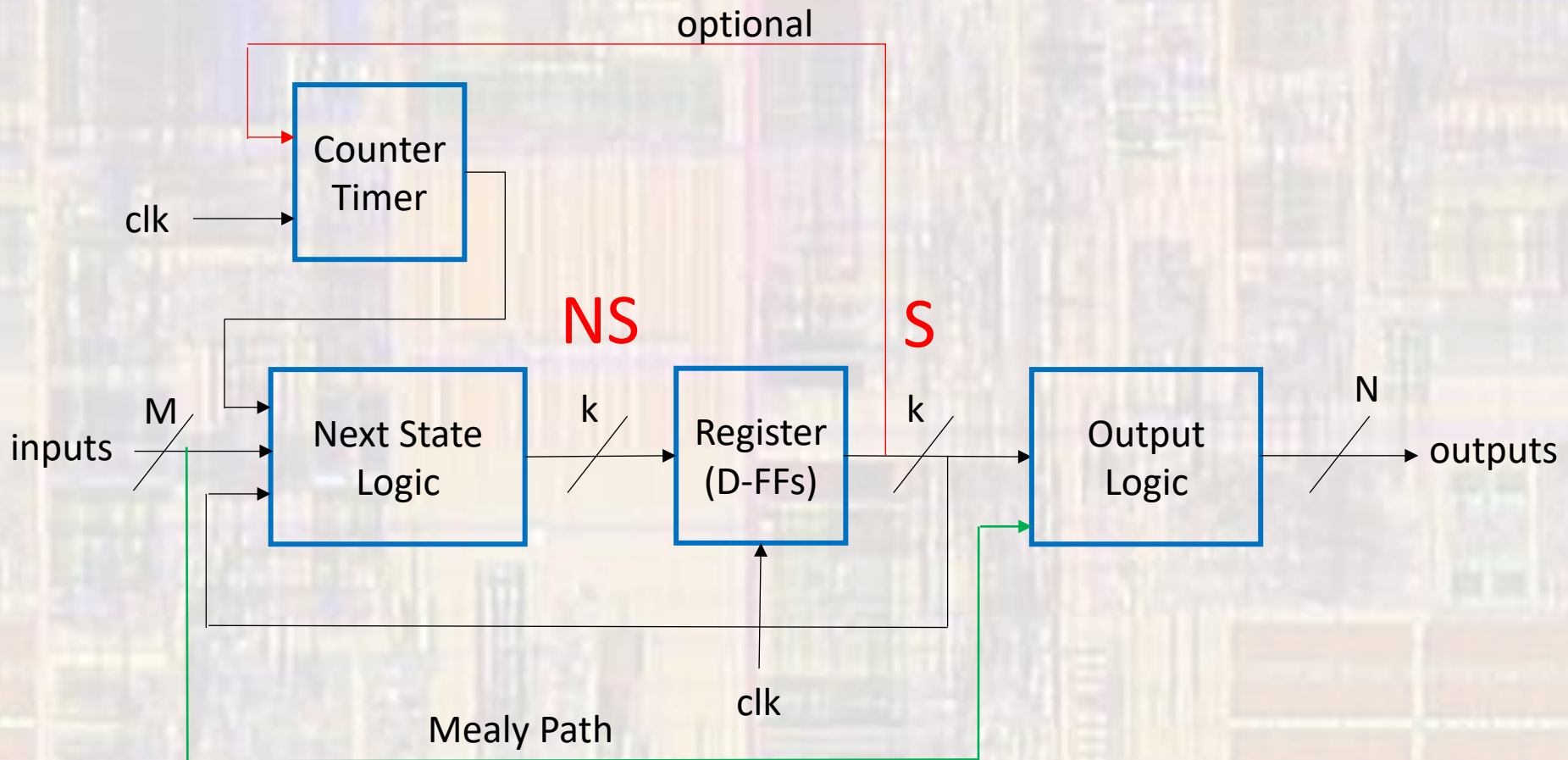- Finite State Machine with Free Running Counter/Timer



Advanced VHDL FSMs

- Sequence Generator
 - Run each of 4 output values for different amounts of time
 - 1111 for 6 clks, 0110 for 7 clks, 1001 for 11 clks, 0000 for 8 clks, restart → total of 32 clks
 - run input to start/stop the sequence
- inputs: clk, rstb, run
- outputs: sequence signal
- States: IDLE, S0, S1, ... S31

Advanced VHDL FSMs

- Sequence Generator – timed
 - Run each of 4 output values for different amounts of time
 - 1111 for 6 clks, 0110 for 7 clks, 1001 for 11 clks, 0000 for 8 clks, restart → total of 32 clks
 - run input to start/stop the sequence
- inputs: clk, rstb, run
- outputs: sequence signal
- States: IDLE, A, B, C, D

Advanced VHDL FSMs

- Sequence Generator – timed

```
-----
-- fsm_pattern_gen_free_run_clk.vhdl
-- created 4/21/26
-- tj
-- rev 0
-----
--
-- Example of using a free running clock in an FSM
-- generates a timed bit val for each of 4 states
--
-- 1111 for 6 clks, 0110 for 7 clks, 1001 for 11 clks, 0000 for 8 clks, restart
-- total of 32 clks
--
-----
--
-- this is for illustrative purposes
-- we would not hardcode the values
-- we would not use a free-running clock in most situations
--
-----
-- states: IDLE, A, B, C, D
-- Inputs: i_rstb, i_clk, i_run
-- Outputs: o_val
--
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity fsm_pattern_gen_free_run_clk is
port (
    i_clk : in std_logic;
    i_rstb : in std_logic;
    i_run : in std_logic;
    o_val : out std_logic_vector(3 downto 0)
);
end entity;
```

```
architecture behavioral of fsm_pattern_gen_free_run_clk is
--
-- internal signals
--
type STATE_TYPE is (IDLE, A, B, C, D);
signal state: STATE_TYPE;
signal state_next: STATE_TYPE;

-- unsigned cnt signal -- to allow addition and comparison
signal cnt_sig: unsigned(4 downto 0);

begin
--
-- counter logic - free running, auto wrap
--
process(i_clk, i_rstb, state)
begin
if(i_rstb = '0') then
cnt_sig <= to_unsigned(0,5);
elsif (state = IDLE) then
cnt_sig <= to_unsigned(0,5);
elsif(rising_edge(i_clk)) then
cnt_sig <= cnt_sig + 1;
end if;
end process;
```

Advanced VHDL FSMs

- Sequence Generator – timed



```
--  
-- next state logic  
--  
process(state, i_run, cnt_sig)  
begin  
  if(i_run = '0') then  
    state_next <= IDLE;  
  
  else  
  
    case state is  
      when IDLE =>  
        state_next <= A;  
      when A =>  
        if (cnt_sig = 5) then -- remember 0 counts, 6 clks --> cnt = 5  
          state_next <= B;  
        else  
          state_next <= A;  
        end if;  
      when B =>  
        if (cnt_sig = 12) then  
          state_next <= C;  
        else  
          state_next <= B;  
        end if;  
      when C =>  
        if (cnt_sig = 23) then  
          state_next <= D;  
        else  
          state_next <= C;  
        end if;  
      when D =>  
        if (cnt_sig = 31) then  
          state_next <= A;  
        else  
          state_next <= D;  
        end if;  
      when others => state_next <= IDLE;  
    end case;  
  
  end if;  
end process;
```

```
--  
-- Register logic  
--  
process(i_clk, i_rstb)  
begin  
  -- reset  
  if (i_rstb = '0') then  
    state <= IDLE;  
  -- rising i_clk edge  
  elsif (rising_edge(i_clk)) then  
    state <= state_next;  
  end if;  
end process;  
  
--  
-- Output logic  
--  
process(state)  
begin  
  case state is  
    when IDLE => o_val <= "0000";  
    when A => o_val <= "1111";  
    when B => o_val <= std_logic_vector(to_unsigned(6,4));  
    when C => o_val <= std_logic_vector(to_unsigned(9,4));  
    when D => o_val <= "1010";  
    when others => o_val <= (others => '0');  
  end case;  
end process;
```

end behavioral;

Advanced VHDL FSMs

- Sequence Generator – timed

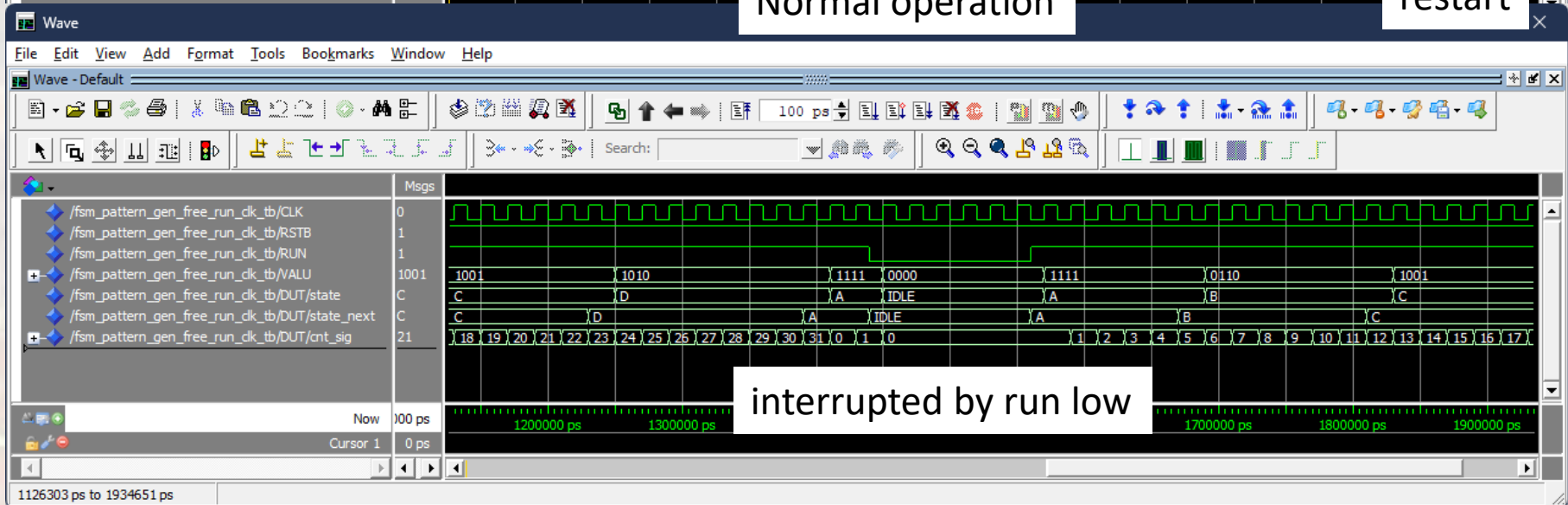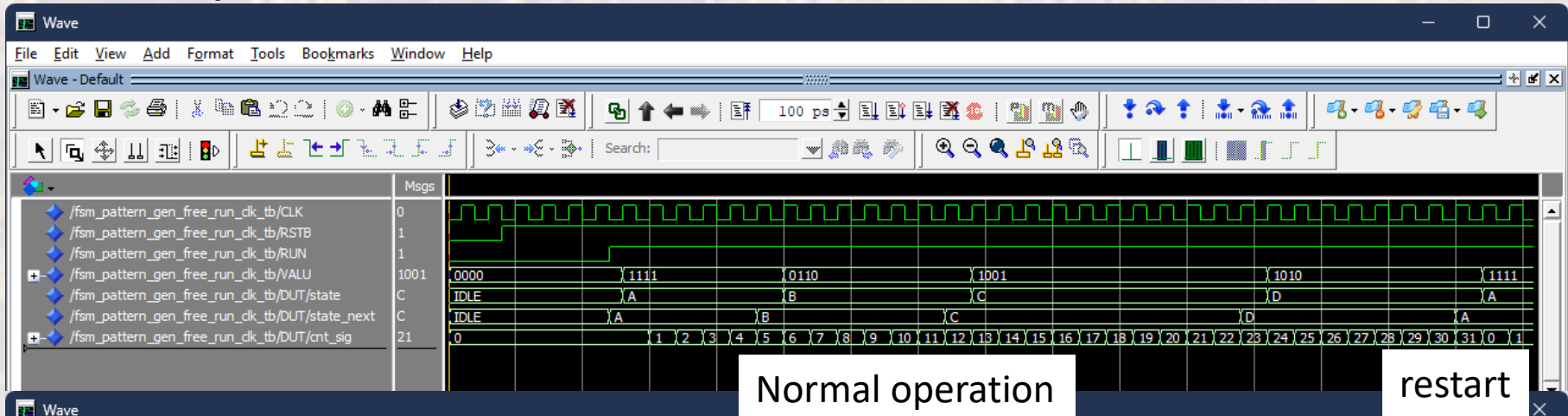


Advanced VHDL FSMs

- Stoplight – timed
 - 4 way stoplight – Adir and Bdir
 - A RG for 20 clks, A RY for 3 clks, A GR for 20 clks, A YR for 3 clks, restart → total of 46 clks
- inputs: clk, rstb
- outputs: sequence signal
- States: ARG, ARY, AGR, AYR

Advanced VHDL FSMs

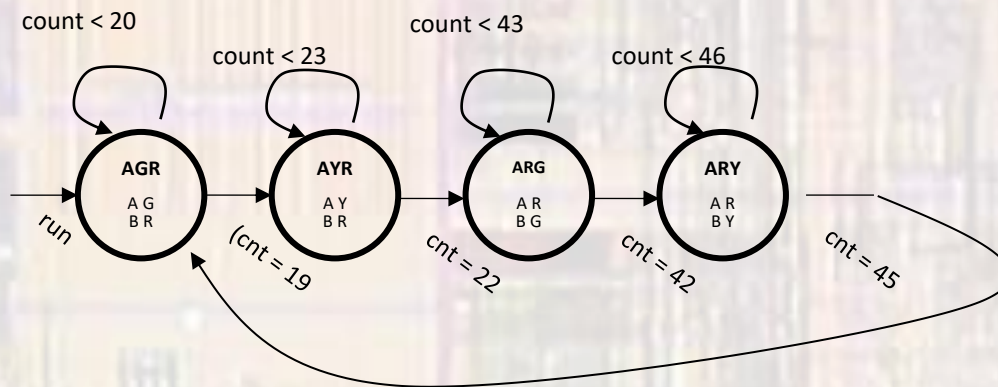- Stoplight – timed
 - 4 way stoplight – A dir and B dir
 - A RG for 20 clks, A RY for 3 clks, A GR for 20 clks, A YR for 3 clks, restart → total of 46 clks



Advanced VHDL FSMs

- Stoplight - timed

```
-----  
-- stoplight_timed_free_running.vhdl  
-- created 3/30/18  
-- tj  
-- rev 0  
-----  
-- timed 4 way stoplight  
-----  
-- Inputs: i_rstb, i_clk,  
-- Outputs: o_lights_Adir, o_lights_Bdir  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity stoplight_timed_free_running is  
  port (  
    i_clk : in std_logic;  
    i_rstb : in std_logic;  
  
    o_lights_Adir : out std_logic_vector(1 downto 0);  
    o_lights_Bdir : out std_logic_vector(1 downto 0)  
  );  
end entity;
```

```
architecture behavioral of stoplight_timed_free_running is  
  --  
  -- internal signals  
  --  
  type STATE_TYPE is (AGR, AYR, ARG, ARY);  
  signal state: STATE_TYPE;  
  signal state_next: STATE_TYPE;  
  
  signal cnt_sig: unsigned(5 downto 0);  
  
  --  
  -- create constants to allow changing the encoding  
  -- in one place  
  -- could also use generics  
  --  
  constant green: std_logic_vector := "00";  
  constant yellow: std_logic_vector := "01";  
  constant red: std_logic_vector := "10";  
  
begin  
  --  
  -- counter logic - free running, auto wrap  
  -- need count from 0 - 45 - not a power of 2  
  -- --> modulo counter  
  --  
  process(i_clk, i_rstb, state)  
  begin  
    if(i_rstb = '0') then  
      cnt_sig <= to_unsigned(0,6);  
    elsif(rising_edge(i_clk)) then  
      if(cnt_sig < 45) then  
        cnt_sig <= cnt_sig + 1;  
      else  
        cnt_sig <= to_unsigned(0,6);  
      end if;  
    end if;  
  end process;  
end architecture;
```

Advanced VHDL FSMs

- Stoplight - timed



```
-- next state logic
--
process(state, cnt_sig)
begin
  case state is
    when AGR =>
      if(cnt_sig = 19) then
        state_next <= AYR;
      else
        state_next <= AGR;
      end if;
    when AYR =>
      if(cnt_sig = 22) then
        state_next <= ARG;
      else
        state_next <= AYR;
      end if;
    when ARG =>
      if(cnt_sig = 42) then
        state_next <= ARY;
      else
        state_next <= ARG;
      end if;
    when ARY =>
      if(cnt_sig = 45) then
        state_next <= AGR;
      else
        state_next <= ARY;
      end if;
    when others =>
      -- cant just jump to an unexpected state
      -- freeze the current state until resolved
      state_next <= state;
  end case;
end process;
```

```
--
-- Register logic
--
process(i_clk, i_rstb)
begin
  -- reset
  if (i_rstb = '0') then
    state <= AGR;
  -- rising i_clk edge
  elsif (rising_edge(i_clk)) then
    state <= state_next;
  end if;
end process;

--
-- Output logic
--
process(state)
begin
  case state is
    when AGR =>
      o_lights_Adir <= green;
      o_lights_Bdir <= red;
    when AYR =>
      o_lights_Adir <= yellow;
      o_lights_Bdir <= red;
    when ARG =>
      o_lights_Adir <= red;
      o_lights_Bdir <= green;
    when ARY =>
      o_lights_Adir <= red;
      o_lights_Bdir <= yellow;
    when others =>
      -- something went wrong - force red-red
      o_lights_Adir <= red;
      o_lights_Bdir <= red;
  end case;
end process;
end behavioral;
```


Advanced VHDL FSMs

- Stoplight - timed

 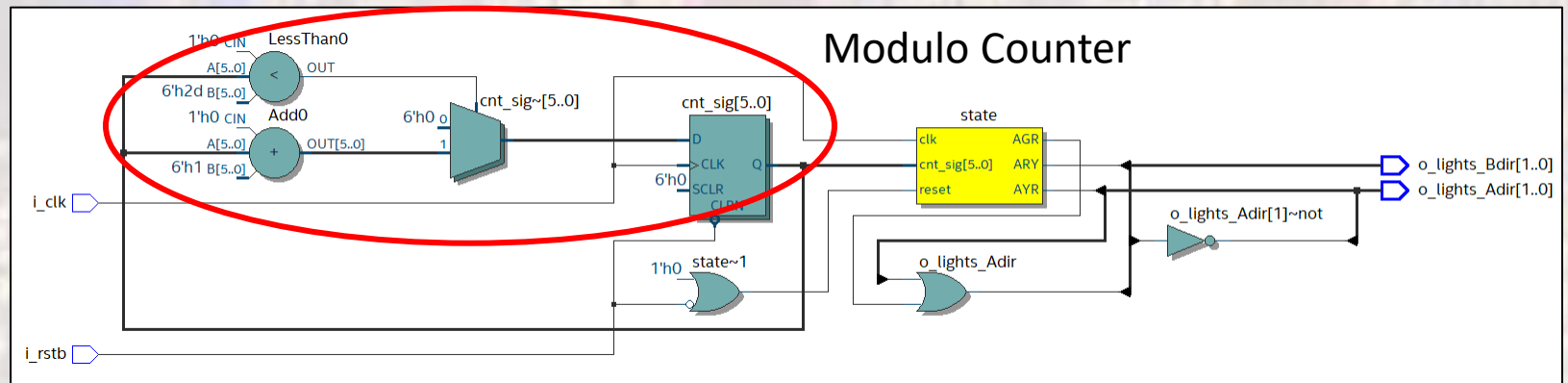

Advanced VHDL FSMs

- Stoplight - timed

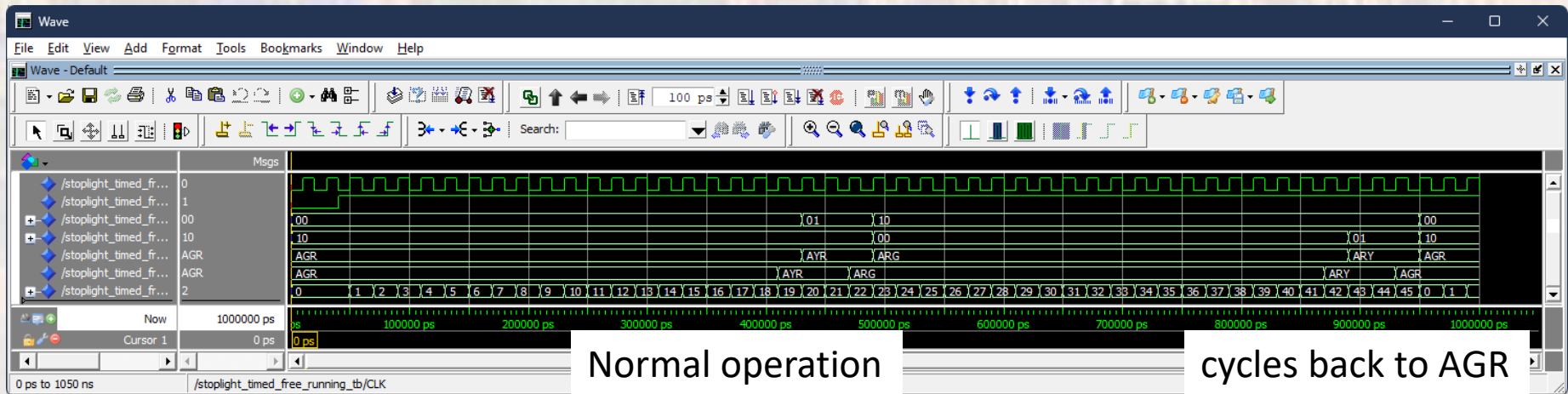

Normal operation

cycles back to AGR

Advanced VHDL FSMs


- Stoplight – timed
 - Improvements
 - Add a state for flashing red in both directions if something fails
 - Use generics or constants for the times
 - Can we calculate the modulo???
 - Maintenance, emergency, short RR after YR and RY

Advanced VHDL FSMs

- Accumulator – counting 1's
 - Generate a 1 clk wide pulse for every N^{th} 1 entered
 - generic: target count
 - inputs: clk, rstb, din
 - outputs: pulse
- States: IDLE, COLLECT, PULSE

Advanced VHDL FSMs

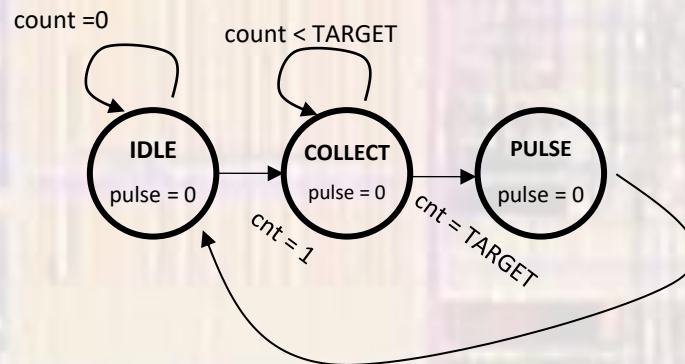- Accumulator – counting 1's
 - Generate a 1 clk wide pulse for every N^{th} 1 entered



Advanced VHDL FSMs

- Accumulator – counting 1's

```
-----  
-- ones_counter.vhdl  
-- created 3/30/18  
-- tj  
-- rev 0  
-----  
-- Counts a defined number of 1's, then outputs a pulse  
-----  
-- Inputs: i_rstb, i_clk, i_din  
-- Outputs: o_pulse  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use ieee.math_real.all;  
entity ones_counter is  
  generic(  
    CNT_TARGET: positive := 5  
  );  
  port (  
    i_clk: in std_logic;  
    i_rstb: in std_logic;  
    i_din: in std_logic;  
  
    o_pulse: out std_logic  
  );  
end entity;
```

```
architecture behavioral of ones_counter is  
  -- internal signals  
  --  
  type STATE_TYPE is (IDLE, COLLECT, PULSE);  
  signal state: STATE_TYPE;  
  signal state_next: STATE_TYPE;  
  
  constant CNT_SIZE: positive := integer(ceil(log2(real(CNT_TARGET))));  
  signal cnt_sig: unsigned((CNT_SIZE - 1) downto 0);  
  
begin  
  
  -- --> modulo CNT_TARGET  
  --  
  process(i_clk, i_rstb, i_din)  
    begin  
      if(i_rstb = '0') then  
        cnt_sig <= to_unsigned(0,CNT_SIZE);  
      elsif(rising_edge(i_clk)) then  
        if(cnt_sig < CNT_TARGET) then  
          if(i_din = '1') then  
            cnt_sig <= cnt_sig + 1;  
          else  
            cnt_sig <= cnt_sig;  
          end if;  
        else  
          cnt_sig <= to_unsigned(0,CNT_SIZE);  
        end if;  
      end if;  
    end process;
```

Advanced VHDL FSMs



- Accumulator – counting 1's

```
--  
-- next state logic  
--  
process(state, cnt_sig)  
begin  
  case state is  
    when IDLE =>  
      if(cnt_sig = 0) then  
        state_next <= IDLE;  
      else  
        state_next <= COLLECT;  
      end if;  
    when COLLECT =>  
      if(cnt_sig = CNT_TARGET) then  
        state_next <= PULSE;  
      else  
        state_next <= COLLECT;  
      end if;  
    when PULSE =>  
      state_next <= IDLE;  
    when others =>  
      state_next <= IDLE;  
  end case;  
end process;
```

```
--  
-- Register logic  
--  
process(i_clk, i_rstb)  
begin  
  -- reset  
  if (i_rstb = '0') then  
    state <= IDLE;  
  -- rising i_clk edge  
  elsif (rising_edge(i_clk)) then  
    state <= state_next;  
  end if;  
end process;  
  
--  
-- Output logic  
--  
process(state)  
begin  
  case state is  
    when IDLE =>  
      o_pulse <= '0';  
    when COLLECT =>  
      o_pulse <= '0';  
    when PULSE =>  
      o_pulse <= '1';  
    when others =>  
      o_pulse <= '0';  
  end case;  
end process;
```

Advanced VHDL FSMs

- Accumulator – counting 1's

 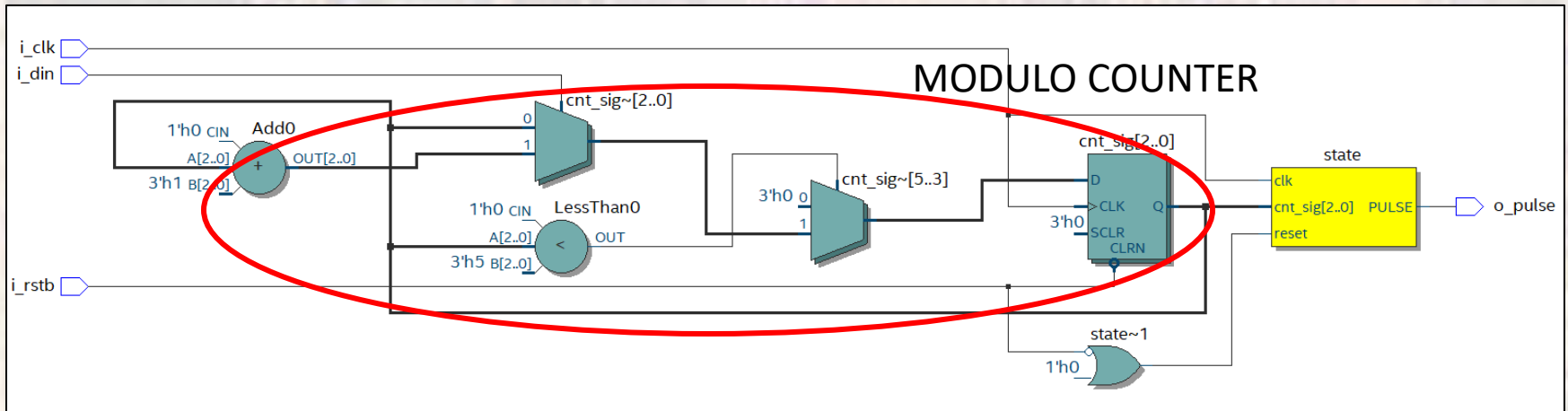

Source State	Destination State	Condition
1 COLLECT	PULSE	(cnt_sig[0], !cnt_sig[1], cnt_sig[2])
2 COLLECT	COLLECT	(!cnt_sig[0] + cnt_sig[0], !cnt_sig[1], !cnt_sig[2] + cnt_sig[0], !cnt_sig[1])
3 IDLE	IDLE	(!cnt_sig[0], !cnt_sig[1], !cnt_sig[2])
4 IDLE	COLLECT	(!cnt_sig[0], !cnt_sig[1], cnt_sig[2] + !cnt_sig[0], !cnt_sig[1] + cnt_sig[0])
5 PULSE	IDLE	

State Table
Transitions / Encoding /


100% 00:00:01

Advanced VHDL FSMs

- Accumulator – vending machine
 - Collect coins and vend when button pushed
 - inputs: clk, rstb, coin (5, 10, 25)
 - outputs: vend
 - States: IDLE, COLLECT, CHECK, VEND

Advanced VHDL FSMs

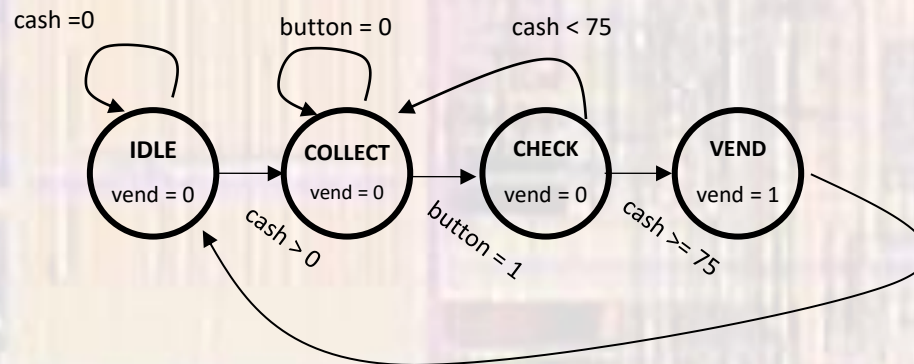- Accumulator – vending machine
 - Collect coins and vend when button pushed



Advanced VHDL FSMs

- Accumulator – vending machine

```
-----  
-- vend_1_item.vhdl  
-- created 4/25/25  
-- tj  
-----  
--  
-- 1 item vending machine - check for cash input  
-- nickles, dimes, quarters  
--    01    10    11  
--  
-----  
-- inputs coin, button, clk, rstb  
-- outputs item  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity vend_1_item is  
  port(  
    i_clk:      in std_logic;  
    i_rstb:     in std_logic;  
    i_coin:     in std_logic_vector(1 downto 0);  
    i_button:   in std_logic;  
  
    o_vend:     out std_logic  
  );  
end entity;
```

```
architecture behavioral of vend_1_item is  
  
  type STATE_TYPE is (IDLE, COLLECT, CHECK, VEND);  
  signal state:      STATE_TYPE;  
  signal state_next: STATE_TYPE;  
  
  -- support for $1 total, although cost is $0.75  
  signal cash_sig:  unsigned(6 downto 0);  
  
begin  
  
  -- cash counter  
  process(i_clk, i_rstb, i_coin, state)  
  begin  
    if(i_rstb = '0') then  
      cash_sig <= to_unsigned(0,7);  
    elsif(rising_edge(i_clk)) then  
      if (state = VEND) then  
        cash_sig <= to_unsigned(0, 7);  
      elsif(i_coin = "01") then  
        cash_sig <= cash_sig + 5;  
      elsif(i_coin = "10") then  
        cash_sig <= cash_sig + 10;  
      elsif(i_coin = "11") then  
        cash_sig <= cash_sig + 25;  
      else  
        cash_sig <= cash_sig;  
      end if;  
    end if;  
  end process;
```

Advanced VHDL FSMs

- Accumulator – vending machine



```
-- next state logic
process(state, cash_sig, i_button)
begin
  case state is
    when idle =>
      if(cash_sig = 0) then
        state_next <= IDLE;
      else
        state_next <= COLLECT;
      end if;
    when collect =>
      if(i_button = '0') then
        state_next <= COLLECT;
      else
        state_next <= CHECK;
      end if;
    when CHECK =>
      if(cash_sig >= to_unsigned(75, 7)) then
        state_next <= VEND;
      else
        state_next <= COLLECT;
      end if;
    when vend =>
      state_next <= idle;
    when others =>
      state_next <= idle;
  end case;
end process;
```

```
-- register logic
process(i_clk, i_rstb)
begin
  -- reset mode
  if(i_rstb = '0') then
    state <= IDLE;
  elsif(rising_edge(i_clk)) then
    state <= state_next;
  end if;
end process;

-- output logic
process(state)
begin
  case state is
    when IDLE =>
      o_vend <= '0';
    when COLLECT =>
      o_vend <= '0';
    when CHECK =>
      o_vend <= '0';
    when VEND =>
      o_vend <= '1';
    when others =>
      o_vend <= '0';
  end case;
end process;
end architecture;
```

Advanced VHDL FSMs

- Accumulator – vending machine

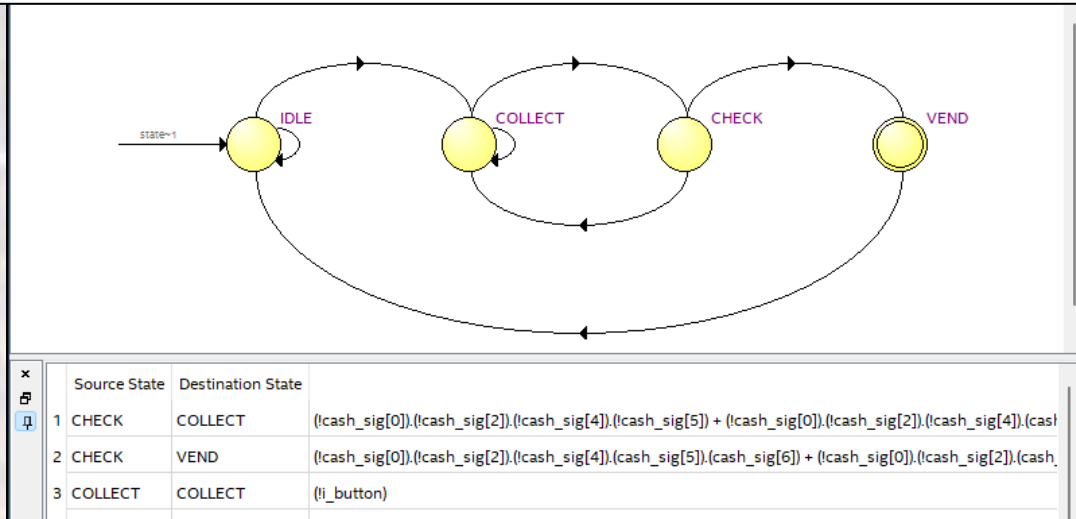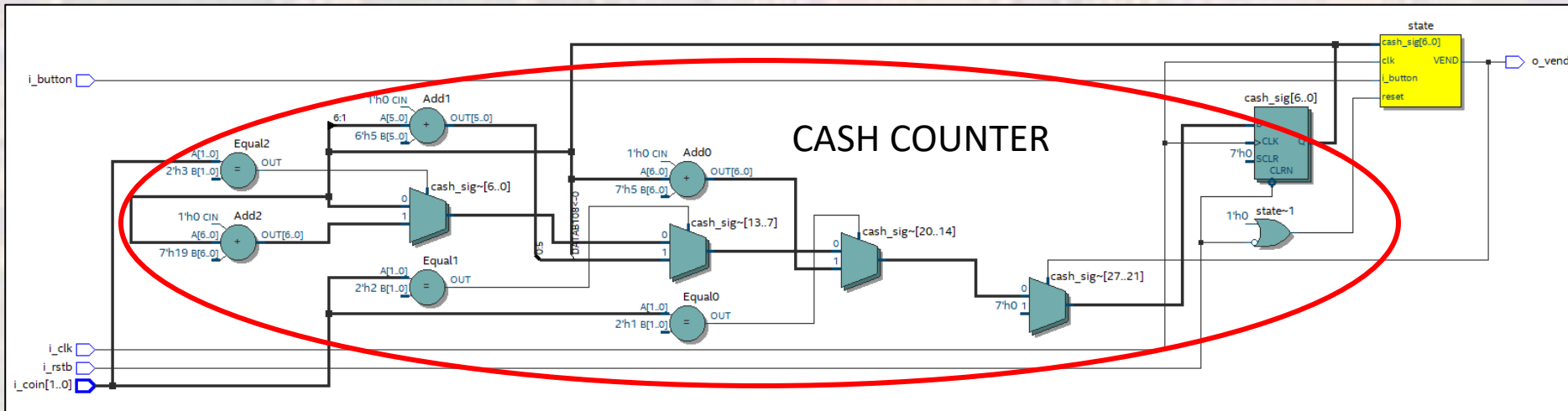

Advanced VHDL FSMs

- Accumulator – vending machine

