

VHDL Memories MUX Based

Last updated 3/26/25

VHDL Memories – Mux Based

- Four major VHDL memory solutions
 - Mux based
 - Only applicable for ROMs
 - FlipFlop based
 - Very large – only acceptable for very small memories
 - Inferred
 - Memory is implemented in a pre-built memory block
 - Memory block must exist in the platform
 - Tightly coupled memory – small but very fast
 - General memory – large and not as fast
 - External
 - The memory interface is implemented
 - The memory itself is a separate chip

VHDL Memories – Mux Based

N words x M bits/word

N array elements x SLV

- VHDL solution for memories
 - An array of `std_logic_vectors`
 - Coded just like the non-optimized long array of data words
- Array construct
 - New type, that has array type as its basis
`type my_new_type is array (0 to depth) of some_vhdl_type`
- Memory construct
 - Uses `std_logic_vector`
 - No understanding of the values (signed/unsigned) is assumed, just bits

```
type my_memory is array (0 to depth) of std_logic_vector((wordwidth - 1) downto 0);
```

VHDL Memories – Mux Based

- ROM – mux based
 - Read only
 - Memory values stored as constants

16 word, 16b/w (2B/w) ROM

```
--  
-- rom_muxbased_constants.vhd1  
-- created 4/25/17  
-- tj  
-- rev 0  
-----  
-- Mux based rom with constants for values  
-----  
-- inputs: addr  
-- outputs: data  
-----  
  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use ieee.math_real.all;  
  
entity rom_muxbased_constants is  
    generic(  
        mem_width: positive := 16;  
        mem_depth: positive := 16  
    );  
    port(  
        i_addr: in std_logic_vector(((integer(ceil(log2(real(mem_depth)))) - 1) downto 0);  
        o_data: out std_logic_vector((mem_width - 1) downto 0)  
    );  
end entity;
```

```
architecture behavioral of rom_muxbased_constants is  
  
    -- ROM structure  
    type rom_type is array (0 to (mem_depth - 1)) of std_logic_vector ((mem_width - 1) downto 0);  
  
    -- ROM contents  
    constant my_ROM: rom_type := (  
        0 => X"C010",  
        1 => X"C04A",  
        2 => X"5180",  
        3 => X"02C0",  
        4 => X"4640",  
  
        8 => X"2E40",  
        9 => X"6B00",  
        10 => X"F000",  
  
        others => X"F000"  
    );  
  
begin  
    o_data <= my_ROM(to_integer(unsigned(i_addr)));  
end architecture;
```

Special exception to "no initialization"

notice the frowny face :=(

We can assign values := because they are constant – just tying a wire high or low in the hardware

Calculating the # of address bits based on the mem-depth
- see next slide

VHDL Memories – Mux Based

- ROM – mux based
 - Address bit calculation

```
i_addr: in std_logic_vector((((integer(ceil(log2(real(mem_depth)))) - 1) downto 0);
```

`mem_depth`

only makes sense to be an integer

`real(mem_depth)`

turns it into a real number (not an int)

`log2(real(mem_depth))`

calculates the log base 2

requires a real input

provides a real output

`ceil(log2(real(mem_depth)))`

rounds up (next largest whole real number)

provides support for non- 2^N sizes

24 → 4.585 → 5.0

`integer(ceil(log2(real(mem_depth))))`



converts the real to an integer

must be integer to use as index

VHDL Memories – Mux Based

- ROM – mux based
 - Memory values stored as constants

Modelled as 1 mux per bit in the word

  

VHDL Memories – Mux Based

- Memory Test Benches
 - A proper memory testbench would test:
 - All addresses