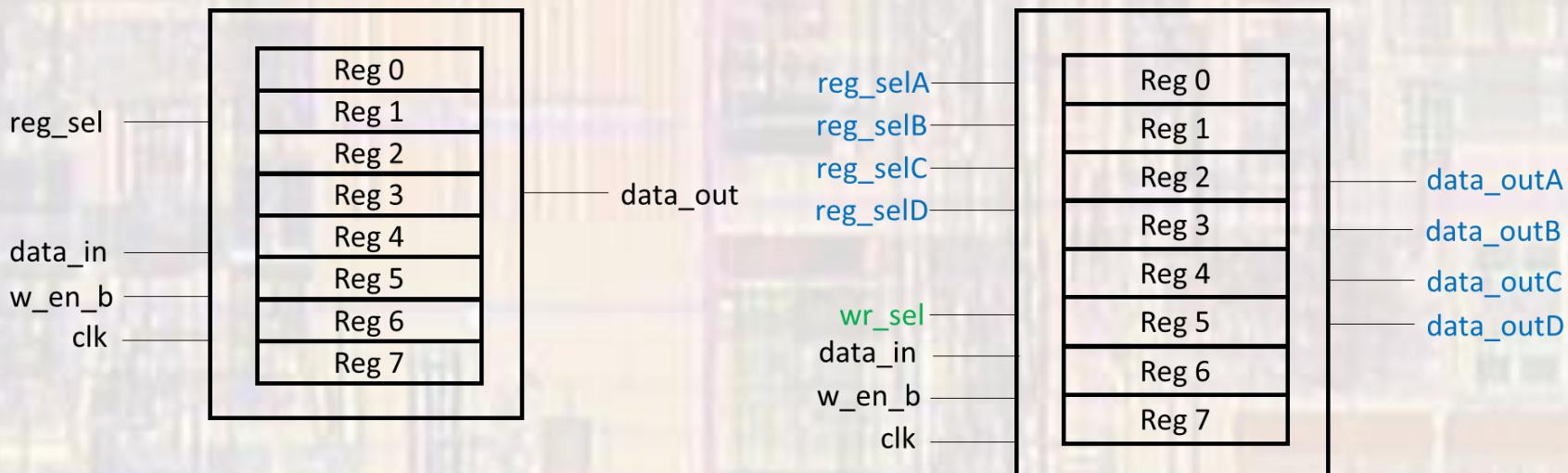


VHDL Register Files

Last updated 1/22/25

Register Files

- Register File
 - A register file is a collection of registers treated as a single entity
 - Commonly used in CPUs (e.g. RA, RB, ...)



VHDL Register Files

- Register File – 8, 16bit registers – 1 in/out

```
-- regfile_16x8x1
-- 8 - 16 bit registers
-- single input/output
-- created by johnsontimoj
-- 5/7/18
-- rev 0
--

-- Inputs: clk, reg_sel, we_bar, data_in
-- Outputs: data_out

-- note - reg files do not have a reset
--


library ieee;
use ieee.std_logic_1164.all;


entity regfile_16x8x1 is
  port (
    i_clk :      in std_logic;
    i_reg_sel :   in std_logic_vector(2 downto 0);
    i_data_in :   in std_logic_vector(15 downto 0);
    i_we_b:       in std_logic;

    o_data_out:  out std_logic_vector(15 downto 0)
  );
end entity;
```

```
architecture behavioral of regfile_16x8x1 is
  --
  -- register signals
  --
  signal reg_0: std_logic_vector(15 downto 0);
  signal reg_1: std_logic_vector(15 downto 0);
  signal reg_2: std_logic_vector(15 downto 0);
  signal reg_3: std_logic_vector(15 downto 0);
  signal reg_4: std_logic_vector(15 downto 0);
  signal reg_5: std_logic_vector(15 downto 0);
  signal reg_6: std_logic_vector(15 downto 0);
  signal reg_7: std_logic_vector(15 downto 0);

begin
  --
  -- register creation and write logic
  --
  process(i_clk)
  begin
    if(rising_edge(i_clk)) then
      if(i_we_b = '0') then
        case(i_reg_sel) is
          when "000" => reg_0 <= i_data_in;
          when "001" => reg_1 <= i_data_in;
          when "010" => reg_2 <= i_data_in;
          when "011" => reg_3 <= i_data_in;
          when "100" => reg_4 <= i_data_in;
          when "101" => reg_5 <= i_data_in;
          when "110" => reg_6 <= i_data_in;
          when "111" => reg_7 <= i_data_in;
          when others => reg_0 <= i_data_in; -- arbitrary
        end case;
      end if;
    end if;
  end process;

  --
  -- output logic
  --
  process(all)
  begin
    case(i_reg_sel) is
      when "000" => o_data_out <= reg_0;
      when "001" => o_data_out <= reg_1;
      when "010" => o_data_out <= reg_2;
      when "011" => o_data_out <= reg_3;
      when "100" => o_data_out <= reg_4;
      when "101" => o_data_out <= reg_5;
      when "110" => o_data_out <= reg_6;
      when "111" => o_data_out <= reg_7;
      when others => o_data_out <= reg_0; -- arbitrary
    end case;
  end process;
end behavioral;
```

 

There are more efficient ways to code this – using an array


VHDL Register Files

- Register File – 8, 16bit registers – 4 outputs

```
-- regfile_16x8x4
-- 8 - 16 bit registers
-- 4 input/output
-- created by johnsontimoj
-- 5/7/18
-- rev 0
--
-- Inputs: clk, reg_sel, wr_sel, we_bar, data_in
-- Outputs: data_out a, b, c, d
-- note - reg files do not have a reset
--
library ieee;
use ieee.std_logic_1164.all;
entity regfile_16x8x4 is
  port (
    i_clk : in std_logic;
    i_reg_selA : in std_logic_vector(2 downto 0);
    i_reg_selB : in std_logic_vector(2 downto 0);
    i_Reg_selC : in std_logic_vector(2 downto 0);
    i_Reg_selD : in std_logic_vector(2 downto 0);
    i_wr_sel : in std_logic_vector(2 downto 0);
    i_data_in : in std_logic_vector(15 downto 0);
    i_we_b: in std_logic;
    o_data_outA: out std_logic_vector(15 downto 0);
    o_data_outB: out std_logic_vector(15 downto 0);
    o_data_outC: out std_logic_vector(15 downto 0);
    o_data_outD: out std_logic_vector(15 downto 0)
  );
end entity;
```

```
architecture behavioral of regfile_16x8x4 is
  -- register signals
  --
  signal reg_0: std_logic_vector(15 downto 0);
  signal reg_1: std_logic_vector(15 downto 0);
  signal reg_2: std_logic_vector(15 downto 0);
  signal reg_3: std_logic_vector(15 downto 0);
  signal reg_4: std_logic_vector(15 downto 0);
  signal reg_5: std_logic_vector(15 downto 0);
  signal reg_6: std_logic_vector(15 downto 0);
  signal reg_7: std_logic_vector(15 downto 0);
begin
  --
  -- write and register creation logic
  --
  process(i_clk)
  begin
    if(rising_edge(i_clk)) then
      if(i_we_b = '0') then
        case(i_wr_sel) is
          when "000" => reg_0 <= i_data_in;
          when "001" => reg_1 <= i_data_in;
          when "010" => reg_2 <= i_data_in;
          when "011" => reg_3 <= i_data_in;
          when "100" => reg_4 <= i_data_in;
          when "101" => reg_5 <= i_data_in;
          when "110" => reg_6 <= i_data_in;
          when "111" => reg_7 <= i_data_in;
          when others => reg_0 <= i_data_in; -- arbitrary
        end case;
      end if;
    end if;
  end process;
```

```
-- output logic
--
process(all)
begin
  case(i_reg_selA) is
    when "000" => o_data_outA <= reg_0;
    when "001" => o_data_outA <= reg_1;
    when "010" => o_data_outA <= reg_2;
    when "011" => o_data_outA <= reg_3;
    when "100" => o_data_outA <= reg_4;
    when "101" => o_data_outA <= reg_5;
    when "110" => o_data_outA <= reg_6;
    when "111" => o_data_outA <= reg_7;
    when others => o_data_outA <= reg_0; -- arbitrary
  end case;
  case(i_reg_selB) is
    when "000" => o_data_outB <= reg_0;
    when "001" => o_data_outB <= reg_1;
    when "010" => o_data_outB <= reg_2;
    when "011" => o_data_outB <= reg_3;
    when "100" => o_data_outB <= reg_4;
    when "101" => o_data_outB <= reg_5;
    when "110" => o_data_outB <= reg_6;
    when "111" => o_data_outB <= reg_7;
    when others => o_data_outB <= reg_0; -- arbitrary
  end case;
  case(i_reg_selC) is
    when "000" => o_data_outC <= reg_0;
    when "001" => o_data_outC <= reg_1;
    when "010" => o_data_outC <= reg_2;
    when "011" => o_data_outC <= reg_3;
    when "100" => o_data_outC <= reg_4;
    when "101" => o_data_outC <= reg_5;
    when "110" => o_data_outC <= reg_6;
    when "111" => o_data_outC <= reg_7;
    when others => o_data_outC <= reg_0; -- arbitrary
  end case;
  case(i_reg_selD) is
    when "000" => o_data_outD <= reg_0;
    when "001" => o_data_outD <= reg_1;
    when "010" => o_data_outD <= reg_2;
    when "011" => o_data_outD <= reg_3;
    when "100" => o_data_outD <= reg_4;
    when "101" => o_data_outD <= reg_5;
    when "110" => o_data_outD <= reg_6;
    when "111" => o_data_outD <= reg_7;
    when others => o_data_outD <= reg_0; -- arbitrary
  end case;
end process;
```

 

There are more efficient ways to code this – using an array