

VHDL Shift Registers

Last updated 1/9/25

VHDL Shift Registers

- Shift Register
 - Shift a series of bits within a register
 - Left/right
 - N bit shift
 - Wrapping (rotate)
 - Load register with load signal
 - Direction
 - Non-wrapping
 - Data input – both sides
 - Direction

DATA	dir	load	Din	result
XXXXX	X	1	00100	00101
00101	R	0	XXXXX	10010
00101	L	0	XXXXX	01010

Din	DATA	dir	result
1	00100	R	10010
0	10010	R	01001
1	01001	L	10011

VHDL Shift Registers

- Non-wrapping - 4 bit
- D shifts in from left or right

using brute force
concatenation
to perform the shift

```
-----
-- reg_shift_4bit.vhdl
-- by: johnsontimoj
-- created: 12/31/24
-- version: 0.0
-----

-- standard 4 bit shift register
-- inputs: clk, rstb, shift, dir, d
--         dir: 0 -> L, 1 -> R
--
-- outputs: q
--
-----

library ieee;
use ieee.std_logic_1164.all;

entity reg_shift_4bit is
    port(
        i_clk:   in std_logic;
        i_rstb:  in std_logic;
        i_shift: in std_logic;
        i_dir:   in std_logic;  -- 0 -> L
        i_D:     in std_logic;


        o_Q:     out std_logic_vector(3 downto 0)
    );
end entity;

architecture behavioral of reg_shift_4bit is
```


```
begin
    process (i_clk, i_rstb)
    begin
        -- asynch
        if (i_rstb = '0') then
            o_Q <= "0000";
        -- synch
        elsif (rising_edge(i_clk)) then
            -- shift?
            if(i_shift = '1') then
                -- L
                if(i_dir = '0') then
                    o_Q <= o_Q(2) & o_Q(1) & o_Q(0) & i_D;
                else
                    o_Q <= i_D & o_Q(3) & o_Q(2) & o_Q(1);
                end if; -- dir
            end if; -- shift - no else needed - FF template being used
        end if; -- main - no else needed - FF template being used
    end process;
end architecture;
```

VHDL Shift Registers

- 4 bit
- D shifts in from left or right

 

Flow Summary	
<<Filter>>	
Flow Status	Successful - Thu Jan 09 12:33:06 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	reg_shift_4bit
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	4
Total registers	4
Total pins	9
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

 

no shift


left shift
4

right shift

VHDL Shift Registers

- n bit
 - D shifts in from left or right

using concatenation
to perform the shift

 


```
-- reg_shift_nbit.vhdl
-- by: johnsontimoj
-- created: 12/31/24
-- version: 0.0
--
-- standard N bit shift register
-- inputs: clk, rstb, shift, dir, d
--         dir: 0 -> L, 1 -> R
--
-- outputs: q
--
--
library ieee;
use ieee.std_logic_1164.all;
entity reg_shift_nbit is
  generic(
    N: positive := 8
  );
  port(
    i_clk:   in std_logic;
    i_rstb:  in std_logic;
    i_shift: in std_logic;
    i_dir:   in std_logic; -- 0 -> L
    i_D:     in std_logic;
    o_Q:     out std_logic_vector((N - 1) downto 0)
  );
end entity;
```

```
architecture behavioral of reg_shift_nbit is
begin
  process (i_clk, i_rstb)
  begin
    -- asynch
    if (i_rstb = '0') then
      o_Q <= (others => '0');
    -- synch
    elsif (rising_edge(i_clk)) then
      -- shift?
      if (i_shift = '1') then
        -- L
        if (i_dir = '0') then
          o_Q <= o_Q((N - 1) - 1) downto 0) & i_D;
        else
          o_Q <= i_D & o_Q((N - 1) downto 1);
        end if; -- dir
      end if; -- shift - no else needed - FF template being used
    end if; -- main - no else needed - FF template being used
  end process;
end architecture;
```

VHDL Shift Registers

 - n – bit (N = 8)
 - D shifts in from left or right



Flow Summary	
<<Filter>>	
Flow Status	Successful - Thu Jan 09 12:51:15 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	reg_shift_nbit
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	8
Total registers	8
Total pins	13
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

VHDL Shift Registers

- n- bit w/load

asynchronous load

```
-----
-- reg_shift_nbit_load.vhdl
-- by: johnsontimoj
-- created: 12/31/24
-- version: 0.0
-----

-- standard N bit shift register with load
-- inputs: clk, rstb, shift, dir, d
-- dir: 0 -> L, 1 -> R
--
-- outputs: q
--
-----

library ieee;
use ieee.std_logic_1164.all;


entity reg_shift_nbit_load is
  generic(
    N: positive := 8
  );
  port(
    i_clk: in std_logic;
    i_rstb: in std_logic;
    i_shift: in std_logic;
    i_dir: in std_logic; -- 0 -> L
    i_load: in std_logic;
    i_D : in std_logic_vector((N - 1) downto 0);

    o_Q : out std_logic_vector((N - 1) downto 0)
  );
end entity;
```

```
architecture behavioral of reg_shift_nbit_load is
begin
  process (i_clk, i_rstb, i_load)
  begin
    -- asynch
    if (i_rstb = '0') then
      o_Q <= (others => '0');
    elsif (i_load = '1') then
      o_Q <= i_D;
    -- synch
    elsif (rising_edge(i_clk)) then
      -- shift?
      if (i_shift = '1') then
        -- L
        if (i_dir = '0') then
          o_Q <= o_Q(((N - 1) - 1) downto 0) & o_Q(N - 1);
        else
          o_Q <= o_Q(0) & o_Q((N - 1) downto 1);
        end if; -- dir
      end if; -- shift - no else needed - FF template being used
    end if; -- main - no else needed - FF template being used
  end process;
end architecture;
```

VHDL Shift Registers


- n- bit w/load

 

Flow Summary	
<<Filter>>	
Flow Status	Successful - Thu Jan 09 13:03:24 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	reg_shift_nbit_load
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	34
Total registers	8
Total pins	21
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

reset

load

 

no shift

8 left shift

no shift

right shift