

# VHDL Signals

Last updated 12/17/24

# VHDL Signals

This is not a programming language  
It is a hardware description language

# VHDL Signals

- VHDL elements fall into 2 categories
  - Synthesizable – types that can be used to create hardware
  - Un-synthesizable – types that cannot be used to create hardware
    - These exist for simulation, test and documentation
- The basic VHDL library is invoked in 2 steps

```
library ieee;  
use ieee.std_logic_1164.all;
```

# VHDL Signals

- A VHDL **signal value** represents a logic value
  - There are 3 values for a VHDL signal that can be synthesized

Value	Definition	Synthesizable
'0'	Forcing 0	Y
'1'	Forcing 1	Y
'Z'	High Impedance	Y

- There are 2 additional values for a VHDL signal used in simulations

Value	Definition	Synthesizable
'U'	Un-initialized	N
'X'	Unknown	N


additional values exist – but are out of the scope of this class

# VHDL Signals

- A VHDL **signal** represents a wire
  - A single wire is identified as a **std\_logic signal**
 
## Declaration

```
signal in1: std_logic;  
signal in2: std_logic;  
signal out1: std_logic;
```



## Behavior

```
out1 <= in1 AND in2;
```



# VHDL Signals

- A VHDL **signal** represents a wire
  - A bus (collection of wires) is identified as a **std\_logic\_vector signal**
    - Includes the dimension of the bus – in wire order – 7 6 5 4 3 2 1 0
      - Format: **std\_logic\_vector((n-1) downto 0)**


Declaration

```
signal inA:      std_logic_vector(7 downto 0);  
signal inB:      std_logic_vector(7 downto 0);  
signal out_AB:   std_logic_vector(7 downto 0);
```

inA     8/  
inB     8/  
out\_AB  8/

Behavior

```
out_AB <= inA OR inB;
```

 


After a SLV signal has been declared – we refer to the entire signal by its name

# VHDL Signals

- Individual wires in a bus can be identified
  - `signal_name(wire number)`
 
## Declaration

```
signal inA:    std_logic_vector(7 downto 0);  
signal out1:  std_logic;
```



## Behavior

```
out1 <= NOT inA(3);
```



# VHDL Signals


- Contiguous wires in a bus can be identified
  - signal\_name(wire range)
  - Format: signal\_name(**n** downto **m**)

Declaration

```
signal inA:    std_logic_vector(7 downto 0);  
signal out1:  std_logic_vector(3 downto 0);
```

Behavior

```
out1 <= NOT inA(6 downto 3);
```

 



# VHDL Signals



- Wires and buses can be combined to create a new signal (bus) name
- **No new wires are created** – just connected to an additional name
- Concatenation operator **&**

## Declaration

```
signal in1:      std_logic;  
signal inA:     std_logic_vector(7 downto 0);  
signal inB:     std_logic_vector(3 downto 0);  
signal new_bus: std_logic_vector(12 downto 0);
```

## Behavior

```
new_bus <= inA & in1 & inB;
```

  

new\_bus: inA(7), inA(6), ... inA(0), in1, inB(3), ...inB(0)