

VHDL Synthesis

Simple Constructs

Last updated 1/7/25

VHDL Synthesis - Simple Constructs

VHDL is not a programming language
It is a hardware description language

VHDL Synthesis - Simple Constructs

- Create a hardware description for an electronic version of a **binary** 4 input combination lock




1/0 inputs

VHDL Synthesis - Simple Constructs

- Create a hardware description for an electronic version of a **binary** 4 input combination lock
 - Design Decisions
 - **Default state** (locked or unlocked)?
 - Input signal **activation condition** (high or low)?
 - Output signal **activation condition** (lock or unlock)?
 - Additional use case information
 - Target customer is private and commercial gym locker rooms
 - Normally the lockers will be unlocked so customers can place items in the locker and then lock it
 - Default to **unlocked**
 - Output signal will be **active high** to **lock**

VHDL Synthesis - Simple Constructs

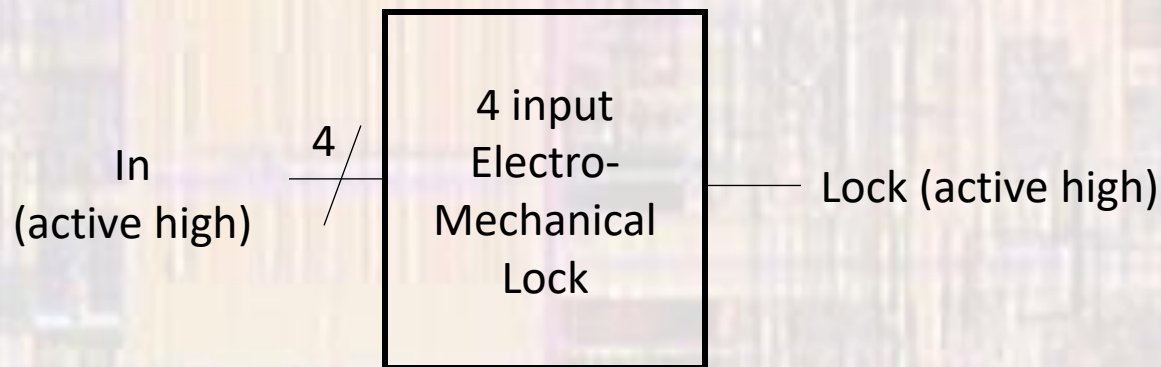- Create a hardware description for an electronic version of a **binary** 4 input combination lock
 - Block Diagram



VHDL Synthesis - Simple Constructs

- Create a hardware description for an electronic version of a **binary** 4 input combination lock

```
-----  
-- lock_4in_binary.vhd1  
-- created 7/5/2018  
-- tj  
-- rev 0  
-----  
-- 4 input (binary) lock - brute-force  
-- active high inputs, active high output - locked  
-----  
--  
-- Inputs: in 4 bits  
-- Outputs: lock  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity lock_4in_binary is  
  generic(  
    COMBINATION: std_logic_vector(3 downto 0) := "1011"  
  );  
  port (  
    i_in: in std_logic_vector(3 downto 0);  
    o_lock: out std_logic  
  );  
end entity;
```


Use generics for values that can be changed in different versions of the design

```
architecture behavioral of lock_4in_binary is  
begin  
  with i_in select o_lock <= '1' when (COMBINATION),  
                           '0' when others;  
end behavioral;
```


can use a signal name instead of an explicit vector

VHDL Synthesis - Simple Constructs

 - Create a hardware description for an electronic version of a **binary** 4 input combination lock





Flow Summary	
<<Filter>>	
Flow Status	Successful - Sat Jan 04 09:50:01 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	lock_4in_binary
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	1
Total registers	0
Total pins	5
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

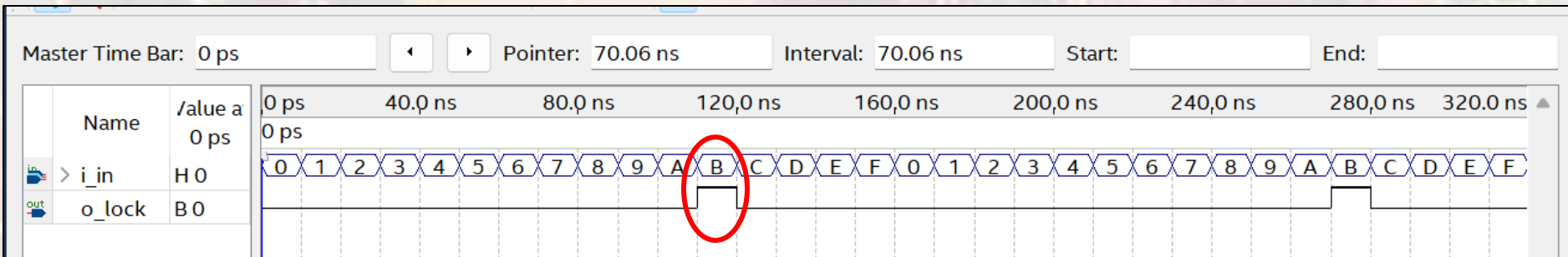

VHDL Synthesis - Simple Constructs

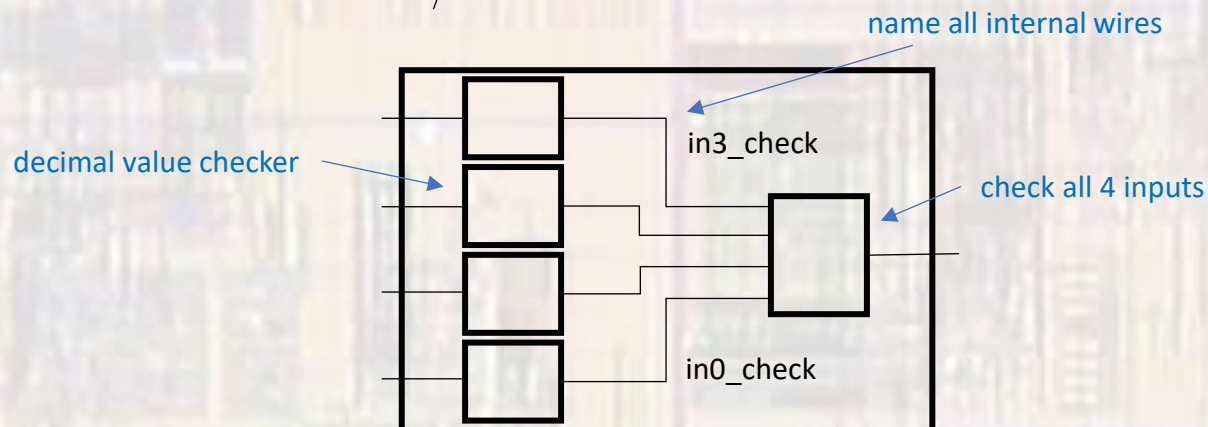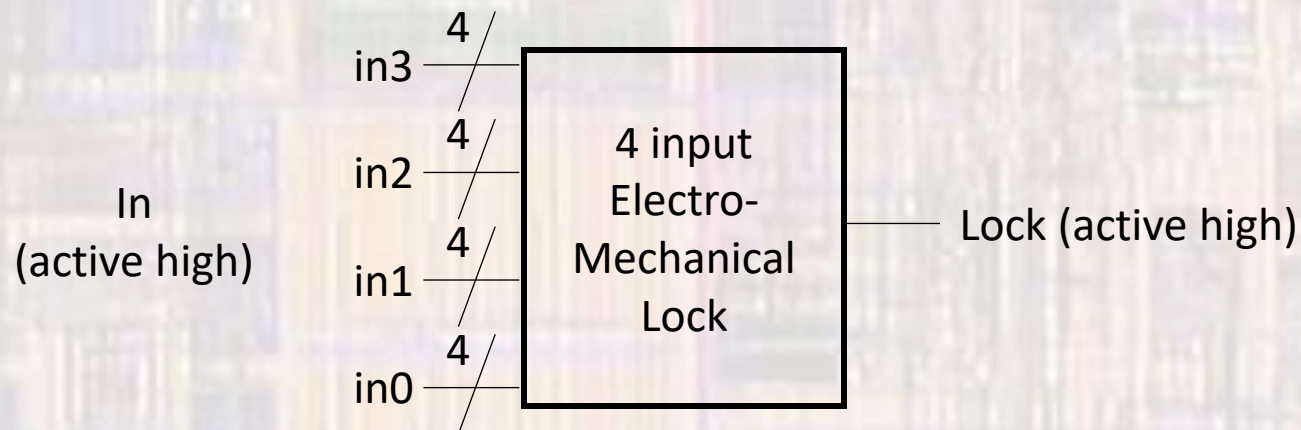- Create a hardware description for an electronic version of a **decimal** 4 input combination lock
 - Block Diagram



VHDL Synthesis - Simple Constructs

- Create a hardware description for an electronic version of a **decimal** 4 input combination lock

```
-- lock_4in_decimal.vhd1
--
-- created 7/5/2018
-- tj
--
-- rev 0
-----
--
-- 4 input (decimal) lock - brute-force
-- active high inputs, active high output - locked
-----
--
-- Inputs: in0 - in3, 4 bits each
-- Outputs: lock
-----
library ieee;
use ieee.std_logic_1164.all;


entity lock_4in_decimal is
  generic(
    COMBINATION0: std_logic_vector(3 downto 0) := "1010";
    COMBINATION1: std_logic_vector(3 downto 0) := "1011";
    COMBINATION2: std_logic_vector(3 downto 0) := "1100";
    COMBINATION3: std_logic_vector(3 downto 0) := "1101"
  );
  port (
    i_in0: in std_logic_vector(3 downto 0);
    i_in1: in std_logic_vector(3 downto 0);
    i_in2: in std_logic_vector(3 downto 0);
    i_in3: in std_logic_vector(3 downto 0);
    o_lock: out std_logic
  );
end entity;
```

```
architecture behavioral of lock_4in_decimal is
  signal in0_check: std_logic;
  signal in1_check: std_logic;
  signal in2_check: std_logic;
  signal in3_check: std_logic;
begin
  with i_in0 select in0_check <=
    '1' when (COMBINATION0),
    '0' when others;
  with i_in1 select in1_check <=
    '1' when (COMBINATION1),
    '0' when others;
  with i_in2 select in2_check <=
    '1' when (COMBINATION2),
    '0' when others;
  with i_in3 select in3_check <=
    '1' when (COMBINATION3),
    '0' when others;



  o_lock <= in0_check AND in1_check AND in2_check AND in3_check;
end behavioral;
```

VHDL Synthesis - Simple Constructs

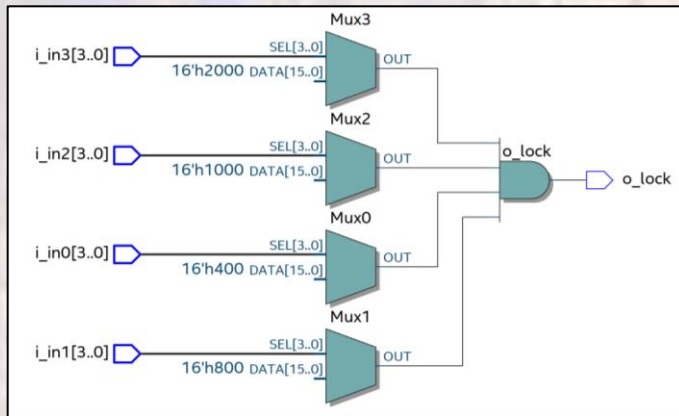- Create a hardware description for an electronic version of a **decimal** 4 input combination lock



Flow Summary	
Flow Status	Successful - Sat Jan 04 10:18:18 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	lock_4in_decimal
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	5
Total registers	0
Total pins	17
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

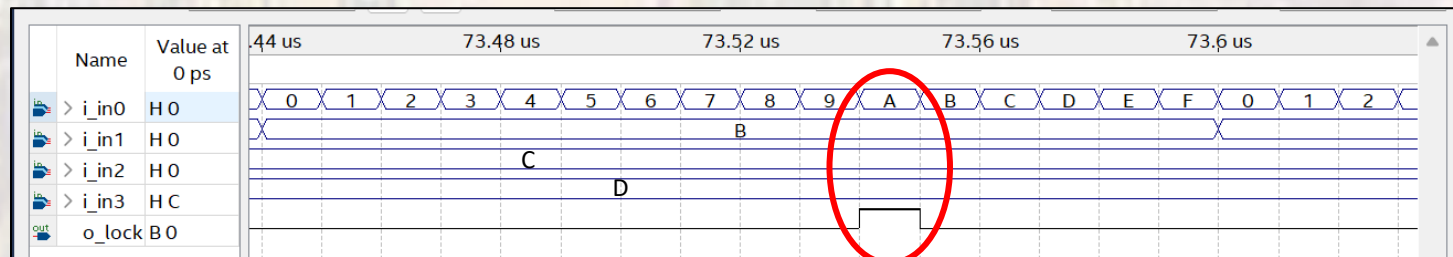 


VHDL Synthesis - Simple Constructs

- Create a hardware description for a car starter mechanism
 - Start conditions
 - Brake on
 - Key in range
 - Not running
 - In park
 - Button pushed
 - All inputs active high
 - Output active high

VHDL Synthesis - Simple Constructs

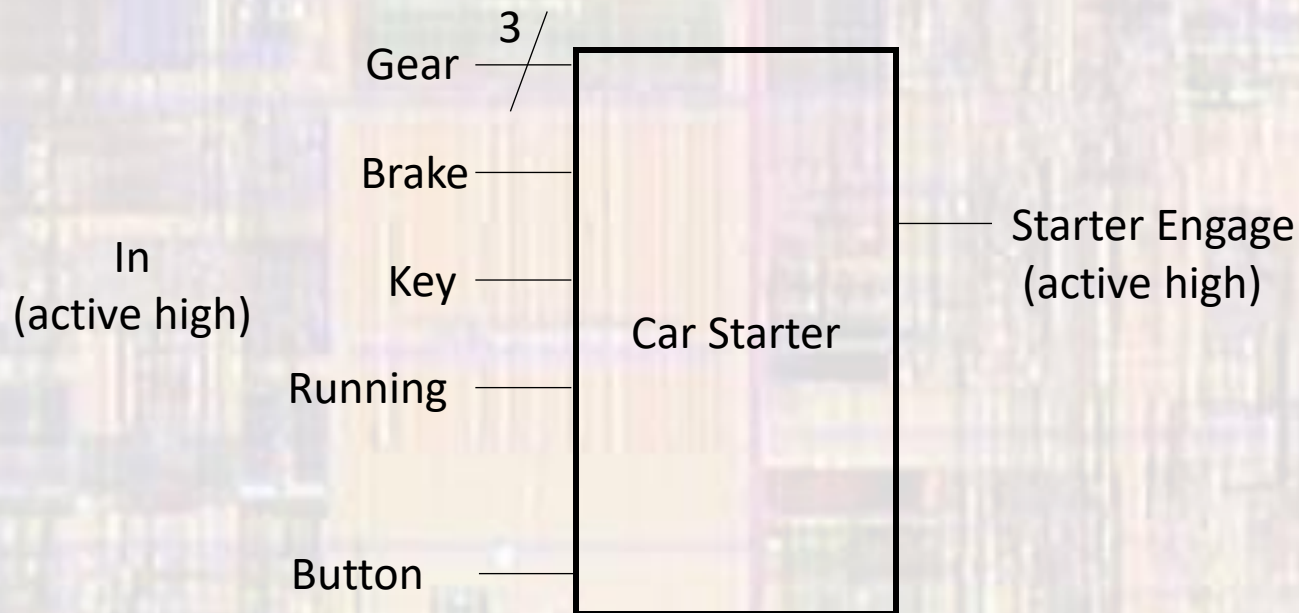- Create a hardware description for a car starter mechanism
 - Block Diagram



Gear encoding: 000 – Park, 001 – Neutral, 100 – Reverse, 010 - L1, 011 – L2

VHDL Synthesis - Simple Constructs


- Create a hardware description for a car starter mechanism

```
-----  
-- starter_car.vhdl  
-- created 7/5/2018  
-- tj  
-- rev 0  
-----  
-- car starter module - brute-force  
-- active high inputs, active high outputs  
-- park - 000  
-----  
-- Inputs: key, brake, gear (3 bit), button, eng running,  
-- Outputs: starter engage  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
entity starter_car is  
  generic(  
    PARK: std_logic_vector(2 downto 0) := "000"  
  );  
  port(  
    i_key:          in std_logic;  
    i_brake:        in std_logic;  
    i_gear:         in std_logic_vector(2 downto 0);  
    i_eng_running:  in std_logic;  
    i_button:       in std_logic;  
    o_starter_engage: out std_logic  
  );  
end entity;
```

```
architecture behavioral of starter_car is  
  signal start_ok: std_logic;  
begin  
  start_ok <= '0' when (i_key = '0')           else  
              '0' when (i_brake = '0')        else  
              '0' when (i_gear /= (PARK))     else  
              '0' when (i_eng_running = '1')  else  
              '1';  
  
  o_starter_engage <= '0' when (start_ok = '0') else  
                     '1' when (i_button = '1') else  
                     '0';  
end architecture;
```

VHDL Synthesis - Simple Constructs


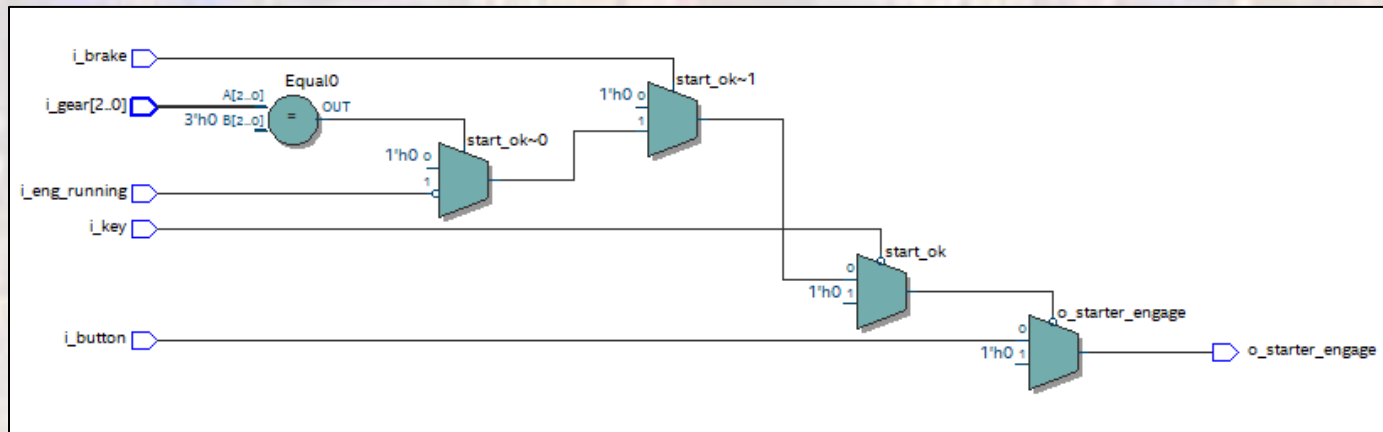
- Create a hardware description for a car starter mechanism



Flow Summary	
Filter	
Flow Status	Successful - Mon Jan 06 09:24:41 2025
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	general
Top-level Entity Name	starter_car
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	2
Total registers	0
Total pins	8
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total PLLs	0
UFM blocks	0
ADC blocks	0

VHDL Synthesis - Simple Constructs

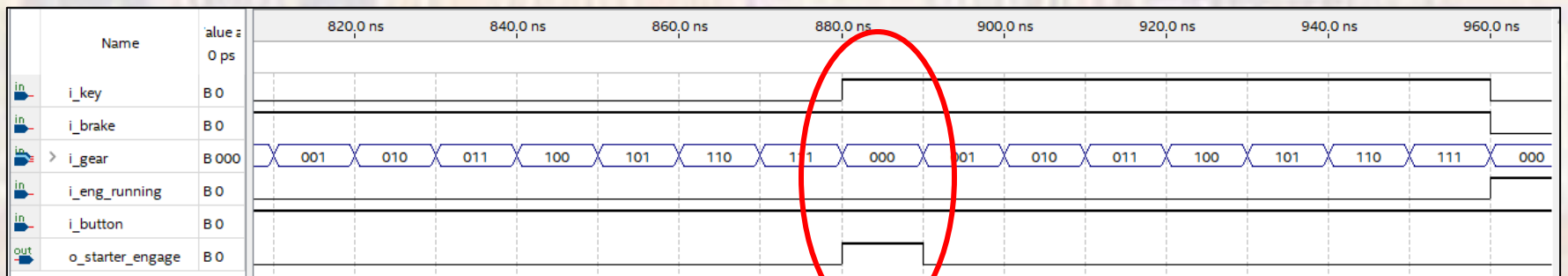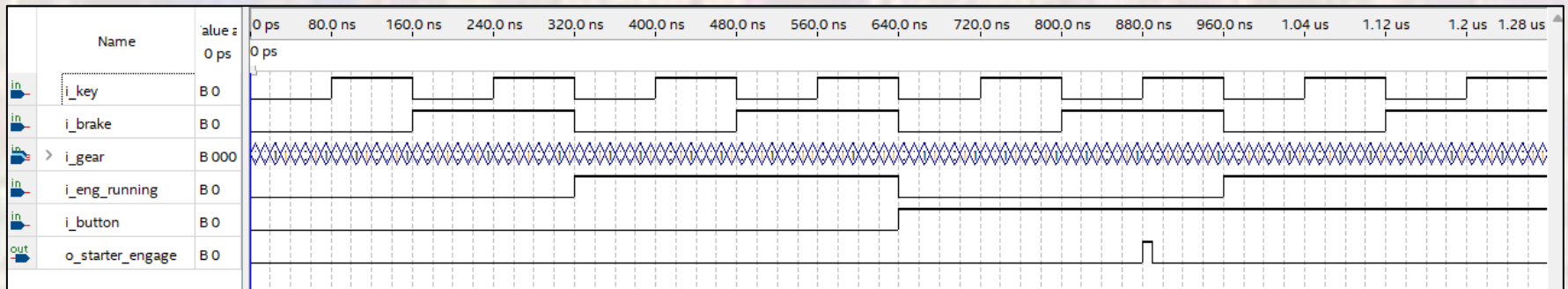- Create a hardware description for a car starter mechanism



key, brake, park, not running, button