

# Logic Review

Common – last updated 3/4/19

# Logic Review


- Buffers

non-Inverting



In	Out
0	0
1	1

Inverting

 

In	Out
0	1
1	0

notA     $\sim A$      $A'$

Tri-State




Tri	In	OUT
0	0	1
0	1	0
1	0	Z
1	1	Z

In	Tri	OUT
A	0	$\sim A$
X	1	Z

# Logic Review

- Simple Gates



AND/NAND

 

A	B	AND OUT	NAND OUT
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

A and B     A nand B  
 $A \wedge B$       $(A \wedge B)'$   
 $A \& B$       $A \& B$   
 $AB$       $A*B$


OR/NOR

  

A	B	OR OUT	NOR OUT
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

A or B     A nor B  
 $A \vee B$       $(A \vee B)'$   
 $A | B$       $A | B$   
 $A + B$

XOR/XNOR

 


A	B	XOR OUT	XNOR OUT
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

A xor B     A xnor B  
 $A \oplus B$       $(A \oplus B)'$

# Logic Review


- Switches

Switch

 


Ctl	State
0	X
1	A = B

Switch

 

Ctl	State
0	X
1	A = B


Tristate

 


In	Tri	Tri bar	Out
A	0	0	U
A	0	1	A'
A	1	0	Z
A	1	1	U

# Logic Review

- Coder / Decoder

 


b3	b2	b1	b0	out 1	out 0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


In 1	In 2	b3	b2	b1	b0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

# Logic Review

- Multiplexer/ Demultiplexer

 


s1	s0	out
0	0	b0
0	1	b1
1	0	b2
1	1	b3

 

s1	s0	b3	b2	b1	b0
0	0	0	0	0	in
0	1	0	0	in	0
1	0	0	in	0	0
1	1	in	0	0	0


# Logic Review

- Logic Analysis

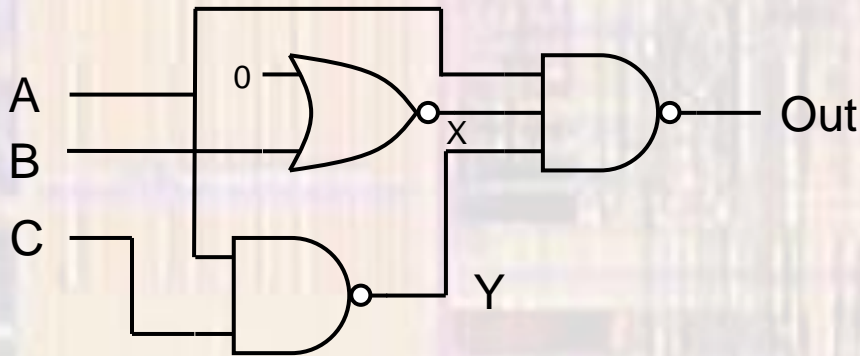

# Logic Review

- Logic Analysis

 

A	B	C	X	Y	Out
			$(B+0)'$	$(AC)'$	$(AXY)'$
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	0	1	1
0	1	1	0	1	1
1	0	0	1	1	0
1	0	1	1	0	1
1	1	0	0	1	1
1	1	1	0	0	1



# Logic Review

- de Morgan's Laws

$$(A \cup B)' = A' \cap B'$$

$$(A \cap B)' = A' \cup B'$$

$$(A')' = A$$

$$\overline{(A + B)} = \overline{A} \overline{B}$$

$$\overline{(AB)} = \overline{A} + \overline{B}$$

$$\overline{\overline{A}} = A$$

# Logic Review

- de Morgan's Laws

$$(A \cup B)' = A' \cap B'$$


$$(A \cap B)' = A' \cup B'$$

$$(A')' = A$$

$$\overline{(A + B)} = \overline{A} \overline{B}$$

$$\overline{(AB)} = \overline{A} + \overline{B}$$

$$\overline{\overline{A}} = A$$

 

# Logic Review

- de Morgan's Laws

$$(A \cup B)' = A' \cap B'$$


$$(A \cap B)' = A' \cup B'$$

$$(A')' = A$$

$$\overline{(A + B)} = \overline{A} \overline{B}$$

$$\overline{(AB)} = \overline{A} + \overline{B}$$

$$\overline{\overline{A}} = A$$

 

$$\begin{aligned} \text{Out} &= \overline{\overline{A}XY} \\ &= \overline{A(\overline{B+0})(\overline{AC})} \\ &= \overline{A} + (B+0) + (AC) \\ &= \overline{A} + B + AC \end{aligned}$$

# Logic Review

- Sum-of-Products, Product-of-Sums

Sum-of-Products

$$(A \cap B) \cup (C \cap D) \cup (E \cap F)$$

$$AB + CD + EF$$

Product-of-Sums

$$(A \cup B) \cap (C \cup D) \cap (E \cup F)$$

$$(A + B)(C + D)(E + F)$$

Why ???

# Logic Review

- minterm / maxterm


A	B	Y	minterm	maxterm
0	0	0	$A'B'$	$A + B$
0	1	1	$A'B$	$A + B'$
1	0	0	$AB'$	$A' + B$
1	1	1	$AB$	$A' + B'$

- SOP:  $Y = A'B + AB$
- POS:  $Y = (A + B)(A' + B)$

# Logic Review

- Karnaugh Maps

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

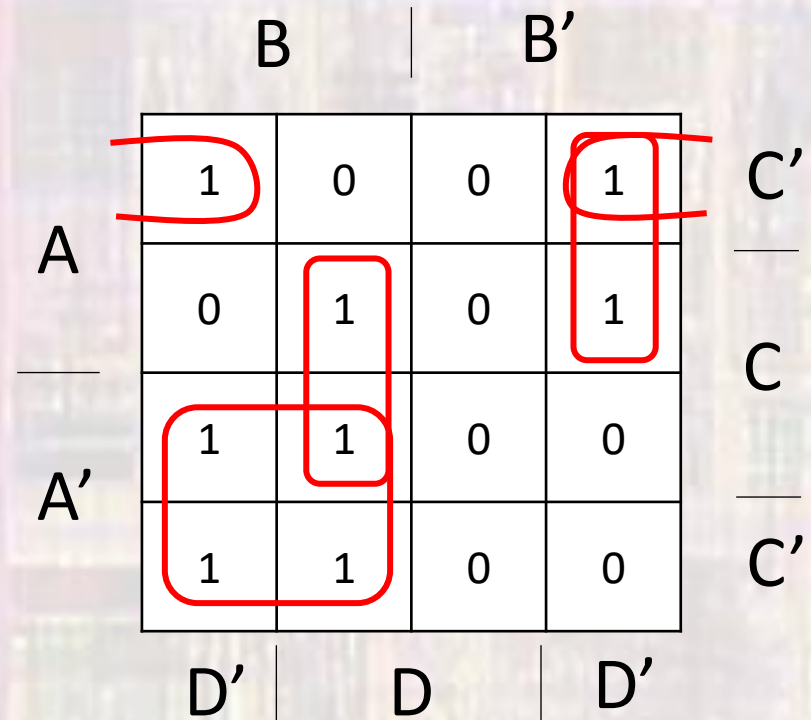


$$A'B + BCD + AB'D' + AC'D'$$
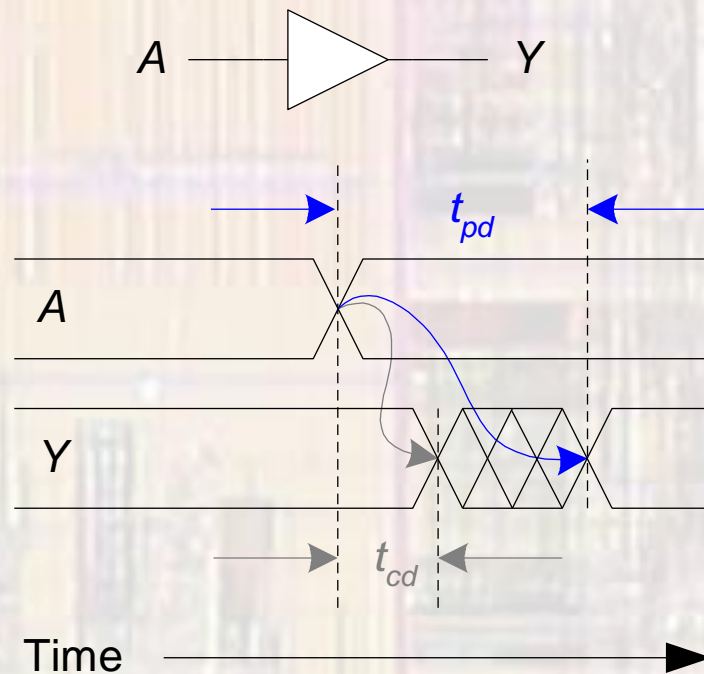
# Logic Review


- Delays

- $t_{pd}$  = propagation delay
  - delay from input to valid output (max delay)
- $t_{cd}$  = contamination delay
  - delay from input to first movement on output (min delay)



# Logic Review





- Shortcuts

 





# Logic Review

- Latches

   
 


# Logic Review

- Latches

  


S	R	Q	QB
0	0	No change	No change
0	1	0	1
1	0	1	0
1	1	<b>0</b>	<b>0</b>

  

SB	RB	Q	QB
0	0	<b>1</b>	<b>1</b>
0	1	1	0
1	0	0	1
1	1	No change	No change
 
# Logic Review

- Flip-Flops
  - Edge Triggered
    - Outputs only change on a rising or falling clock edge (**synchronous**)
    - Outputs depend on the state of the inputs **at the clock edge**
  - Some have **asynchronous** set or reset inputs




# Logic Review

- Flip-Flops

- Edge Triggered **D** Flip-Flop

- Outputs depend on the state of the inputs **at the rising clock edge**

 - Some have asynchronous set or reset inputs



Set	Reset Bar	D	Q	QB
0	1	0	0	1
0	1	1	1	0
1	1	x	1	0
0	0	x	0	1

} D at the rising clock edge


# Logic Review

- Flip-Flops

- Edge Triggered **T** Flip-Flop (Toggle)

- Outputs depend on the state of the inputs **at the rising clock edge**

 - Some have asynchronous set or reset inputs



T	Q	QB
0	$Q_{OLD}$	$QB_{OLD}$
1	$QB_{OLD}$	$Q_{OLD}$


} T at the rising clock edge

T	Q	QB
0	No Change	No Change
1	Toggle	Toggle

} T at the rising clock edge
 
# Logic Review

- Flip-Flops
  - Edge Triggered **SR** Flip-Flop (Set/Reset)
    - Outputs depend on the state of the inputs **at the rising clock edge**
  - Some have asynchronous set or reset inputs




R	S		Q	QB
0	0		$Q_{OLD}$	$QB_{OLD}$
0	1		1	0
1	0		0	1
1	1		N/A	N/A

**S,R at the rising clock edge**
 
# Logic Review

- Flip-Flops
  - Edge Triggered **JK** Flip-Flop
    - Outputs depend on the state of the inputs **at the rising clock edge**
  - Some have asynchronous set or reset inputs




J	K		Q	QB
0	0		$Q_{OLD}$	$QB_{OLD}$
0	1		0	1
1	0		1	0
1	1		Toggle	Toggle

J,K at the rising  
clock edge

# Logic Review


- Parallel Data Register

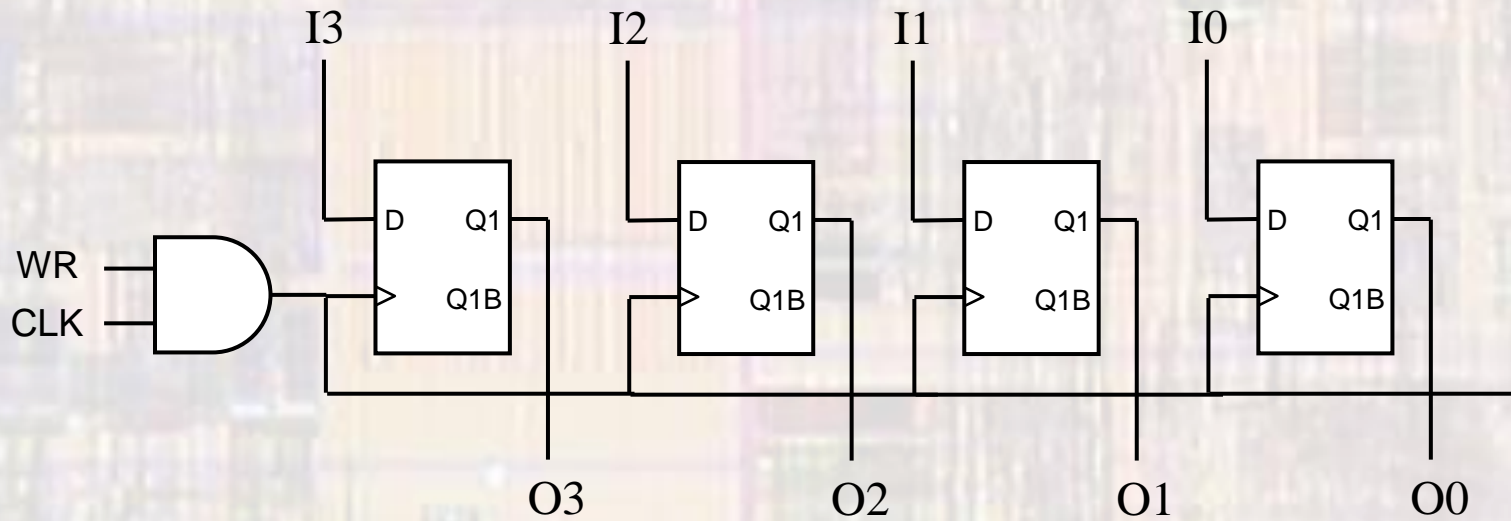





# Logic Review

- Shift Register

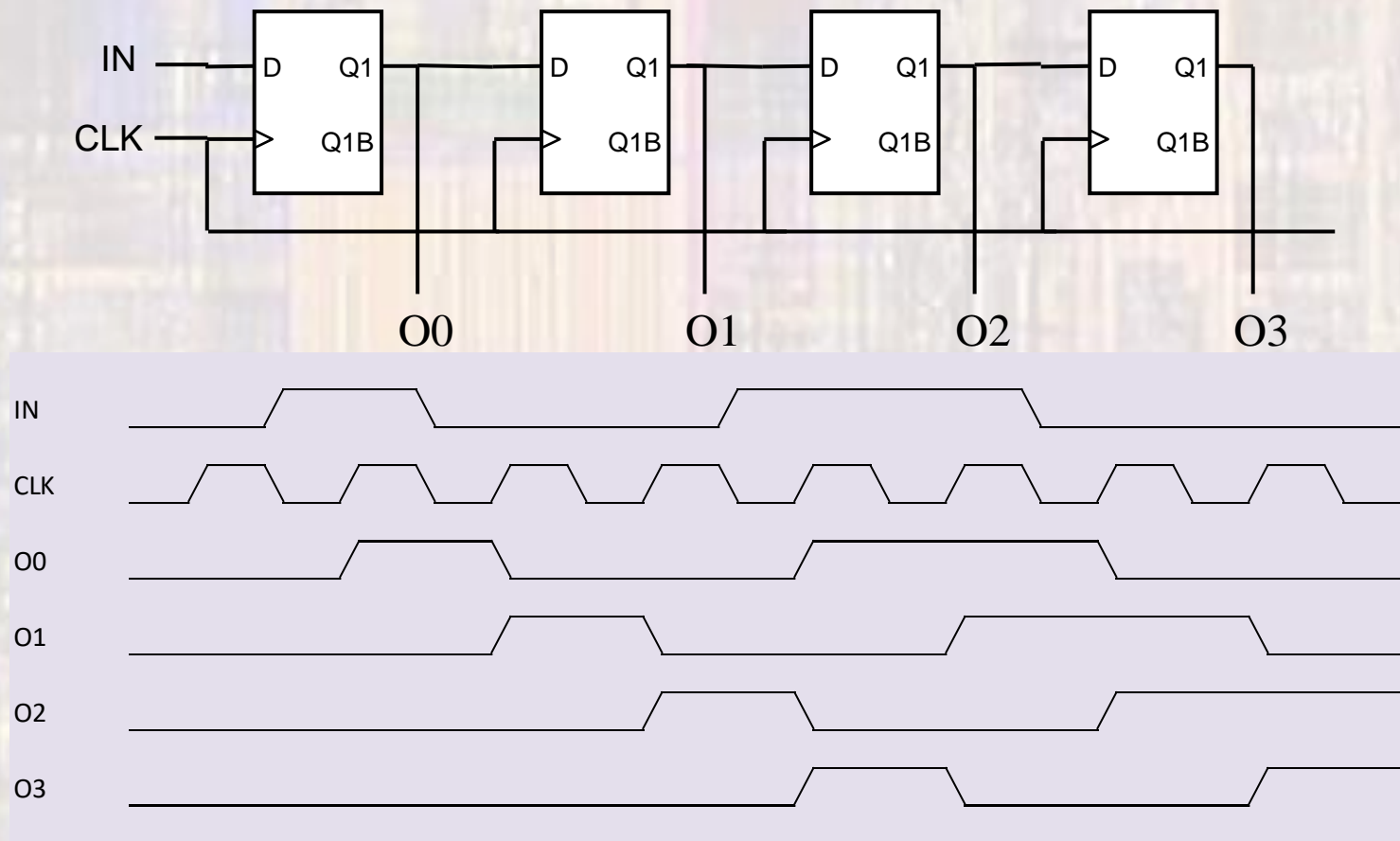

# Logic Review

- Counter

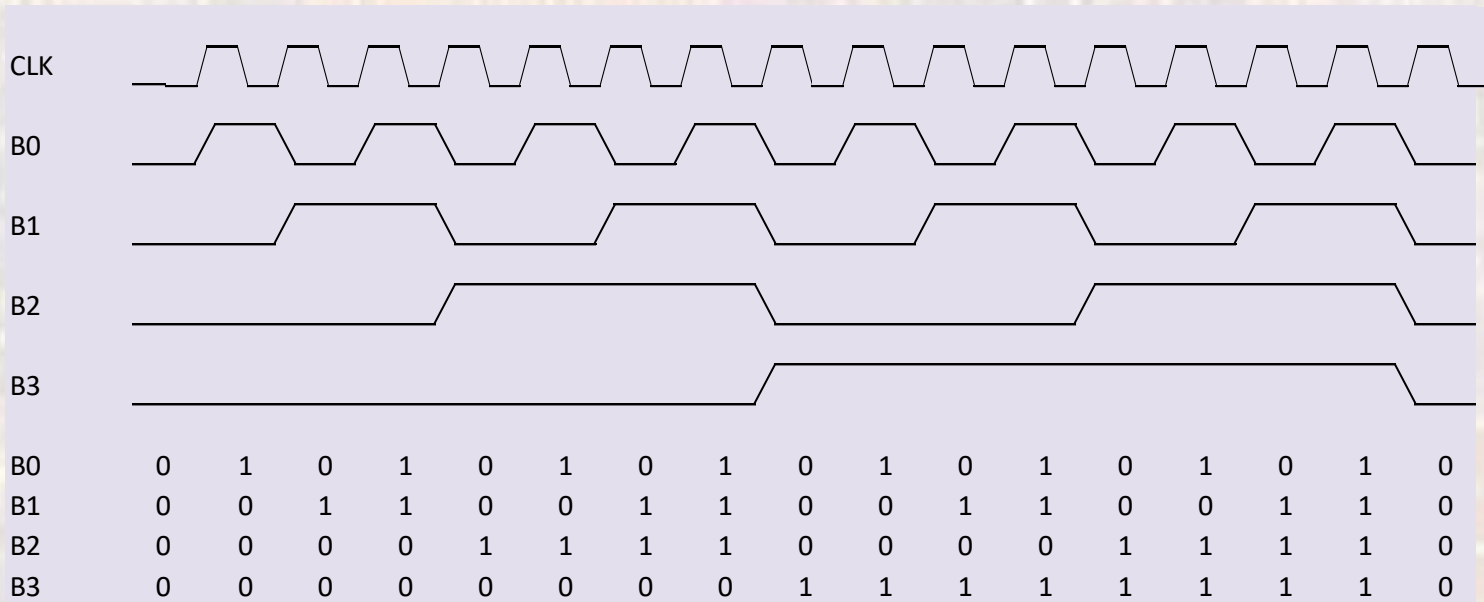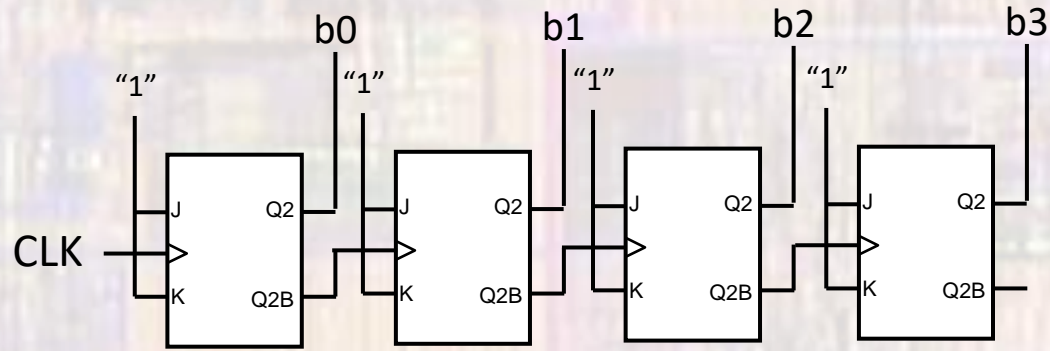

# Logic Review

- Physical world
  - Voltage levels
    - System/Circuit dependent
    - Ideal:

3.3v System

'1' = 3.3v

'0' = 0.0v

1.8v System

'1' = 1.8v

'0' = 0.0v


1.2v System

'1' = 1.2v

'0' = 0.0v


- Real world:

3.3v System

 

# Logic Review

- Clock Systems

 


$$F \text{ (frequency)} = 1/T$$


$$\text{Duty Cycle} = \text{High} / T$$

$$50\text{MHz} \leftrightarrow 20\text{ns}$$
 
$$\text{High} = 10\text{ns}, \text{Low} = 10\text{ns}$$



25% duty cycle, 12.5MHz

 

75% duty cycle, 12.5MHz