

Button Basics

Last updated 11/4/20

Button Basics

- 2 pin Button
- Button not pushed – open circuit between the pins




- Button pushed – short circuit between the pins





Button Basics

- 2 pin Button

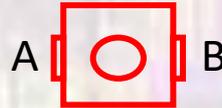


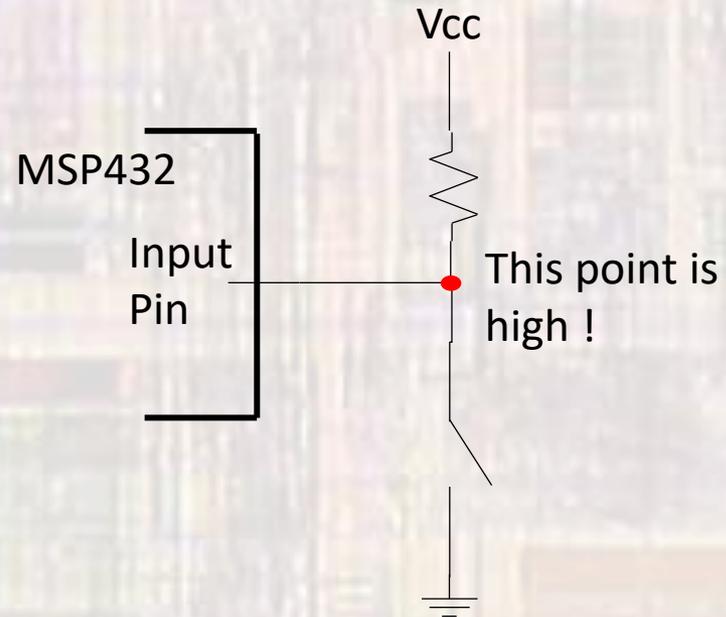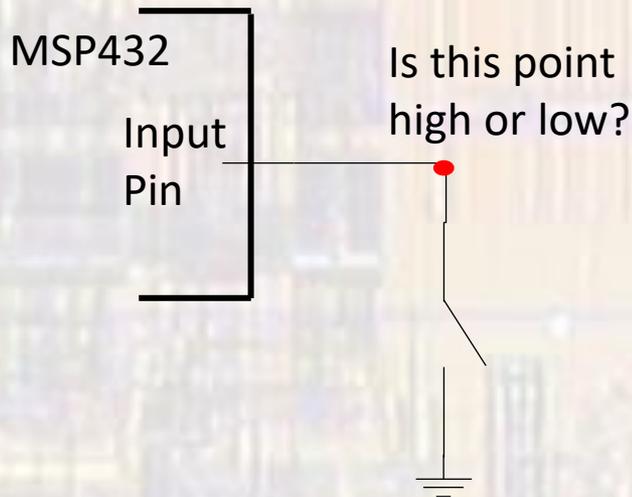- Need some kind of resistor in our design to ensure we know what state the MSP432 pin is in



Button Basics

- 2 pin Button

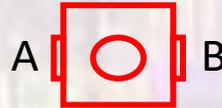


- What resistor value?
 - Too small → wasted current (power)
 - Typically several KΩ

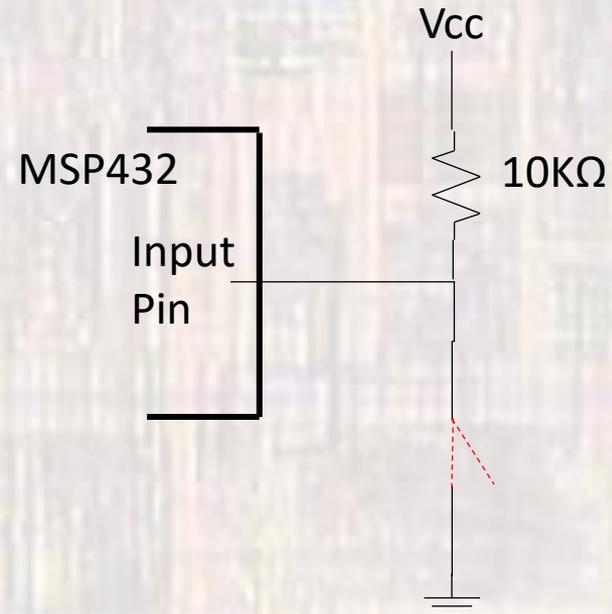- Example

- 10KΩ
- Switch open → no current (pin high)
- Switch closed →

$$\begin{aligned} (V_{cc} - Gnd) / 10,000\Omega &= \\ 3.3V / 10,000\Omega &= 330\mu A \\ \text{(pin low)} & \end{aligned}$$



Button Basics

- 2 pin Button
- Setting up the input pin (pin 5 example)


```
// Hardware setup
// Note: pin 5 is Port 4 bit 1
// 0 on the direction bit indicates an Input
P4->DIR &= ~0x02;           // Input
```

- Reading the pin (pin 5 example)

```
// Note: pin 5 is Port 4 bit 1
int pin5State;
...
pin5State = P4->IN & 0x02;           // reads 0 or 4
// or
pin5State = ((P4->IN & 0x02) != 0); // reads 0 or 1//
// or
pin5State = ((P4->IN & 0x02) && 1); // logical and - reads 0 or 1//
```


Button Basics

- 4 pin Button

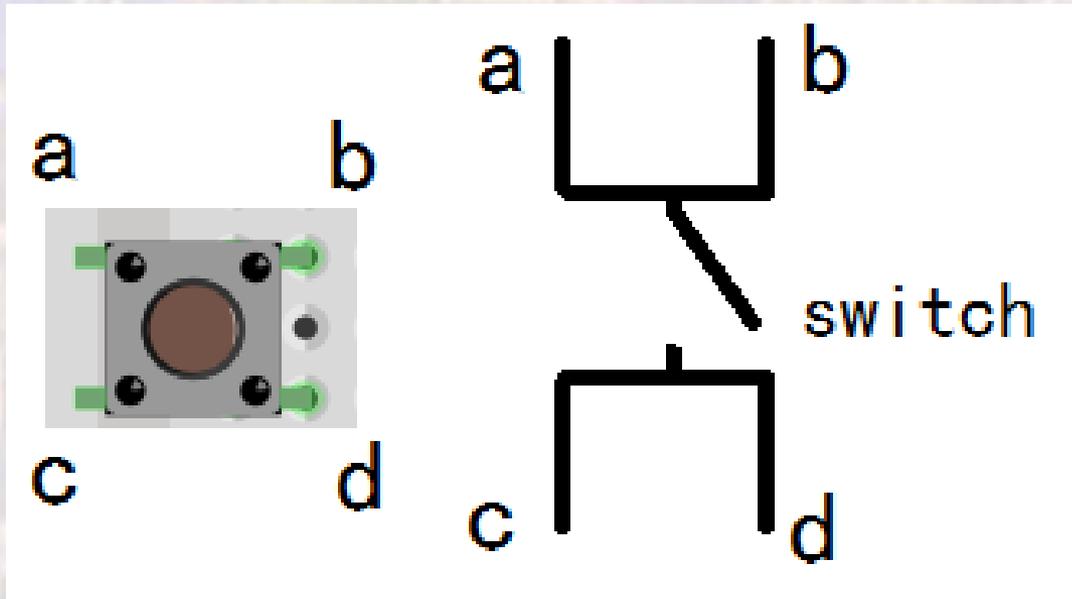


Button Basics

- 2 pin Button

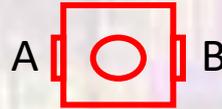

- Pull-up alternative

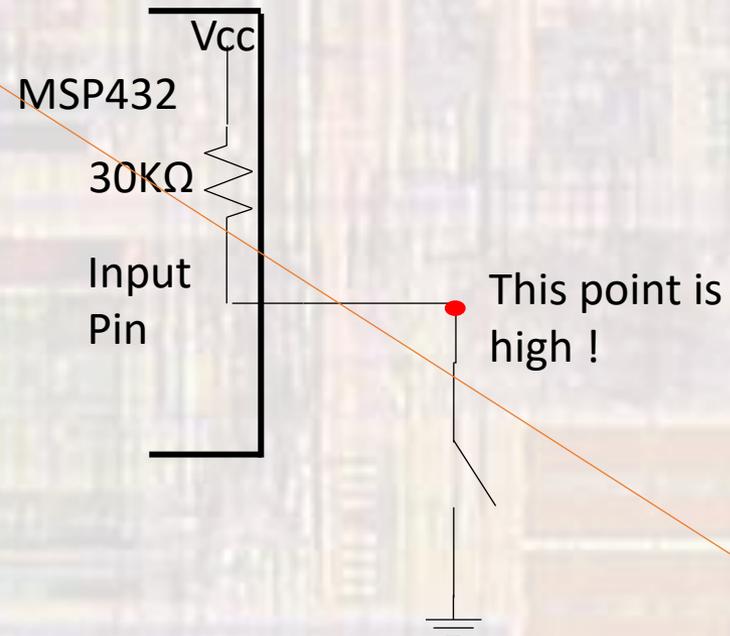- If we make our pin an INPUT with the pull-up enabled an internal resistor is tied from the pin to Vcc



Button Basics

- 2 pin Button
 - Setting up the input pin (pin 5 example)

- Internal pullup

```
// Hardware setup
// Note: pin 5 is Port 4 bit 1
P4->DIR &= ~0x02;           // Input
P4->REN |= 0x02;           // Pull U/D enabled
P4->OUT |= 0x02;           // Connect Pull UP
```

- Reading the pin (pin 5 example)

```
// Note: pin 5 is Port 4 bit 1
int pin5State;
...
pin5State = P4->IN & 0x02;           // reads 0 or 4
// or
pin5State = ((P4->IN & 0x02) != 0); // reads 0 or 1
// or
pin5State = ((P4->IN & 0x02) && 1); // logical and - reads 0 or 1//
```