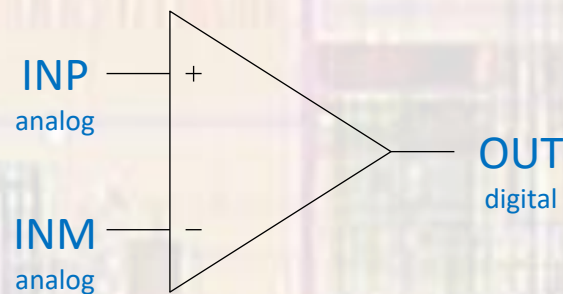


Comparator Basics

Last updated 6/23/21

Comparator Basics

- Comparator Characteristics
 - 2 analog inputs
 - 1 digital output
 - Saturating high gain amplifier
 - Output = '0' if $V_{INP} < V_{INM}$
 - Output = '1' if $V_{INP} > V_{INM}$
 - Kind of like a 1 bit ADC with INM as the reference and INP as the input



Comparator Basics

- Comparator Characteristics

- Designed to allow very fast transitions
 - Special output circuitry – makes it different than an OpAmp
- Some designs include hysteresis
 - Does not switch exactly when $V_{INP} = V_{INM}$
 - Requires the plus input to be a little above the minus input when switching from 0 \rightarrow 1
 - Requires the plus input to a little below the minus input when switching from 1 \rightarrow 0
 - Stops the output from flipping back and forth when INP is very close to INM

