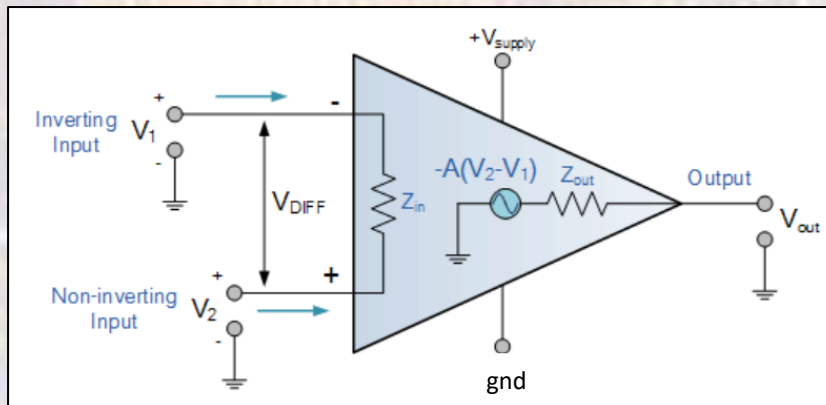


# OpAmp Basics

Last updated 6/24/21

# OpAmp Basics

- OpAmp Characteristics
  - 2 analog inputs
  - 1 analog output
  - High gain amplifier
    - Typical Open-Loop DC gain of 10,000 to 100,000
    - $V_{OUT} = -G(V_+ - V_-)$



# OpAmp Basics

- OpAmp Characteristics

- High input impedance – do not load the src
- Low output impedance – drive loads easily
- Input offset – fixed error in  $V_{diff} = V_+ - V_- + V_{input-offset}$ 
  - Typically in the mV range
- Gain-Bandwidth Product – how far out in frequency the amplifier operates linearly – (when in a fixed gain configuration)
  - 1MHz G-BW
    - At a gain of 1 – operates out to 1MHz
    - At a gain of 10 – operates out to 100KHz
    - At a gain of 100 – operates out to 10KHz
    - ...

