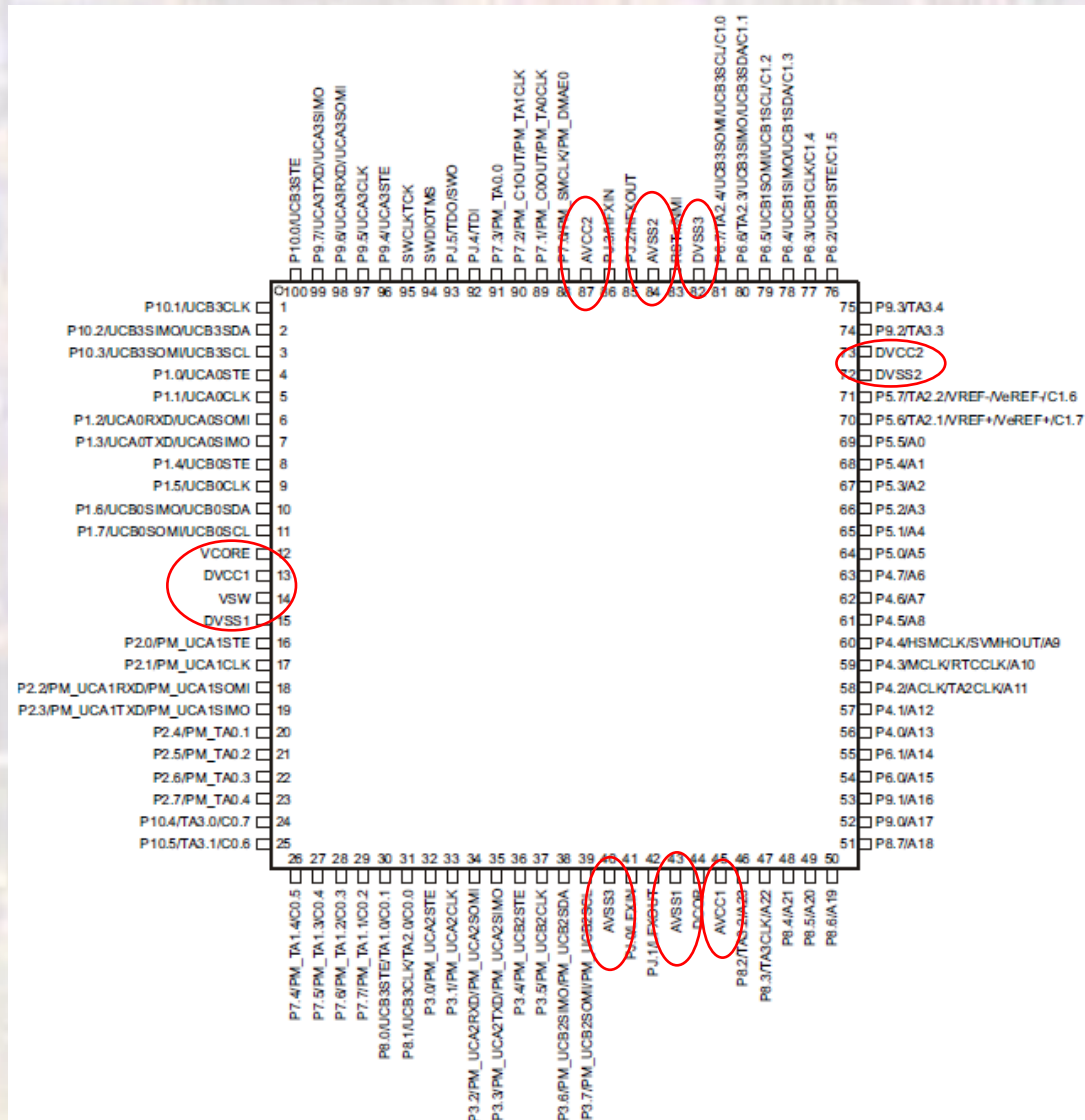


Voltage Supplies

Last updated 6/17/19



Voltage Supplies

- Pinout



Voltage Supplies

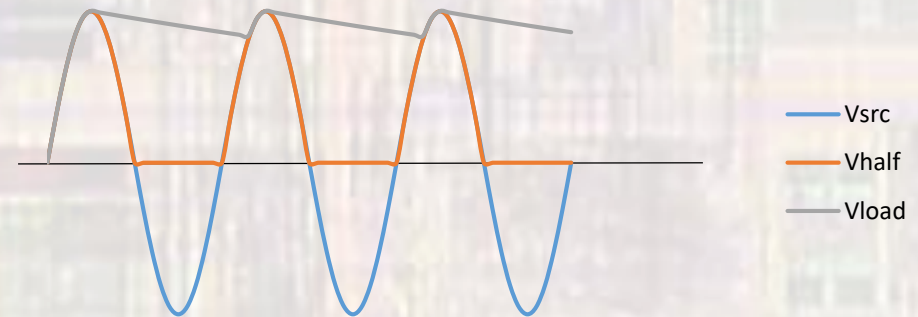
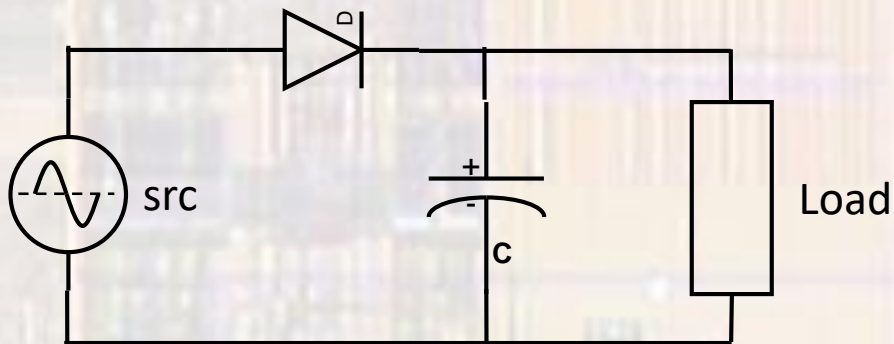
- Rectifiers
 - Convert AC to DC
 - Half Wave topology



Ideal Diode

Voltage Supplies

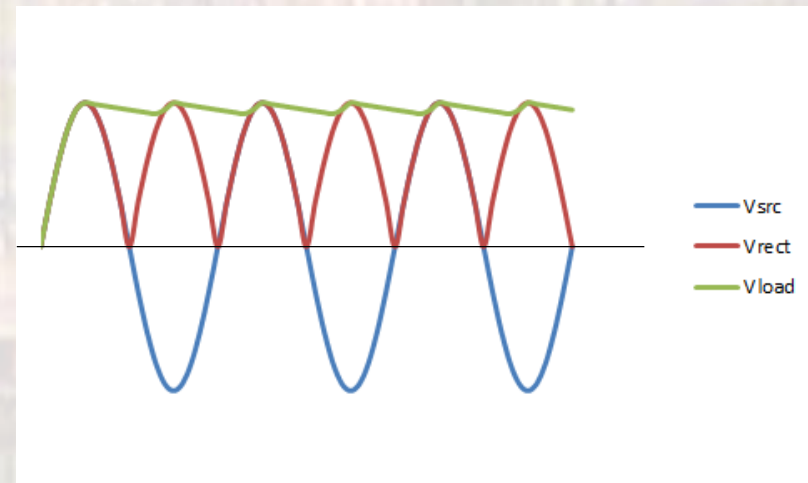
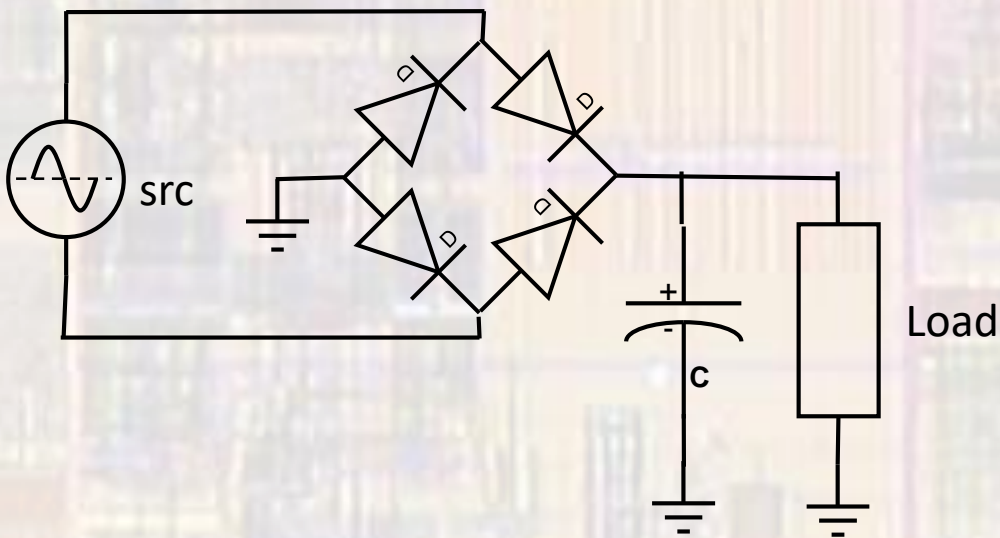
- Rectifiers
 - Convert AC to DC
 - Full Wave topology



Ideal Diode

Voltage Supplies

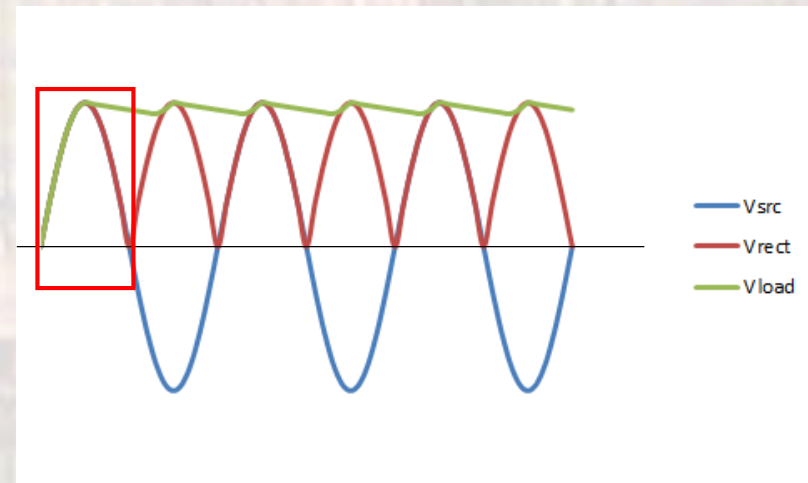
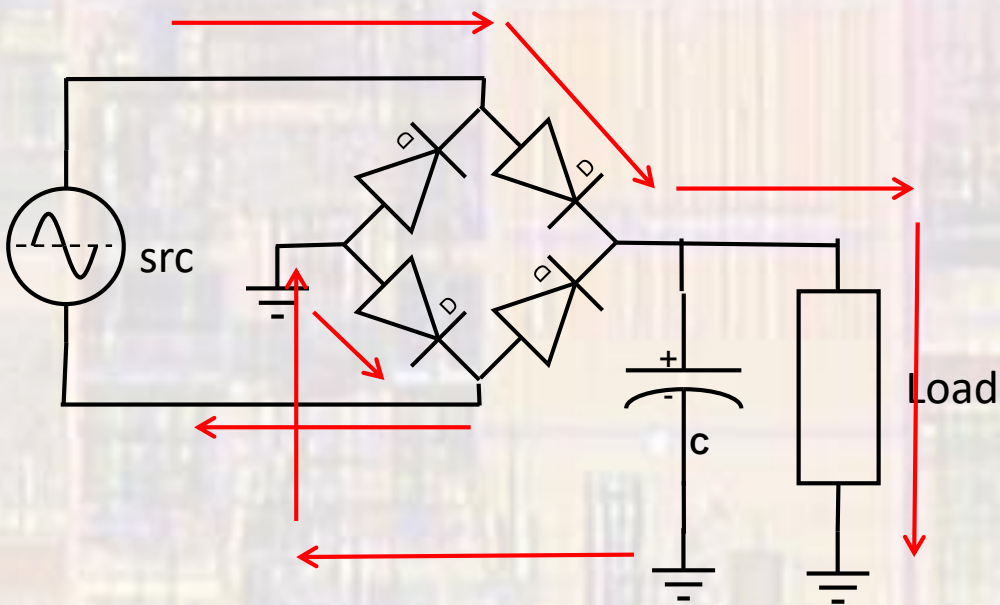
- Rectifiers
 - Convert AC to DC
 - Full Wave topology – positive half cycle



Ideal Diode

Voltage Supplies

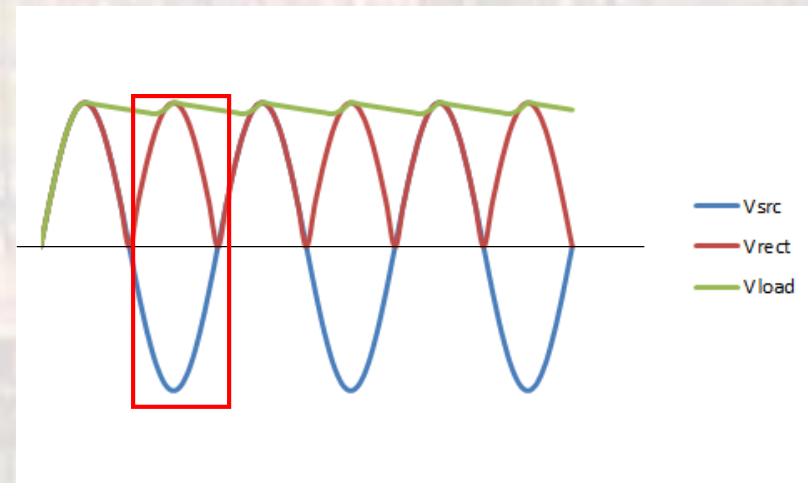
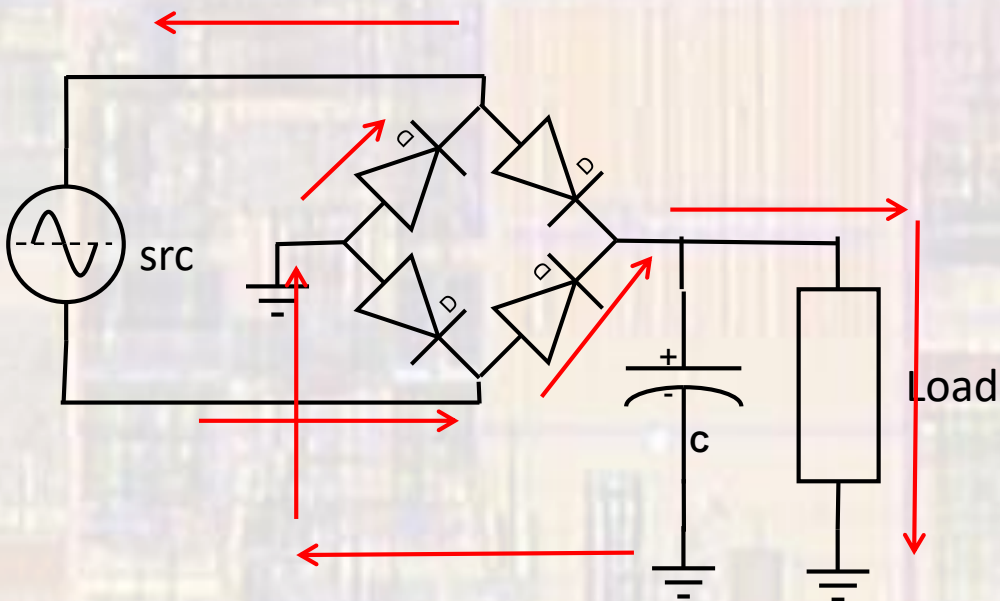
- Rectifiers
 - Convert AC to DC
 - Full Wave topology – negative half cycle



Ideal Diode

Voltage Supplies

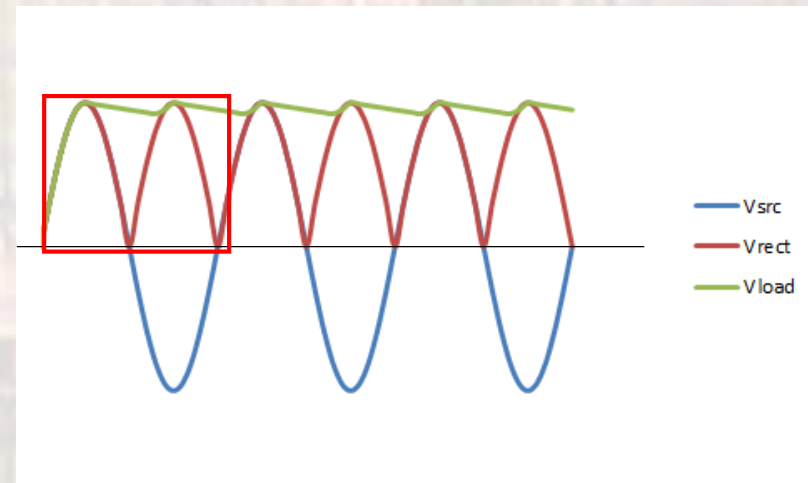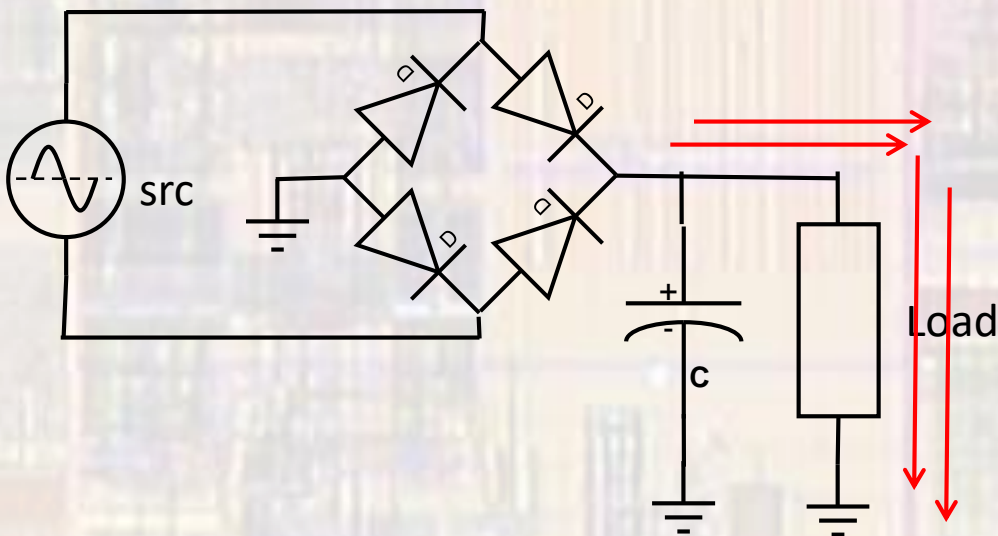
- Rectifiers
 - Convert AC to DC
 - Full Wave topology – both cycles provide current to the load



Ideal Diode

Voltage Supplies

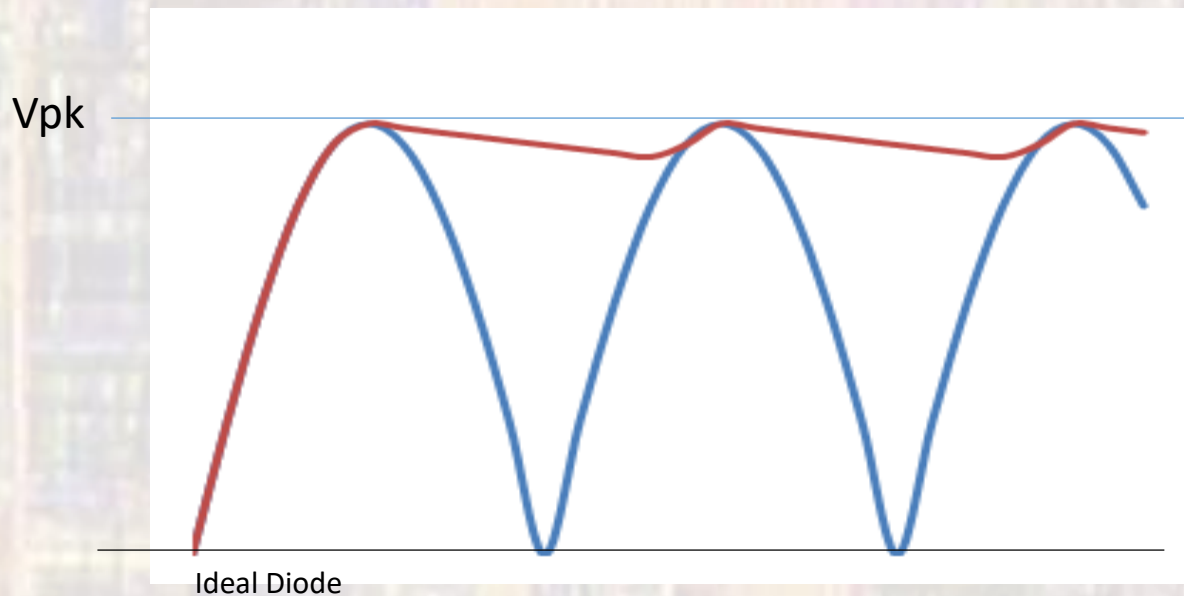- Rectifiers
 - Convert AC to DC
 - Full Wave topology – V_{peak} (V_{pk})



In the ideal diode case:

$$V_{\text{pk}} = V_{\text{in}_{\text{peak}}}$$

In the non-ideal diode case:


$$V_{\text{pk}} = V_{\text{in}_{\text{peak}}} - 2V_{\text{d}}$$

Remember:

$$V_{\text{in}_{\text{peak}}} = \sqrt{2} \times V_{\text{in}_{\text{rms}}}$$

Voltage Supplies

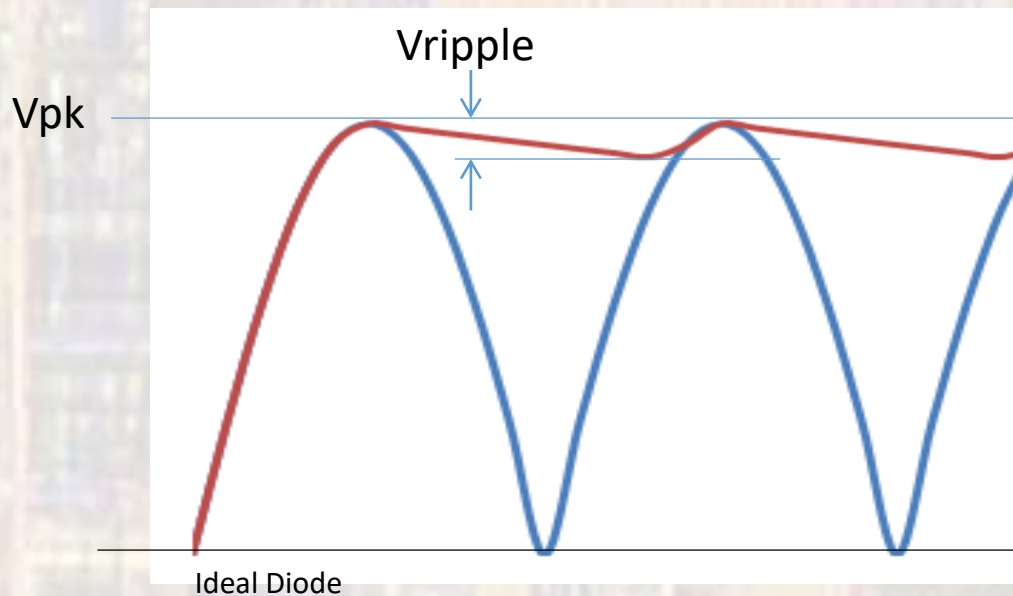- Rectifiers
 - Convert AC to DC
 - Full Wave topology – Vripple



Assume a resistive load R_L

R_L and C form an RC circuit with time constant $\tau = R_L C$

$$V_{out} = V_{pk} \times e^{-t/\tau}$$

during the decay time

so

$$V_{ripple} < 2 \times V_{pk} \times (1 - e^{-T/4\tau})$$

where T is the period of the input sine wave

Voltage Supplies

- Rectifiers

- Example

- A 100Hz, $8v_{\text{rms}}$ sine wave is rectified using an ideal full wave rectifier. Assuming the load impedance is $1K\Omega$ and the filter capacitor is $100\mu\text{F}$:

1) what is the approximate amount of ripple on the output?

$$8v_{\text{rms}} \rightarrow 11.3v \text{ peak} \quad 100\text{Hz} \rightarrow T=10\text{ms}$$

$$\tau = RC = (100\mu\text{F})(1K\Omega) = 100\text{ms}$$

$$V_{\text{ripple}} < 2 \times V_{\text{pk}} \times (1 - e^{-T/4\tau})$$

$$V_{\text{ripple}} < 2 \times 11.3v \times (1 - e^{-10\text{ms}/4(100\text{ms})}) = 558\text{mv}$$



$$V_{\text{out}_{\text{min}}} = V_{\text{peak}} - V_{\text{ripple}} = 11.3v - 558\text{mv} = 10.74v$$

Voltage Supplies

- Unregulated Supply
- Wall Wart




Typical "Wall Wart"

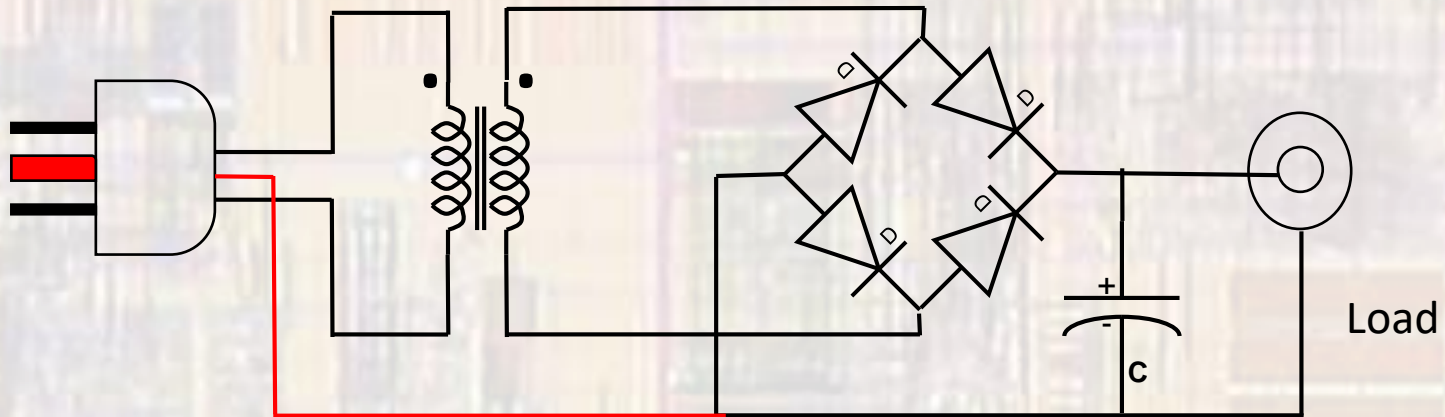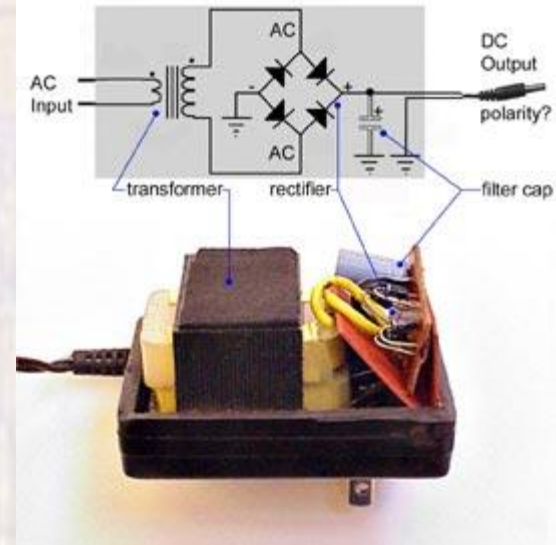

Voltage Supplies

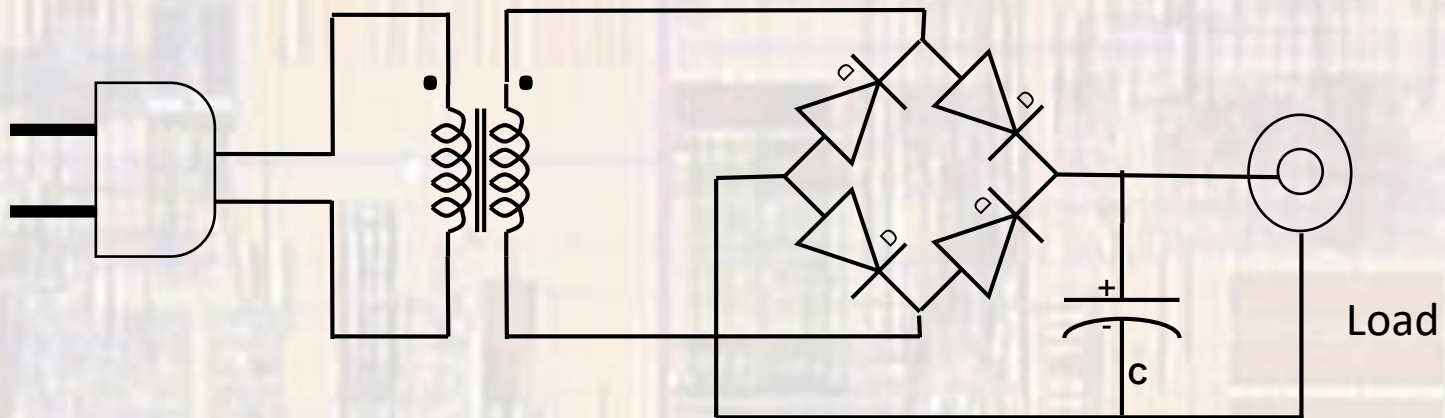- Unregulated Supply
 - Wall Wart
 - US residential power standards
 - 120vrms +/- 5% → 114vrms – 126vrms
 - 60Hz +/- 0.05Hz



Voltage Supplies

- Unregulated Supply

- Example


- Desire 12v dc output from a typical wall wart

assume $V_d = 0.7\text{v}$ for the diodes \rightarrow need $12\text{v} + 1.4\text{v} = 13.4\text{v}$ for V_{pk}

allow for 200mv of ripple $\rightarrow 13.4\text{v} + 0.2\text{v} = 13.6\text{v}$ for V_{pk}

$V_{pk} = 13.6\text{v} \rightarrow 9.61\text{v}_{\text{rms}}$ for the transformer output

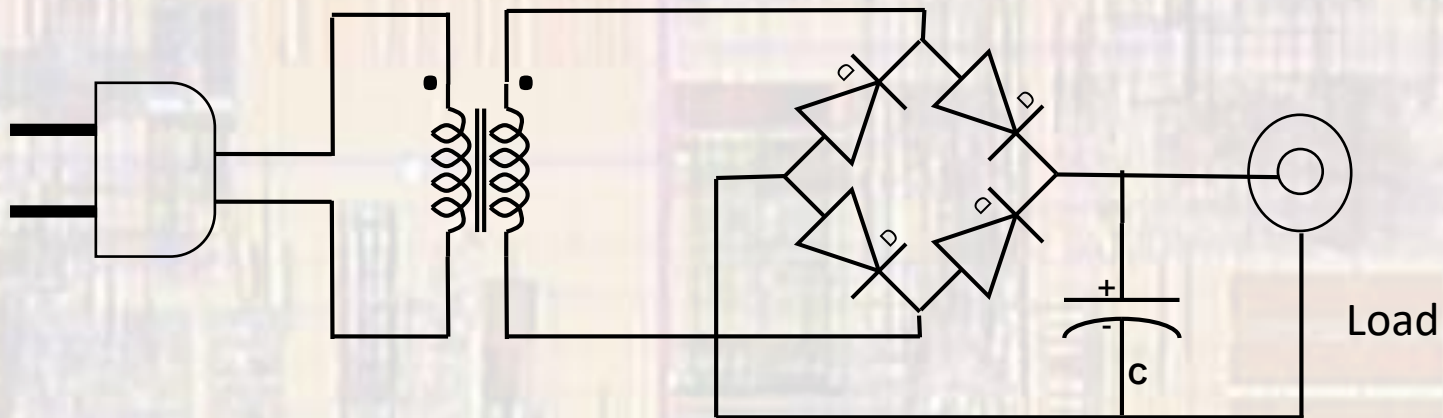$9.61\text{vrms} \rightarrow 120\text{vrms} / 9.61\text{vrms} = 12.48$ turns ratio for the transformer



Voltage Supplies

- Unregulated Supply

This design actually varies from 13.1V at high temp, low load, to 8.7V at low temp, high load
50% variation
→ need regulation

- Example


- Desire 12v dc output from a typical wall wart

assume $V_d = 0.7v$ for the diodes → need $12v + 1.4v = 13.4v$ for V_{pk}

allow for 200mv of ripple → $13.4v + 0.2v = 13.6v$ for V_{pk}

$V_{pk} = 13.6v \rightarrow 9.61v_{rms}$ for the transformer output

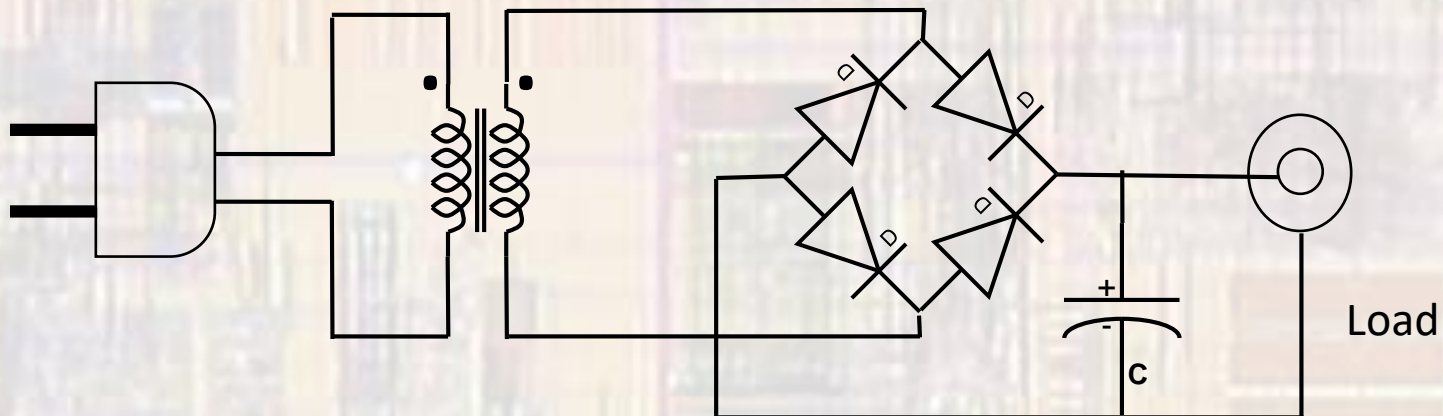$9.61v_{rms} \rightarrow 120v_{rms} / 9.61v_{rms} = 12.48$ turns ratio for the transformer




Voltage Supplies


- Regulated Supply

Need something to control the output voltage over variations of temperature, input voltage and load

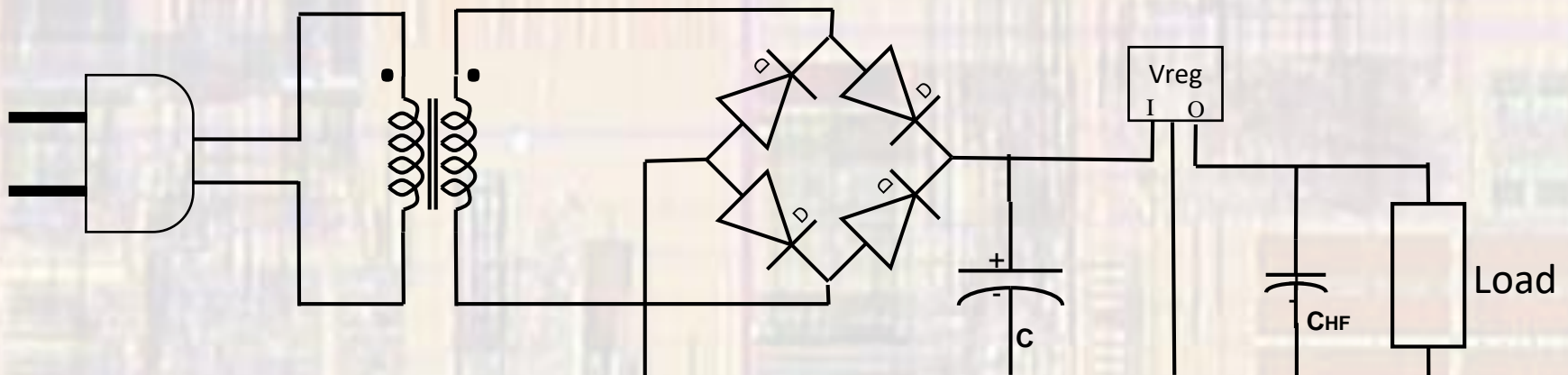- Linear voltage regulator
 - uses active circuitry to maintain the output voltage
 - LDO – Low Drop Out versions require minimal overhead voltage



Voltage Supplies

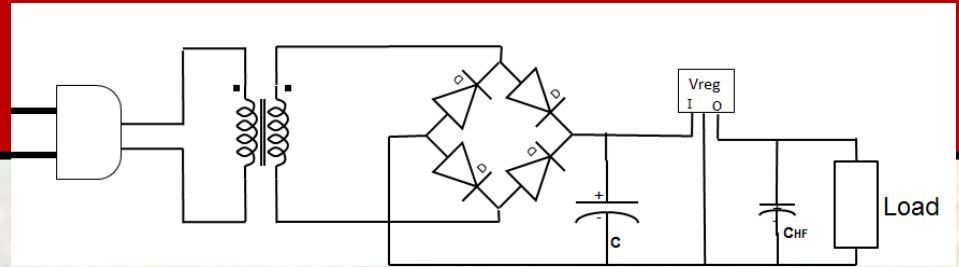


- Regulated Supply


Need something to control the output voltage over variations of temperature, input voltage and load

- Linear voltage regulator

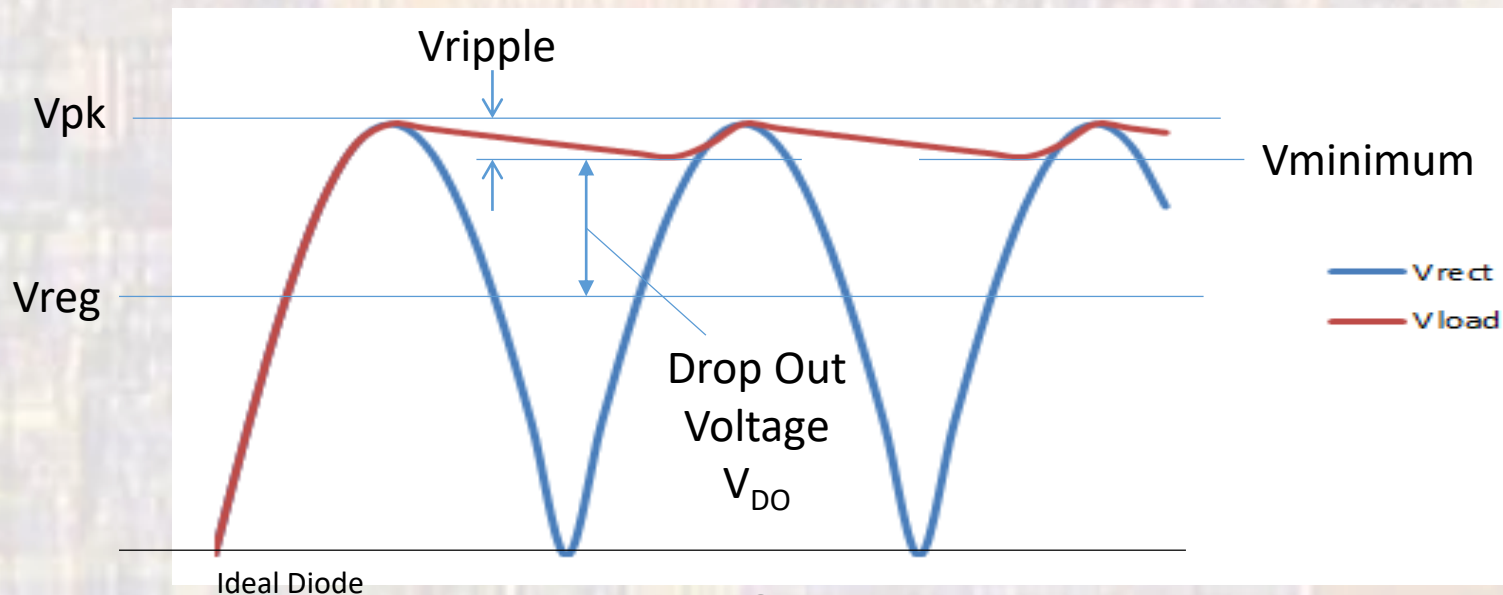- Design the filter cap and transformer to ensure V_{minimum} is greater than $V_{\text{reg}} + V_{\text{DO}}$
- The regulator will then maintain the output voltage



Voltage Supplies

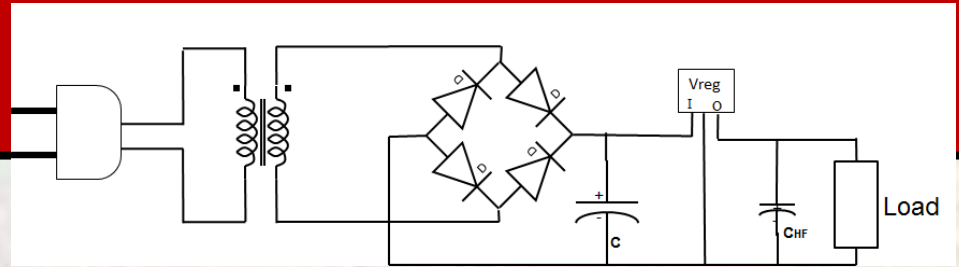

- Regulated Supply

Need something to control the output voltage over variations of temperature, input voltage and load

- TI LDO Specifications

wide input voltage range
wide load current range

+/- 5% output voltage

1 - 1.5%
Regulation


2V
drop out
voltage

LM78LXX Electrical Characteristics LM78L05AC / LM78L05I

Symbol	Parameter	Conditions	Min	Typ	Max	Units
V_O	Output Voltage	$7V \leq V_{IN} \leq 20V$ $1mA \leq I_O \leq 40mA$ (1)	4.8	5	5.2	V
		$1mA \leq I_O \leq 70mA$ (1)	4.75		5.25	
			4.75		5.25	
ΔV_O	Line Regulation	$7V \leq V_{IN} \leq 20V$		18	75	mV
		$8V \leq V_{IN} \leq 20V$		10	54	
ΔV_O	Load Regulation	$1mA \leq I_O \leq 100mA$		20	60	mV
		$1mA \leq I_O \leq 40mA$		5	30	
I_Q	Quiescent Current			3	5	mA
ΔI_Q	Quiescent Current Change	$8V \leq V_{IN} \leq 20V$ $1mA \leq I_O \leq 40mA$			1.0 0.1	
V_n	Output Noise Voltage	$f = 10 \text{ Hz to } 100 \text{ kHz}^{(2)}$		40		μV
$\Delta V_{IN}/\Delta V_{OUT}$	Ripple Rejection	$f = 120 \text{ Hz}$ $8V \leq V_{IN} \leq 18V$	47	62		dB
I_{PK}	Peak Output Current			140		mA
$\Delta V_O/\Delta T$	Average Output Voltage Tempco	$I_O = 5mA$		-0.65		mV/°C
$V_{IN}(\text{Min})$	Minimum Value of Input Voltage Required to Maintain Line Regulation			6.7	7	V
θ_{JA}	Thermal Resistance (8-Bump micro SMD)			230.9		°C/W


(2) Recommended minimum load capacitance of 0.01 μF to limit high frequency noise.

Figure 1. SOIC-8 (D)
(Top View, Narrow Body)

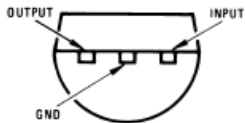

Voltage Supplies

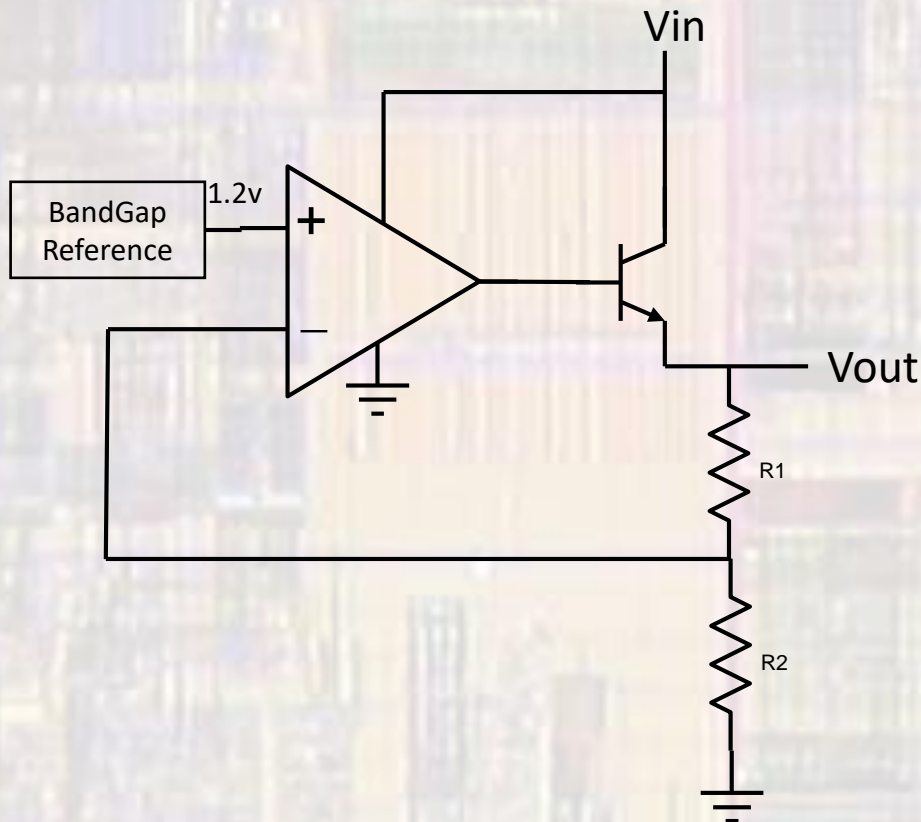- Regulated Supply
- Super Simple Regulator




$$\frac{R2}{R1 + R2} V_{out} = V_{bg}$$

$$V_{out} = V_{bg} \frac{R1 + R2}{R2}$$


Voltage Supplies

- Regulated Supply
- Simple Regulator

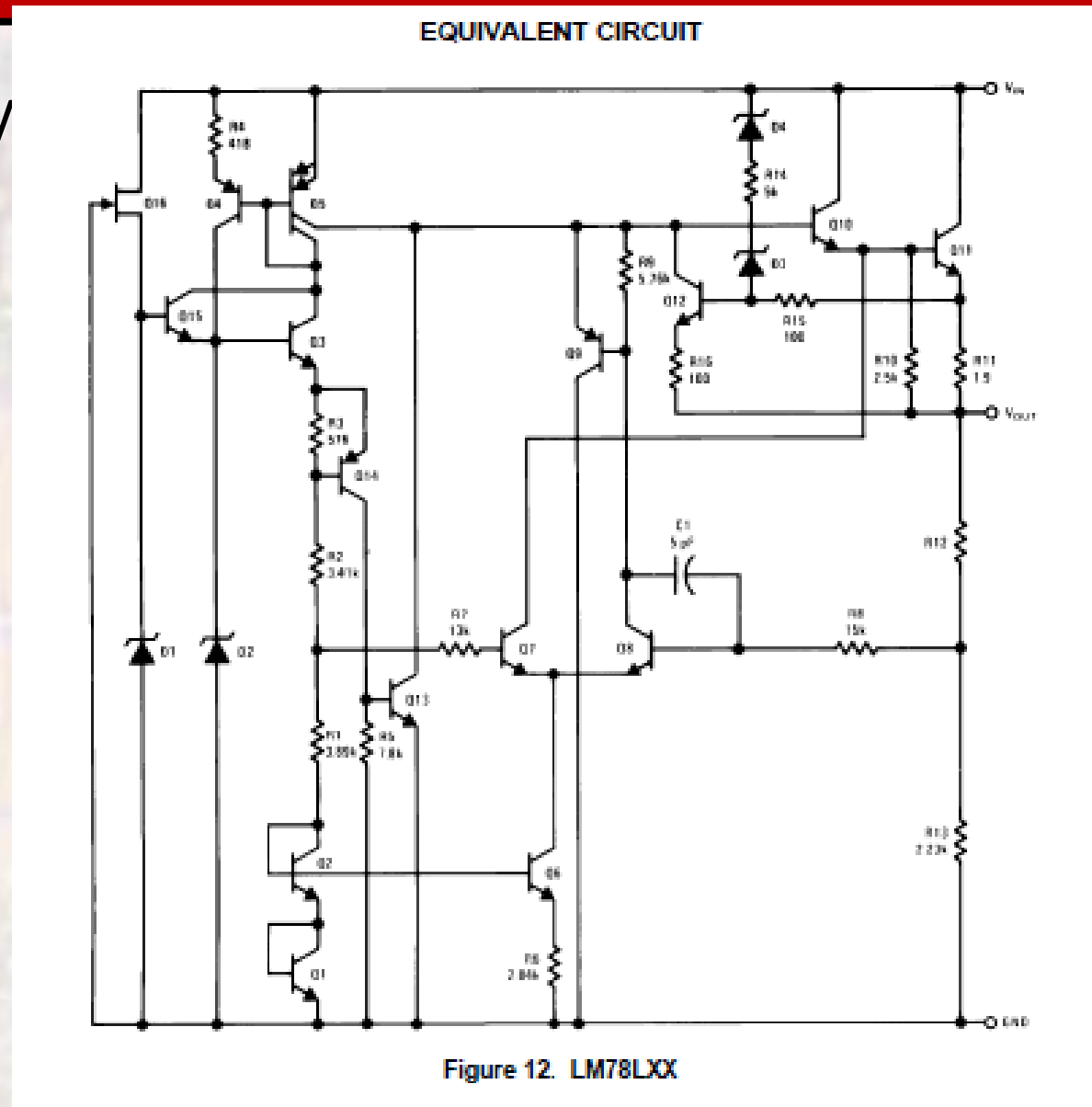

Voltage Supplies

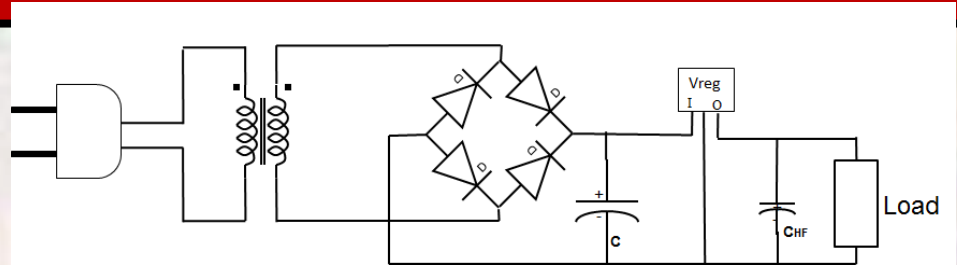- Regulated Supply
- Power Considerations




- With a 12V rectifier output and 50mA load current $\rightarrow P_{\text{sourced}} = 600\text{mW}$
- In our example the load only sees 5V and 50mA $\rightarrow P_{\text{dissipated}} = 250\text{mW}$
- Where does the other power go? \rightarrow dissipated in the regulator

- Efficiency = Power provided to the load / total power dissipated

In this case Efficiency = 42% **Over half the power is lost as heat!**

Design tradeoff:

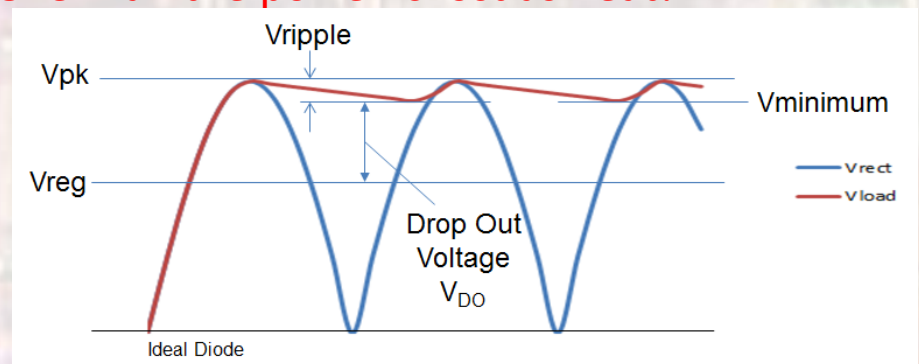More ripple \rightarrow lower cost components
 \rightarrow lower efficiency




Voltage Supplies

- Supply Decoupling
 - Digital circuits create current spikes on the supply pins
 - Shoot through current
 - Charging and discharging current
 - I/O switching
 - While the average supply current may be a few tens of milliamps, spikes associated with an 8 bit I/O switching can be hundreds of milliamps and a few nanoseconds wide
 - Power supplies and realistic circuit board traces cannot support these current spikes → noise on the supply voltage
 - Supply voltage noise can disrupt the normal operation of the processor or other circuits

Voltage Supplies

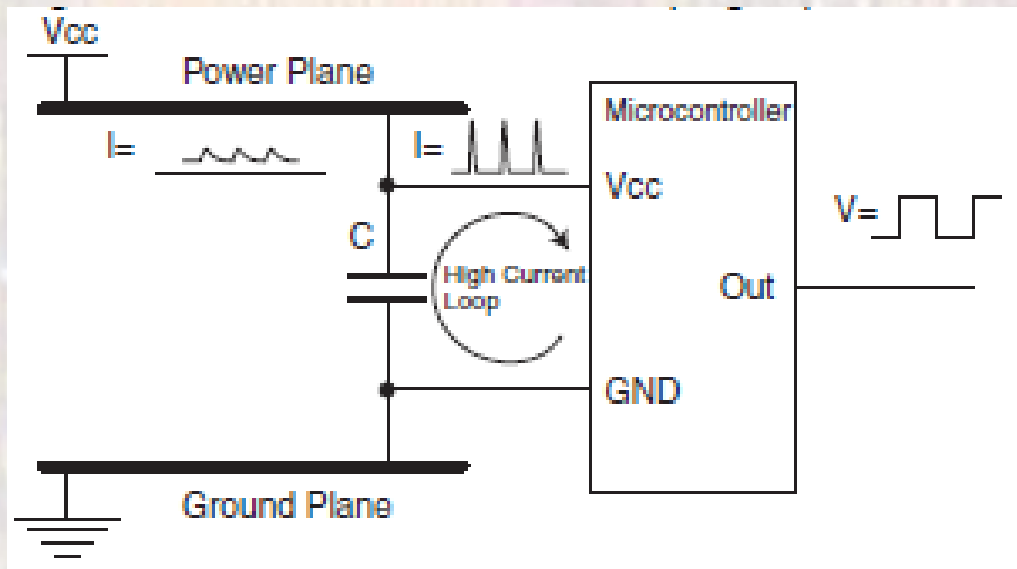
- Supply Decoupling
 - Coupling (bypass) capacitors are used to supply these spikes of current, preventing noise on the supply voltage pins



Voltage Supplies



- Supply Decoupling
- Realistic capacitor model

ABBREVIATION	EXPLANATION	SOURCE AND DETAILS
ESR	Equivalent Series Resistance	Wire and connections to the plate Produces heat
ESL	Equivalent Series Inductance	Depends on package type Surface mount better Smaller SMD better
RLEAK	Leakage Resistance	Type of dielectric

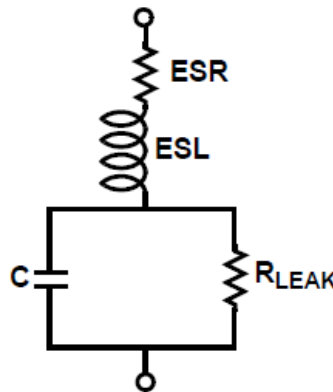



Voltage Supplies

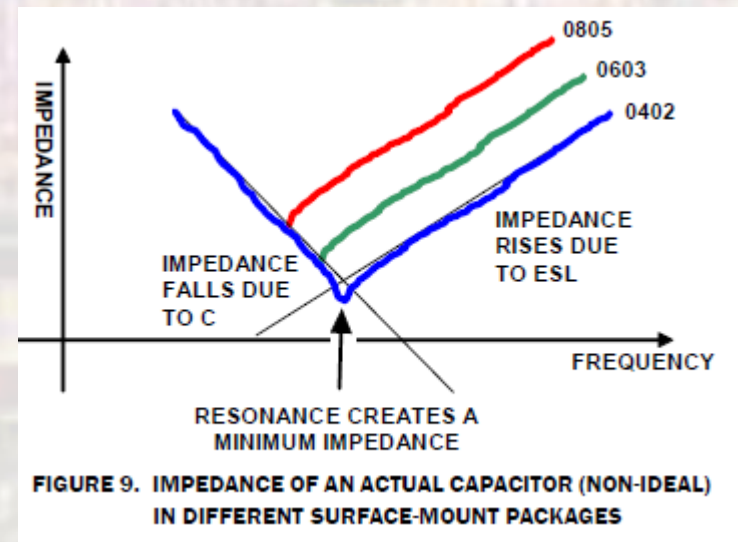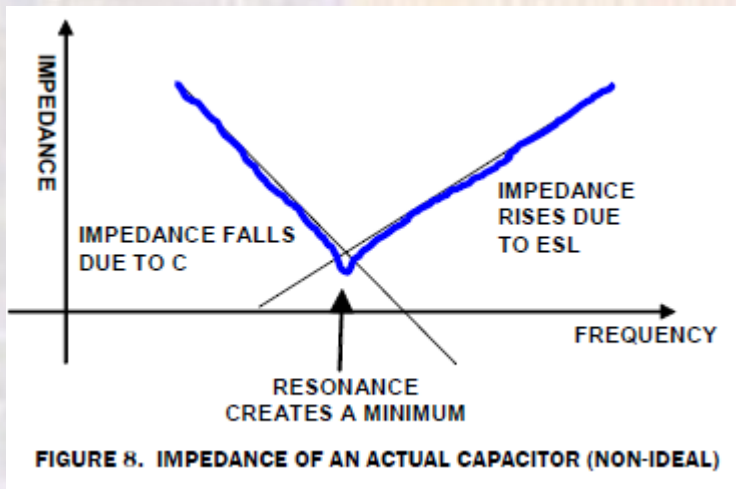- Supply Decoupling
- Realistic capacitor model



Voltage Supplies

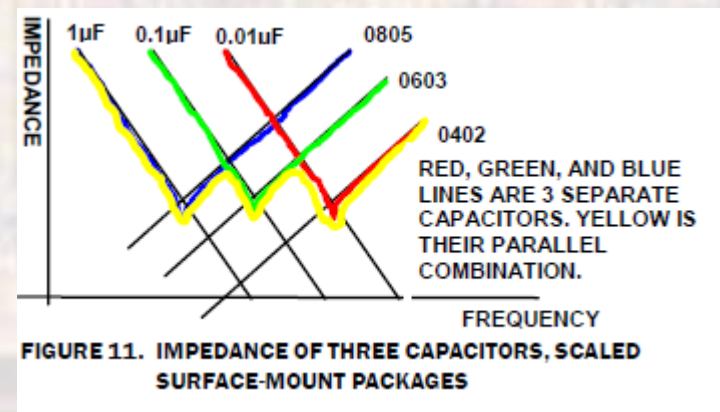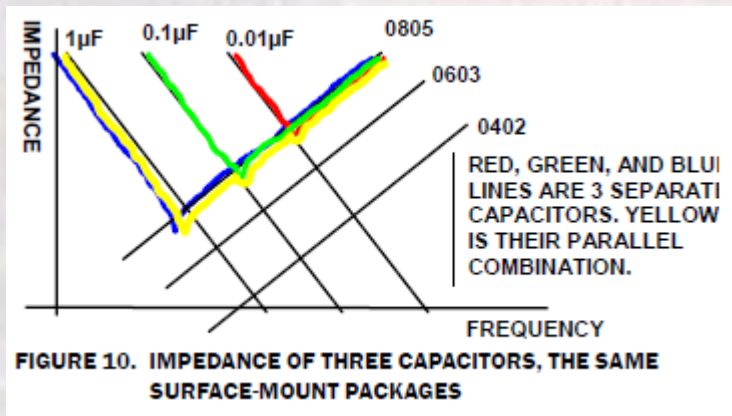- Supply Decoupling
 - Realistic capacitor model



Voltage Supplies

- Supply Decoupling
 - Most systems use 2 decoupling capacitors
 - 1 μ F - 10 μ F for low frequency high current spikes
 - .001 μ F - .01 μ F for high frequency spikes
 - Placed as close to the IC as possible to reduce inductance

