

DC Motor Basics

Last updated 12/2/19

DC Motors

- Basic construction

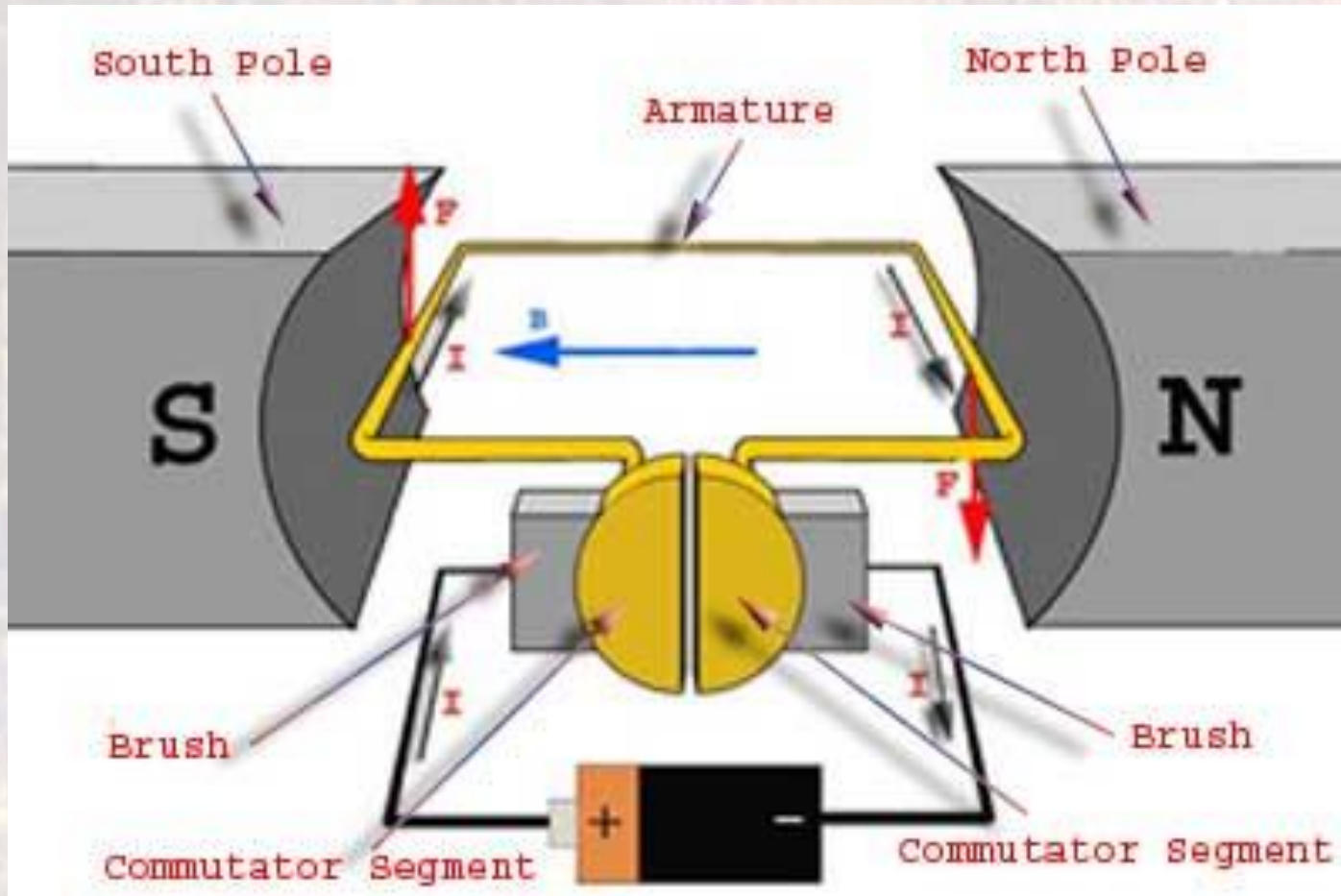


image src: <http://www.electrical4u.com/>

DC Motors

- Basic operation

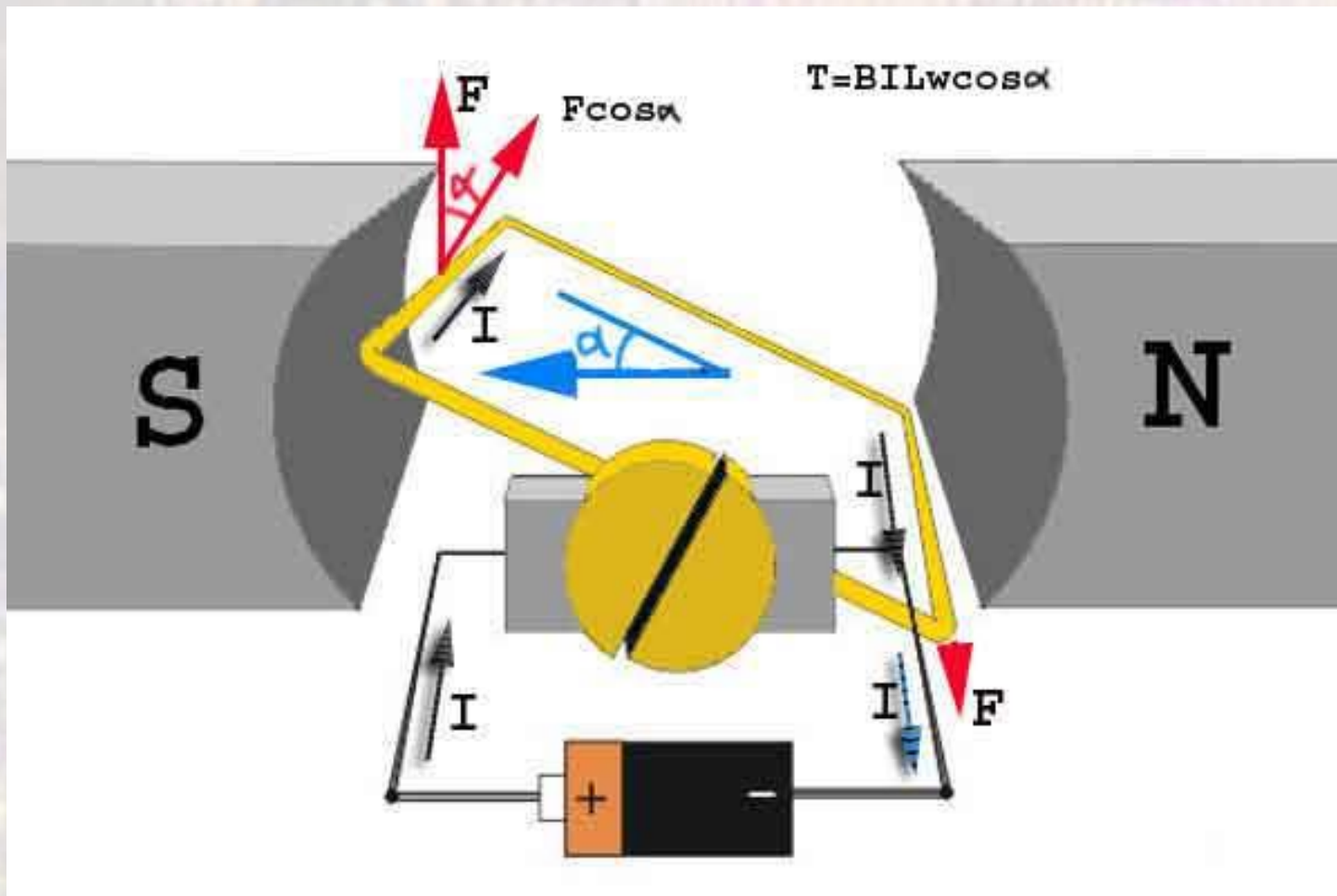


image src: <http://www.electrical4u.com/>

DC Motors

- Rotational speed

$$s = k_2 (V - RI) / \Phi$$

= constant of proportionality * effective voltage / flux

k_2 – fixed

R – fixed

Φ - fixed

We can change the speed by changing V

DC Motors

- Torque

$$\tau = k_1 I \Phi$$

= constant of proportionality * I * Flux

k_1 – fixed

Φ - fixed

We can change the torque by changing I

DC Motors



- Motor control
 - We want to vary speed of the motor (V)
 - allows for variation in speed
 - allows for change in direction with independent motors
 - Want to maximize the torque (I)
 - Need to push another bot out of the ring

DC Motors

- Motor control
 - With our microcontroller we have no true analog output capability
 - Must use PWM
 - Fortunately, the motor looks like a low pass filter
 - PWM signal will look like a DC signal for well chosen frequencies
 - Vary pulse width to modulate speed
 - BUT – what pulse widths, what frequency

DC Motors

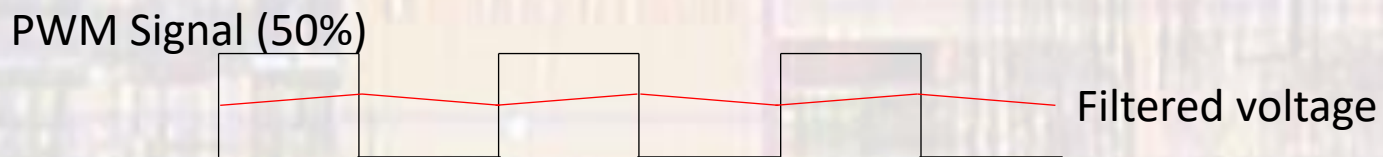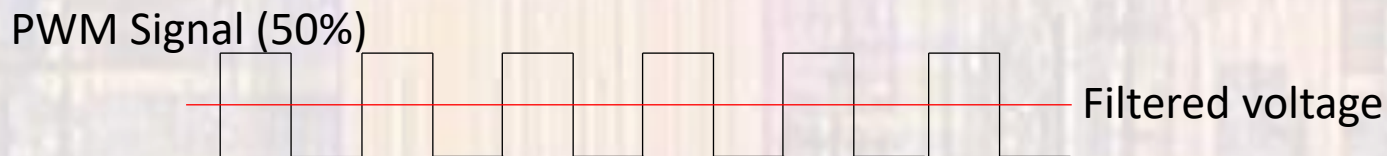- Motor control
 - PWM Low Frequency Considerations




DC Motors

- Motor control
 - PWM Pulse Width and High Frequency Concerns

PWM Signal



PWM Signal

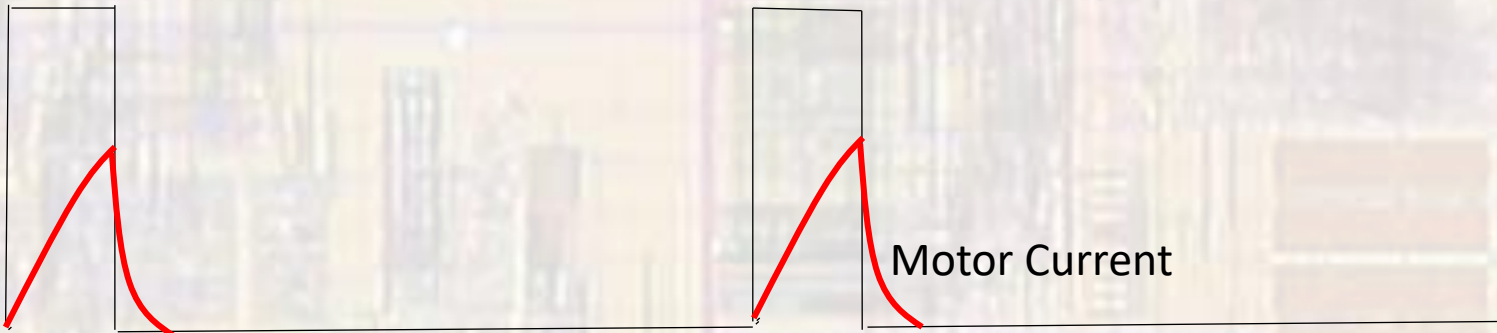

DC Motors

- Motor control
 - For our motors and using the motor driver the “best” PWM frequency is ???
 - You should experiment a little and determine this yourself

DC Motors

- Motor control
 - Still want to maximize voltage and current
 - MSP432 is limited to 3.3V and 6mA (20mA) for a digital output

but

- We have five 1.5V batteries → 7.5V available
 - need to control the 7.5V with a 3.3V digital signal
 - would like to get more than 6mA (20mA) for the motor


DC Motors

- Motor control
 - Driver chip – TB6612FNG
 - 1.2A ave output current per channel
 - 3.2A peak output current(non repetitive) per channel
 - Enable/Standby
 - Thermal shutdown
 - Up to 13.5V motor supply voltage
 - 2.7 – 5.5V logic/control supply voltage
 - PWM frequency up to 100KHz

DC Motors


- Motor control
- Driver chip - TB6612FNG

Output pin; 01, 02

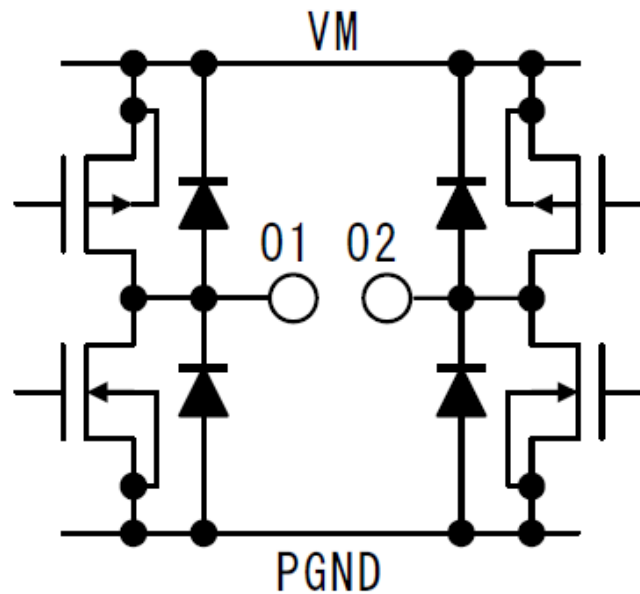



DC Motors

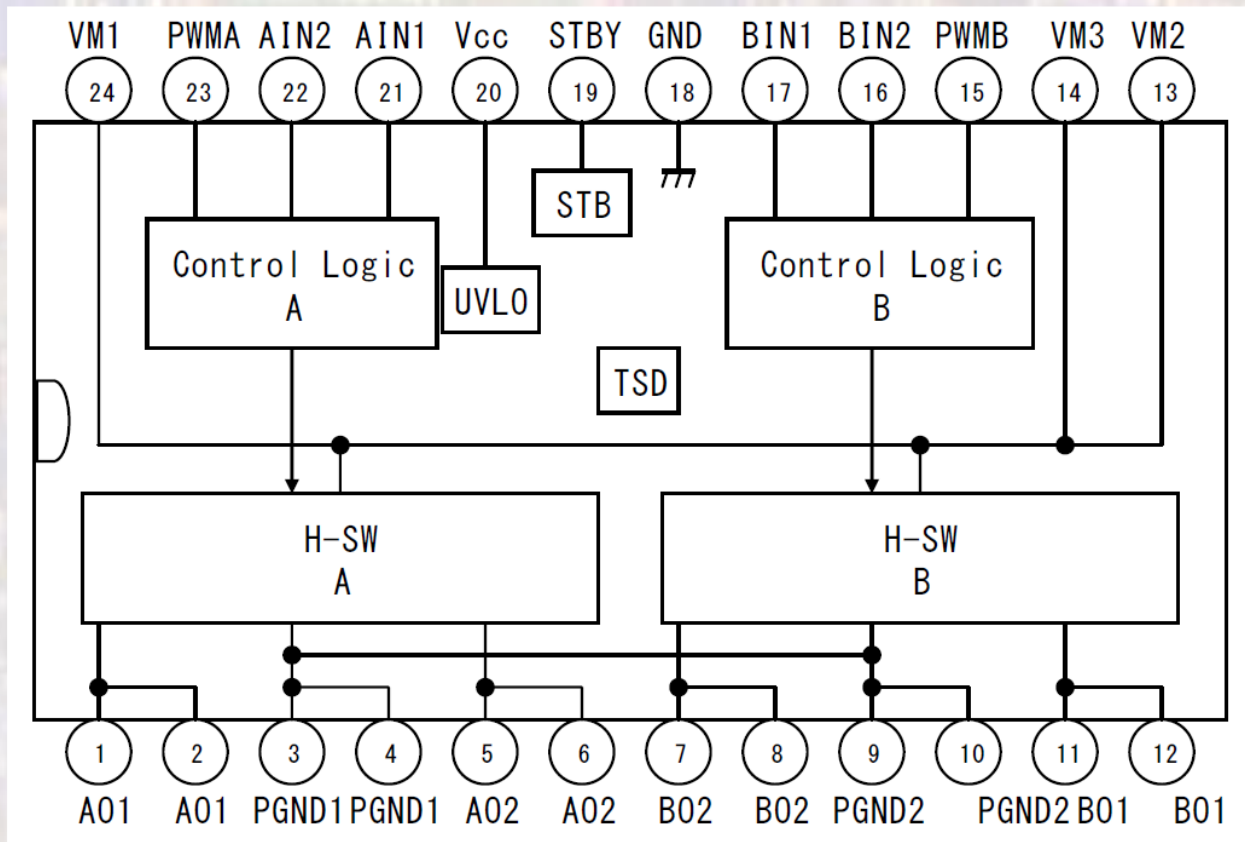- Motor control
- Driver chip - TB6612FNG



DC Motors

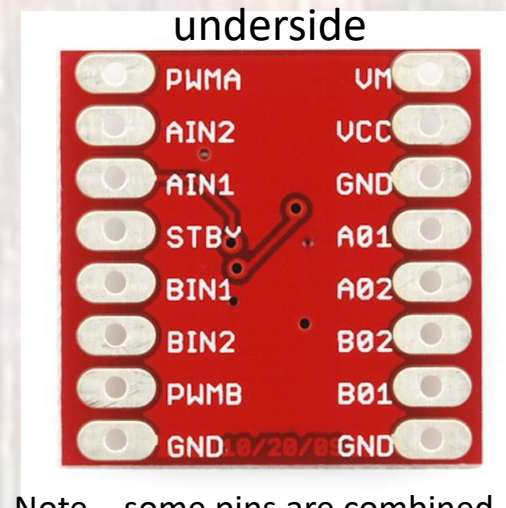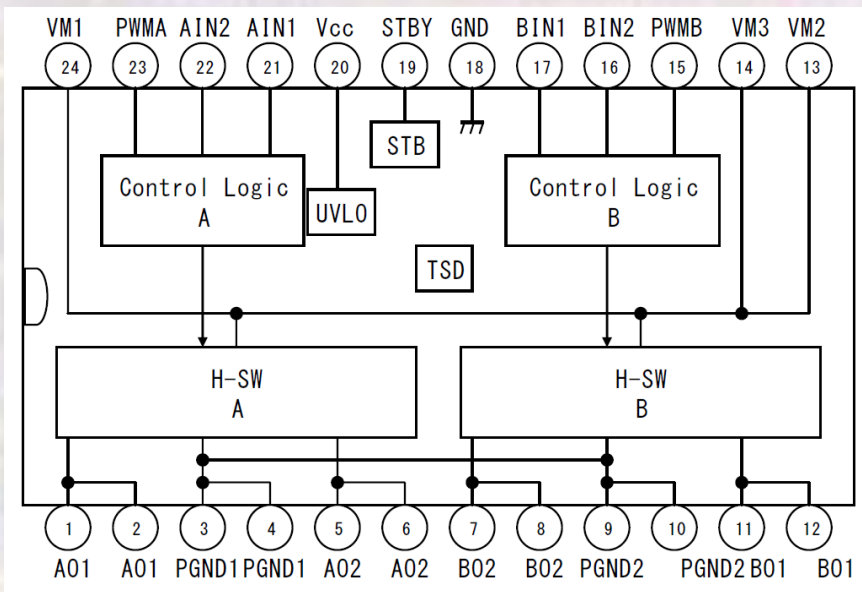
- Motor control
- Driver chip - TB6612FNG-breakout board



Note – some pins are combined on the board

DC Motors


- Motor control
 - Nominal Setup

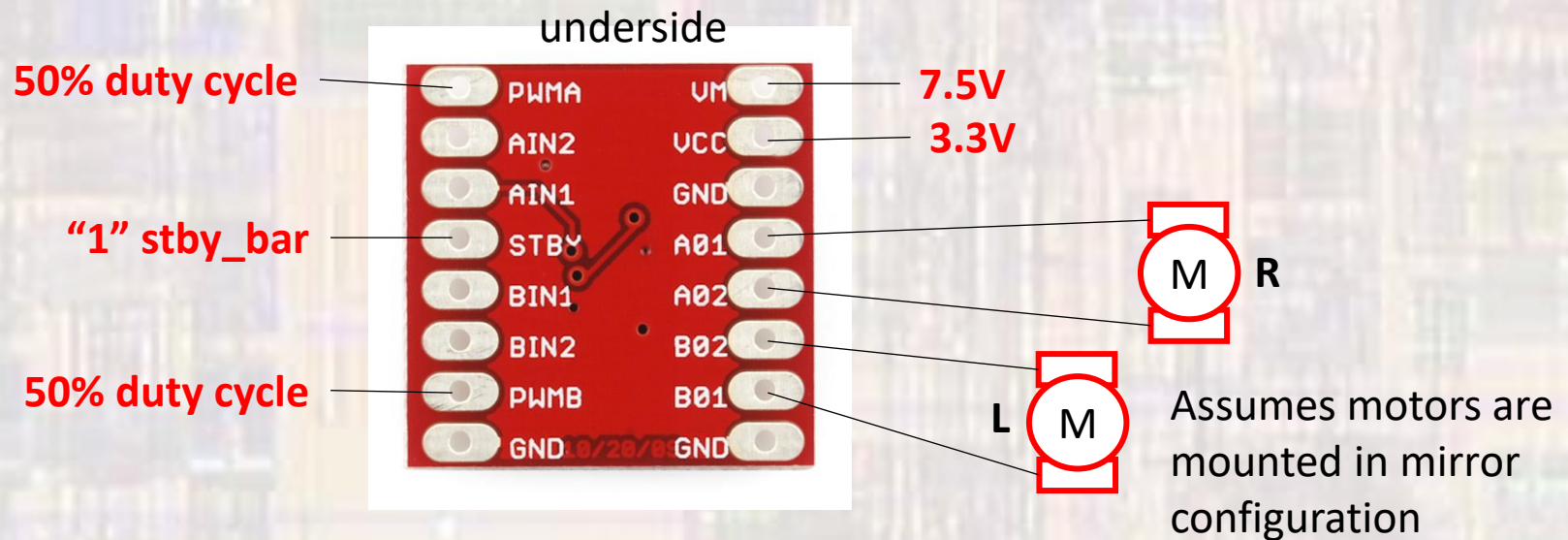

Note: Supply Decoupling and GND connection not shown

DC Motors

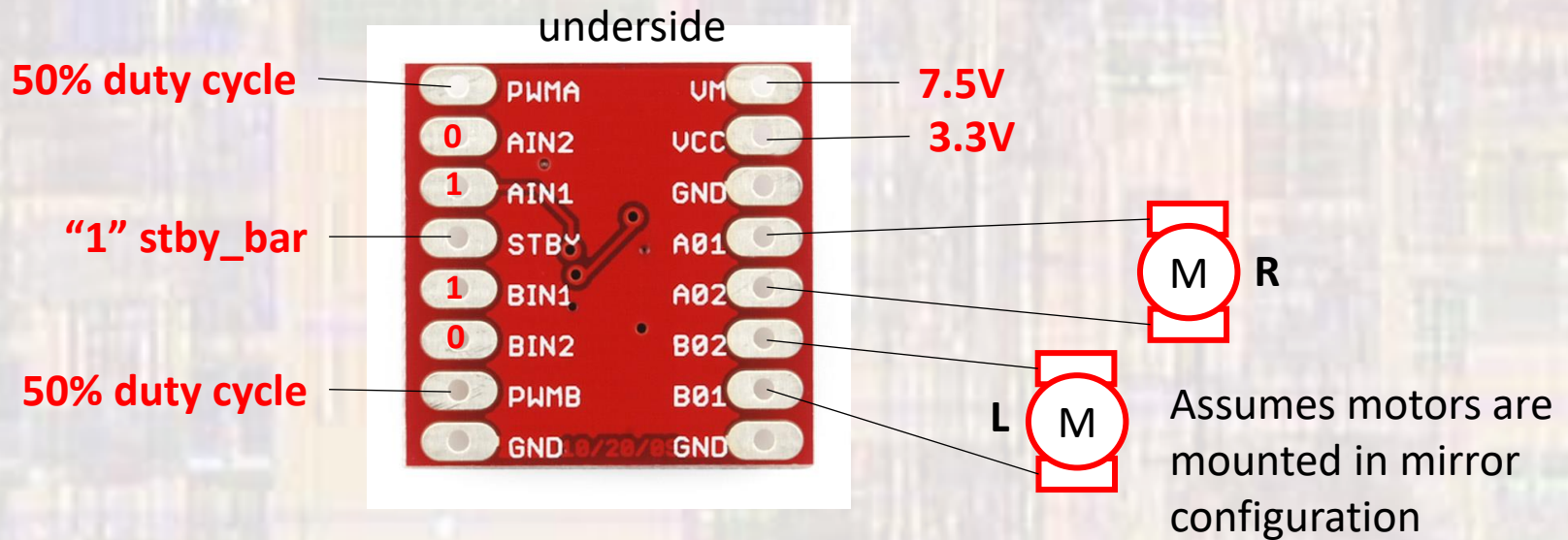
- Motor control
 - Example 1 forward together (lt and rt wheel fwd)



Note: Supply Decoupling and GND connection not shown

DC Motors

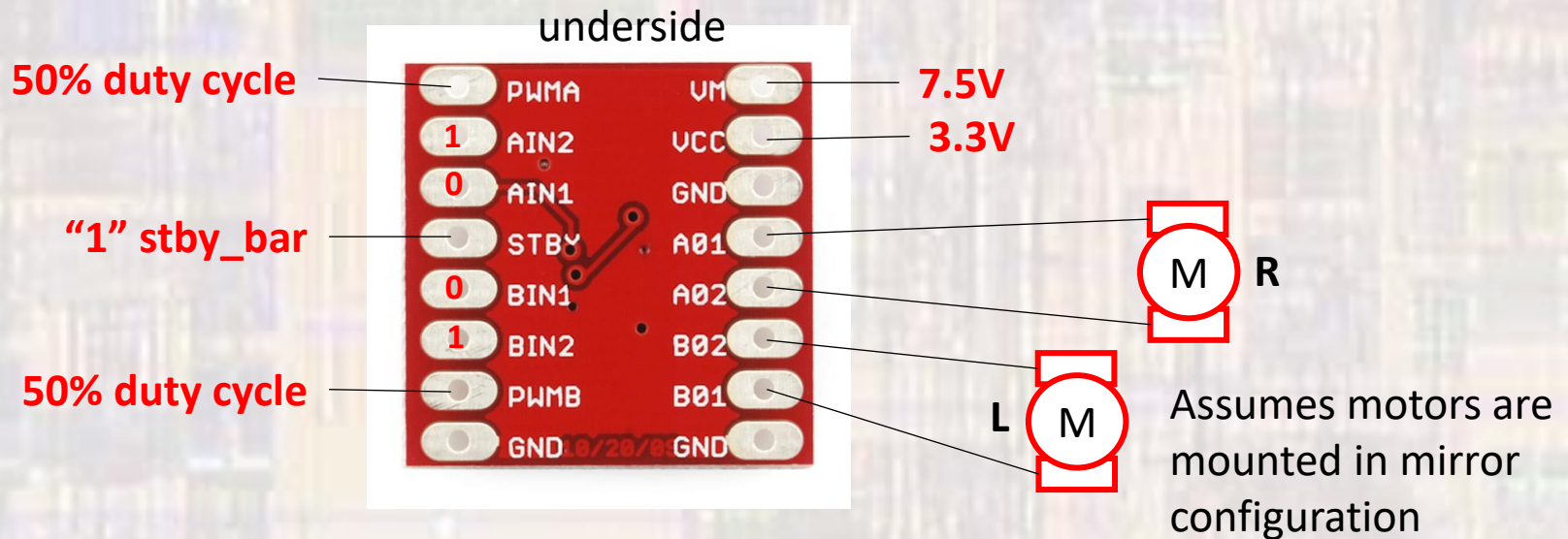
- Motor control
 - Example 2 backwards together (lt and rt wheel bwd)



Note: Supply Decoupling and GND connection not shown

DC Motors

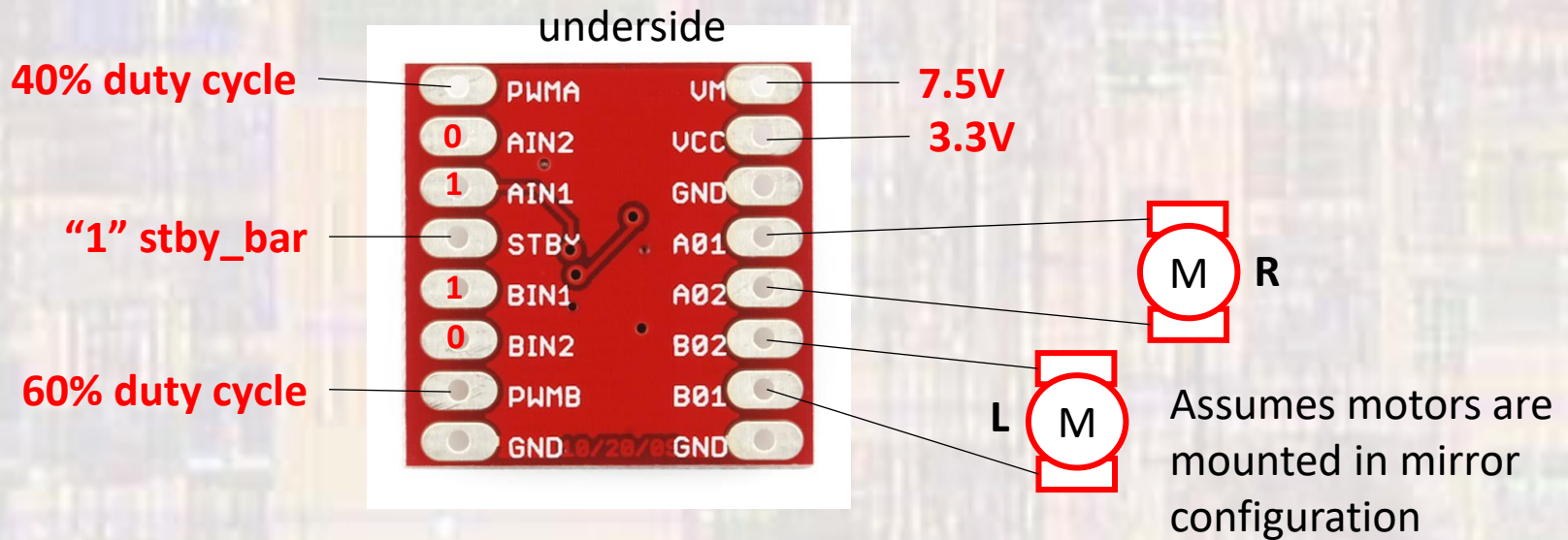
- Motor control
 - Example 3 wide right turn (lt wheel fwd fast, rt wheel fwd slow)



Note: Supply Decoupling and GND connection not shown

DC Motors

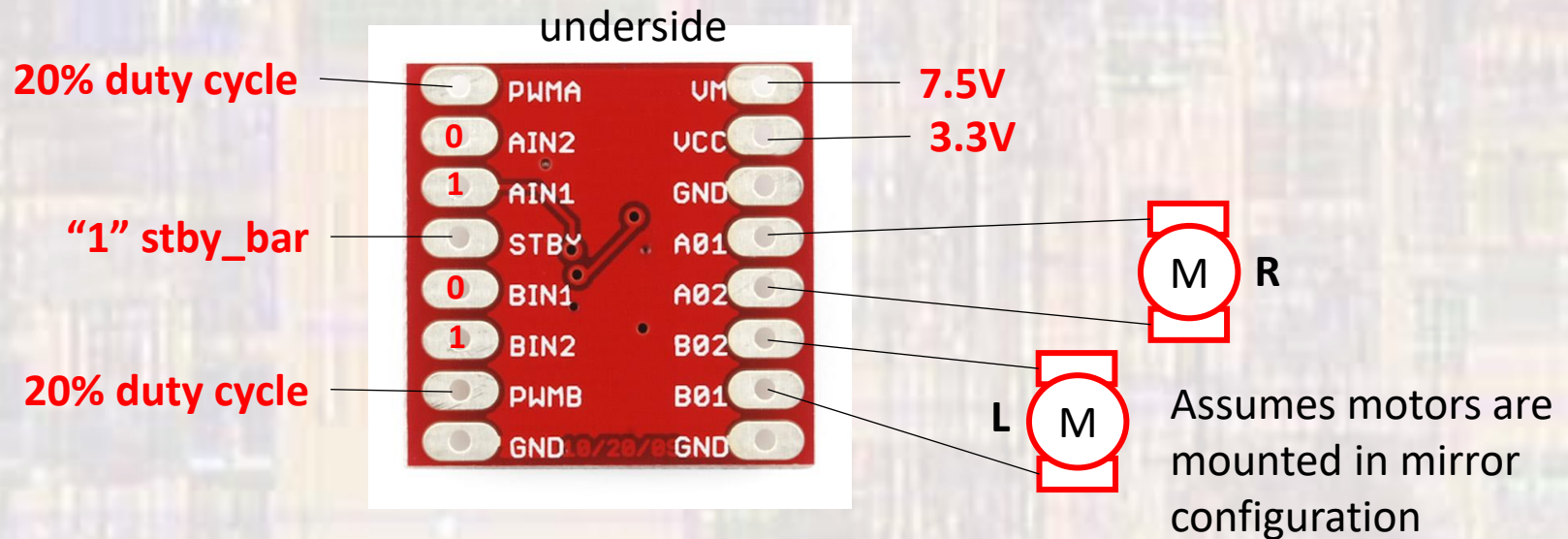
- Motor control
 - Example 4 slow tight left turn (lt wheel bwd, rt wheel fwd)



Note: Supply Decoupling and GND connection not shown

DC Motors

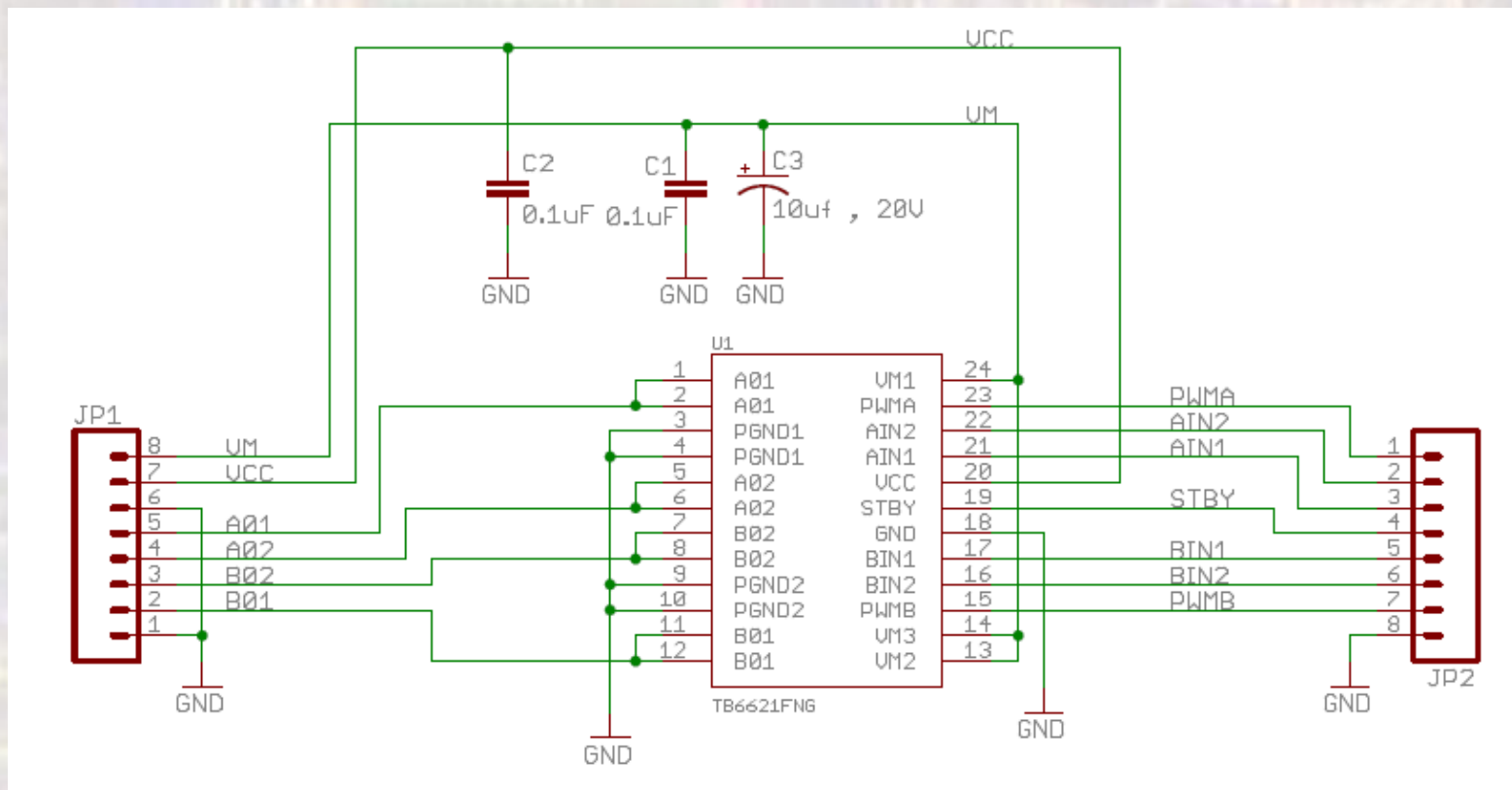- Motor control
 - Supply decoupling already on the breakout board



DC Motors

- Motor control
 - Noise Suppression
- 0.1uF ceramic capacitors
- $0.1\mu\text{f} = 100,000\text{pf} \rightarrow 10 + 4 \text{ zeros}$
 $\rightarrow 104$ marked on the capacitor

