

# Clock Dividers

Last updated 5/15/20

# Counters

These slides review the design for several types of clock dividers

Upon completion: You should be able to design an efficient clock divider

# Clock Dividers

- Clock Divider
  - Normally we do not use a clock divider  
Effectively a gated clock

BUT

- In order to see operation of designs on the DE10 we need to slow down the system clock (50MHz)
- To operate at 1 HZ → divide by 50,000,000

\* Note – we should really do this another way – but with small designs and all of our design running on the same clock we can get by

# Clock Dividers

- Clock Divider

```
-----  
-- clock_1hz_original.vhdl  
-- created 2/20/18  
-- tj  
-- rev 0  
-----  
-- 1Hz clock divider  
-- assume a 50MHz external clock  
-----  
-- Inputs: rstb, clk_50MHz  
-- Outputs: clk_out  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity clock_1hz_original is  
  port (  
    i_clk_50MHz : in std_logic;  
    I_rstb      : in std_logic;  
    o_clk_1Hz   : out std_logic  
  );  
end entity;
```

```
architecture behavioral of clock_1hz_original is  
  -- constants and parameters  
  constant CLKS_PER_HALF_PERIOD: unsigned(24 downto 0) := to_unsigned(((50_000_000 / 2) - 1), 25);  
  -- internal signals  
  signal cnt: unsigned(24 downto 0);  
  signal clk_sig: std_logic;  
begin  
  process(i_clk_50MHz, i_rstb)  
    begin  
      -- reset  
      if (i_rstb = '0') then  
        cnt <= (others => '0');  
        clk_sig <= '0';  
      elsif (rising_edge(i_clk_50MHz) ) then  
        cnt <= cnt + 1;  
        -- check if half way  
        if (cnt = CLKS_PER_HALF_PERIOD) then  
          cnt <= (others => '0');  
          clk_sig <= not clk_sig;  
        end if;  
      end if;  
    end process;  
    -- output logic  
    o_clk_1Hz <= clk_sig;  
  end behavioral;
```


# Clock Dividers

- Clock Divider

## Flow Summary

<<Filter>>


Flow Status	Successful - Wed Dec 18 08:32:16 2019
Quartus Prime Version	18.0.0 Build 614 04/24/2018 SJ Lite Edition
Revision Name	general_hdl
Top-level Entity Name	clock_1hz_original
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	47 / 49,760 (< 1 %)
Total registers	26
Total pins	3 / 360 (< 1 %)
Total virtual pins	0
Total memory bits	0 / 1,677,312 (0 %)
Embedded Multiplier 9-bit elements	0 / 288 (0 %)
Total PLLs	0 / 4 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 2 (0 %)

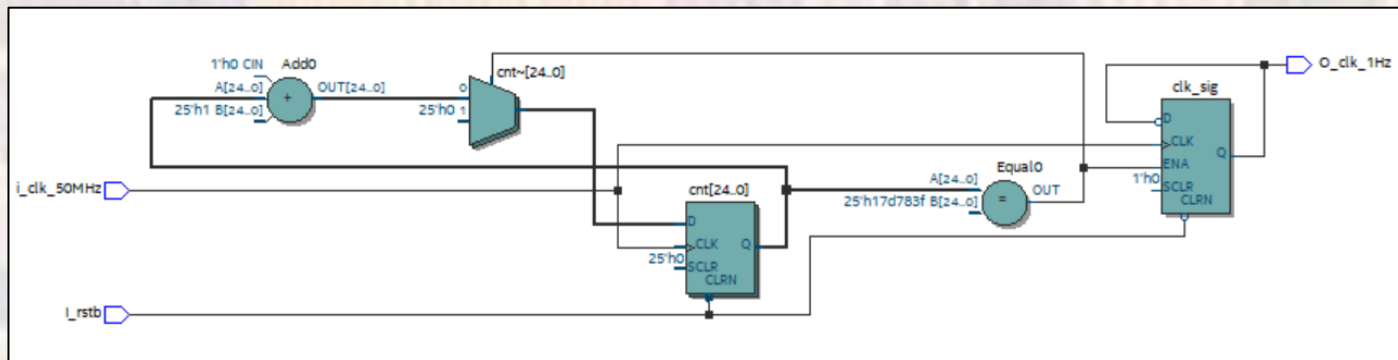


 
# Clock Dividers

- Clock Divider
  - original
  - modified to  $\text{CLOCKS\_PER\_HALF\_PERIOD} = (10 - 1)$



# Clock Dividers

- Clock Divider – enhanced (count down)

why is the bit width larger?

```
-- clock_1hz.vhdl
-- created 2/20/18
-- tj
--
-- rev 0
-----
-- 1Hz clock divider
-- assume a 50MHz external clock
-----
-- Inputs: rstb, clk_50MHz
-- Outputs: clk_out
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;


entity clock_1hz is
  port (
    i_clk_50MHz : in std_logic;
    I_rstb      : in std_logic;
    o_clk_1Hz  : out std_logic
  );
end entity;
```

```
architecture behavioral of clock_1hz is
  -- constants and parameters
  constant CLOCKS_PER_HALF_PERIOD: signed(25 downto 0) := to_signed(((50_000_000 / 2) - 2), 26);
  -- internal signals
  signal cnt: signed(25 downto 0);
  signal clk_sig: std_logic;
begin
  process(i_clk_50MHz, i_rstb)
  begin
    -- reset
    if (i_rstb = '0') then
      cnt <= CLOCKS_PER_HALF_PERIOD;
      clk_sig <= '0';
    elsif (rising_edge(i_clk_50MHz) ) then
      cnt <= cnt - 1;
      -- check if half way
      if (cnt < 0) then
        cnt <= CLOCKS_PER_HALF_PERIOD;
        clk_sig <= not clk_sig;
      end if;
    end if;
  end process;

  -- output logic
  o_clk_1Hz <= clk_sig;
end behavioral;
```

# Clock Dividers

- Clock Divider - enhanced

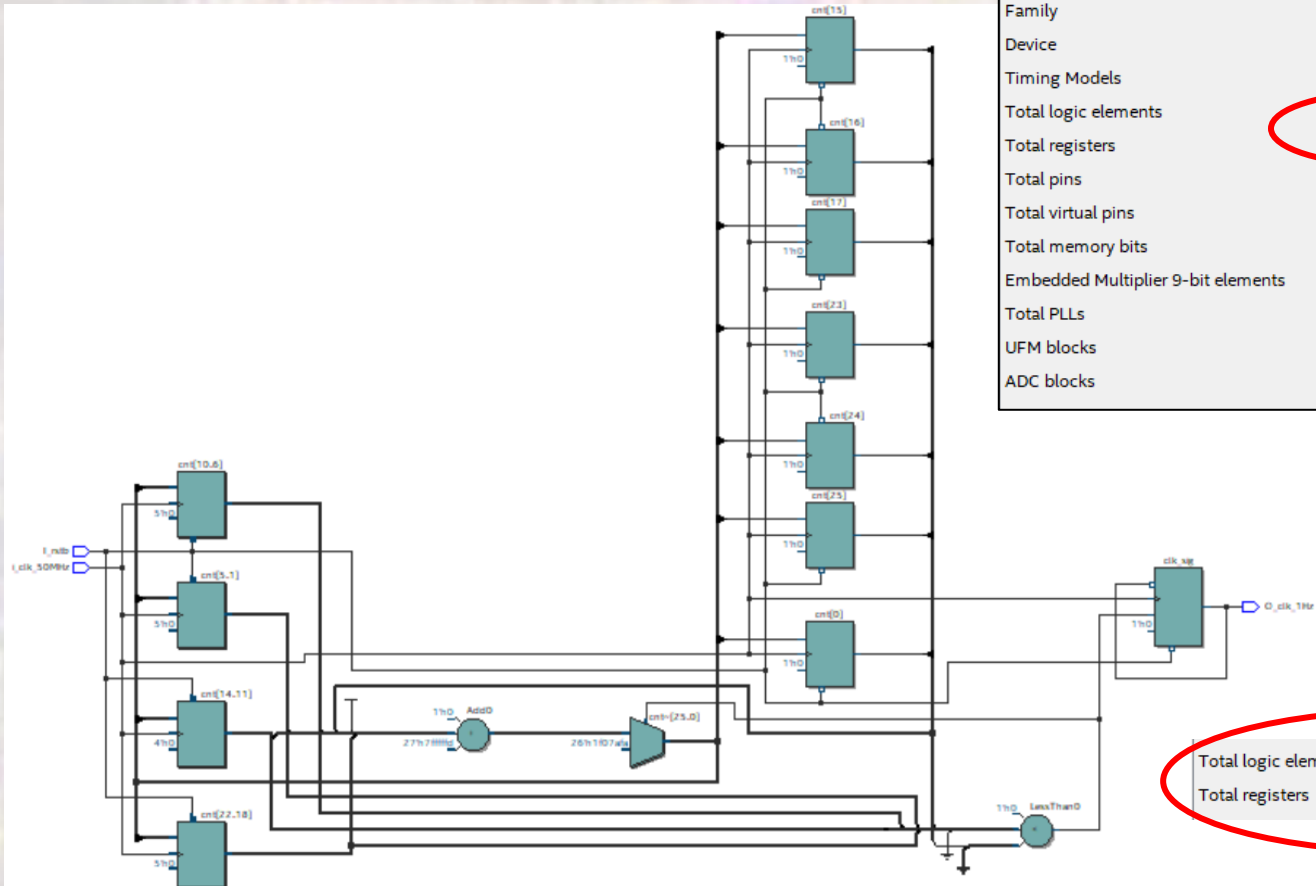

Flow Summary	
Flow Status	Successful - Wed Dec 18 08:43:43 2019
Quartus Prime Version	18.0.0 Build 614 04/24/2018 SJ Lite Edition
Revision Name	general_hdl
Top-level Entity Name	clock_1hz
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	28 / 49,760 (< 1 %)
Total registers	27
Total pins	3 / 360 (< 1 %)
Total virtual pins	0
Total memory bits	0 / 1,677,312 (0 %)
Embedded Multiplier 9-bit elements	0 / 288 (0 %)
Total PLLs	0 / 4 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 2 (0 %)

original

Total logic elements	47 / 49,760 (< 1 %)
Total registers	26





# Clock Dividers

- Clock Divider – enhanced → 10Hz

```
-----  
-- clock_10hz.vhd1  
-- created 2/20/18  
-- tj  
-- rev 0  
-----  
-- 10Hz clock divider  
-- assume a 50MHz external clock  
-----  
-- Inputs: rstb, clk_50MHz  
-- Outputs: clk_out  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity clock_10hz is  
    port (  
        i_clk_50MHz : in std_logic;  
        I_rstb      : in std_logic;  
        o_clk_10Hz  : out std_logic  
    );  
end entity;
```

```
architecture behavioral of clock_10hz is  
    -- constants and parameters  
    constant CLOCKS_PER_HALF_PERIOD: signed(22 downto 0) := to_signed((((50_000_000 / 2) / 10) - 2), 23);  
    -- internal signals  
    signal cnt: signed(22 downto 0);  
    signal clk_sig: std_logic;  
begin  
    process(i_clk_50MHz, i_rstb)  
        begin  
            -- reset  
            if (i_rstb = '0') then  
                cnt <= CLOCKS_PER_HALF_PERIOD;  
                clk_sig <= '0';  
            elsif (rising_edge(i_clk_50MHz) ) then  
                cnt <= cnt - 1;  
                -- check if half way  
                if (cnt < 0) then  
                    cnt <= CLOCKS_PER_HALF_PERIOD;  
                    clk_sig <= not clk_sig;  
                end if;  
            end if;  
        end process;  
    -- Output logic  
    o_clk_10Hz <= clk_sig;  
end behavioral;
```