

Finite State Machine w/ Data Path

Last updated 9/24/20


FSMD

These slides review FSM's with Datapath

Upon completion: You should be able to design and simulate FSM's with Datapath



FSMD

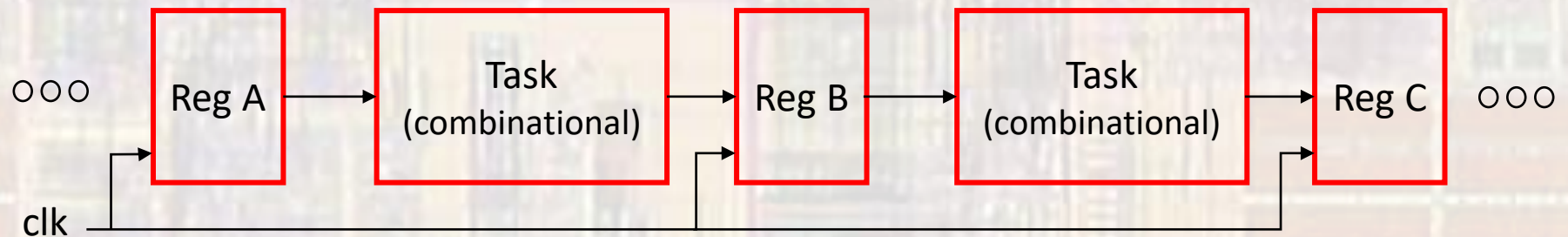- FSMD
 - FSM with Data Path
 - FSM
 - Control the Data Path
 - Data Path
 - Sequential circuitry to accomplish a task
 - Typically register transfer operations




FSMD

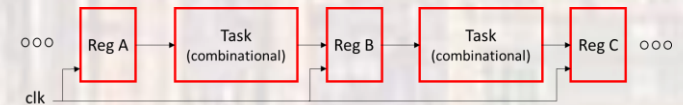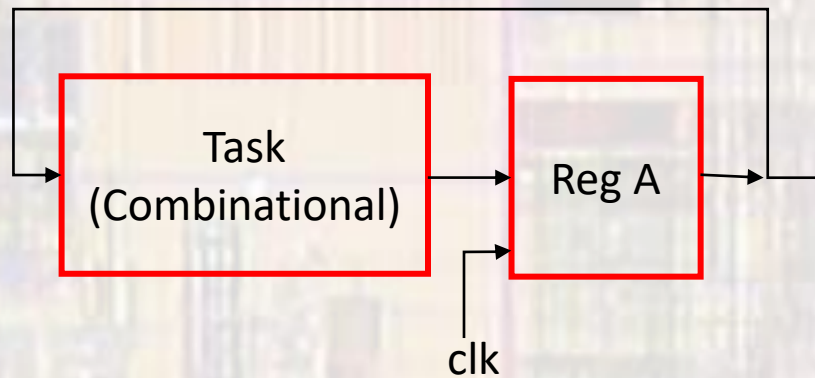- FSMD
 - FSM with Data Path
 - Data Path
 - Sequential circuitry to accomplish a task
 - Typically register transfer operations



FSMD

- FSMD

 

FSMD

- Fibonacci – FSMD

$$\text{fib}(i) = \begin{cases} 0 & i = 0 \\ 1 & i = 1 \\ \text{fib}(i-1) + \text{fib}(i-2) & i > 1 \end{cases}$$


for i= 6
0-1-1-2-3-5-8

FSMD

- Fibonacci – FSMD
 - Input Signals
 - clk, rstb
 - num_cycles – how many numbers to generate - vector
 - startb – start generating (bar)
 - Output Signals
 - complete – generation complete
 - result_latched – Final Fibonacci value
 - States
 - Idle
 - Run
 - Complete


FSMD

- Fibonacci – FSMD

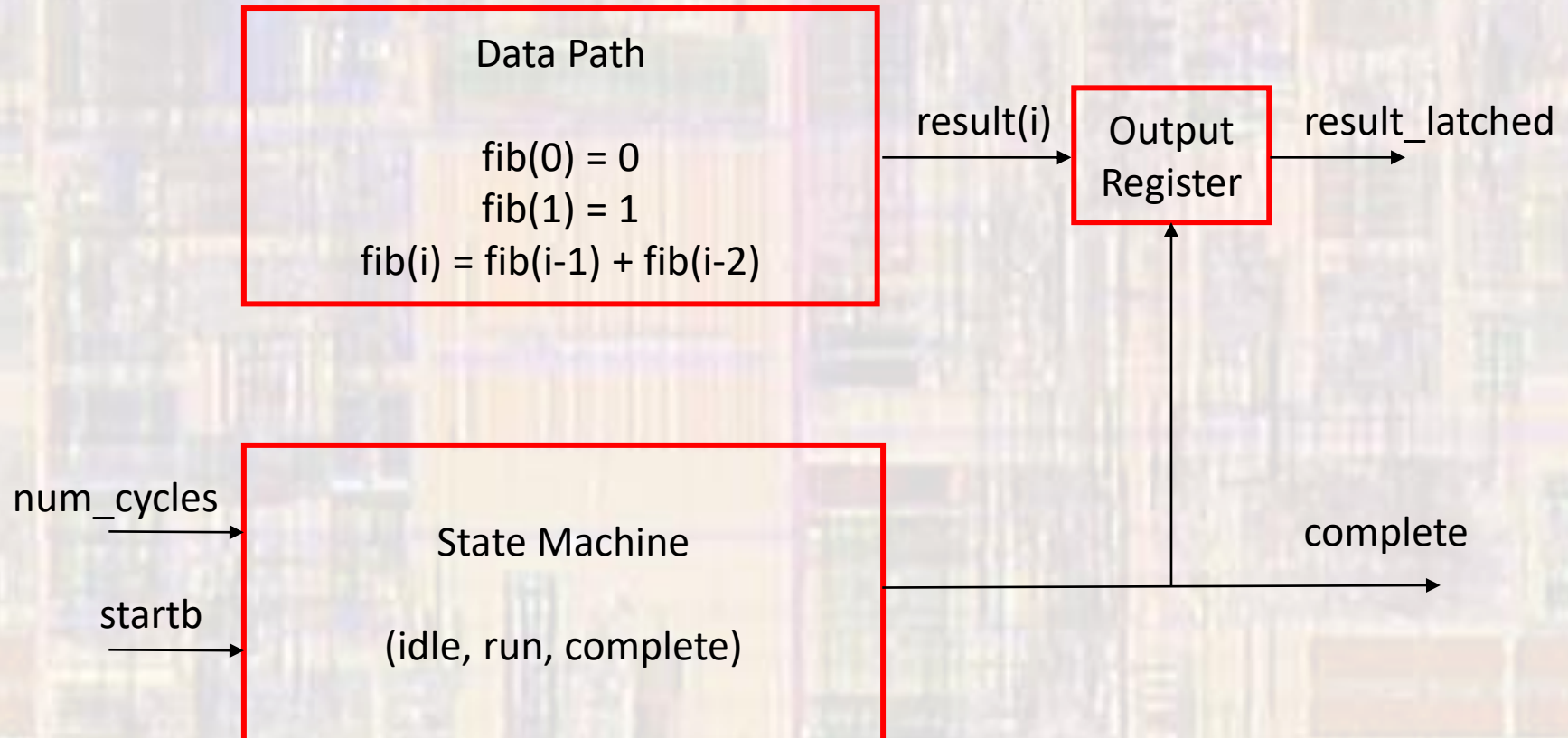


FSMD

- Fibonacci – FSMD

 

FSMD


- Fibonacci – FSMD
- Control Path

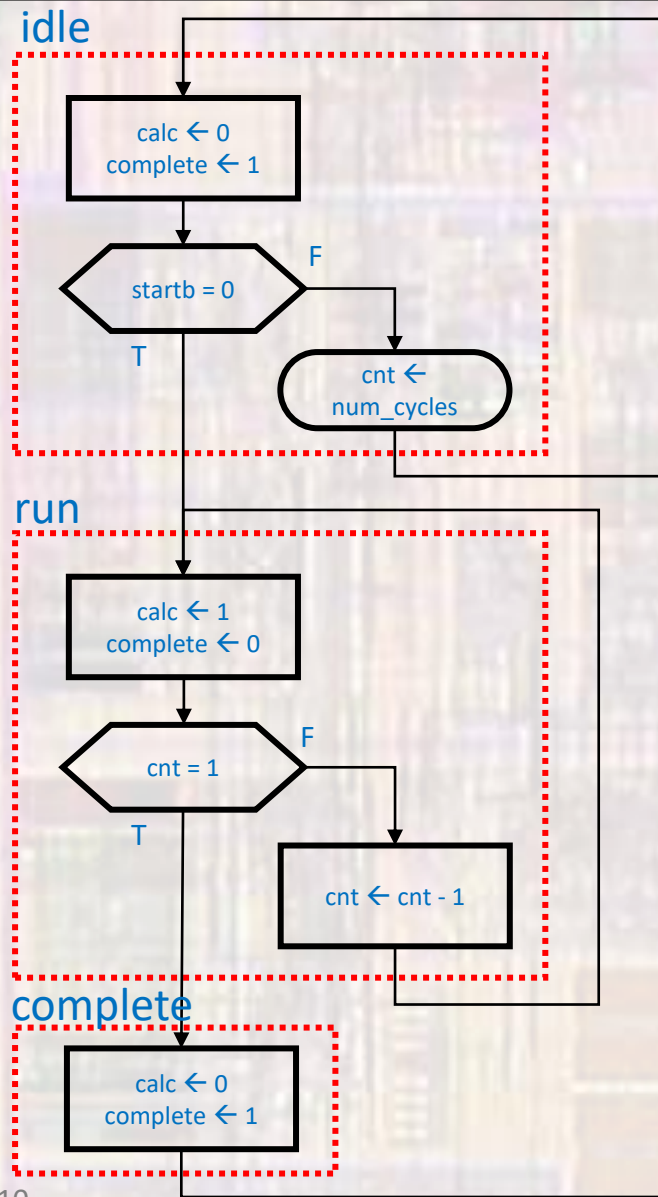

FSMD


- Fibonacci – FSMD

- Data Path

 


FSMD

- Fibonacci – FSMD

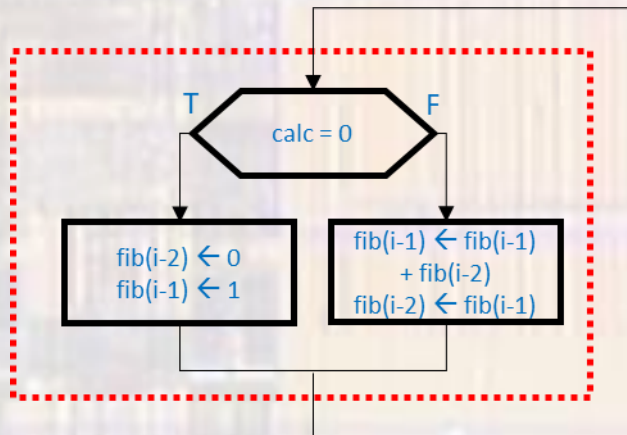

← calc

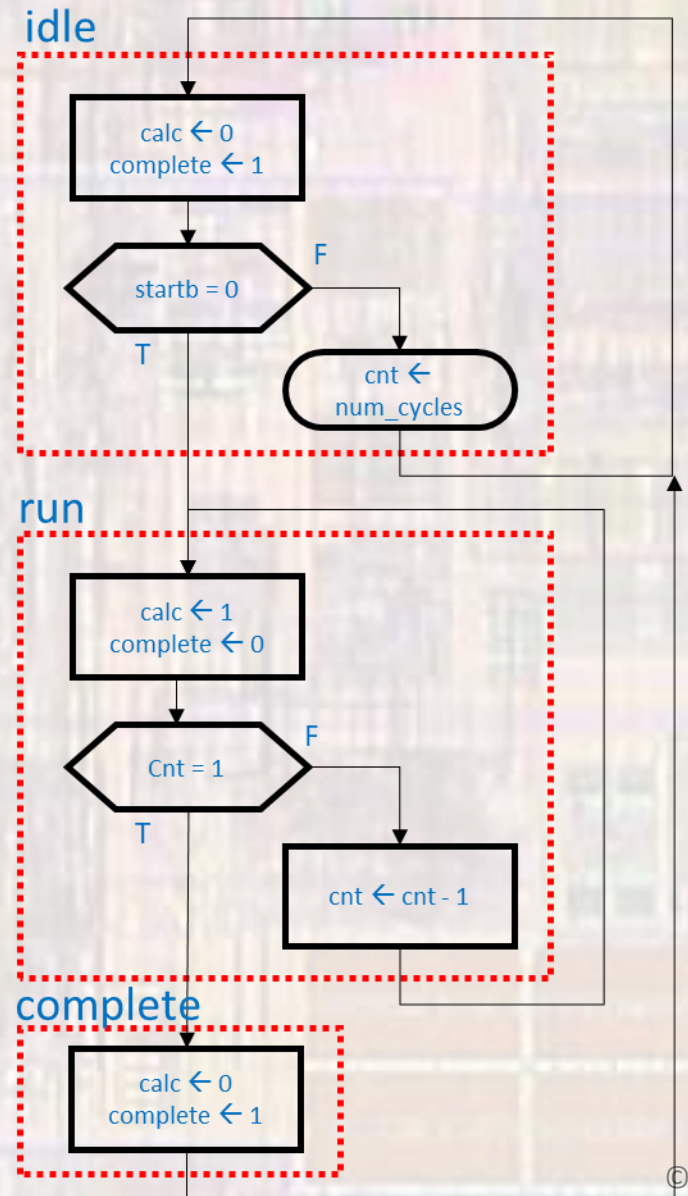

FSMD

- Fibonacci – FSMD - FSM

```
-- fibonacci_fsm.vhdl
-- created 4/16/17
-- tj
-- rev 0
-----
-- FSM for fibonacci
-----
-- Inputs: rstb, clk, startb, num_cycles
-- Outputs: complete, calc
--
-- NOTE: N is the width of the num_cycles bus
-- 2**N specifies the maximum # of iterations
--
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity fibonacci_fsm is
  generic(
    N: natural := 5
  );
  port (
    i_clk:          in std_logic;
    i_rstb:         in std_logic;
    i_startb:       in std_logic;
    i_num_cycles:   in std_logic_vector((N - 1) downto 0);

    o_calc:         out std_logic;
    o_complete :    out std_logic
  );
end entity;
```

```
architecture behavioral of fibonacci_fsm is
  -- State Types
  --
  type STATE_TYPE is (Idle, Run, Finish);
  signal state:     STATE_TYPE;
  signal state_next: STATE_TYPE; --

  -- FSM signals
  --
  signal cnt:       unsigned((N-1) downto 0);

begin
  -- next state logic
  --
  process(all)
  begin
    case state is
      when Idle=>
        if(i_startb = '0') then
          state_next <= Run;
        else
          state_next <= Idle;
        end if;
      when Run =>
        if(cnt = 1) then
          state_next <= Finish;
        else
          state_next <= Run;
        end if;
      when others =>
        state_next <= Idle;
    end case;
  end process;

  -- State Register logic
  --
  process(i_clk, i_rstb)
  begin
    -- reset
    if (i_rstb = '0') then
      state <= Idle;
    -- rising clk edge
    elsif (rising_edge(i_clk)) then
      state <= state_next;
    end if;
  end process;
```

FSMD

- Fibonacci – FSMD - FSM

```
--  
-- counter logic  
--  
process(i_clk, i_rstb)  
begin  
  -- reset  
  if (i_rstb = '0') then  
    cnt <= (others => '0');  
  elsif (i_startb = '0') then  
    cnt <= unsigned(i_num_cycles);  
  -- rising clk edge  
  elsif (rising_edge(i_clk)) then  
    cnt <= cnt - 1;  
  end if;  
end process;
```

```
--  
-- output logic  
--  
process(all)  
begin  
  case state is  
    when Idle=>  
      o_complete <= '1';  
      o_calc <= '0';  
    when Run =>  
      o_complete <= '0';  
      o_calc <= '1';  
    when Finish =>  
      o_complete <= '1';  
      o_calc <= '0';  
    when others =>  
      o_complete <= '0';  
      o_calc <= '0';  
  end case;  
end process;  
end behavioral;
```

FSMD

- Fibonacci – FSMD - data path

```
-----  
-- fibonacci_datapath.vhd1  
-- created 4/16/17  
-- tj  
--  
-- rev 0  
-----  
--  
-- fibonacci datapath  
-- Limited to N values  
-----  
--  
-- Inputs: clk, start, count  
-- Outputs: fib  
--  
-- NOTE: N is the width of the num_cycles bus  
-- 2**N specifies the maximum # of iterations  
--  
-- NOTE: The width of the result is calculated from  
-- using an equation for the 2**Nth value  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use ieee.math_real.all;  
  
entity fibonacci_datapath is  
  generic(  
    N: natural := 5  
  );  
  port (  
    i_clk: in std_logic;  
    i_calc: in std_logic;  
  
    o_fib: out std_logic_vector(((integer(ceil(log2(((1.0 + sqrt(5.0))/2.0)**(2**(N-1)) - ((1.0 - sqrt(5.0))/2.0)**(2**(N-1)))/sqrt(5.0)))) - 1) downto 0)  
  );  
end entity;
```

FSMD

- Fibonacci – FSMD - data path

```
architecture behavioral of fibonacci_datapath is
  constant result_w: integer := integer(ceil(log2(((1.0 + sqrt(5.0))/2.0)**(2**(N-1)) - ((1.0 - sqrt(5.0))/2.0)**(2**(N-1)))/sqrt(5.0)));
  -- data path signals
  signal f_minus1:    unsigned((result_w - 1) downto 0);
  signal f_minus1_next: unsigned((result_w - 1) downto 0);
  signal f_minus2:    unsigned((result_w - 1) downto 0);
  signal f_minus2_next: unsigned((result_w - 1) downto 0);
begin
  --
  -- data path - D next state logic
  --
  process(all)
  begin
    if (i_calc = '0') then
      f_minus2_next <= (others => '0');
      f_minus1_next <= (to_unsigned(1,result_w));
    else
      f_minus2_next <= f_minus1;
      f_minus1_next <= f_minus1 + f_minus2;
    end if;
  end process;

  --
  -- Datapath register logic
  --
  process(i_clk)
  begin
    -- rising clk edge
    if (rising_edge(i_clk)) then
      f_minus2 <= f_minus2_next;
      f_minus1 <= f_minus1_next;
    end if;
  end process;

  --
  -- Output logic
  --
  o_fib <= std_logic_vector(f_minus1);
end behavioral;
```


FSMD

- Fibonacci – FSMD

```
-----  
-- fibonacci_fsmd.vhd  
-- created 9/7/18  
-- tj  
-- rev 0  
-----  
-- FSMD for fibonacci  
-----  
-- Inputs: rstb, clk, startb, num_cycles  
-- Outputs: result_latched, complete  
--  
-- NOTE: N is the width of the num_cycles bus  
-- 2**N specifies the maximum # of iterations  
--  
-- NOTE: The width of the result is calculated from  
-- using an equation for the 2**Nth value  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
use ieee.math_real.all;  
entity fibonacci_fsmd is  
    generic(  
        N: natural := 6  
    );  
    port (  
        i_clk           : in std_logic;  
        i_rstb          : in std_logic;  
        i_startb        : in std_logic;  
        i_num_cycles    : in std_logic_vector((N - 1) downto 0);  
  
        o_result_latched : out std_logic_vector((((integer(ceil(log2(((1.0 + sqrt(5.0))/2.0)**(2**(N-1)) - ((1.0 - sqrt(5.0))/2.0)**(2**(N-1)))/sqrt(5.0)))))) - 1) downto 0);  
        o_complete      : out std_logic  
    );  
end entity;
```

FSMD

- Fibonacci – FSMD

```
architecture behavioral of fibonacci_fsmd is
-- structural signals
signal calc:      std_logic;
signal result:    std_logic_vector((((integer(ceil(log2((((1.0 + sqrt(5.0))/2.0)**(2**(N-1)) - ((1.0 - sqrt(5.0))/2.0)**(2**(N-1)))/sqrt(5.0)))))) - 1) downto 0);

-----
-- Component prototype
-----
COMPONENT fibonacci_fsm
generic(
  N: natural := 5
);
port (
  i_clk:      in std_logic;
  i_rstb:     in std_logic;
  i_startb:   in std_logic;
  i_num_cycles: in std_logic_vector((N - 1) downto 0);

  o_calc:     out std_logic;
  o_complete : out std_logic
);
END COMPONENT;

COMPONENT fibonacci_datapath
generic(
  N: natural := 5
);
port (
  i_clk:      in std_logic;
  i_calc:     in std_logic;

  o_fib : out std_logic_vector((((integer(ceil(log2((((1.0 + sqrt(5.0))/2.0)**(2**(N-1)) - ((1.0 - sqrt(5.0))/2.0)**(2**(N-1)))/sqrt(5.0)))))) - 1) downto 0)
);
END COMPONENT;
```

FSMD

- Fibonacci – FSMD





```
begin
-----
-- Device instantiations
-----
fsm: fibonacci_fsm
  generic map(
    N => N
  )
  port map(
    i_clk           => i_clk,
    i_rstb          => i_rstb,
    i_startb        => i_startb,
    i_num_cycles    => i_num_cycles,
    o_calc          => calc,
    o_complete      => o_complete
  );

datapath: fibonacci_datapath
  generic map(
    N => N
  )
  port map(
    i_clk           => i_clk,
    i_calc          => calc,
    o_fib           => result
  );

-- latch the result so it doesnt reset
--
process(i_clk, i_rstb)
begin
  if(i_rstb = '0') then
    o_result_latched <= (others => '0');
  elsif(rising_edge(i_clk)) then
    if (o_complete = '0') then
      o_result_latched <= result;
    end if;
  end if;
end process;
end behavioral;
```

FSMD



- Fibonacci

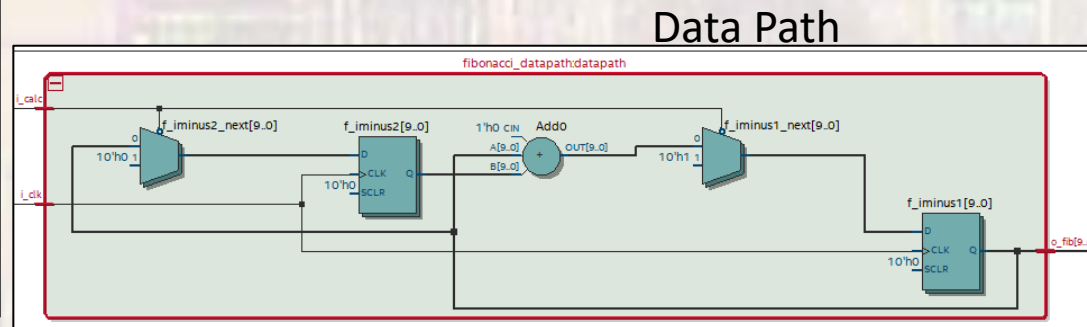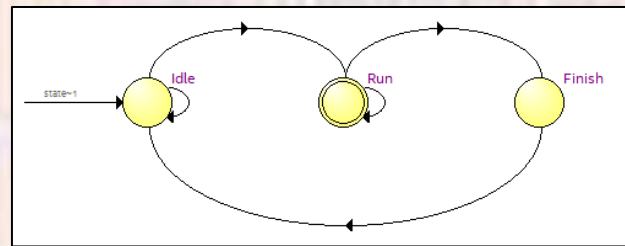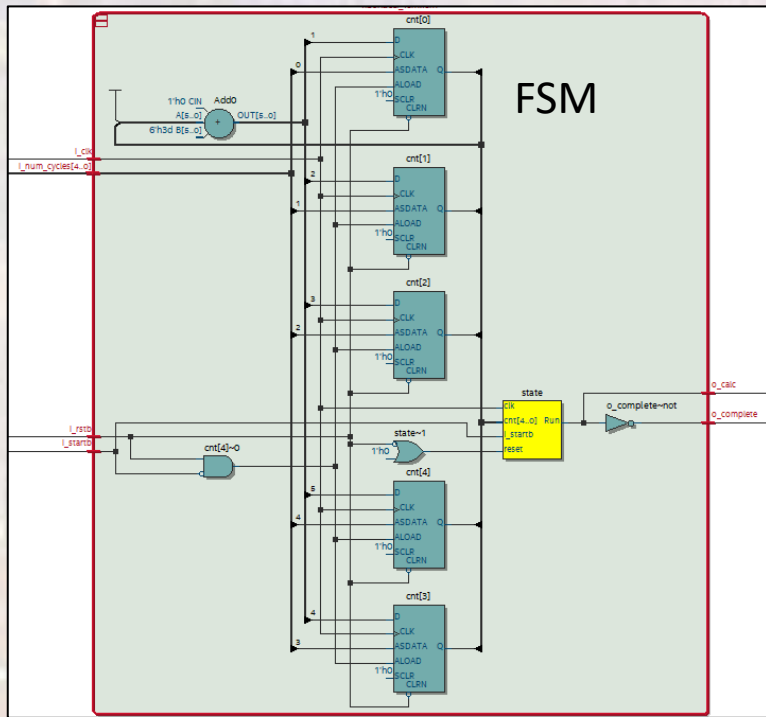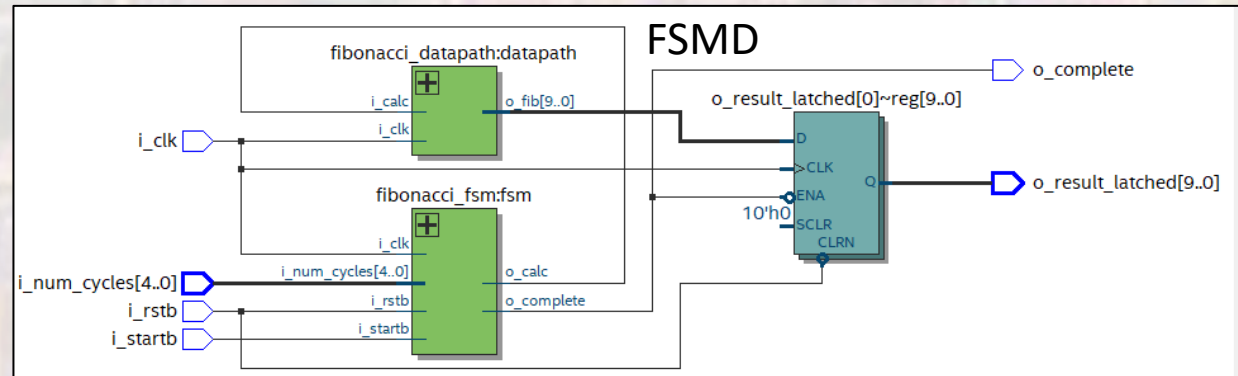


FSMD

- Fibonacci

Results and intermediate values

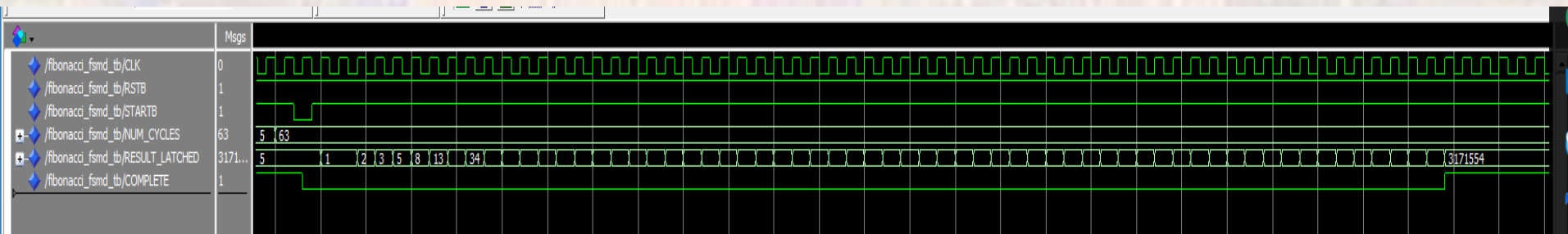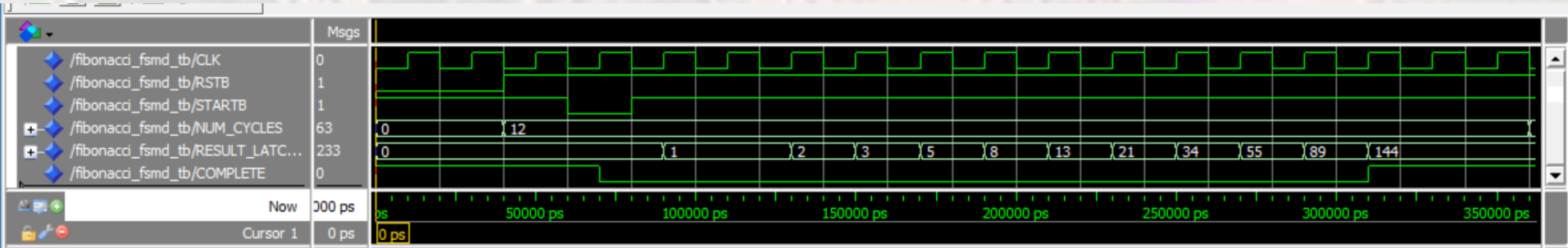

N = 6

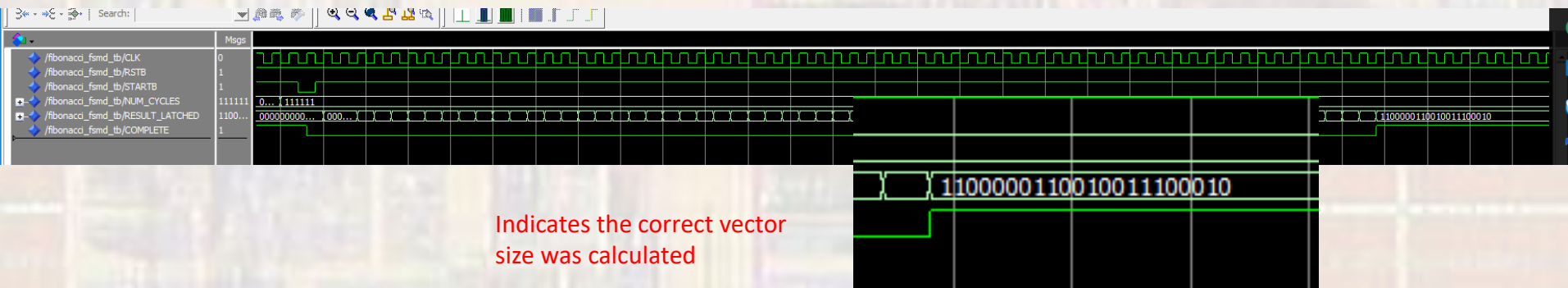

Indicates the correct vector size was calculated

FSMD

- Multiplication
 - Shift and add

$$\begin{array}{r} 1110 \\ \times 0011 \\ \hline \end{array} \quad \rightarrow \quad \begin{array}{r} 11111110 \\ \times 00000011 \\ \hline \end{array}$$

$$\begin{array}{r} 11111110 \\ \times 00000011 \\ \hline 11111110 \\ 11111110 \\ 00000000 \\ 00000000 \\ 00000000 \\ 00000000 \\ 00000000 \\ 00000000 \\ \hline 11111010 \end{array}$$

FSMD


- Multiplication
 - Want a process that is repetitive
 - Repetitive addition multiplication

$5 \times 4 = 5 + 5 + 5 + 5$ i.e. the **multiplicand** added the **multiplier** times

- Requires integers – or non-fractional binary numbers for the multiplier


FSMD

- Multiplier

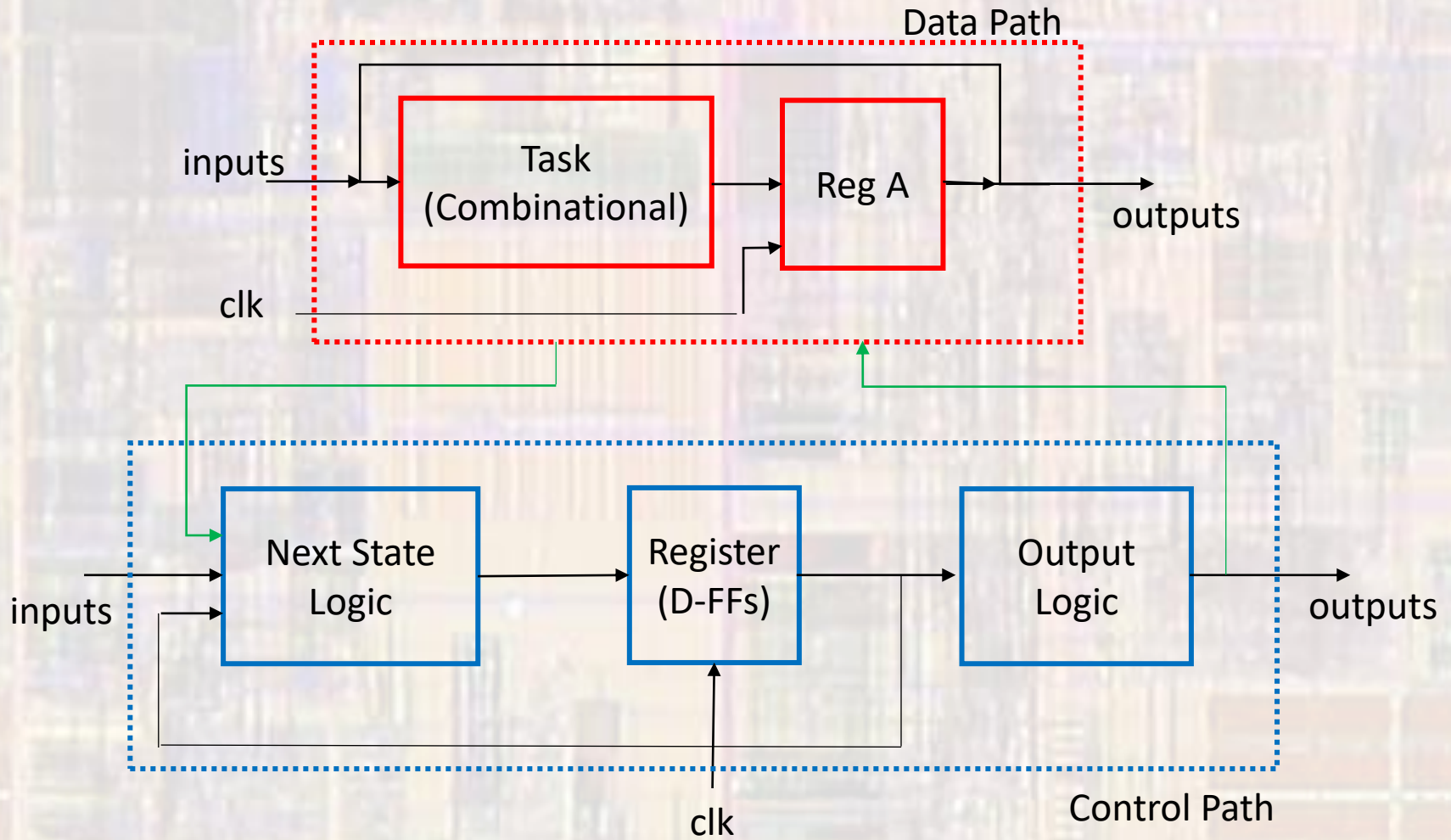

FSMD


- Multiplier – FSMD
- Control Path

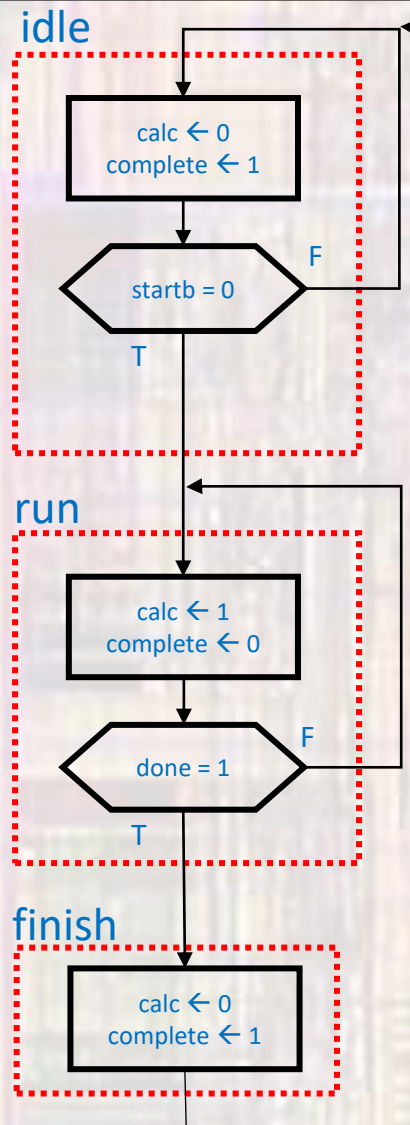

FSMD



- Multiplier – FSMD

- Data Path

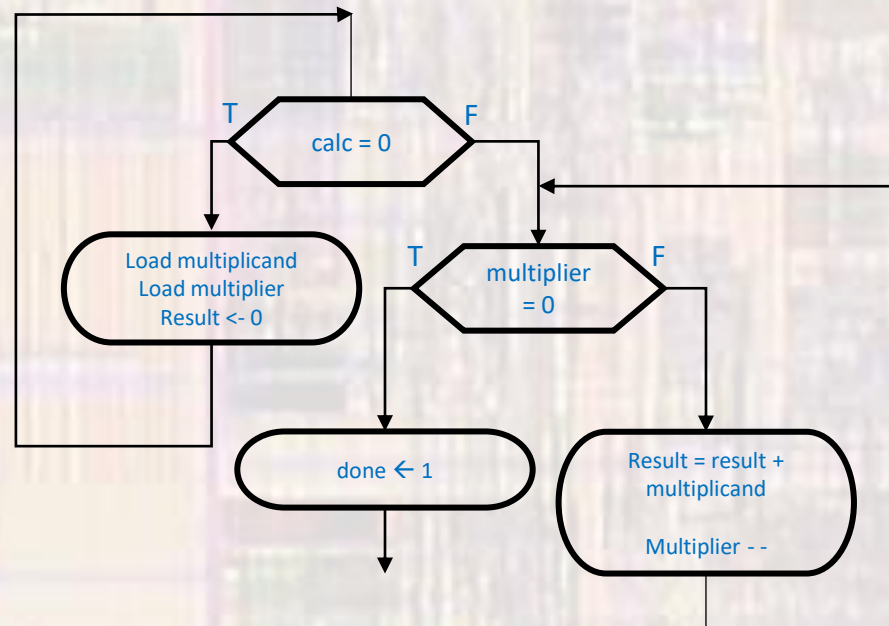

FSMD

- Multiplier – FSMD

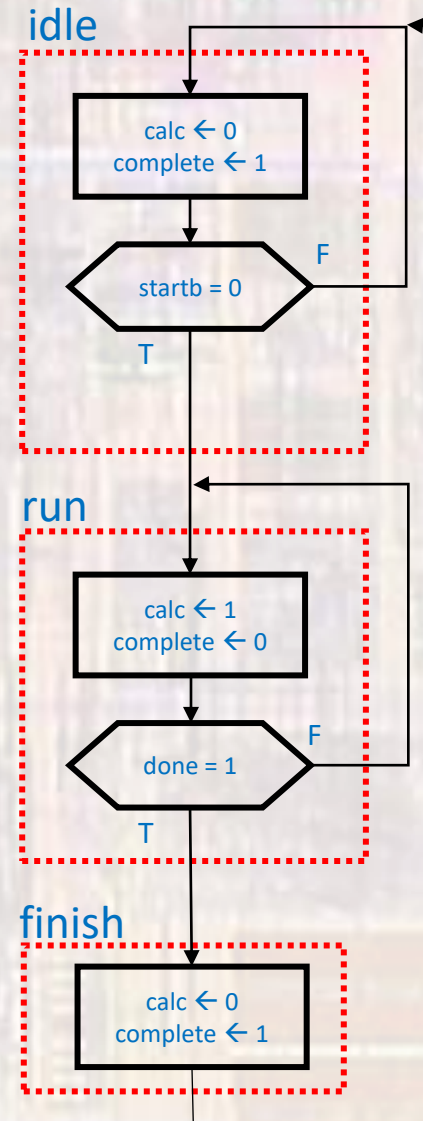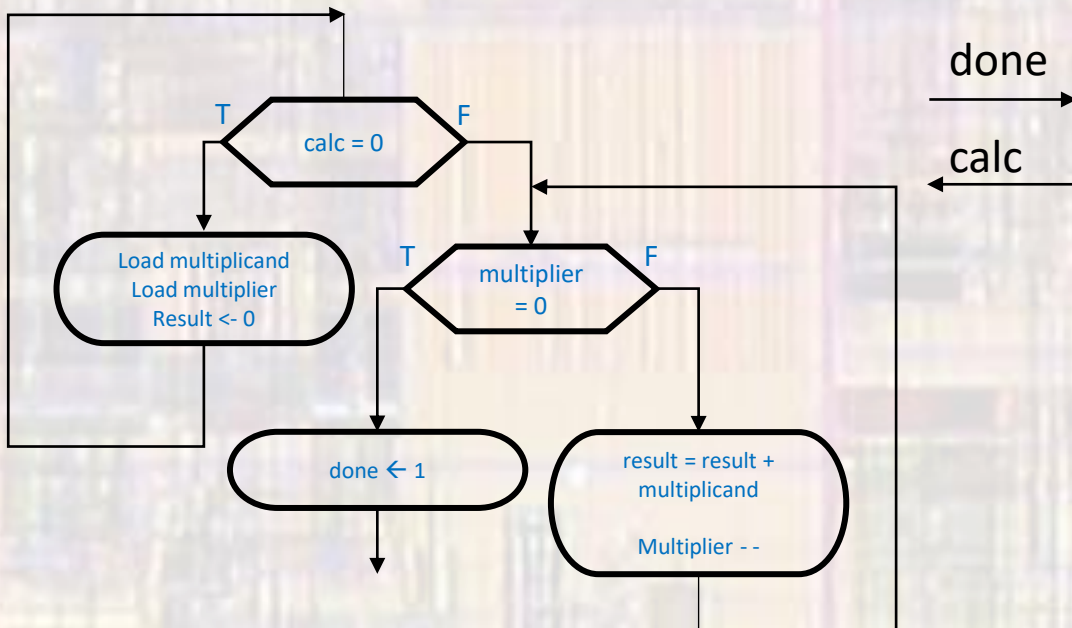

FSMD

- Multiplier – FSMD - FSM

```
-----  
-- mult_rep_add_4bit_fsm.vhdl  
--  
-- created 9/12/18  
-- tj  
-- rev 0  
-----  
--  
-- FSM for repetitive addition multiplier  
-- tells the datapath when to calculate (calc) and uses  
-- done from the datapath to know its complete  
-----  
--  
-- Inputs: rstb, clk, startb, done  
-- Outputs: calc, complete  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity mult_rep_add_4bit_fsm is  
  port (  
    i_clk          : in std_logic;  
    i_rstb         : in std_logic;  
    i_startb       : in std_logic;  
    i_done         : in std_logic;  
  
    o_calc         : out std_logic;  
    o_complete    : out std_logic  
  );  
end entity;
```

```
architecture behavioral of mult_rep_add_4bit_fsm is  
  --  
  -- State Types  
  --  
  type STATE_TYPE is (Idle, Run, Finish);  
  signal state:      STATE_TYPE;  
  signal state_next: STATE_TYPE;  
  
begin  
  --  
  -- next state logic  
  --  
  process(all)  
  begin  
    case state is  
      when Idle=>  
        if(i_startb = '0') then  
          state_next <= Run;  
        else  
          state_next <= Idle;  
        end if;  
      when Run =>  
        if(i_done = '1') then  
          state_next <= Finish;  
        else  
          state_next <= Run;  
        end if;  
      when Finish =>  
        state_next <= Idle;  
    end case;  
  end process;
```


FSMD

- Multiplier – FSMD - FSM

```
--  
-- State Register logic  
--  
process(i_clk, i_rstb)  
begin  
    -- reset  
    if (i_rstb = '0') then  
        state <= Idle;  
    -- rising clk edge  
    elsif (rising_edge(i_clk)) then  
        state <= state_next;  
    end if;  
end process;
```

```
--  
-- output logic  
--  
process(all)  
begin  
    case state is  
        when Idle=>  
            o_complete <= '1';  
            o_calc <= '0';  
        when Run =>  
            o_complete <= '0';  
            o_calc <= '1';  
        when Finish =>  
            o_complete <= '1';  
            o_calc <= '0';  
    end case;  
end process;  
end behavioral;
```


FSMD

- Multiplier – FSMD – Data path

```
-----  
-- mult_rep_add_4bit_datapath.vhdl  
-- created 9/12/18  
-- tj  
-- rev 0  
-----  
-- Data Path for repetitive addition multiplier  
-- adds the multiplicand multiplier number of times  
-----  
-- Inputs: clk, start, multiplicand, multiplier  
-- Outputs: result, complete  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity mult_rep_add_4bit_datapath is  
  port (  
    i_clk           : in std_logic;  
    i_multiplicand  : in std_logic_vector(3 downto 0);  
    i_multiplier    : in std_logic_vector(3 downto 0);  
    i_calc          : in std_logic;  
  
    o_result        : out std_logic_vector(7 downto 0);  
    o_done          : out std_logic  
  );  
end entity;
```

```
architecture behavioral of mult_rep_add_4bit_datapath is  
  -- structural signals  
  --  
  signal multiplicand_sig:    unsigned(3 downto 0);  
  signal Multiplier_sig:     unsigned(3 downto 0);  
  signal Multiplier_sig_next: unsigned(3 downto 0);  
  signal result_sig:         unsigned(7 downto 0);  
  signal result_sig_next:    unsigned(7 downto 0);  
  signal zero_fill:          unsigned(7 downto 0);  
  
begin  
  -- datapath registers  
  --  
  process(i_clk)  
  begin  
    if (rising_edge(i_clk)) then  
      if(i_calc = '0') then  
        multiplicand_sig <= unsigned(i_multiplicand);  
        multiplier_sig <= unsigned(i_multiplier);  
        result_sig <= (others => '0'); --result_sig;  
      else  
        multiplicand_sig <= unsigned(i_multiplicand);  
        multiplier_sig <= multiplier_sig_next;  
        result_sig <= result_sig_next;  
      end if;  
    end if;  
  end process;
```

FSMD

- Multiplier – FSMD – Data path

```
--  
-- next state logic  
--  
process(all)  
begin  
    if(multiplier_sig = 0) then  
        multiplier_sig_next <= multiplier_sig;  
        result_sig_next <= result_sig;  
        o_done <= '1';  
    else  
        multiplier_sig_next <= multiplier_sig - 1;  
        result_sig_next <= ("0000" & multiplicand_sig) + result_sig;  
        o_done <= '0';  
    end if;  
end process;  
  
--  
-- output logic  
--  
o_result <= std_logic_vector(result_sig);  
end behavioral;
```

FSMD

- Multiplier – FSMD

```
-----  
-- mult_rep_add_4bit_fsmd.vhdl  
-- created 9/7/18  
-- tj  
-- rev 0  
-----  
--  
-- FSMD for repetitive addition multiplier  
-- adds the multiplicand multiplier number of times  
-----  
--  
-- Inputs: rstb, clk, start, multiplicand, multiplier  
-- Outputs: result, complete  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity mult_rep_add_4bit_fsmd is  
  port (  
    i_clk          : in std_logic;  
    i_rstb         : in std_logic;  
    i_startb       : in std_logic;  
    i_multiplicand : in std_logic_vector(3 downto 0);  
    i_multiplier   : in std_logic_vector(3 downto 0);  
  
    o_result_latched : out std_logic_vector(7 downto 0);  
    o_complete       : out std_logic  
  );  
end entity;
```

```
architecture behavioral of mult_rep_add_4bit_fsmd is  
  -- structural signals  
  --  
  signal calc:          std_logic;  
  signal done:          std_logic;  
  signal complete_sig: std_logic;  
  signal result:        std_logic_vector(7 downto 0);  
  
  -----  
  -- Component prototype  
  -----  
  COMPONENT mult_rep_add_4bit_fsm  
  PORT(  
    i_clk      : IN STD_LOGIC;  
    i_rstb     : IN STD_LOGIC;  
    i_startb   : IN STD_LOGIC;  
    i_done     : IN STD_LOGIC;  
    o_calc     : OUT STD_LOGIC;  
    o_complete : OUT STD_LOGIC  
  );  
  END COMPONENT;  
  
  COMPONENT mult_rep_add_4bit_datapath  
  port (  
    i_clk          : in std_logic;  
    i_calc         : in std_logic;  
    i_multiplicand : in std_logic_vector(3 downto 0);  
    i_multiplier   : in std_logic_vector(3 downto 0);  
  
    o_done         : out std_logic;  
    o_result       : out std_logic_vector(7 downto 0)  
  );  
  END COMPONENT;
```



FSMD

- Multiplier – FSMD


```
-----  
-- Device instantiations  
-----  
fsm: mult_rep_add_4bit_fsm  
  port map(  
    i_clk      => i_clk,  
    i_rstb    => i_rstb,  
    i_startb  => i_startb,  
    i_done    => done,  
    o_calc    => calc,  
    o_complete => complete_sig  
  );  
  
datapath: mult_rep_add_4bit_datapath  
  port map(  
    i_clk      => i_clk,  
    i_calc     => calc,  
    i_multiplicand => i_multiplicand,  
    i_multiplier  => i_multiplier,  
    o_done     => done,  
    o_result   => result  
  );  
  
--  
-- latch the result so it doesnt reset  
--  
process(i_clk)  
begin  
  if(rising_edge(i_clk)) then  
    if (complete_sig = '0') then  
      o_result_latched <= result;  
    end if;  
  end if;  
end process;  
  
--  
-- output logic  
--  
o_complete <= complete_sig;  
end behavioral;
```

FSMD


- Multiplier

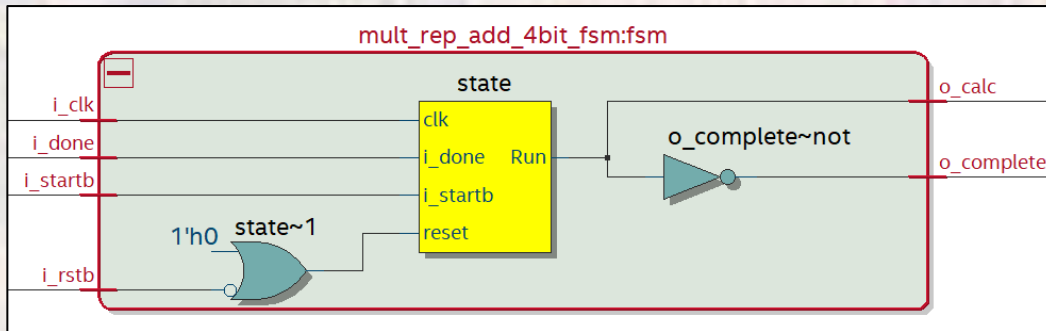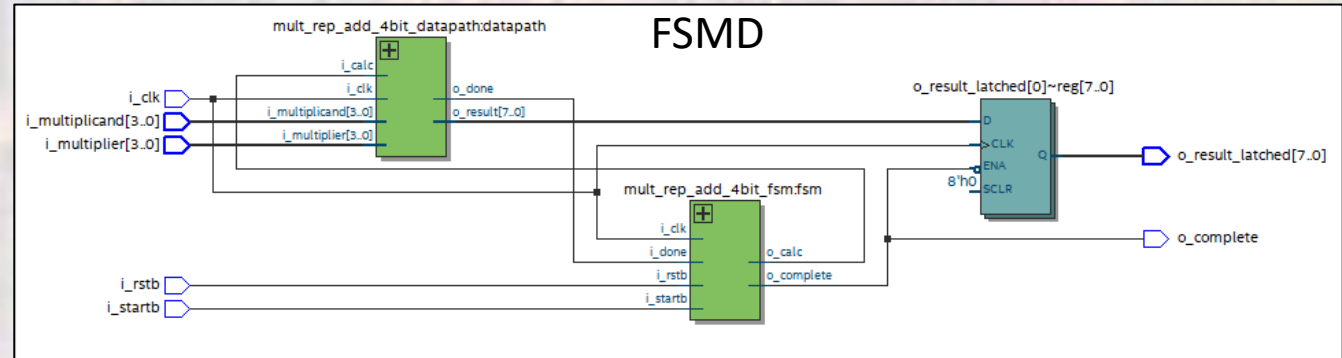

FSM

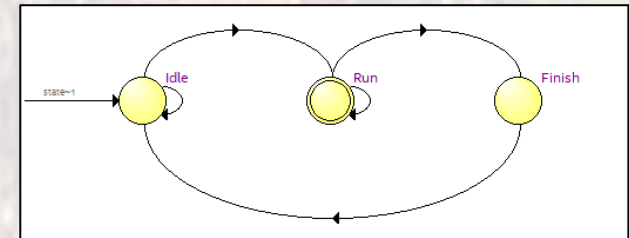


Data Path

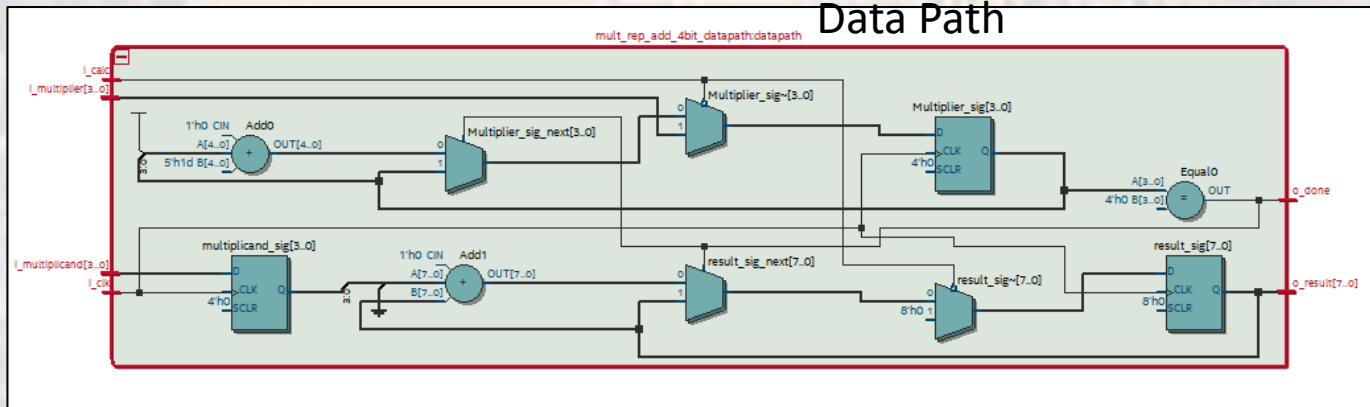

FSMD

- Multiplier - FSMD

Results and intermediate values

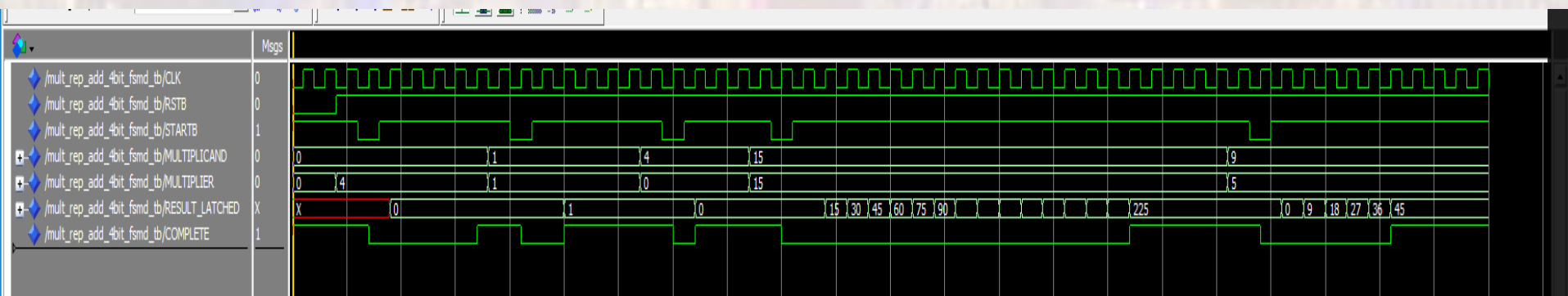

Note: Takes “multiplier” number of clock cycles
Takes a variable number of clock cycles