

EE 3921


Dr. Johnson

Homework 1

1 – Calculate the fastest possible clock frequency

20pts

 $t_{PD\ INV} = 10ps$
 $t_{PD\ NAND} = 17ps$
 $t_{CQ} = 22ps$
 $t_{setup} = 5ps$
 $t_{hold} = 2ps$



2 – Word Match, Identify the best matching number on the left for each item on the right. (no duplicates) 10pts

- 1 Analysis and Elaboration
- 2 Analyze Current File
- 3 Analysis and Synthesis
- 4 Start Fitter
- 5 Pin Planner
- 6 RTL Viewer
- 7 Signal Tap II
- 8 Model Sim
- 9 State Machine Viewer
- 10 Chip Planner

- View Schematic
- State machine schematic/logic
- Creates the physical design
- Creates logic
- Allows access to the physical design
- Checks for syntax errors
- Debug Tool
- Simulates RTL
- Creates RTL
- Assign/view pins

3) Given the VHDL code below and the indicated inputs, provide the expected signal values

30pts

a=1, b=0, c=0, d=1
 e=0110, f=1001
 g=0111, h=1110

i=
 j=
 p=
 q=
 r=
 s=
 u=
 v=
 aa=
 bb=
 cc=
 ee=
 ff=
 gg=
 hh=

```

-----
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;

-- IGNORING NAMING CONVENTION --

entity arithHW is
generic( NNN: INTEGER := 4);
port ( a,b,c,d: in STD_LOGIC;
       e,f,g,h: in STD_LOGIC_VECTOR(NNN-1 downto 0);
       i,j,k,l: out STD_LOGIC;
       m,n: out STD_LOGIC_VECTOR(NNN-1 downto 0);
       o,p,z: out STD_LOGIC_VECTOR(2*NNN-1 downto 0);

       foo: out std_logic_vector(65 downto 0)
);
end entity;

Architecture behavioral of arithHW is

    signal q,r,s,t,u,v: SIGNED((NNN-1) downto 0);
    signal aa,bb,cc,dd,ee,ff: UNSIGNED((NNN-1) downto 0);
    signal gg: SIGNED((2*NNN-1) downto 0);
    signal hh: UNSIGNED((2*NNN-1) downto 0);

begin
    q <= SIGNED(f);
    r <= SIGNED(g);
    aa <= UNSIGNED(f);
    bb <= UNSIGNED(g);

    i <= ((a or b) and c) xor d;
    j <= a and (e(1) or e(2));

    s <= q + r;
    gg <= q * r;
    u <= q / r;
    v <= q mod r;

    cc <= aa + bb;
    hh <= aa * bb;
    ee <= aa / bb;
    ff <= aa mod bb;

    p <= ('1' & h(2) & "00" & g(3 downto 1) & '1');

end architecture;
    
```

4 – Write your own behavioral VHDL code for a JK Flip-Flop
Provide code and a simulation

40pts

