

VHDL Review

Last updated 5/13/20

VHDL Basics

- VHDL
- VHSIC Hardware Description Language
- Very High Speed Integrated Circuit

VHDL Basics

- Concurrent vs Sequential Logic in HDL
 - Concurrent activities are happening all the time (in parallel)
 - Assignment: `<=`
 - with-select
 - when-else

`z <= (b or c) when (d = '0') else (e and f);` -- z can change if any value
-- changes, immediately

VHDL Basics

- Concurrent vs Sequential Logic in HDL
 - Sequential activities only happen in certain situations
 - Rising edge of clock
 - Sequential activities are identified by placing them in a “process” block
 - Process blocks are only executed when a signal in the blocks “sensitivity list” changes
 - The code in a process block is evaluated sequentially but signals are **ONLY updated at the end of the process block**
 - Process blocks themselves are concurrent activities

VHDL Basics

- Process block format

```
process (sensitivity list)
begin
    actions
end process;
```

```
label process (sensitivity list)
begin
    actions
end process;
```

VHDL Basics

• Basic VHDL file

```
-----  
--  
-- basic_vhdl.vhdl  
-- Created: 7/16/18  
-- By: johnsontimoj  
-- For: EE3921  
--  
-- File Overview ---  
--  
-- This file demonstrates basic VHDL file structure  
--  
-- File Details ---  
-----
```

Header
Information

```
-- Library inclusions  
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

Library
Inclusions

```
-- Entity definition  
entity basic_vhdl is  
  generic( N: positive := 8);  
  port(  
    i_a: in std_logic;  
    i_b: in std_logic;  
    i_c: in std_logic;  
    i_p: in std_logic_vector(N-1 downto 0);  
    i_q: in std_logic_vector(N-1 downto 0);  
    i_r: in std_logic_vector(N-1 downto 0);  
    o_x: out std_logic;  
    o_y: out std_logic_vector(N-1 downto 0)  
  );  
end entity;
```

Entity

```
-- Behavioral Architecture Definition  
architecture behavioral of basic_vhdl is  
  signal e: std_logic;  
  signal f: std_logic;  
  signal g: std_logic;  
  signal t: unsigned(N-1 downto 0);  
  signal u: signed(N-1 downto 0);
```

Architecture

Begin

```
e <= i_a and i_b;  
f <= i_c nor i_a;  
g <= e xor f;  
o_x <= g and not i_p(3);
```

Internal
signals

```
t <= unsigned(i_p xor i_q);  
u <= signed("11" & i_a & t(4) & i_r(3 downto 2) & i_a & g);  
o_y <= (7 => '1', 4 => u(5), 1 => i_a, 5 => t(4), others => '1'); -- array assignment
```

Architectural
Definition

```
end architecture;
```


Generic

Ports

VHDL Basics

- Basic VHDL file
 
```
e <= i_a and i_b;  
f <= i_c nor i_a;  
g <= e xor f;  
o_x <= g and not i_p(3);  
  
t <= unsigned(i_p xor i_q);  
u <= signed("11" & i_a & t(4) & i_r(3 downto 2) & i_a & g);  
o_y <= (7 => '1', 4 => u(5), 1 => i_a, 5 => t(4), others => '1');
```



```
port(  
  i_a: in    std_logic;  
  i_b: in    std_logic;  
  i_c: in    std_logic;  
  i_p: in    std_logic_vector(N-1 downto 0);  
  i_q: in    std_logic_vector(N-1 downto 0);  
  i_r: in    std_logic_vector(N-1 downto 0);  
  o_x: out   std_logic;  
  o_y: out   std_logic_vector(N-1 downto 0)  
);
```

VHDL Basics

- Basic VHDL – Structural file


- Full Adder

```
-----  
--  
-- full_adder.vhdl  
--  
-- by: johnsontimoj  
--  
-- created: 7/5/2017  
--  
-- version: 0.0  
--  
-----  
-----  
--  
-- 1 bit full adder  
--  
-- inputs: a, b, cin  
--  
-- outputs: s, cout  
--  
-----  
  
library IEEE;  
use ieee.std_logic_1164.all;
```

```
entity full_adder is  
    port( i_a:    in std_logic;  
          i_b:    in std_logic;  
          i_cin:  in std_logic;  
          o_s:    out std_logic;  
          o_cout: out std_logic  
    );  
end entity;  
  
architecture behavioral of full_adder is  
  
    signal p: std_logic;  
    signal g: std_logic;  
  
begin  
  
    p <= i_a xor i_b;  
    g <= i_a and i_b;  
  
    o_s <= p xor i_cin;  
    o_cout <= g or (p and i_cin);  
  
end;
```


VHDL Basics

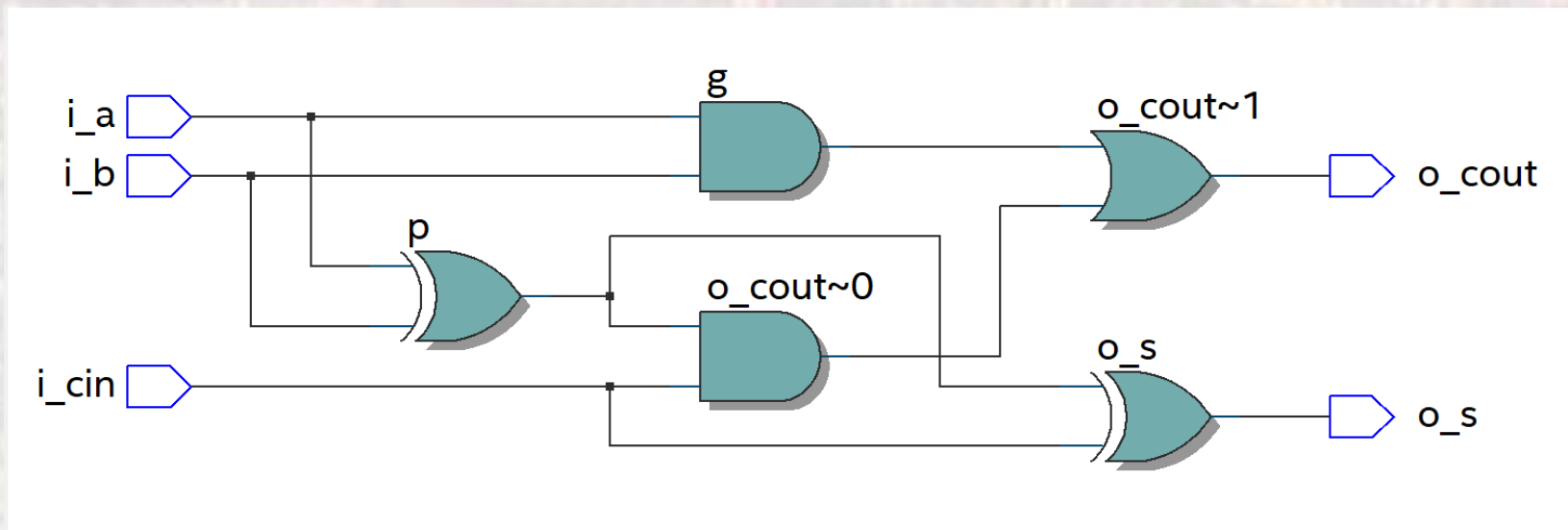- Basic VHDL – Structural file
- Full Adder



VHDL Basics

• Basic VHDL – Structural file

```
-----  
--  
-- adder_4bit.vhdl  
--  
-- by: tj  
--  
-- created: 7/5/2017  
--  
-- version: 0.0  
--  
-----  
--  
-- 4 bit adder to show cell instantiation  
--  
-- inputs: - a, b, cin  
--  
-- outputs: - sum, cout  
--  
-----  
library IEEE;  
use ieee.std_logic_1164.all;  
  
entity adder_4bit is  
    port( i_A:      in std_logic_vector(3 downto 0);  
          i_B:      in std_logic_vector(3 downto 0);  
          i_CIN:    in std_logic;  
          o_SUM:    out std_logic_vector(3 downto 0);  
          o_COUT:   out std_logic  
    );  
end entity;
```

Top Level
Entity

```
architecture structural of adder_4bit is
```

```
-----  
-- 1 bit full adder prototype  
-----  
component full_adder is  
    port( i_a:      in std_logic;  
          i_b:      in std_logic;  
          i_cin:    in std_logic;  
          o_s:      out std_logic;  
          o_cout:   out std_logic  
    );  
end component;
```

Component
Prototype

```
-----  
-- intermediate carries mapped to co  
-- with 1st stage Cout mapped to co(0) and 4th stage cout mapped to co(3)  
-----  
signal co: STD_LOGIC_VECTOR(3 downto 0); -- intermediate carries  
-- no vector interpretation
```


```
begin  
  
    add_0: full_adder port map( i_a => i_A(0),  
                                i_b => i_B(0),  
                                i_cin => i_CIN,  
                                o_s => o_SUM(0),  
                                o_cout => co(0)  
    );  
  
    add_1: full_adder port map( i_a => i_A(1),  
                                i_b => i_B(1),  
                                i_cin => co(0),  
                                o_s => o_SUM(1),  
                                o_cout => co(1)  
    );  
  
    add_2: full_adder port map( i_a => i_A(2),  
                                i_b => i_B(2),  
                                i_cin => co(1),  
                                o_s => o_SUM(2),  
                                o_cout => co(2)  
    );  
  
    add_3: full_adder port map( i_a => i_A(3),  
                                i_b => i_B(3),  
                                i_cin => co(2),  
                                o_s => o_SUM(3),  
                                o_cout => co(3)  
    );  
  
    o_COUT <= co(3);  
  
end architecture;
```

Instantiations

Explicit
Port
Mapping

VHDL Basics

- Basic VHDL – Structural file

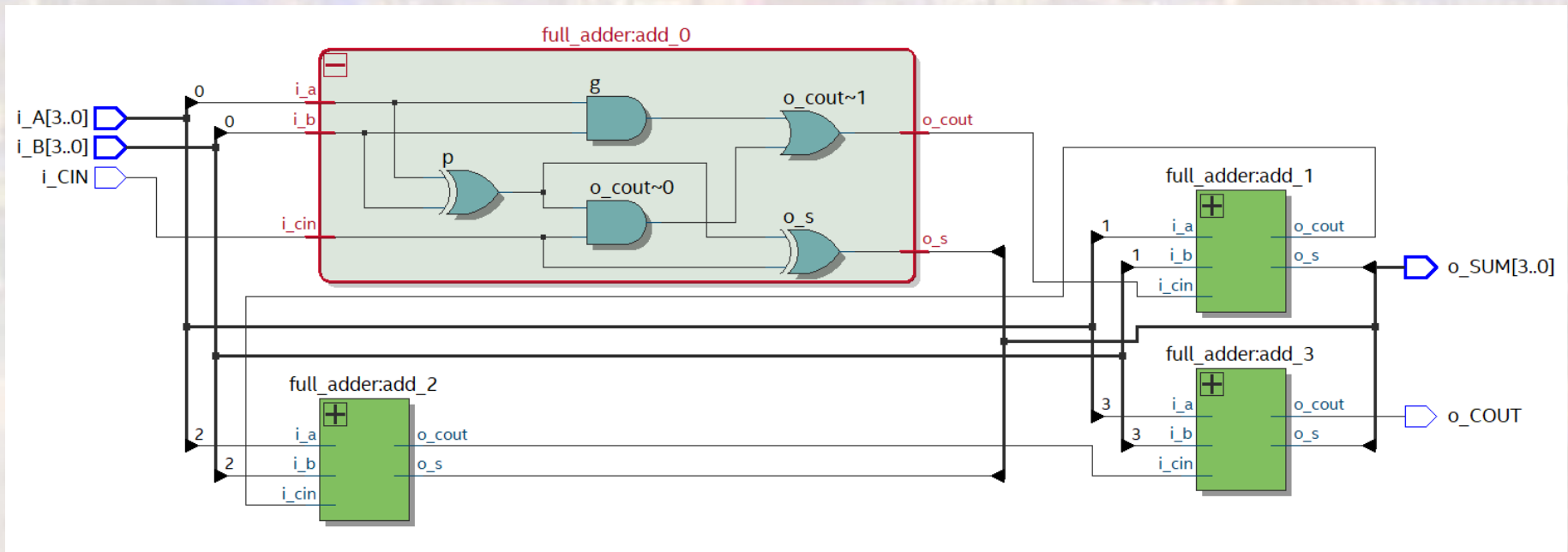

VHDL Basics

- VHDL – Selection

- `with-select`

- Choose a value when a certain situation exists

```
with decision_signal select result_signal <=      -- exhaustive list
result_value when decision_value,
result_value when decision_value,
result_value when decision_value,
result_value when decision_value;
```

Limitation: Only one result signal

VHDL Basics

- VHDL – Selection
 - with-select

Exhaustive List

```
with inA select outA <= "0100" when "01",  
                        "0010" when "10",  
                        "0001" when "11",  
                        "1010" when "00",  
                        "0000" when others;
```

Partial List

```
with inA select outA <= "0100" when "01",  
                        "0010" when "10",  
                        "0000" when others;
```

Partially Common Result

```
with inA select outA <= "0100" when "01",  
                        "0010" when "10",  
                        "0001" when ("11" or "00"),  
                        "0000" when others;
```

Complex Selection

```
with (inA and inB) select outA <= "0100" when "01",  
                                  "0010" when "10",  
                                  "0001" when "00",  
                                  "0000" when others;
```

VHDL Basics

- VHDL – Selection
 - with-select

```
-----  
--  
-- with_select.vhdl  
--  
-- created 7/5/2018  
-- tj  
--  
-- rev 0  
-----  
--  
-- with-select example  
--  
-----  
--  
-- Inputs: C  
-- Outputs: V  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity with_select is  
  port (  
    i_C:  in std_logic_vector(3 downto 0);  
    o_V:  out std_logic_vector(3 downto 0)  
  );  
end entity;
```

architecture behavioral of with_select is

begin

-- Code to show mux


```
  with i_C select o_V <=  
    "0001" when "0000",  
    "0010" when "0001",  
    "0011" when "0010",  
    "0100" when "0011",  
    "0101" when "0100",  
    "0110" when "0101",  
    "0111" when "0110",  
    "1000" when "0111",  
    "1001" when "1000",  
    "0000" when others;
```

end behavioral;

VHDL Basics

- VHDL – Selection
 - with-select

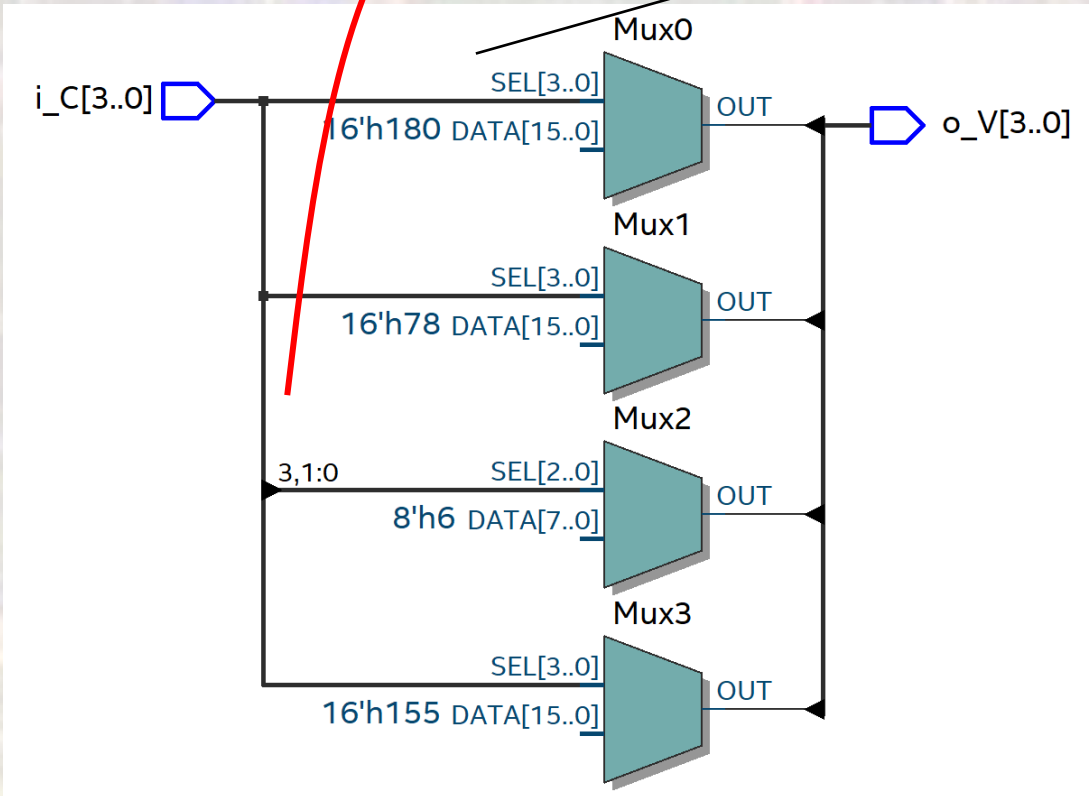Mux3 0000 0001 0101 0101
 0000 0000 0110 0110
 0000 0000 0111 1000
 Mux0 0000 0001 1000 0000



i_C = 1111	0000 0001 0101 0101	o_V
i_C = 0111	0000 0000 0110 0110	
i_C = 0111	0000 0000 0111 1000	
i_C = 0000	0000 0001 1000 0000	

"0111" when "0110",
 "1000" when "0111",
 "....." when "....."

VHDL Basics

- VHDL – Selection
 - `when-else`
 - Choose a value when a certain situation exists

```
result_signal <= result_value when decision_signal = decision_value else  
result_value when decision_signal = decision_value else  
result_value when decision_signal = decision_value else  
result_value;
```

Limitation: Only one result signal

VHDL Basics

- VHDL – Selection
 - when-else

Exhaustive List

```
outA <= "1000" when inA = "00" else  
       "0100" when inA = "01" else  
       "0010" when inA = "10" else  
       "0010" when inA = "11" else  
       "0001";
```

Partial List

```
outA <= "1000" when inA = "00" else  
       "0100" when inA = "01" else  
       "0001";
```

Partially Common Result

```
outA <= "1000" when inA = "00" else  
       "0100" when inA = "01" else  
       "0010" when inA = ("10" or "11") else  
       "0001";
```

Complex Selection

```
outA <= "1000" when (inA or inB) = "00" else  
       "0100" when (inA or inB) = "01" else  
       "0010" when (inA or inB) = "10" else  
       "0001";
```

VHDL Basics

- VHDL – Selection
 - when-else

```
-----  
--  
-- when_else.vhdl  
--  
-- created 7/5/2018  
-- tj  
--  
-- rev 0  
-----  
--  
-- when-else example  
--  
-----  
--  
-- Inputs: C  
-- Outputs: V  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity when_else is  
    port (  
        i_C:  in std_logic_vector(3 downto 0);  
        o_V:  out std_logic_vector(3 downto 0)  
    );  
end entity;
```

architecture behavioral of when_else is


begin

```
    o_V <=  "0001" when i_C = "0000" else  
           "0010" when i_C = "0001" else  
           "0011" when i_C = "0010" else  
           "0100" when i_C = "0011" else  
           "0101" when i_C = "0100" else  
           "0110" when i_C = "0101" else  
           "0111" when i_C = "0110" else  
           "1000" when i_C = "0111" else  
           "1001" when i_C = "1000" else  
           "0000";
```

end behavioral;

VHDL Basics

- VHDL – Selection
 - when-else

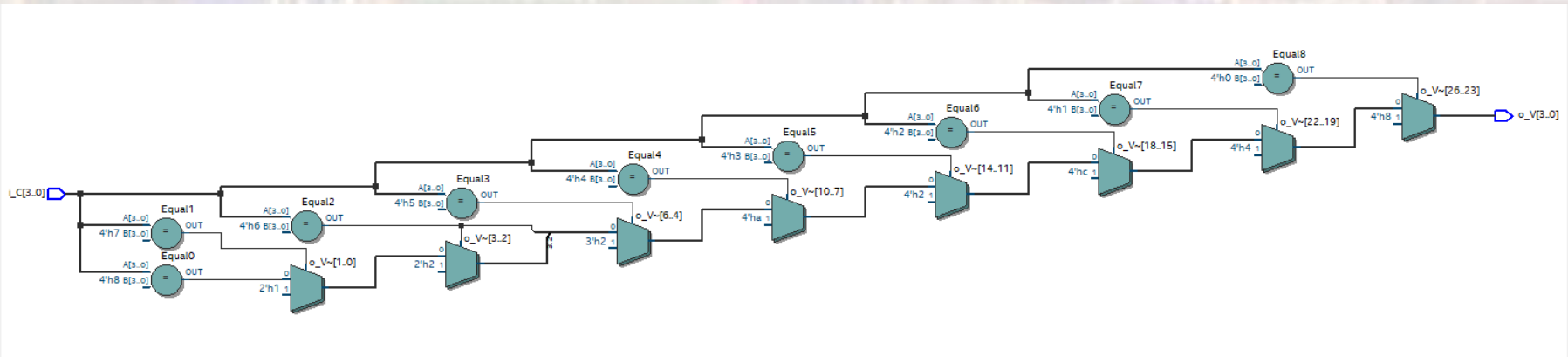

VHDL Basics

- VHDL – Selection
 - if-else
 - Choose a value when a certain situation exists

```
if (decision_signal = decision_value_X) then
    result_signal_1 <= result_value_1;
    result_signal_2 <= result_value_2;
    result_signal_3 <= result_value_3;
elsif (decision_signal = decision_value_Y) then
    result_signal_1 <= result_value_1a;
    result_signal_2 <= result_value_2b;
    result_signal_3 <= result_value_3c;
else
    result_signal_1 <= result_value_a;
    result_signal_2 <= result_value_b;
    result_signal_3 <= result_value_c;
end if;
```

Typically use the same decision signal
Exception – creating registers (Flip-Flops)

Limitation: Must be used in a process

VHDL Basics

- VHDL – Selection
 - if-else

Exhaustive List

```
if(inA = "00") then
  outW <= "1000";
elsif(inA = "01") then
  outW <= "0100";
elsif(inA = "10") then
  outW <= "0010";
elsif(inA = "11") then
  outW <= "0011";
else
  outW <= "0000";
end if;
```

Partial List

```
if(inA = "00") then
  outX <= "1000";
elsif(inA = "01") then
  outX <= "0100";
else
  outX <= "0000";
end if;
```

Partially Common Result

```
if(inA = "00") then
  outY <= "1000";
elsif(inA = "01") then
  outY <= "0100";
elsif((inA = "10") or (inA = "11")) then
  outY <= "0110";
else
  outX <= "0000";
end if;
```

Complex Selection

```
if((inA or inB) = "00") then
  outZ <= "1000";
elsif((inA or inB) = "01") then
  outZ <= "0100";
else
  outZ <= "0000";
end if;
```

VHDL Basics

- VHDL – Selection
 - **if-else**


```
-----  
--  
-- if_else.vhdl  
--  
-- created 7/5/2018  
-- tj  
--  
-- rev 0  
-----  
--  
-- if-else example  
--  
-----  
--  
-- Inputs: C  
-- Outputs: V  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity if_else is  
    port (  
        i_C:  in std_logic_vector(3 downto 0);  
        o_V:  out std_logic_vector(3 downto 0)  
    );  
end entity;
```

architecture behavioral of if_else is

```
begin  
    process(i_C)  
        begin  
            if(i_C = "0000") then  
                o_V <= "0001";  
            elsif(i_C = "0001") then  
                o_V <= "0010";  
            elsif(i_C = "0010") then  
                o_V <= "0011";  
            elsif(i_C = "0011") then  
                o_V <= "0100";  
            elsif(i_C = "0100") then  
                o_V <= "0101";  
            elsif(i_C = "0101") then  
                o_V <= "0110";  
            elsif(i_C = "0110") then  
                o_V <= "0111";  
            elsif(i_C = "0111") then  
                o_V <= "1000";  
            elsif(i_C = "1000") then  
                o_V <= "1001";  
            else  
                o_V <= "0000";  
            end if;  
        end process;  
    end behavioral;
```

VHDL Basics

- VHDL – Selection
 - if-else

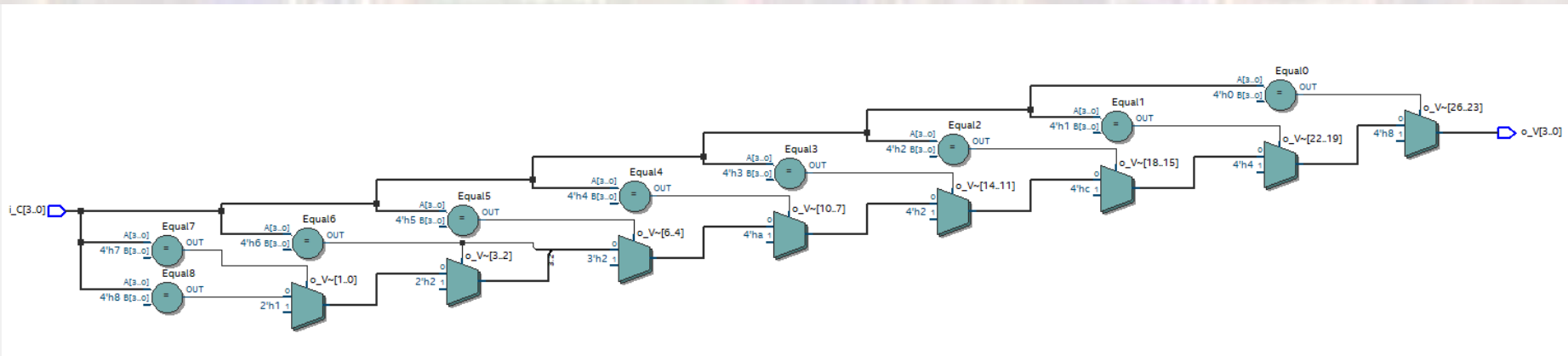

VHDL Basics

- VHDL – Selection

- **case**

- Choose a value when a certain situation exists

```
case decision_signal is
  when decision_value_X => result_signal_1 <= result_value_1;
                           result_signal_2 <= result_value_2;
                           result_signal_3 <= result_value_3;
  when decision_value_Y => result_signal_1 <= result_value_1a;
                           result_signal_2 <= result_value_2b;
                           result_signal_3 <= result_value_3c;
  when others =>          result_signal_1 <= result_value_a;
                           result_signal_2 <= result_value_b;
                           result_signal_3 <= result_value_c;
end case;
```

Limitations: Must be used in a process
Only one decision signal

VHDL Basics

- VHDL – Selection
 - case

Exhaustive List

```
case inA is
  when "00" => outW <= "1000";
  when "01" => outW <= "0100";
  when "10" => outW <= "0010";
  when "11" => outW <= "0011";
  when others => outW <= "0000";
end case;
```

Partial List

```
case inA is
  when "00" => outX <= "1000";
  when "01" => outX <= "0100";
  when others => outX <= "0000";
end case;
```

Partially Common Result

```
case inA is
  when "00" => outY <= "1000";
  when "01" => outY <= "0100";
  when ("10" or "11") => outY <= "0010";
  when others => outY <= "0000";
end case;
```

Complex Selection

```
case (inA or inB) is
  when "00" => outW <= "1000";
  when "01" => outW <= "0100";
  when "10" => outW <= "0010";
  when "11" => outW <= "0011";
  when others => outW <= "0000";
end case;
```

VHDL Basics

- VHDL – Selection
 - case

```
-----  
--  
-- case_ex.vhdl  
--  
-- created 7/5/2018  
-- tj  
--  
-- rev 0  
-----  
--  
-- case example  
--  
-----  
--  
-- Inputs: C  
-- Outputs: V  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity case_ex is  
    port (  
        i_C:  in std_logic_vector(3 downto 0);  
        o_V:  out std_logic_vector(3 downto 0)  
    );  
end entity;
```

architecture behavioral of case_ex is


```
begin  
    process(all)  
    begin  
        case i_C is  
            when "0000" => o_V <= "0001";  
            when "0001" => o_V <= "0010";  
            when "0010" => o_V <= "0011";  
            when "0011" => o_V <= "0100";  
            when "0100" => o_V <= "0101";  
            when "0101" => o_V <= "0110";  
            when "0110" => o_V <= "0111";  
            when "0111" => o_V <= "1000";  
            when "1000" => o_V <= "1001";  
            when others => o_V <= "0000";  
        end case;  
    end process;  
end behavioral;
```

VHDL Basics

- VHDL – Selection

- case

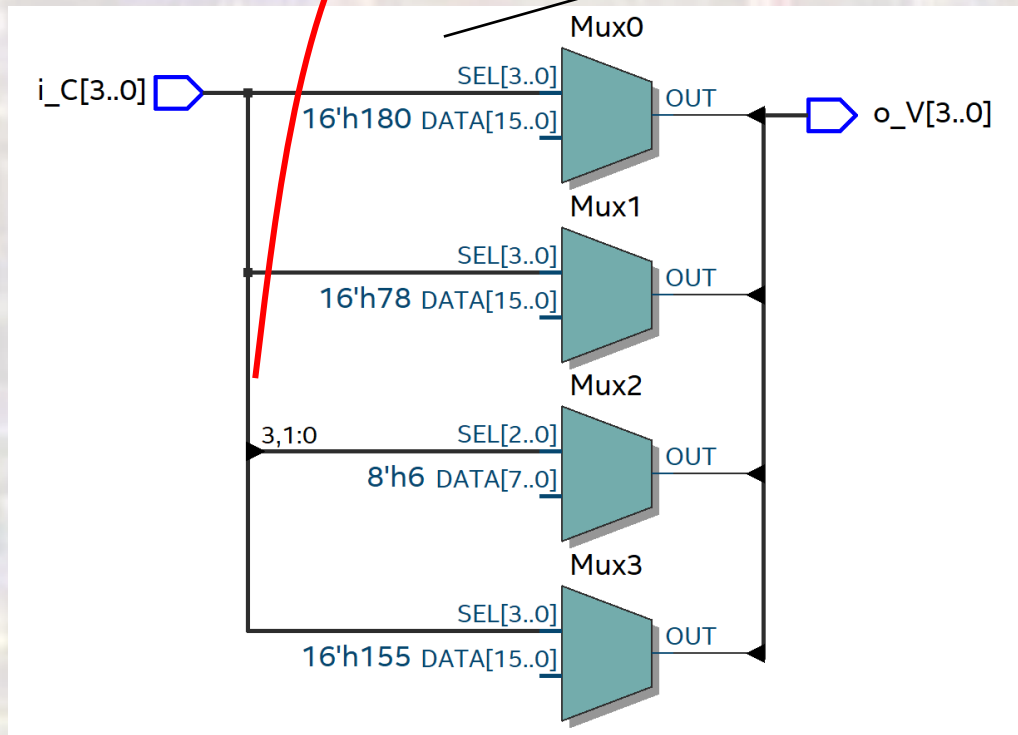Mux3 0000 0001 0101 0101
 0000 0000 0110 0110
 0000 0000 0111 1000
 Mux0 0000 0001 1000 0000



i_C = 1111	0000 0001 0101 0101	} o_V
i_C = 0111	0000 0000 0110 0110	
	0000 0000 0111 1000	
i_C = 0000	0000 0001 1000 0000	

when "0110" => o_V <= "0111";
 when "0111" => o_V <= "1000";

VHDL Basics

- Registers (Flip-Flops) are recognized by a pre-defined VHDL template

```
process (clock signal)
begin
  if(clock edge detection) then
    actions
  end if;
end process;
```

note:

- here the else is not required because the synthesizer recognizes the edge detection
- you can include an else for clarity

```
process (clk)
begin
  if(clk'event and clk = 1) then
    q <= d;
  end if;
end process;
```

```
process (clk)
begin
  if(rising_edge(clk)) then
    q <= d;
  end if;
end process;
```

2008 release

VHDL Basics


- D-FF w/ asynchronous rstb

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity dff_a is  
  port(  
    i_clk:  in std_logic;  
    i_rstb: in std_logic;  
    i_D :   in std_logic;  
  
    o_Q :  out std_logic  
  );  
end entity;
```

```
architecture behavioral of dff_a is  
begin  
  process (i_clk, i_rstb)  
  begin  
    if (i_rstb = '0') then  
      o_Q <= '0';  
    elsif (rising_edge(i_clk)) then  
      o_Q <= i_D;  
    end if;  
  end process;  
end architecture;
```

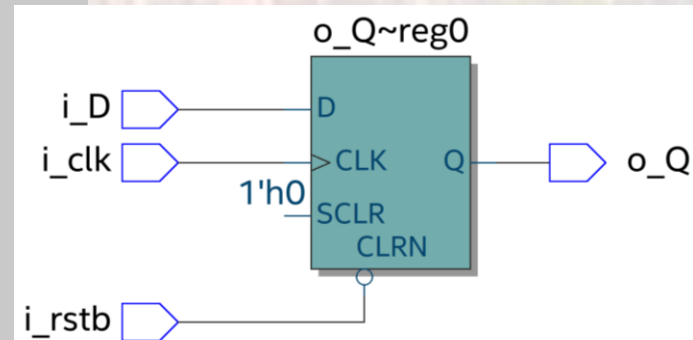Note addition
of rstb to the
sensitivity list



Most of our designs will use DFFs with an asynchronous reset
Data Path designs will use DFFs with no reset


VHDL Basics

- N bit register

```
entity reg_n_bit is
  generic(
    N: integer := 8
  );
  port (
    i_D :    in std_logic_vector((N - 1) downto 0);
    i_clk :  in std_logic;
    i_rstb : in std_logic;

    o_Q :    out std_logic_vector((N - 1) downto 0)
  );
end entity;

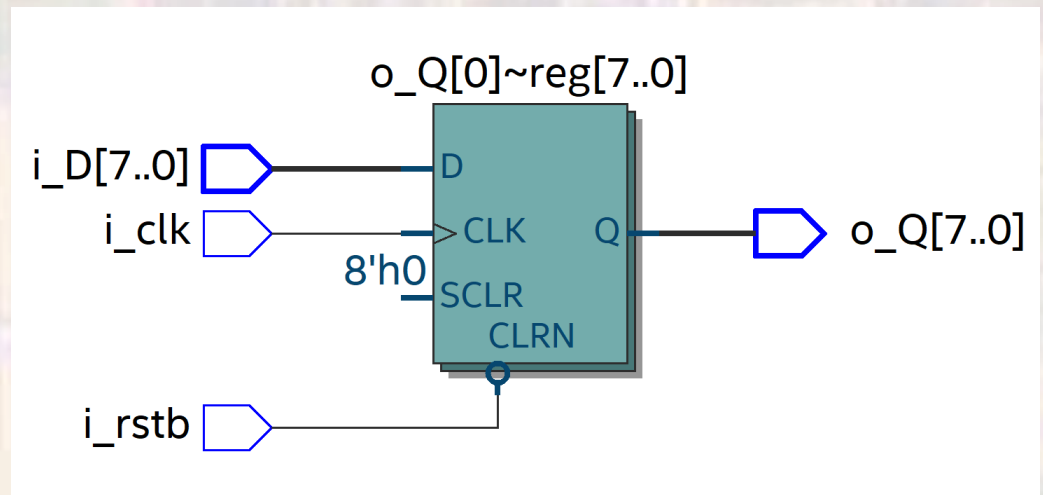architecture behavioral of reg_n_bit is
begin
  process(i_clk, i_rstb)
  begin
    if (i_rstb = '0') then
      o_Q <= (others => '0');
    elsif (rising_edge(i_clk)) then
      o_Q <= i_D;
    end if;
  end process;
end behavioral;
```



VHDL Basics

- Warning – Warning – Warning
 - Most (maybe all) of the times you do not complete an **if-else** with an **else** a latch will be created
 - All cases must be covered
- We do not want latches - EVER

