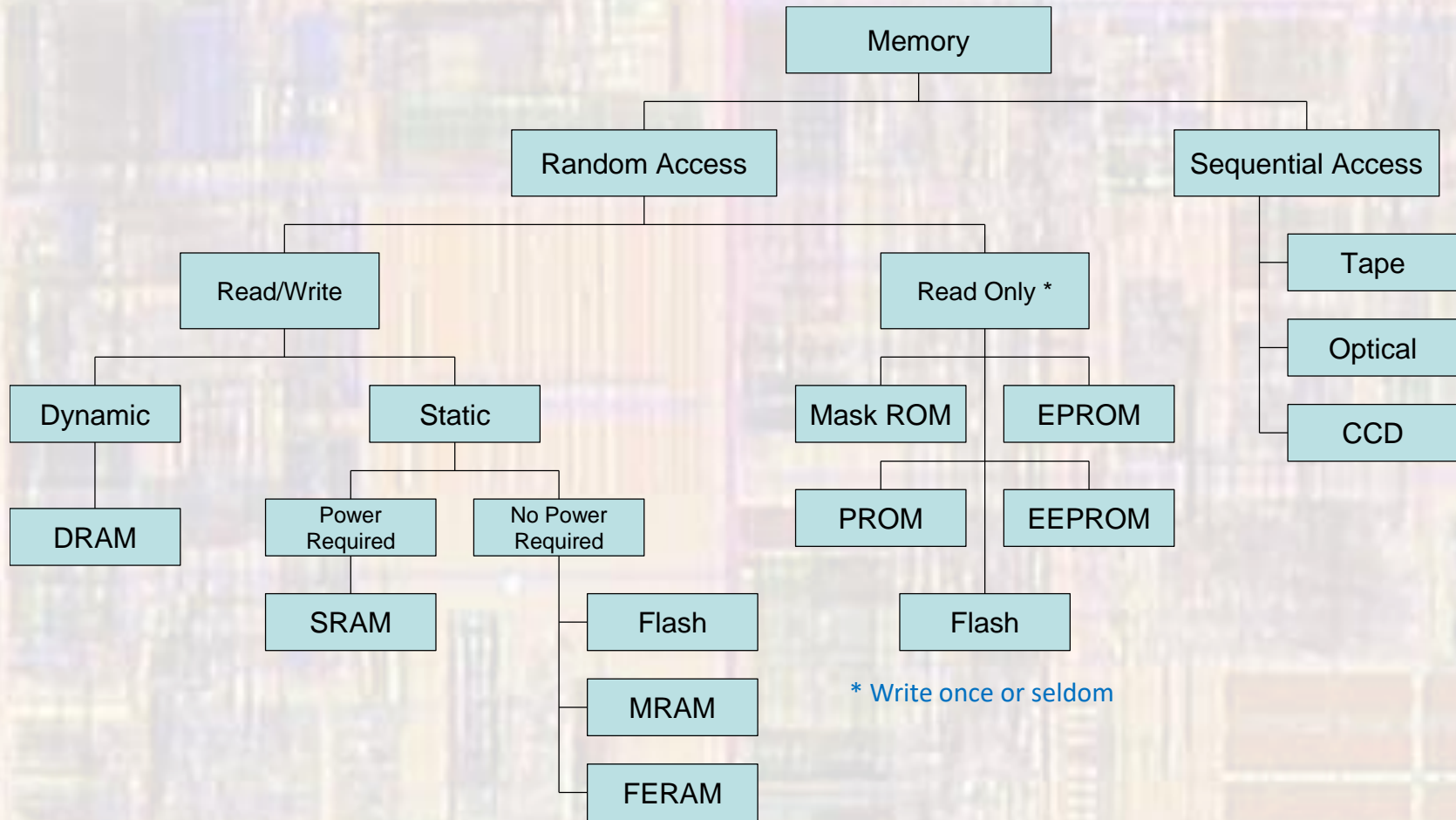


SDRAM

Last updated 3/1/21


Memory - SDRAM

- Memory Taxonomy




Memory - SDRAM

- SDRAM – Synchronous Dynamic Random Access Memory
 - Memory cell (1 bit) is based on capacitor charge storage
 - Bit value decays over time
 - must be recharged – called a refresh cycle
 - Standard SDRAM transfers 1 word each array access
 - DDR – double data rate – transfers 2 words each array access
 - DDR2, DDR3, DDR4 – transfer 4,8,16 words each array access
 - Medium speed
 - Highest density
 - Used as main memory

 

Memory - SDRAM



- SDRAM – Cell

 

Src: IEDM

Memory - SDRAM

  - SDRAM — Synchronous Dynamic Random Access Memory
 - Write
 - All Word lines low
 - Read Enable (RE) disabled (low)
 - Place $\overline{B0}$, $\overline{B1}$, $\overline{B2}$, $\overline{B3}$ on inputs
 - Pull write enable bar (\overline{WE}) low
 - Strobe the desired word line high
 - Bit lines write to the bit cell capacitors




Memory - SDRAM

- SDRAM — Synchronous Dynamic Random Access Memory

- Read

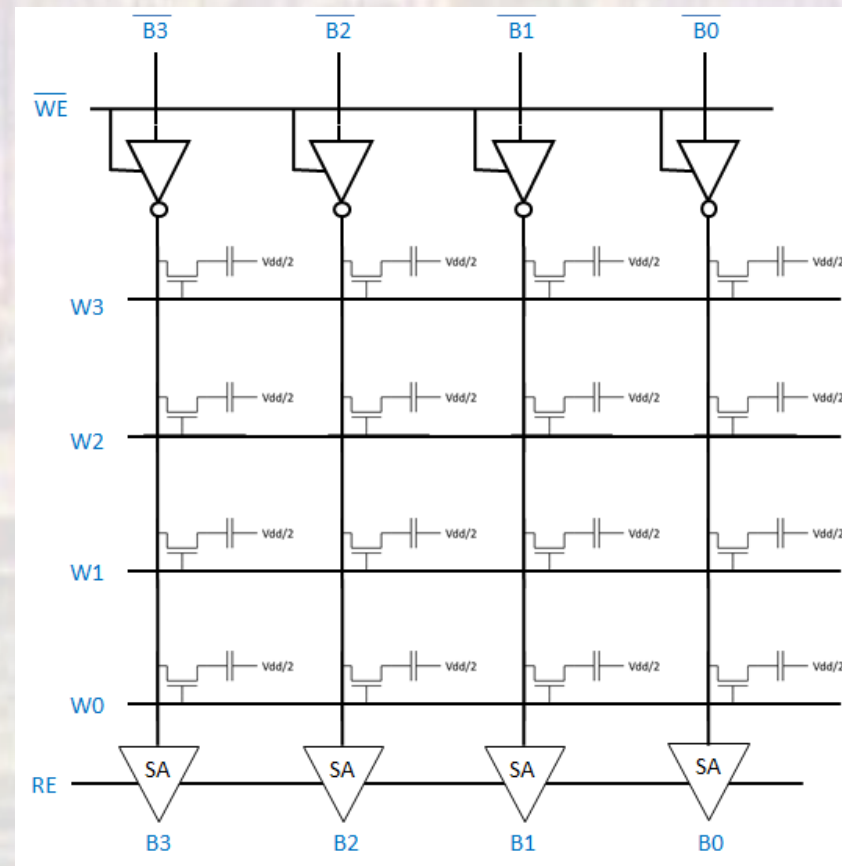- All Word lines low
- Write enable bar (\overline{WE}) high
 - inverters tristated
- Read Enable (RE) high
- Strobe the desired word line high
- Sense amplifiers read the value of the capacitors
- The read process is destructive !
 - WHY?



Memory - SDRAM

- SDRAM – Dynamics

- $C_{\text{cell}} \sim 1/10 C_{\text{bitline}}$


- Charge redistribution \rightarrow small voltage changes

- Cell charge = $Q_{\text{cell}} = +/- (V_{\text{dd}}/2 * C_{\text{cell}})$

- Bitline charge = $Q_{\text{bitline}} = V_{\text{dd}}/2 * C_{\text{bitline}}$

- Assuming V_{bitline} precharged to $V_{\text{dd}}/2$

 
- $\Delta V = \frac{V_{\text{dd}}}{2} \times \left(\frac{C_{\text{cell}}}{C_{\text{cell}} + C_{\text{bitline}}} \right) = 0.045V_{\text{dd}} = 122\text{mV @ } 2.7\text{V}$



Memory - SDRAM


- SDRAM – Dynamics

- Use a differential amplifier for sensing
 - But what is the second input?
 - Break the array into pieces
 - Precharge all bitlines
 - Compare a bitline from selected wordline to one from a non-selected wordline
- Open Bitline array
 - Control the signal swing by size of bitline segments
 - Compare precharged non-word selected bitlines with small swing word selected bitlines
- Alternate configurations include folded and twisted
 - Less dense but offer better noise characteristics
 - Trade off size of segments for # of sense amps

 


Memory - SDRAM

- SDRAM — Sense amplifier
 - WRITE

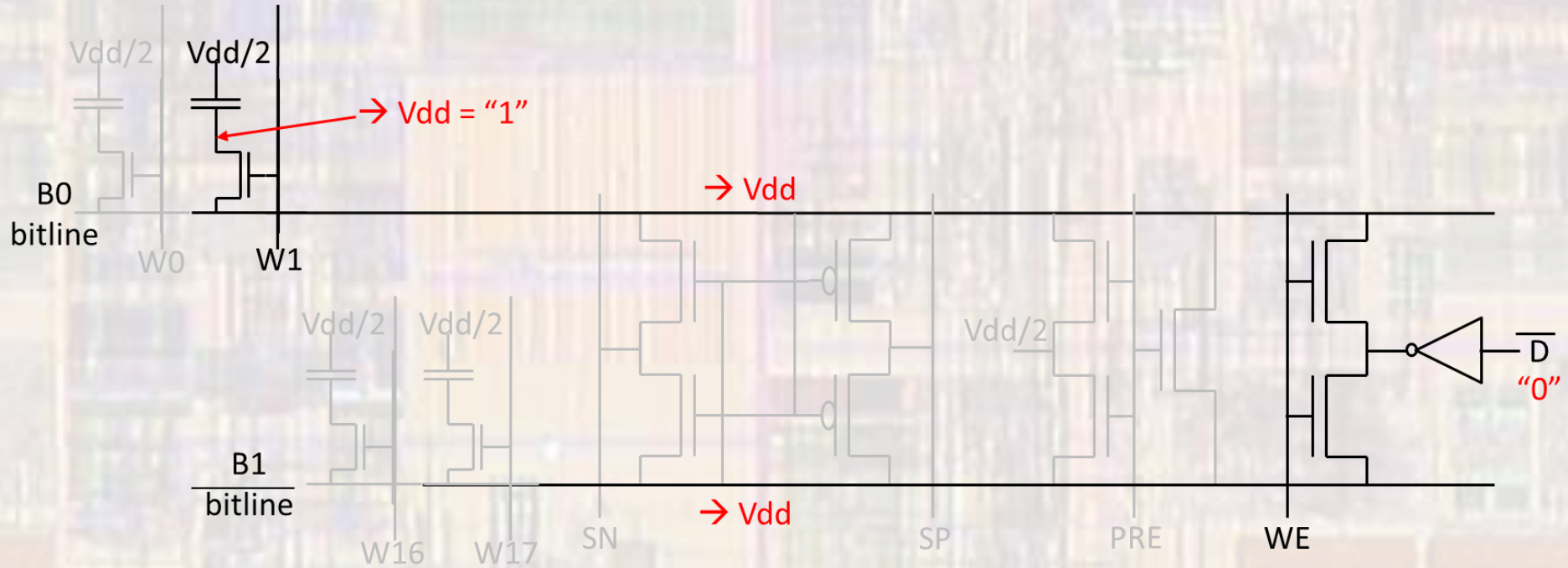


Memory - SDRAM

- SDRAM — Sense amplifier

 

Memory - SDRAM

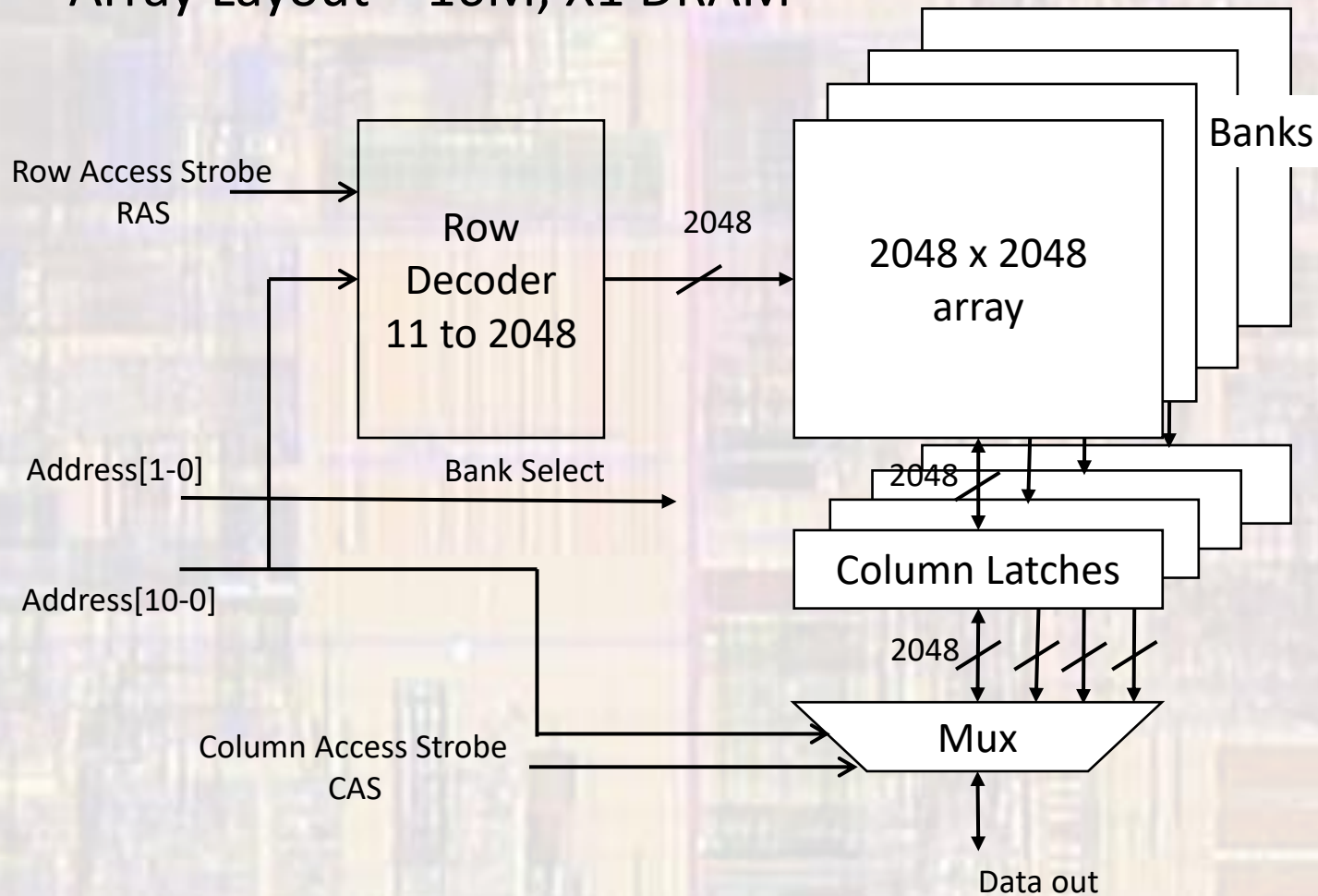- SDRAM - Banks
 - Array Layout – 16M, X1 DRAM



Memory - SDRAM


- SDRAM – Pipelining
 - Allow next read/write process to start while current r/w is in process
 - With proper timing you can achieve 100% throughput on
 - Access to a new column on an open row
 - Opening a new row on an alternate bank
- More to come

Memory - SDRAM

- SDRAM – Strobe Based Data Bus
 - Very high operating speeds lead to concerns about
 - Trace lengths, transmission line effects, clock skew, ...
 - Add a strobe signal for every output beat (DQS)
 - On reads
 - Strobe is generated by the SDRAM edge aligned with the data
 - MMU offsets the strobe by 90 degrees and uses it to capture the data
 - On writes
 - Strobe is generated by the MMU and offset by 90 degrees wrt data
 - SDRAM uses the strobe to capture the write data
 - Strobes include a preamble, postamble and write leveling

Memory - SDRAM

 - SDRAM – On Die Termination (ODT)
 - Very high operating speeds lead to concerns about
 - Trace lengths, transmission line effects, clock skew, ...
 - Place programmable resistors on die to terminate the transmission lines for critical signals, DQ, DQS, CLK



Memory - SDRAM

- SDRAM – Write Leveling

