

# Wireless Charging

Last updated 5/4/20



# Wireless Charging

- Transformer

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

$$\frac{V_s}{V_p} = \frac{I_p}{I_s}$$




$$\frac{I_s}{I_p} = \frac{N_p}{N_s}$$

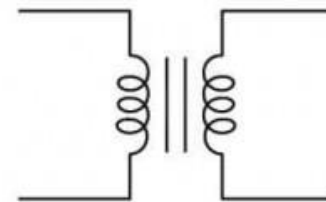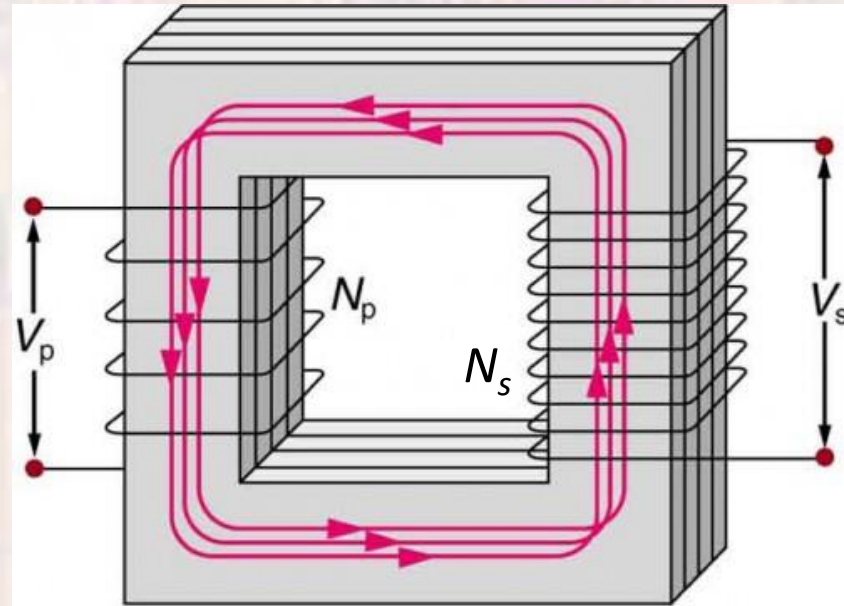

Transformer symbol


# Wireless Charging

- Power Supply

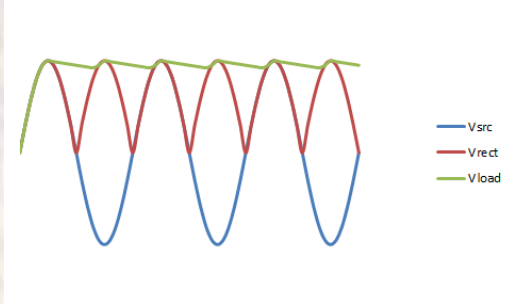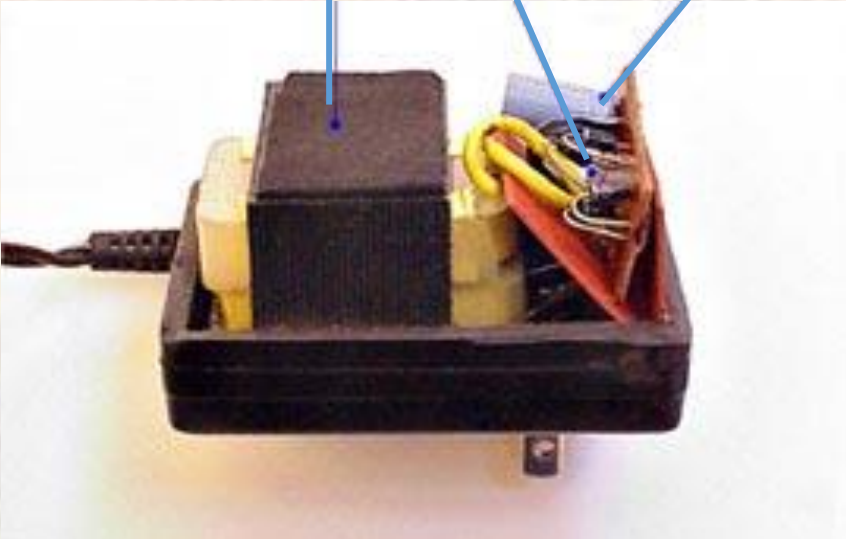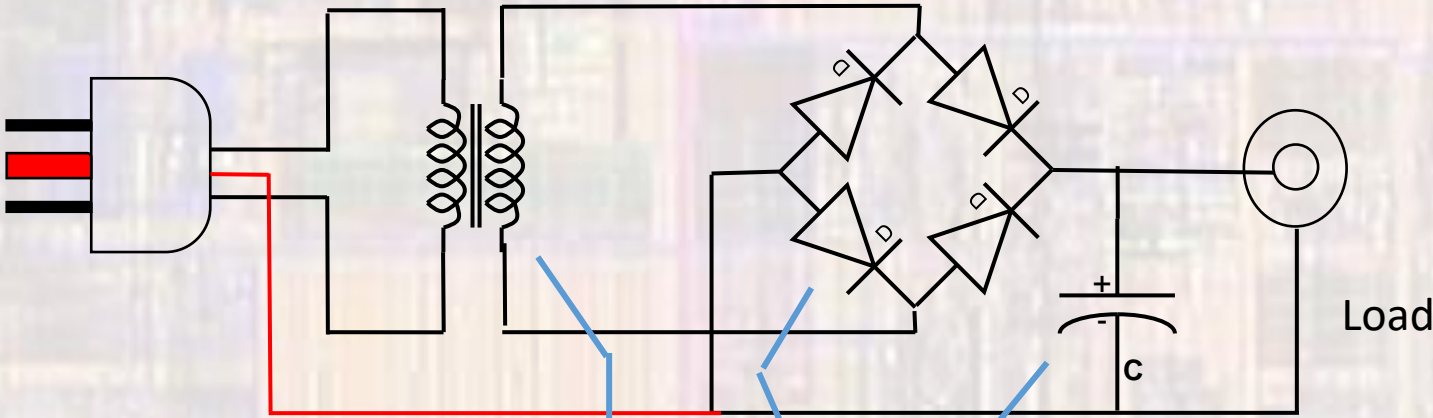


# Wireless Charging

- Power Supply
  - Regulated supply

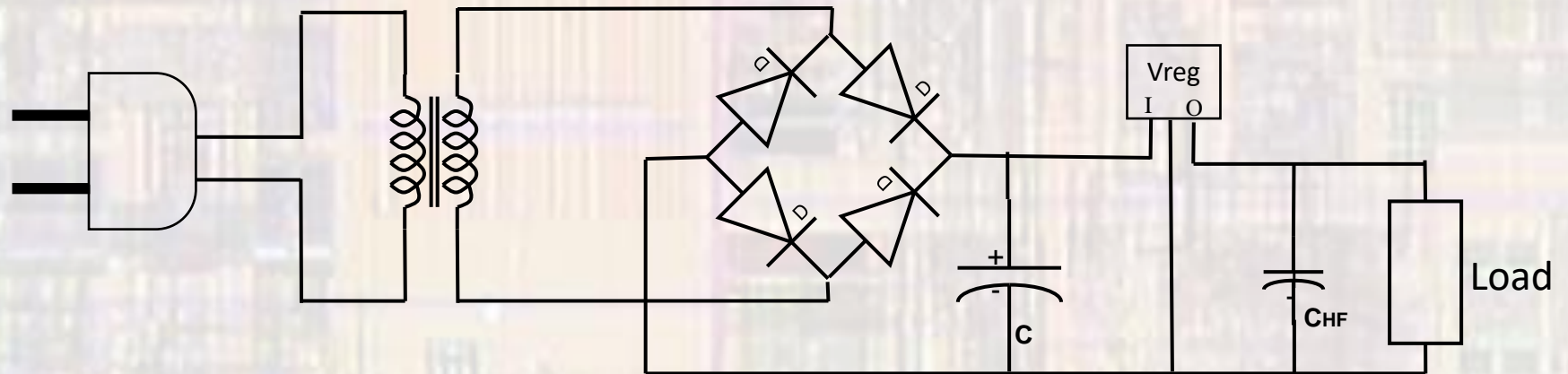

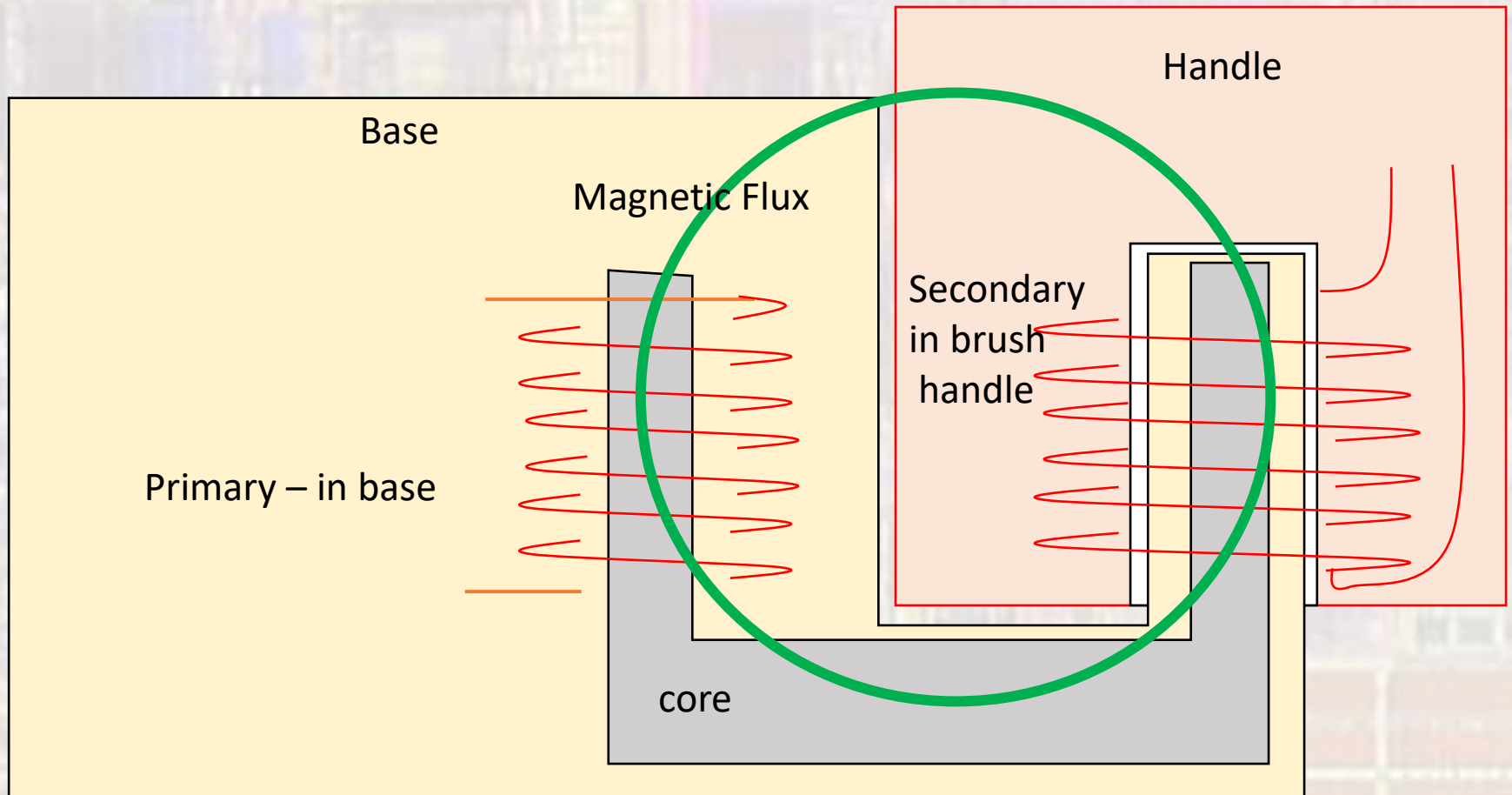
# Wireless Charging

- Toothbrush
  - Handle placed on pedestal




# Wireless Charging

- Toothbrush

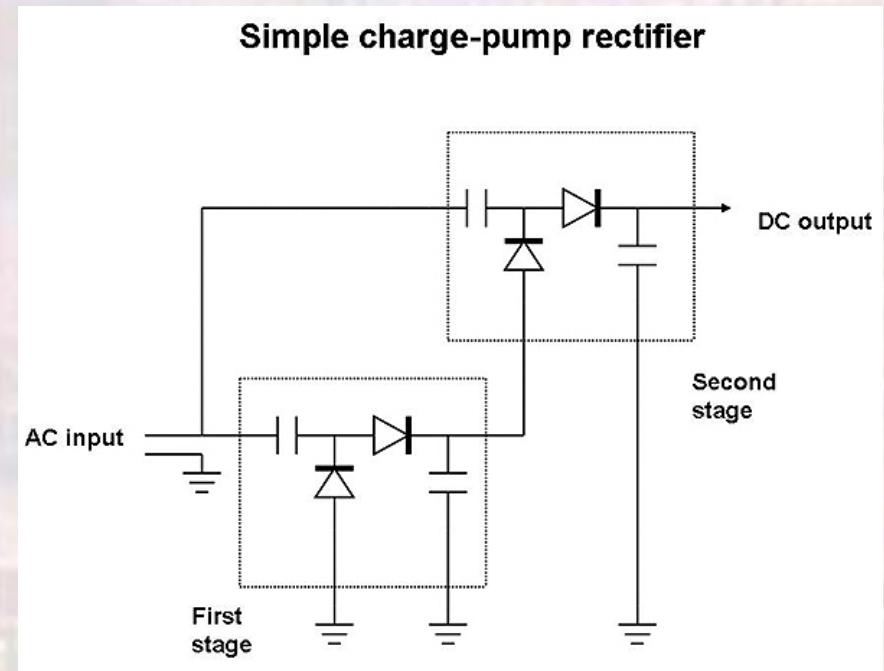

# Wireless Charging



- Inductive Charging

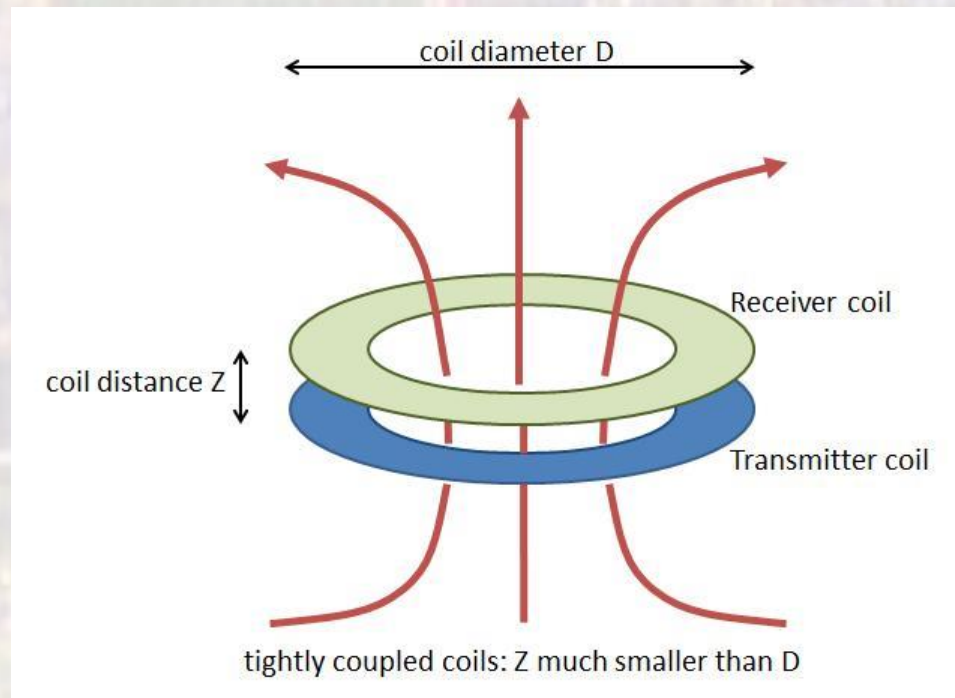

src: WPC

# Wireless Charging

- Inductive Charging

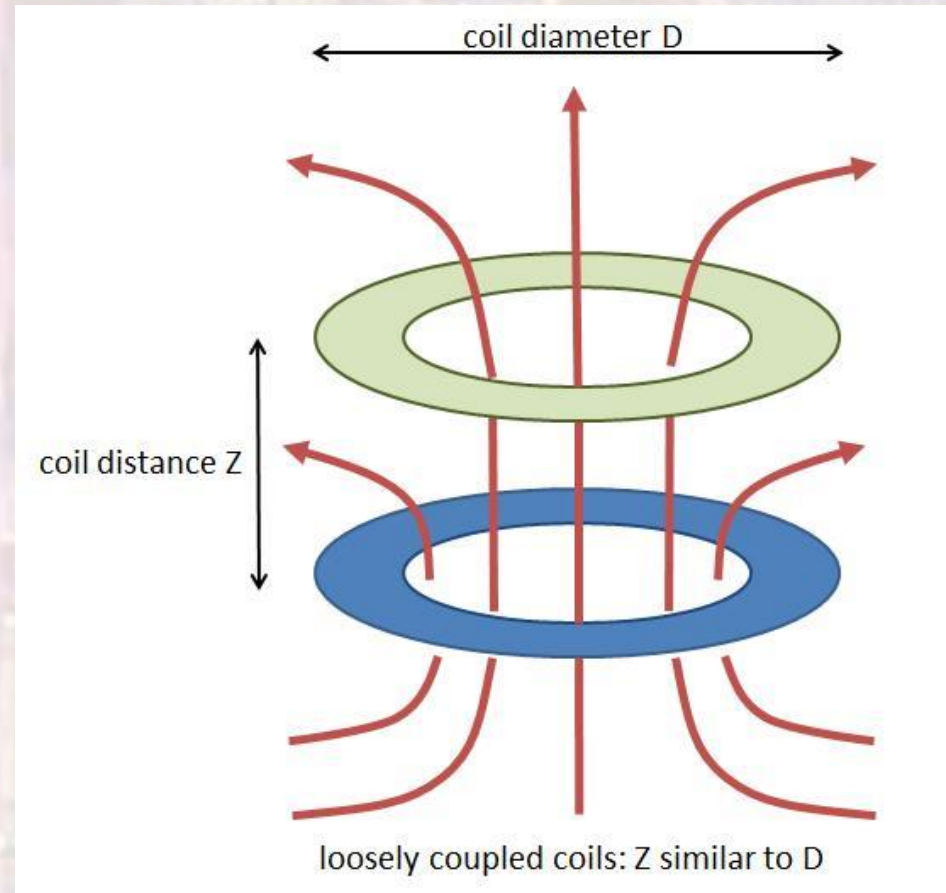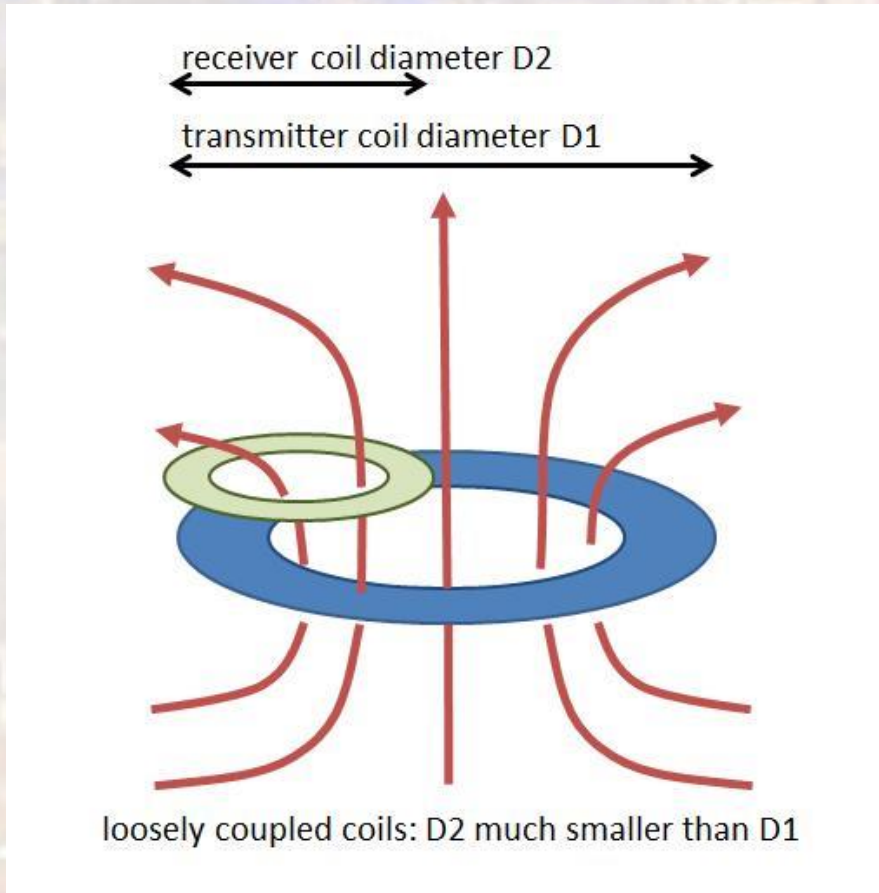


src: WPC


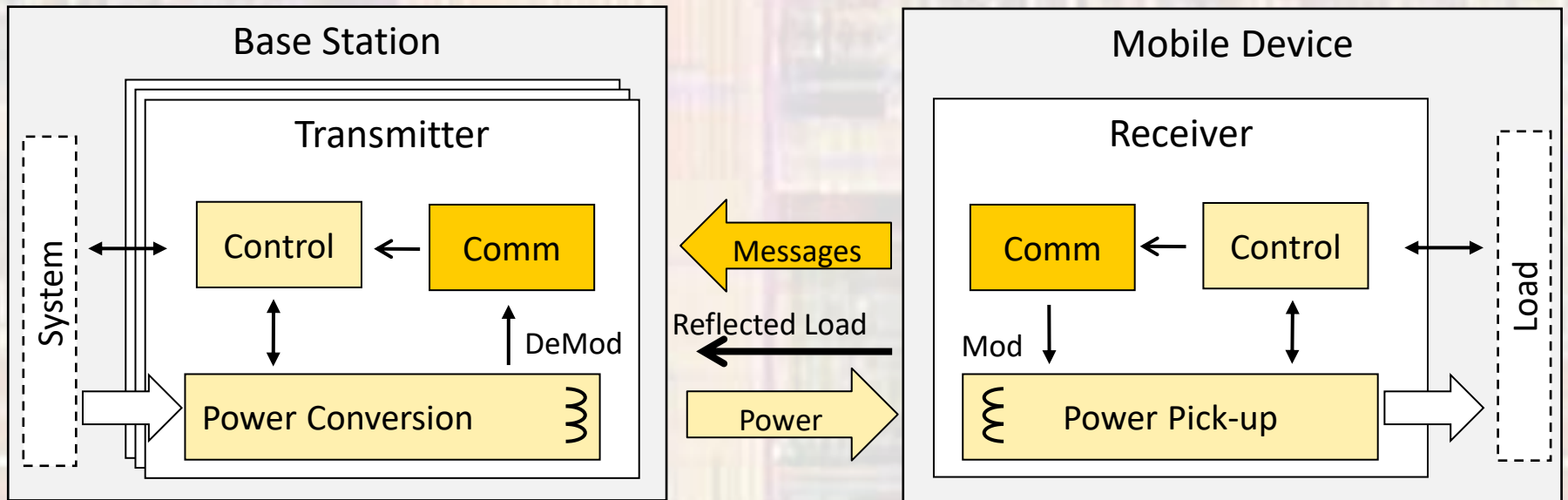
# Wireless Charging


- Inductive Charging
  - Base
    - One or more transmitters
    - Control system to manage transmitted power
  - Device
    - Receiver to convert power to a usable form
    - Feedback to base station to control transmitted power



src: WPC

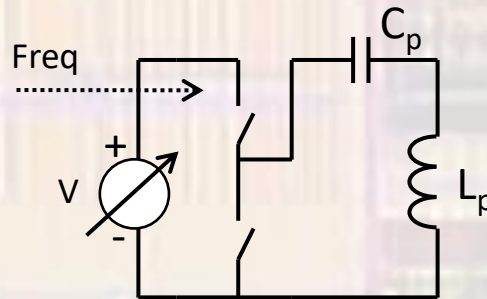
# Wireless Charging

- Transmit Power Generation
  - Transmit coil
  - Half bridge inverter
  - Controlled by
    - Switching frequency
    - Applied voltage



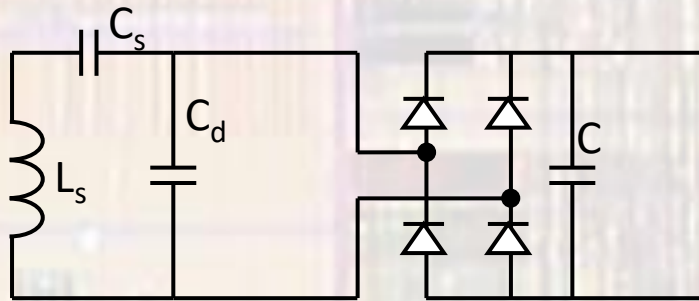
# Wireless Charging

- Receive Power Harvesting
  - Receive coil
  - Full wave rectifier
  - Resonant series capacitor (efficiency)
  - Parallel resonant capacitor (detection)



# Wireless Charging


- Effective Primary Resistance

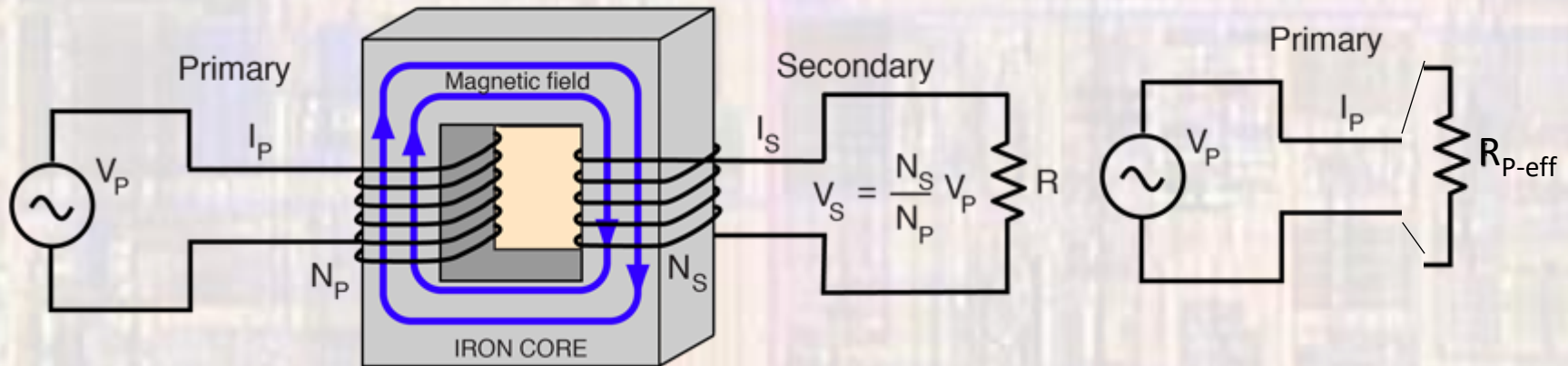

$$R_{P-eff} = \frac{V_S \frac{N_P}{N_S}}{I_S \frac{N_S}{N_P}} = R \left( \frac{N_P}{N_S} \right)^2$$

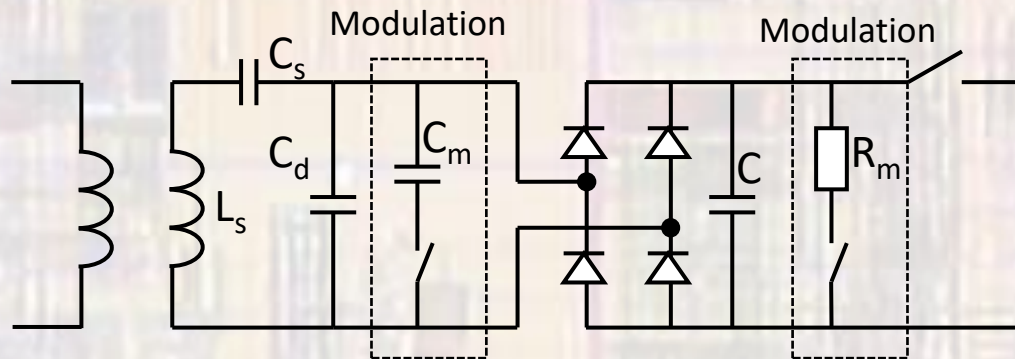
# Wireless Charging

- Communications - Receiver
  - Qi standard (one of many)
  - Modulate the load
    - Switch either
      - Load resistor
      - Resonant capacitor
  - Load gets reflected back to the transmitter through the inductive interface


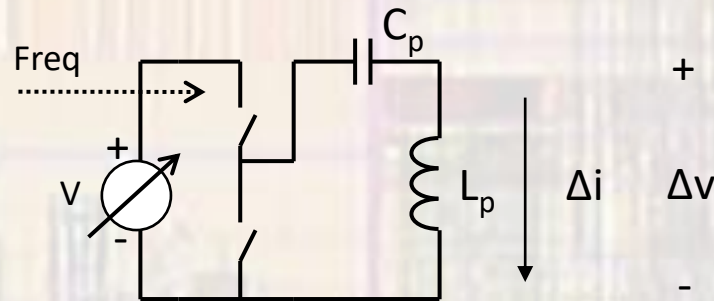
# Wireless Charging


- Communications - Transmitter
  - Qi standard (one of many)
  - Reflected load results in changes to I and V
  - Sense the change to demodulate the communications signal


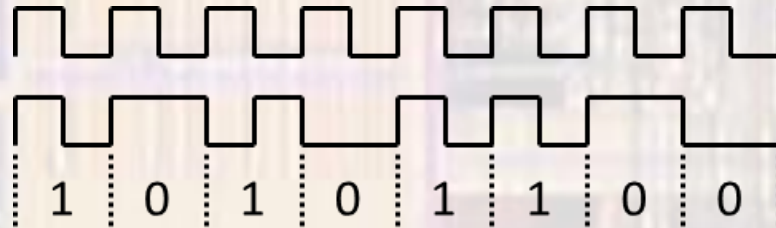
# Wireless Charging


- Communications – Data Format

- 2Kb/s
- Bi-phase encoding
  - Data is in transition or no-transition
  - Every rising edge clock has a transition
  - Check falling edges (or run 2x clk rate) for transition or not
  - No system clock – uses clock recovery




- Byte encoding

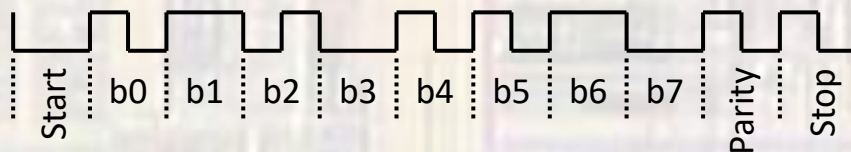- 1 start, 8b - lsb first, 1 parity, 1 stop


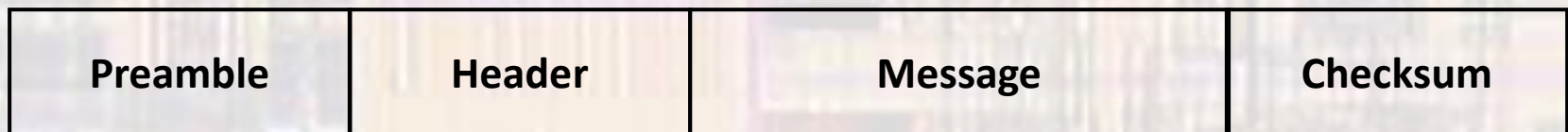
# Wireless Charging

- Communications – Packet Structure
  - Preamble  $\geq 11$ bit
  - Header - 1 Byte
    - Indicates packet type and message length
  - Message - 1 to 27 Bytes
    - One complete message per packet
  - Checksum (1 Byte)






# Wireless Charging
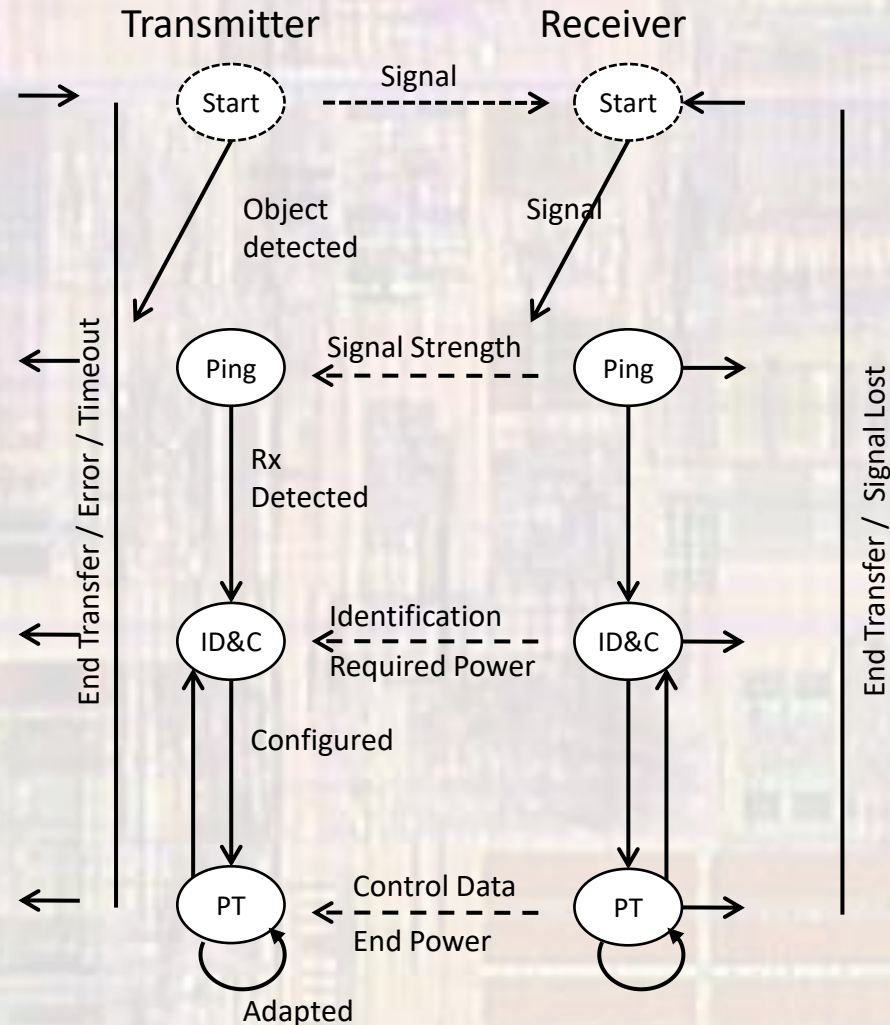
## • Communications – Process

- Start
  - Transmitter provides signal and senses for presence of an object (potential receiver)
  - Receiver waits for signal
- Ping
  - Receiver indicates presence by communicating received signal strength
  - Transmitter detects response of receiver
- Identification & Configuration
  - Receiver communicates its identifier and required power
  - Transmitter configures for power transfer
- Power Transfer
  - Receiver communicates control data
  - Transmitter adapts power transfer



# Wireless Charging


- Communications – Process

- Receiver

- Compares desired operating point to measured operating point


- Transmitter

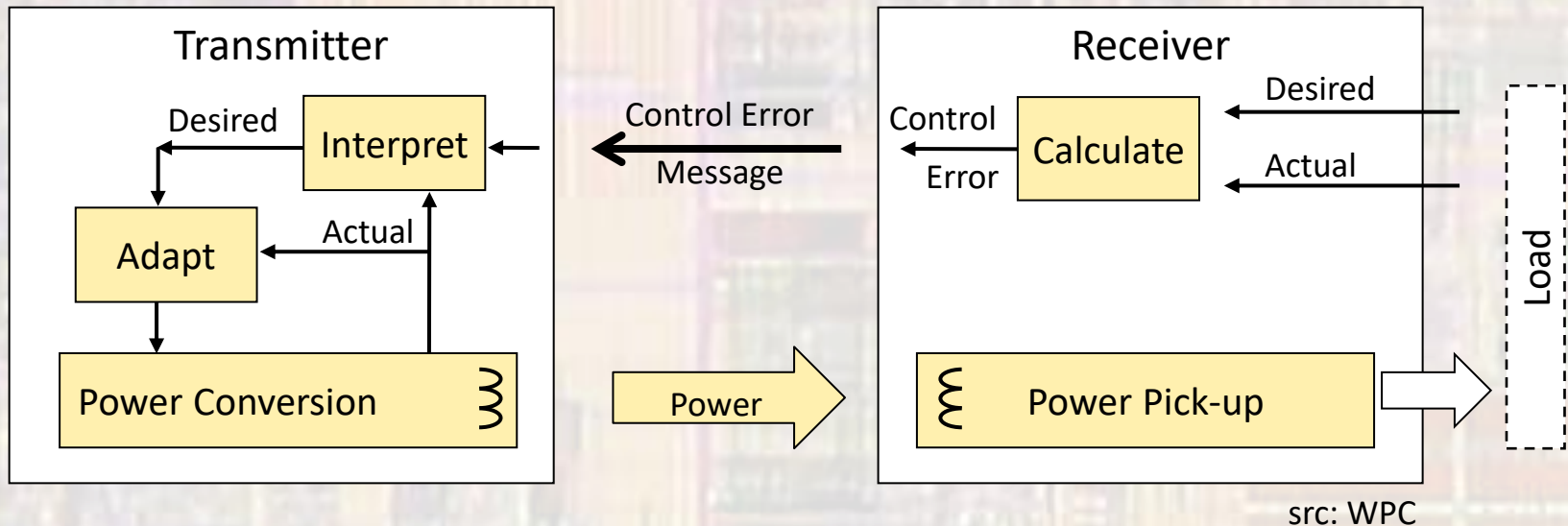- Modifies operating point to reduce communicated error to zero


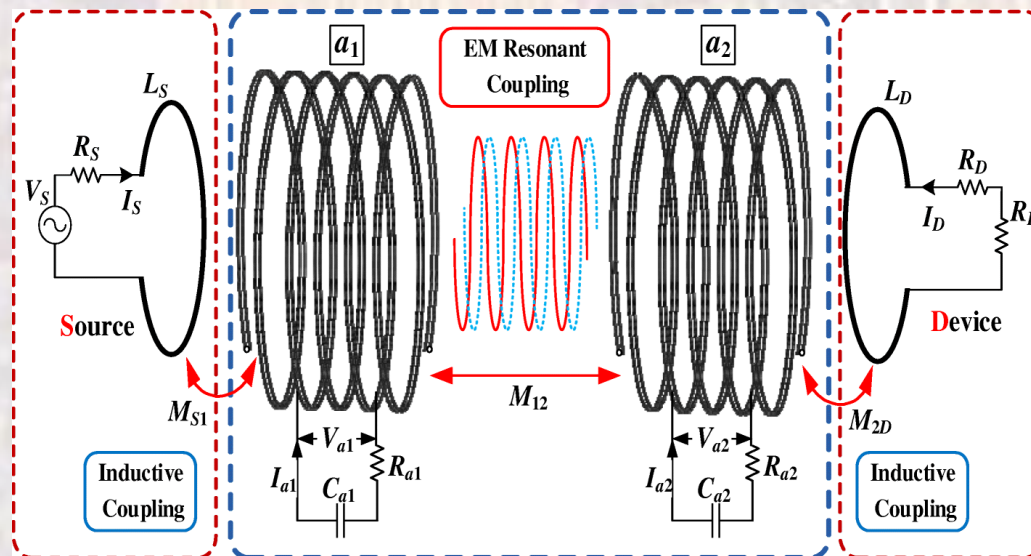
# Wireless Charging


- Resonant Coupling
  - Idea originally attributed to Nikola Tesla
  - Developed at MIT
  - Use “tuned” coil on the receive side (or both sides)
    - Resonates at the transmit frequency
    - Lower transmit field strength required to excite the receiver
      - → more distance



EURASIP Journal on Wireless Communications and Networking, Zhang, X.
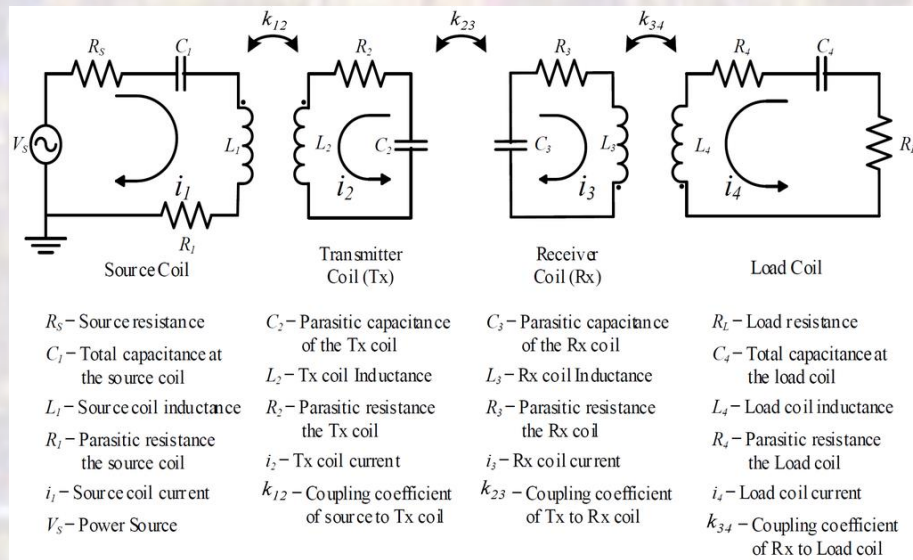
# Wireless Charging

- Resonant Coupling
  - Model
    - Power transfer is a function of coil parameters and distance



$$k_{23} \cong \frac{\mu_0 \pi n^2 r^4}{2Ld_{23}^3}$$


$n$  - # turns  
 $r$  - radius  
 $L$  - self inductance  
 $d_{23}$  - distance

$$|S_{21opt}| = \frac{2k_{12opt}^2 k_{23} Q_1 Q_2^2}{(1 + k_{12opt}^2 Q_1 Q_2)^2 + k_{23}^2 Q_2^2}$$

$Q_1 = Q_4$   
 $Q_2 = Q_3$   
 $k_{12} = k_{34}$

# Wireless Charging


- Resonant Coupling

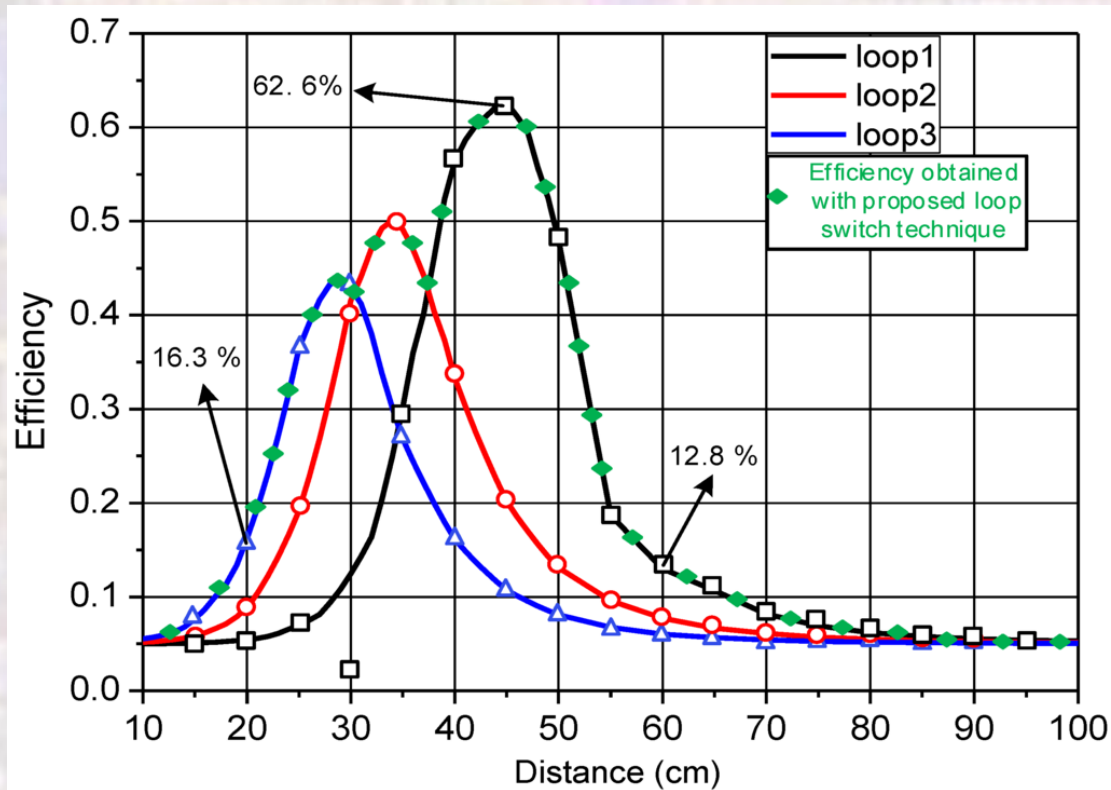

Vijith Vijayakumaran Nair

# Wireless Charging

- Comparison



## Wireless Charging Technology

❖ Inductive vs. Resonant

Type	Inductive	Resonant
Frequency	100~250 kHz (WPC) 232~278 kHz, 205~300 kHz (PMA)	6.78 MHz $\pm$ 15 kHz (A4WP)
Power transmission (Charging)		
Power control (Communication)	In-band (Packet)	Out-band (BLE 2.4 GHz)
Standardization	WPC, AirFuel (PMA)	AirFuel (A4WP)
Characteristics	Compliant with Qi & PMA	Compliant with Rezence Multi device charging Free positioning