
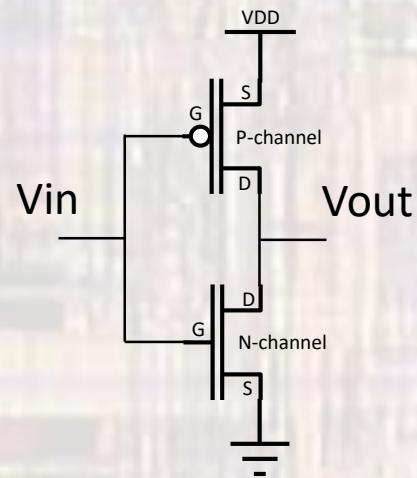


CMOS Inverter Analysis

Last updated 3/22/19




CMOS Inverter

- Inverter Circuit

 


CMOS Inverter

- Inverter Circuit

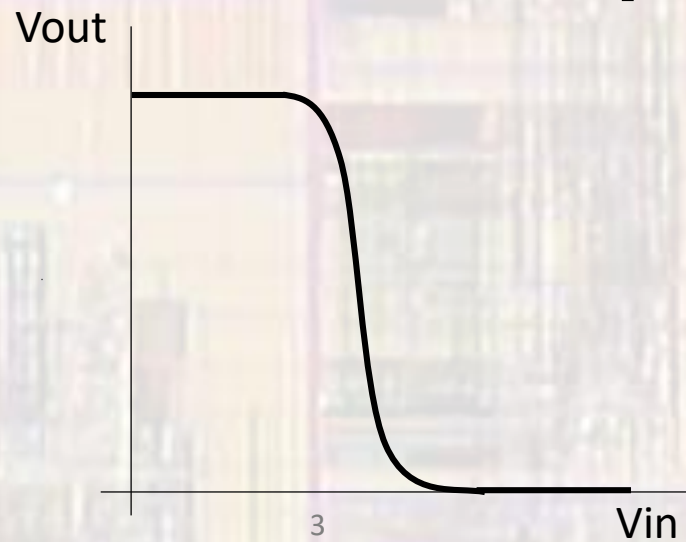 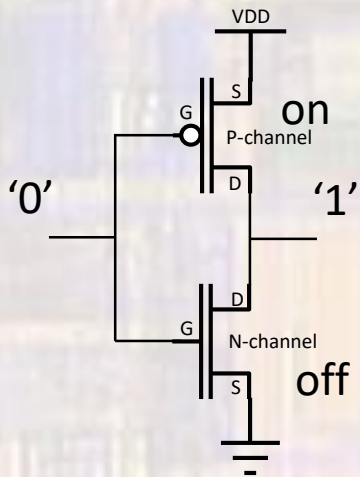

CMOS Inverter

- Inverter Circuit

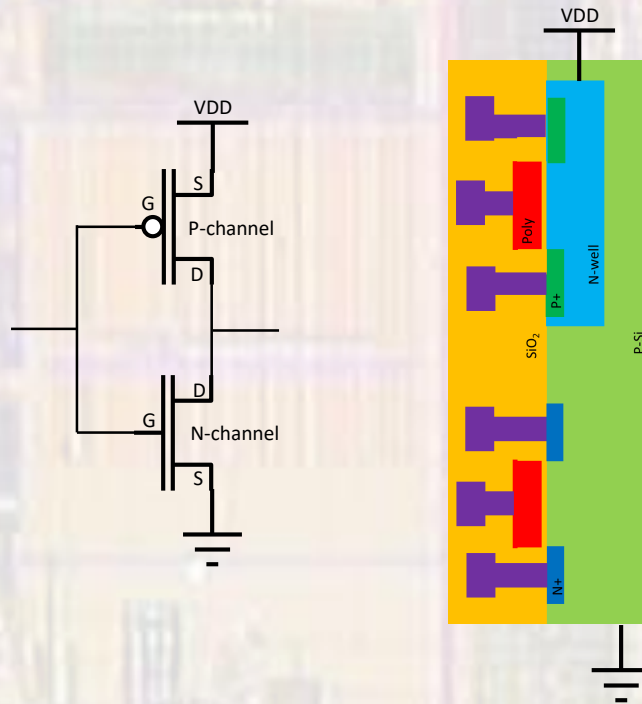

CMOS Inverter

- Inverter Circuit Power



- Static (DC)

- No Active power

- Parasitic currents



All Diodes are reverse or zero biased

→ I_0 currents

  

CMOS Inverter

  - Inverter Circuit Power
 - Static (DC)
 - No Active power
 - Parasitic currents
- All Diodes are reverse or zero biased
→ I_0 currents





'0' in → P-ch on
→ N-ch off

CMOS Inverter

- Inverter Circuit Power


- Switching

  - Shoot through current
 - Short period of time where both P and N are on
 - Very “noisy” in synchronous systems



CMOS Inverter

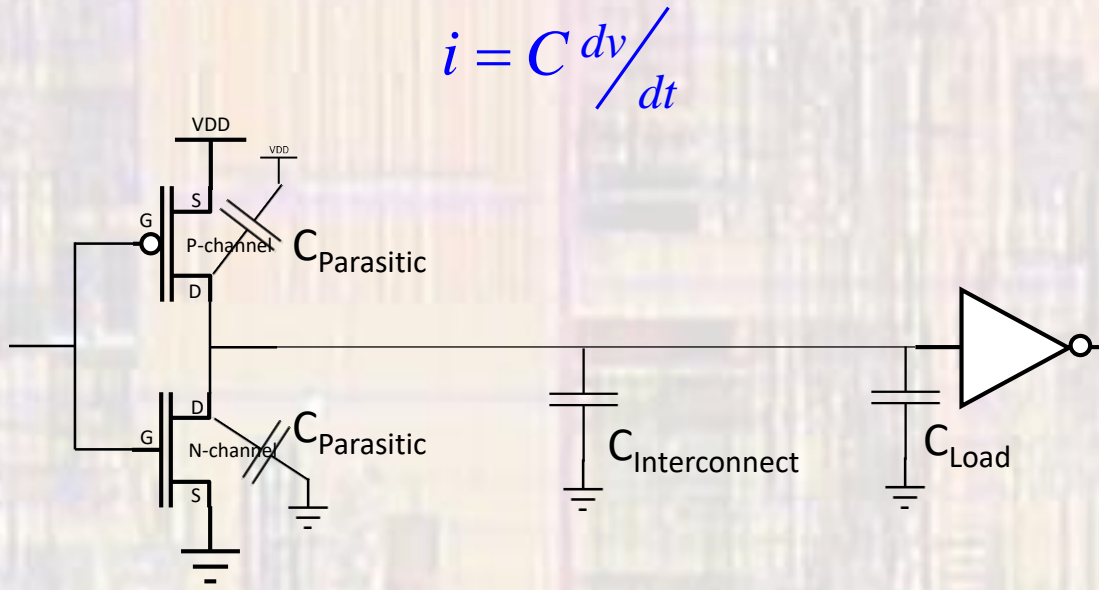- Inverter Circuit Power
 - Switching
 - Charging / discharging currents
 - Very “noisy” in synchronous systems






CMOS Inverter

- Inverter Circuit Power
 - Putting it all together
 - $i = i_{\text{static}} + i_{\text{shoot-through}} + i_{\text{charging}}$
 - $i_{\text{static}} \sim \# \text{ of gates}$
 - $i_{\text{shoot-through}} \sim \# \text{ gates and } F$
 - $i_{\text{charging}} \sim F, \# \text{ gates, wiring}$
 - $i_{\text{charging}} = CVF$
 - $P_{\text{charging}} = CV^2F$
 - \rightarrow reductions in V

CMOS Inverter


- Inverter Switching Analysis (simplified)

- Fall Time
 - 90% \rightarrow 10%

 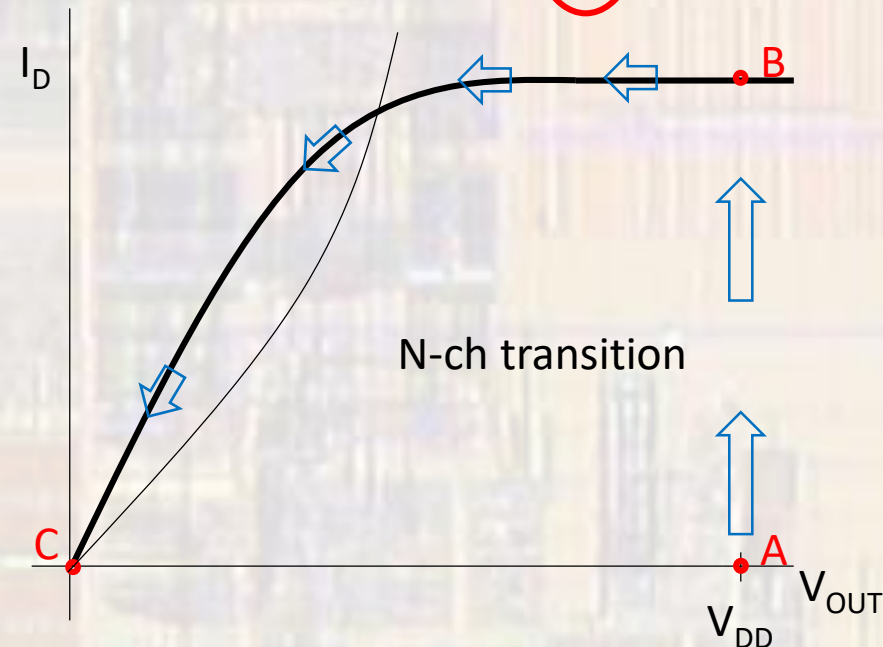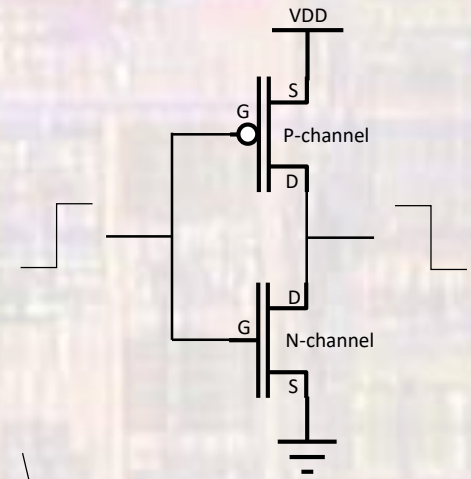


CMOS Inverter

 - Inverter Switching Analysis (simplified)
 - Fall Time



$$C_L \frac{dV_o}{dt} + \frac{\beta_n}{2} (V_{DD} - V_{Tn})^2 = 0$$

$$V_o \geq V_{DD} - V_{Tn}$$

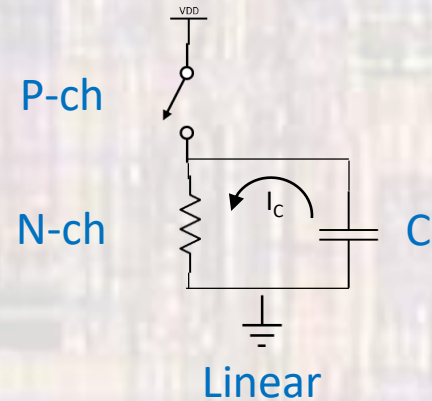

$$C_L \frac{dV_o}{dt} + \beta_n [(V_G - V_{Tn})V_D - V_D^2 / 2] = 0$$

$$V_o < V_{DD} - V_{Tn}$$

CMOS Inverter

- Inverter Switching Analysis (simplified)
 - Fall Time
 - Integrating over the appropriate times

$$t_f = 2 \frac{C_L}{\beta_n (V_{DD} - V_{Tn})} \times \left[\frac{V_{Tn} - 0.1 \times V_{DD}}{V_{DD} - V_{Tn}} + \frac{1}{2} \ln \left(\frac{19 \times V_{DD} - 20 \times V_{Tn}}{V_{DD}} \right) \right]$$

- With $V_{Tn} = 0.45V$ and $V_{DD} = 1.2V$

$$t_f = 4.22 \frac{C_L}{\beta_n} \left(\frac{1}{Volts} \right)$$

$$t_f = 30.6 \times 10^3 \times C \frac{L}{W} \left(\frac{sec}{F} \right)$$

$$\beta = \frac{\mu \epsilon}{t_{ox}} \left(\frac{W}{L} \right)$$

$$\mu_n = 200 \text{ cm}^2 / V - \text{sec}$$

$$\epsilon_{Si} = 3.9 \epsilon_0 = 3.9 \times 10^{-14} \text{ F / cm}$$

$$t_{ox} = 5 \text{ nm}$$



$$\beta_n = \frac{W}{L} \times 138 \mu A / V^2$$

CMOS Inverter

- Inverter Switching Analysis (simplified)
 - Fall Time

$$t_f = 30.6 \times 10^3 \times C \frac{L}{W} \left(\frac{\text{sec}}{F} \right)$$


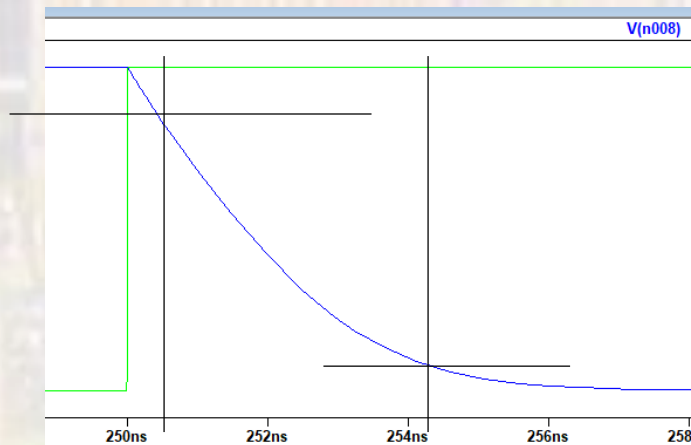
 
$$t_f = 30.6 \times 10^3 \times 1 \text{pF} \frac{100\text{n}}{1000\text{n}} \left(\frac{\text{sec}}{F} \right) = 3.06 \text{ns}$$



CMOS Inverter


- Inverter Switching Analysis (simplified)

- Rise Time
 - 10% → 90%

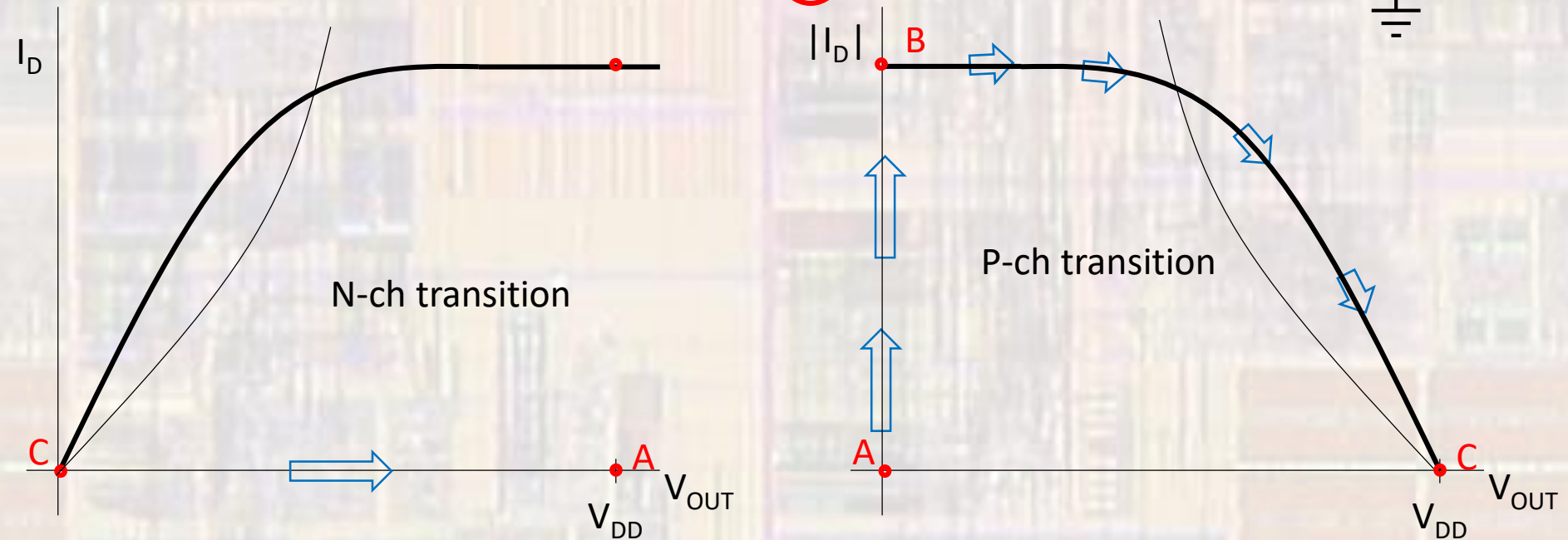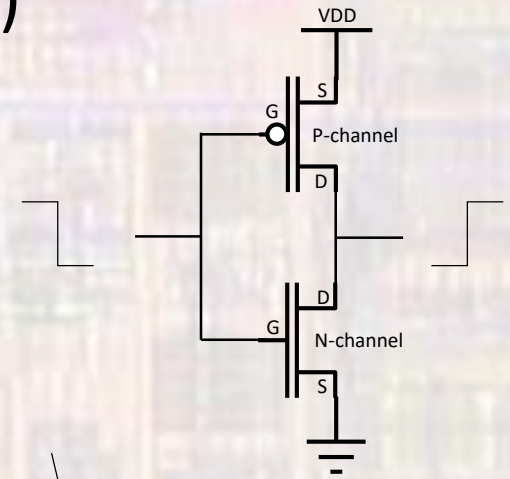 


CMOS Inverter

 - Inverter Switching Analysis (simplified)
 - Rise Time



$$C_L \frac{dV_o}{dt} + \frac{\beta_p}{2} (V_{DD} - V_{Tp})^2 = 0$$

$$V_o \geq V_{DD} - V_{Tp}$$

 

$$C_L \frac{dV_o}{dt} + \beta_p \left[(V_G - V_{Tp}) V_D - V_D^2 / 2 \right] = 0$$

$$V_o < V_{DD} - V_{Tp}$$

CMOS Inverter

- Inverter Switching Analysis (simplified)
 - Rise Time
 - Integrating over the appropriate times

$$t_r = 2 \frac{C_L}{\beta_p (V_{DD} - |V_{Tp}|)} \times \left[\frac{|V_{Tp}| - 0.1 \times V_{DD}}{V_{DD} - |V_{Tp}|} + \frac{1}{2} \ln \left(\frac{19 \times V_{DD} - 20 \times |V_{Tp}|}{V_{DD}} \right) \right]$$

- With $V_{Tp} = 0.45V$ and $V_{DD} = 1.2V$

$$t_r = 8.44 \frac{C_L}{\beta_p} \left(\frac{1}{Volts} \right)$$

$$t_r = 61.2 \times 10^3 \times C \frac{L}{W} \left(\frac{sec}{F} \right)$$

$$\beta = \frac{\mu \epsilon}{t_{ox}} \left(\frac{W}{L} \right)$$

$$\mu_p = 100 \text{ cm}^2 / V - \text{sec}$$

$$\epsilon_{Si} = 3.9 \epsilon_0 = 3.9 \times 10^{-14} \text{ F / cm}$$

$$t_{ox} = 5 \text{ nm}$$



$$\beta_p = \frac{W}{L} \times 69 \mu A / V^2$$

CMOS Inverter

- Inverter Switching Analysis (simplified)
 - Fall Time

$$t_r = 61.2 \times 10^3 \times C \frac{L}{W} \left(\frac{\text{sec}}{F} \right)$$
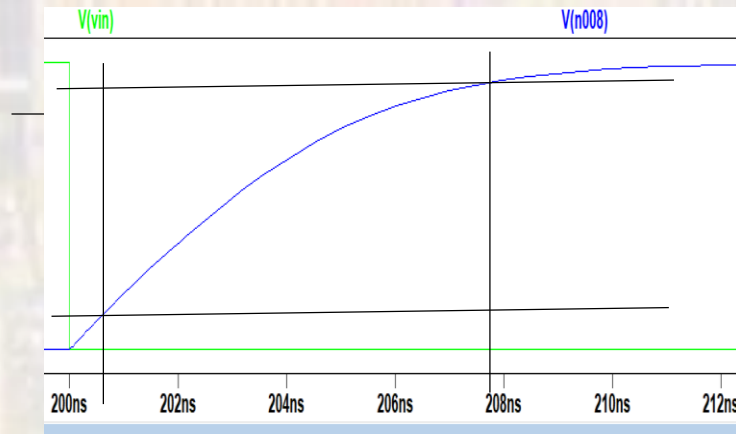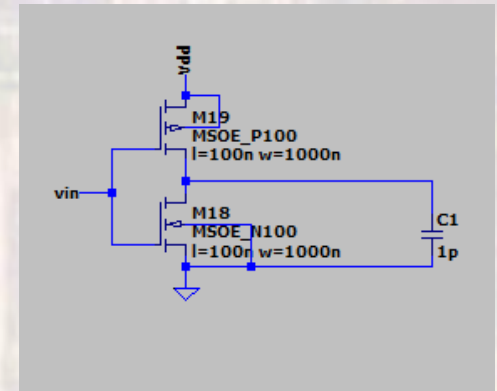
$$t_r = 61.2 \times 10^3 \times 1 \text{pF} \frac{100 \text{n}}{1000 \text{n}} \left(\frac{\text{sec}}{F} \right) = 6.12 \text{ns}$$






CMOS Inverter

- Inverter Switching Analysis (simplified)
 - W/L scaling

$$t_r = 61.2 \times 10^3 \times C \frac{L_p}{W_p} \left(\frac{\text{sec}}{F} \right) \quad t_f = 30.6 \times 10^3 \times C \frac{L_n}{W_n} \left(\frac{\text{sec}}{F} \right)$$

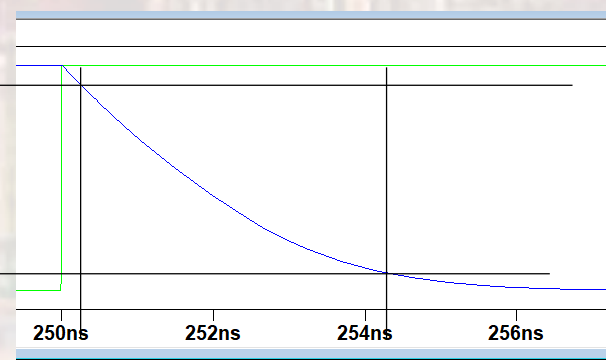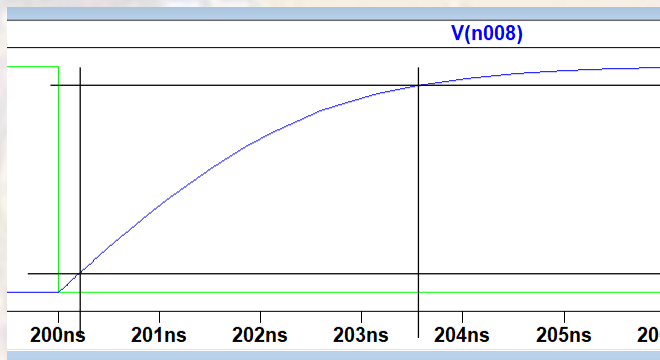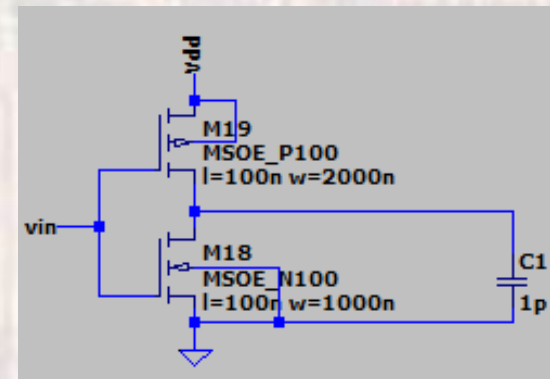- Assuming $L_n = L_p = L_{\text{min}}$
- Scale $W_p = 2 \times W_n$





CMOS Inverter

- Driving large loads
 - Assume the delay of a minimum inverter driving another minimum inverter is τ
 - We expect the delay of an inverter driving an inverter α times the first to be $\alpha\tau$
 - The delay of N stages of progressively growing inverters would be $N\alpha\tau$
- The input capacitance for the inverters is C_G
- Driving a large capacitance C_L
 - $Y = C_L / C_G = \alpha^N$
 - Bigger $\alpha \rightarrow$ smaller N , ...
 - $\ln(Y) = N\ln(\alpha)$
- $N\alpha\tau = [\ln(Y)/\ln(\alpha)] \alpha \tau = \ln(Y) \tau [\alpha / \ln(\alpha)]$

CMOS Inverter

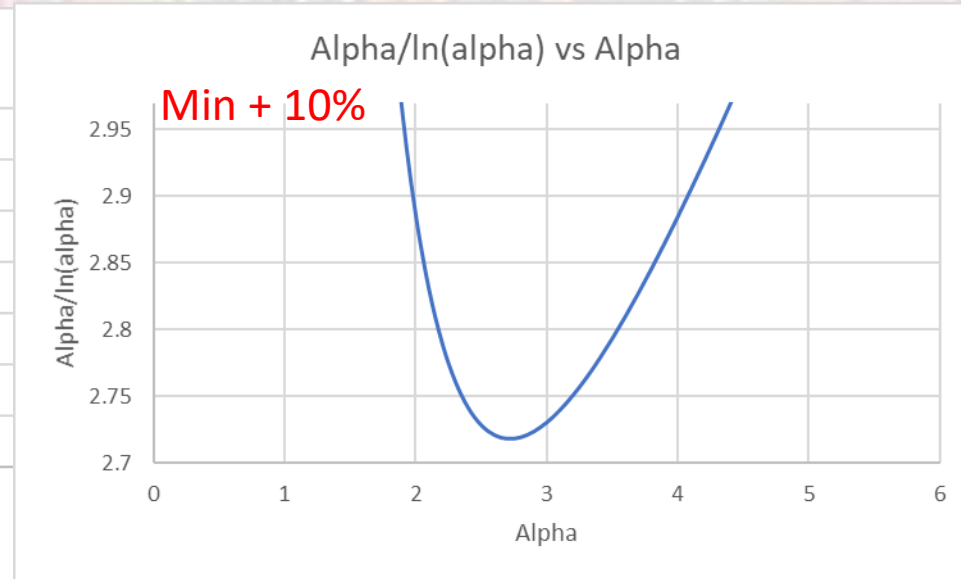 - Driving large loads
 - $N\alpha\tau = [\ln(Y)/\ln(\alpha)] \alpha \tau = \ln(Y) \tau [\alpha / \ln(\alpha)]$
 - Minimizing by taking the derivative $\rightarrow \alpha = e = 2.71$
 - Plotting wrt α



CMOS Inverter

- Driving large loads
 - Typically scale by 2.7x – 4x
 - 2.7x → minimum delay
 - 4x → <10% delay penalty + area savings
- $Y = C_L / C_G = \alpha^N = 256$
- $\alpha = 2.7$: $N = \ln(Y)/\ln(\alpha) = 5.54$
- $1A + 2.7A + 7.29A + 19.68A + 53.14 + 77.47^* = 161.28A$
- $\alpha = 4$: $N = \ln(Y)/\ln(\alpha) = 4$
- $1A + 4A + 16A + 64A = 85A$