

Digital to Analog Converter

Last updated 5/5/2019

D/A

- Digital to Analog Converter
 - Converts a digital word to a fixed analog voltage level
 - Many applications
 - Electronic music
 - Audio conversion – cell phones
 - Video conversion – digital TV
 - Mechanical conversion – valve opening

D/A

- Digital to Analog Converter
 - Converts a digital word to a fixed analog voltage level
 - Many types of D/A converters
 - Resistor DAC
 - Current DAC
 - Switched Capacitor DAC
 - Delta-sigma DAC
 - Pulse width modulator

D/A

- Digital to Analog Converter Performance
 - Resolution
 - n-bit digital word can represent 2^n levels
 - 8-bit DAC → 256 levels
 - Frequency
 - Outputs are provided at a fixed rate – data rate
 - Desired output is limited by the Nyquist criteria
 - Signals can be re-constructed iff
 - data rate > 2 * Maximum signal frequency content
 - Accuracy
 - Linearity
 - Noise
 - Many others

D/A

- Digital to Analog Converter Performance


- 4 bit DAC, 5v range
 - $5\text{v} / 2^4 \rightarrow 0.3125\text{v}/\text{step}$

Code	Output
0000	0.0v
0001	0.3125v
0010	0.625v
0011	0.9375v
...	
1101	4.0625v
1110	4.375v
1111	4.6875v

D/A


- Digital to Analog Converter Performance

- 4 bit DAC, 5v range

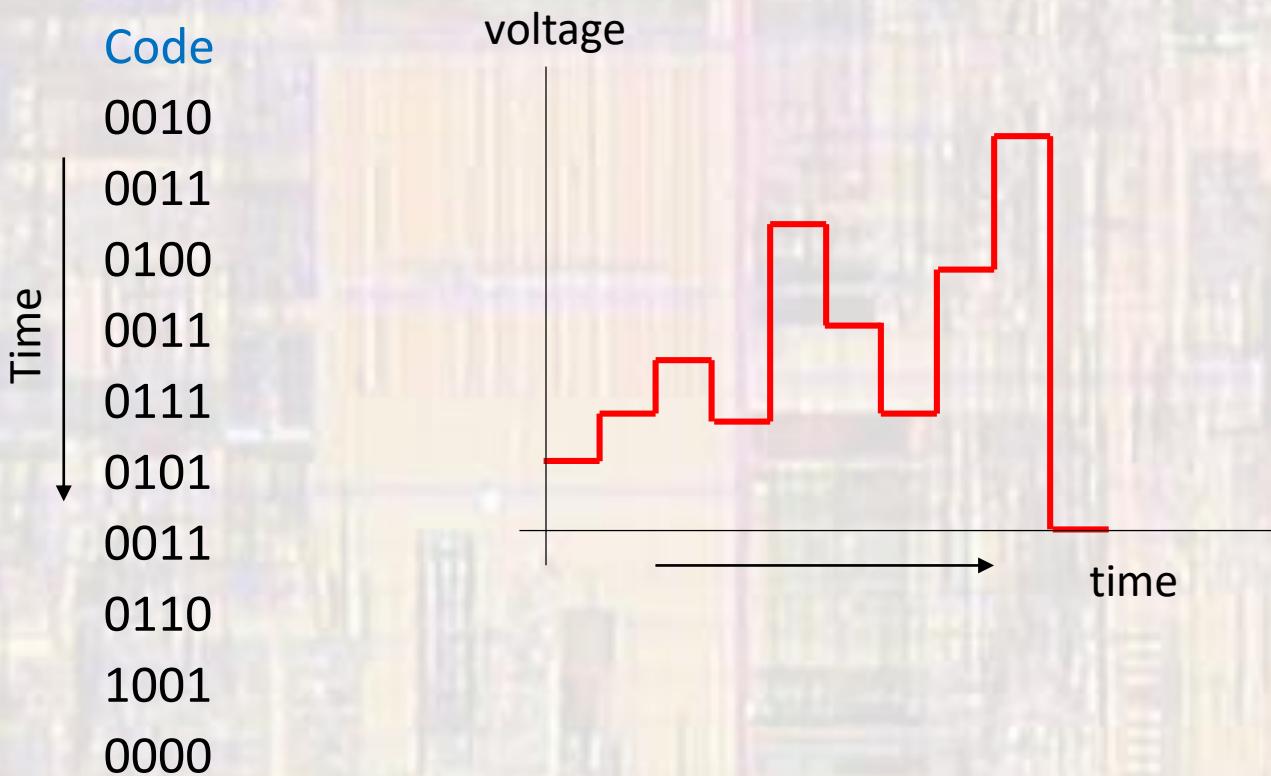

D/A

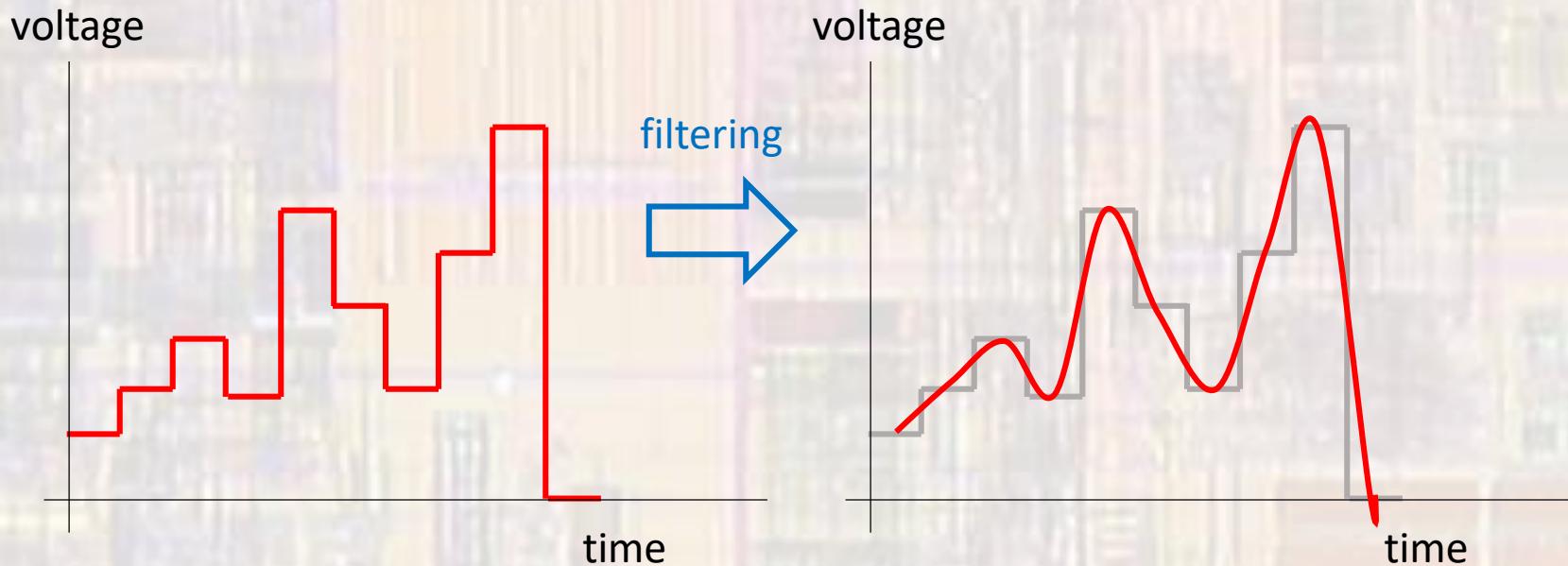- Digital to Analog Converter Performance
 - Typically additional signal conditioning is required to 'clean up' the output



D/A

- Example

3.3V Vref
8 bit convertor

Code	Steps	Volts
0000 0000	0	0
0000 0001	1	0.013
0001 0000	16	0.206
0111 1111	127	1.637
1000 0000	128	1.650
1100 0000	192	2.475
1111 1111	255	3.287

$$\begin{aligned}3.3v / 2^8 \text{ steps} \\= 12.89\text{mv/step}\end{aligned}$$

D/A

- R-2R DAC

- Converts a digital word to a fixed voltage level

- example: 4 bit code

$$0000 \rightarrow V_{out} = V_{refL}$$

$$1111 \rightarrow V_{out} = V_{refL} + (V_{refH} - V_{refL}) \left(\frac{15}{16} \right)$$

b0 contributes $1/16$


b1 contributes $1/8$

b2 contributes $1/4$

b3 contributes $1/2$

$$0110 \rightarrow V_{out} = V_{refL} + (V_{refH} - V_{refL}) \left(\frac{1}{4} + \frac{1}{8} \right)$$



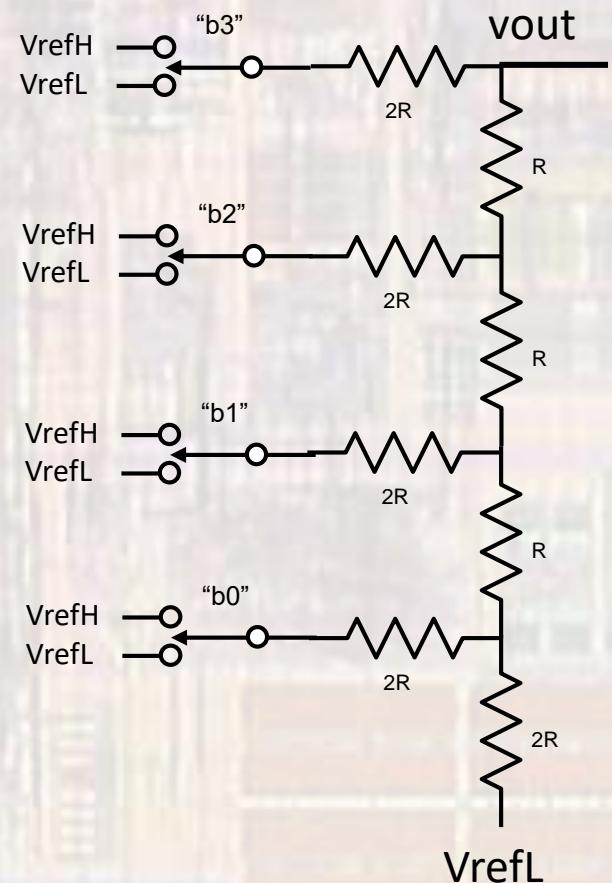
$$1000 \rightarrow V_{out} = V_{refL} + (V_{refH} - V_{refL}) \left(\frac{1}{2} \right)$$



D/A



- R-2R DAC

- Superposition and Thevenin Equivalents

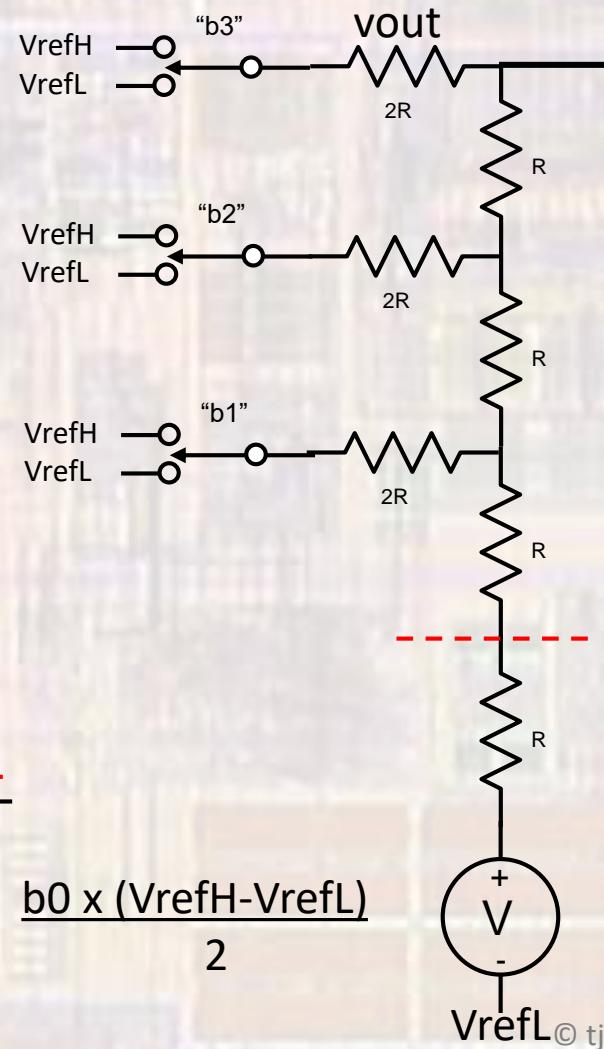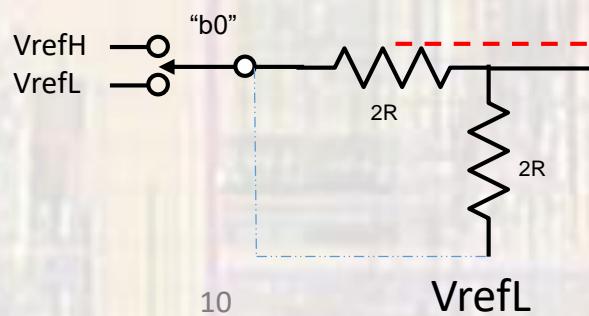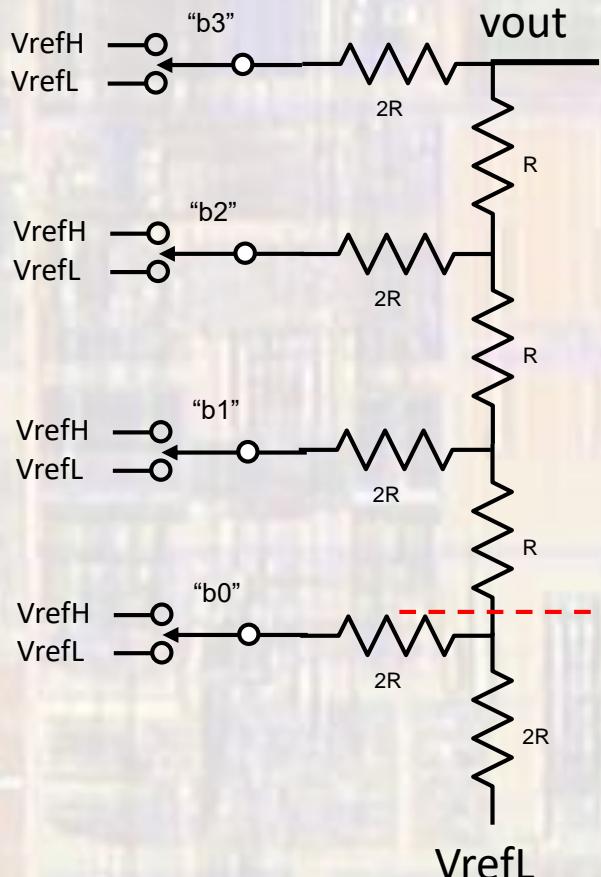


D/A

- R-2R DAC

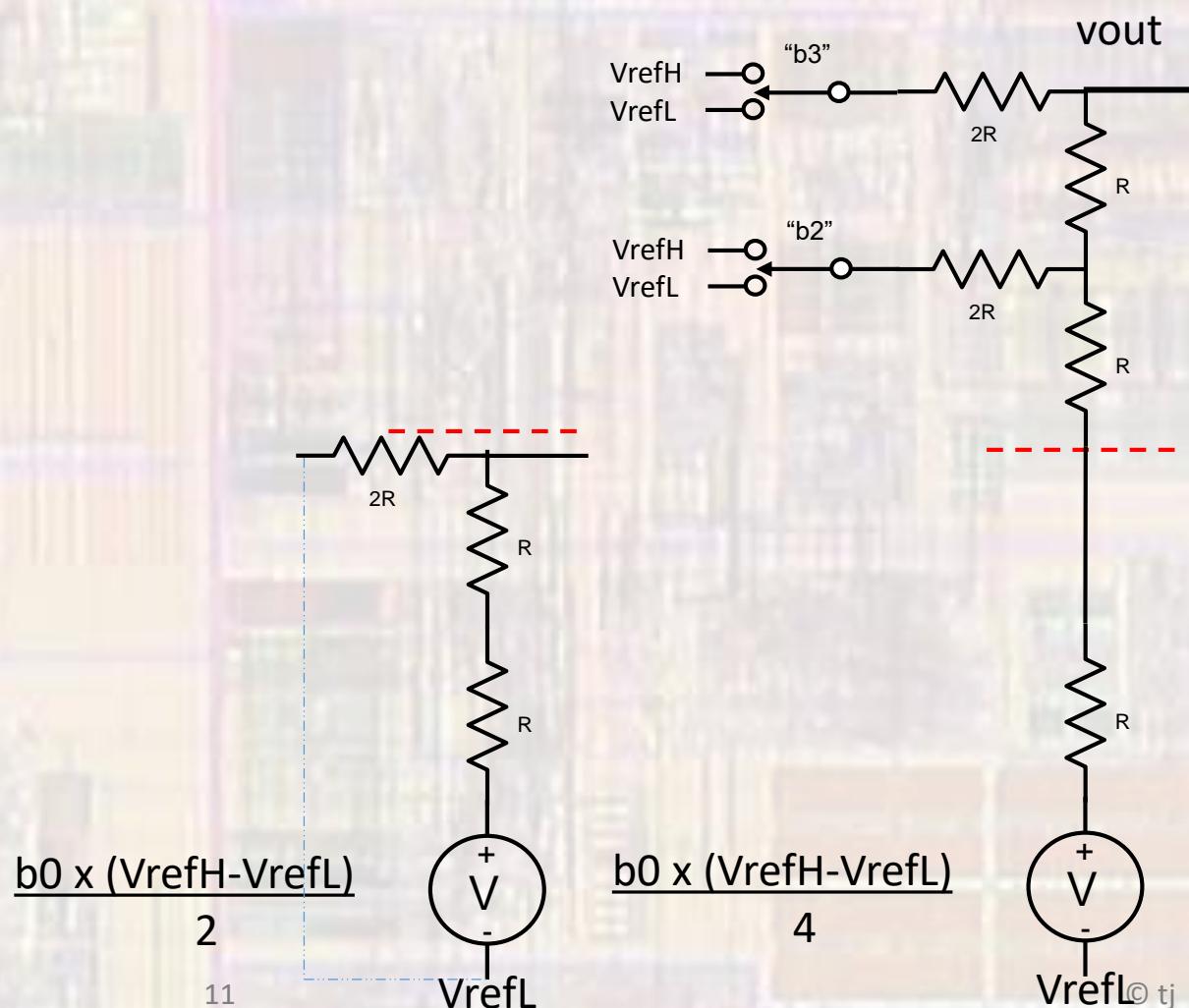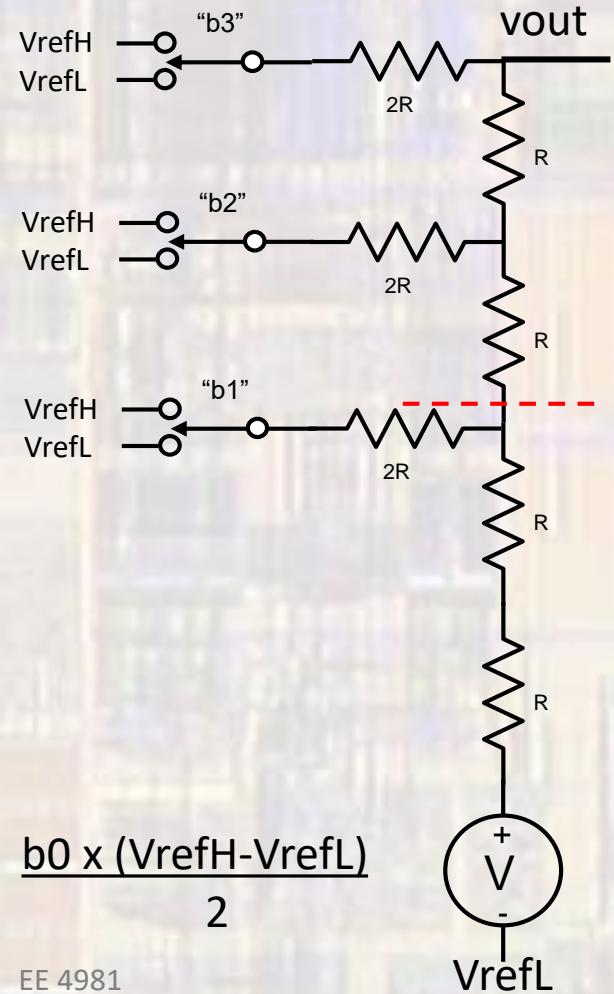

D/A


- R-2R DAC

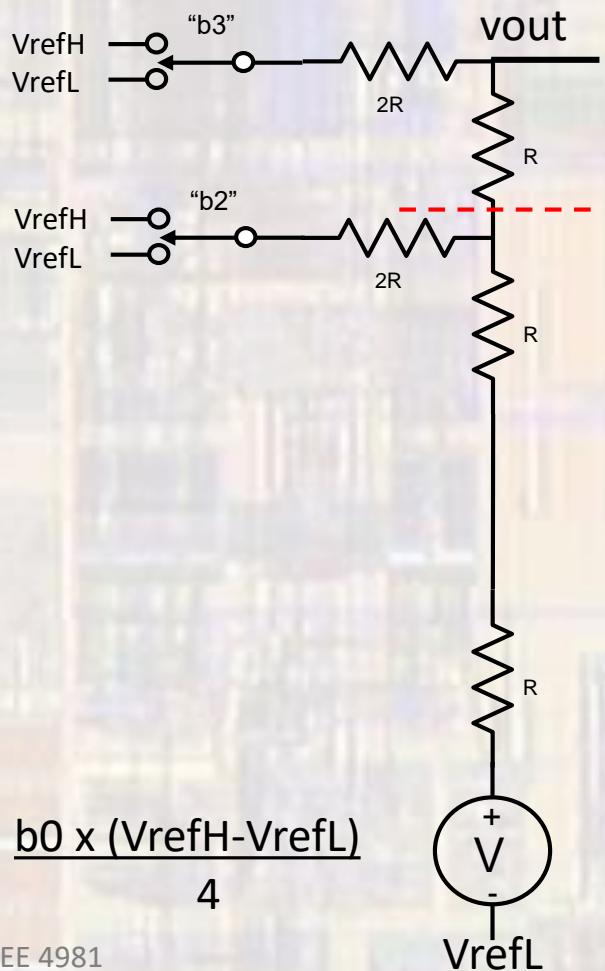

$$\frac{b0 \times (V_{refH} - V_{refL})}{4}$$

$$\frac{b0 \times (V_{refH} - V_{refL})}{4}$$

12

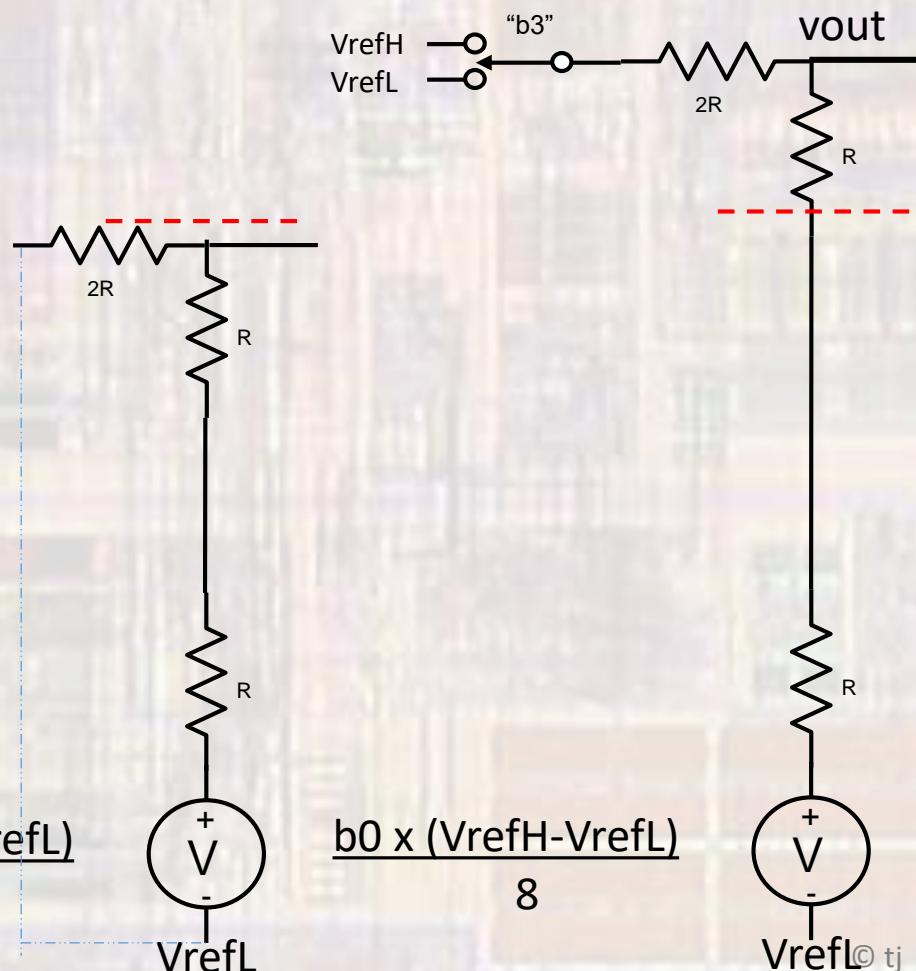


$$\frac{b0 \times (V_{refH} - V_{refL})}{8}$$

\odot tj


D/A

- R-2R DAC

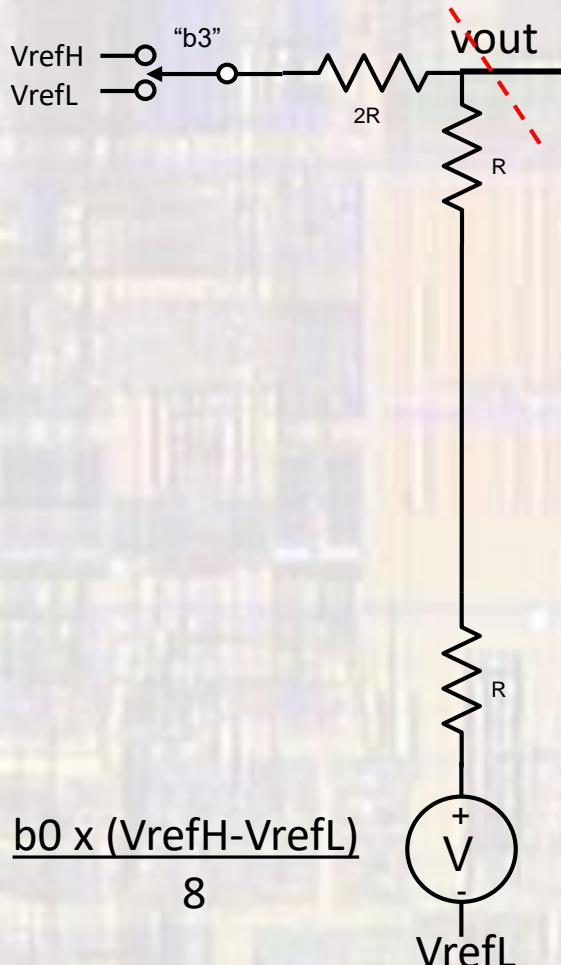

$$b0 \times (V_{refH} - V_{refL})$$

8

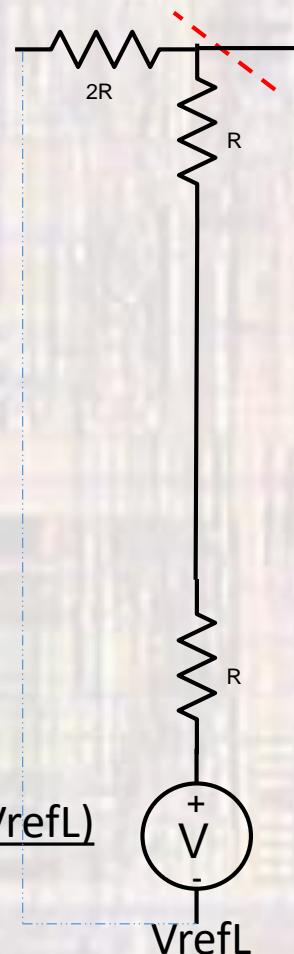

$$b0 \times (V_{refH} - V_{refL})$$

16






$\oplus t_j$

13

D/A

- R-2R DAC




- b2 analysis

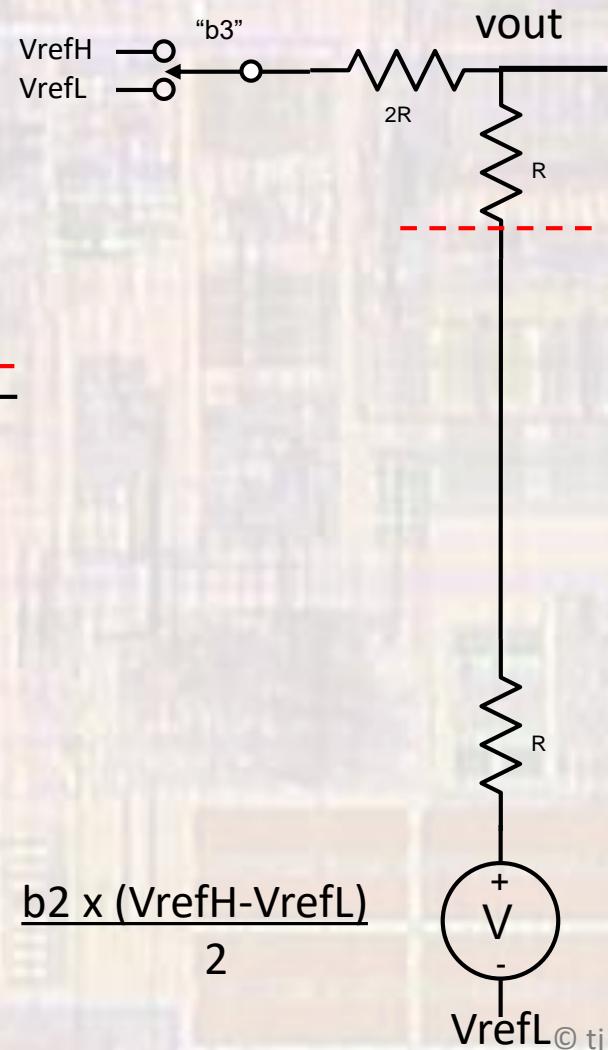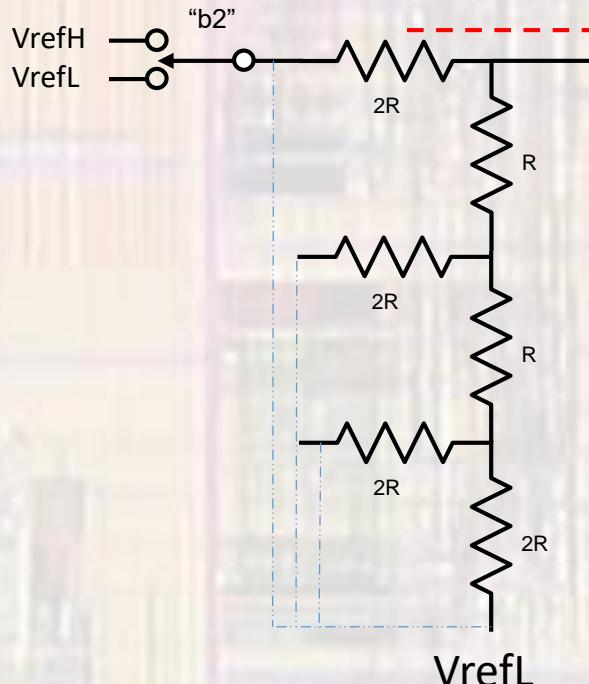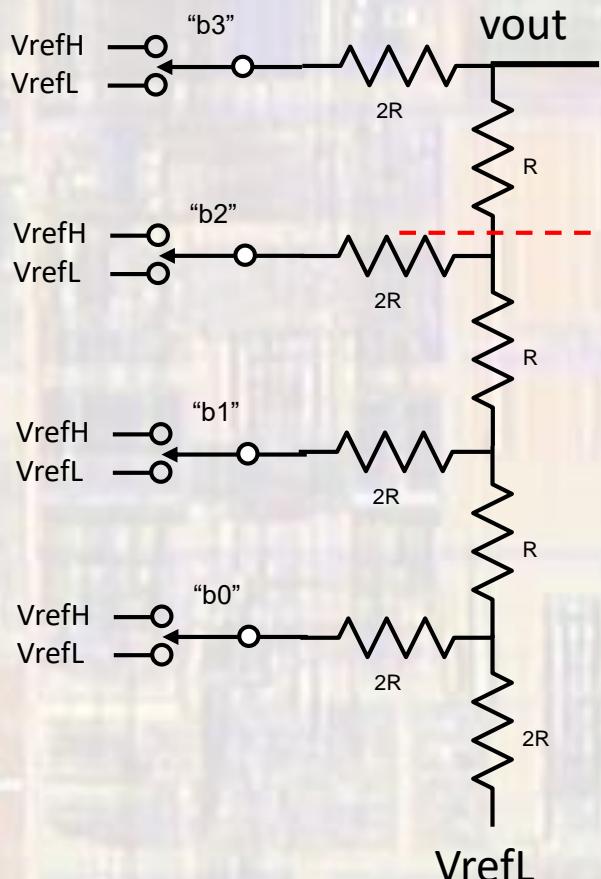

$$\frac{b_2 \times (V_{refH} - V_{refL})}{2}$$

D/A


- R-2R DAC

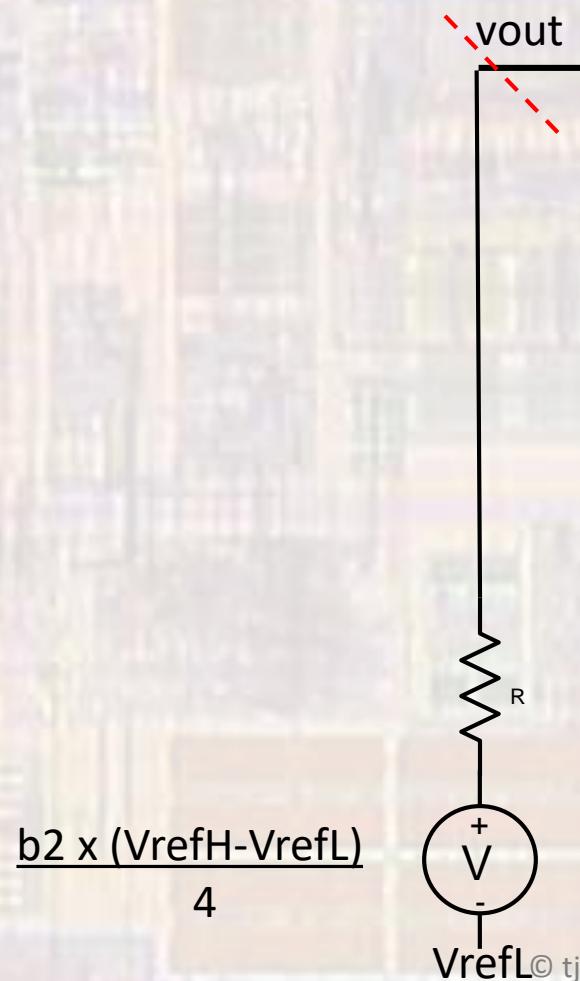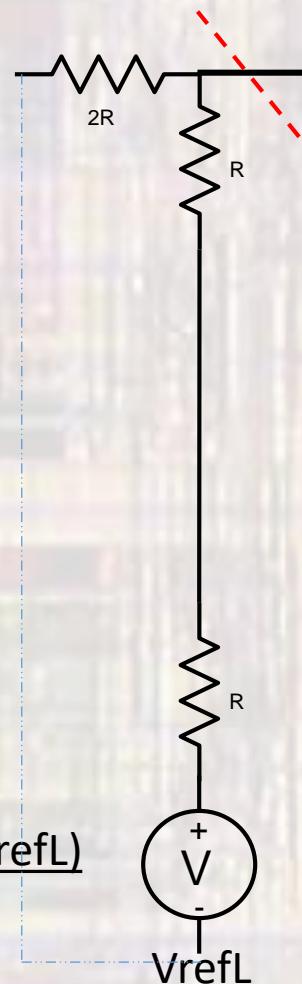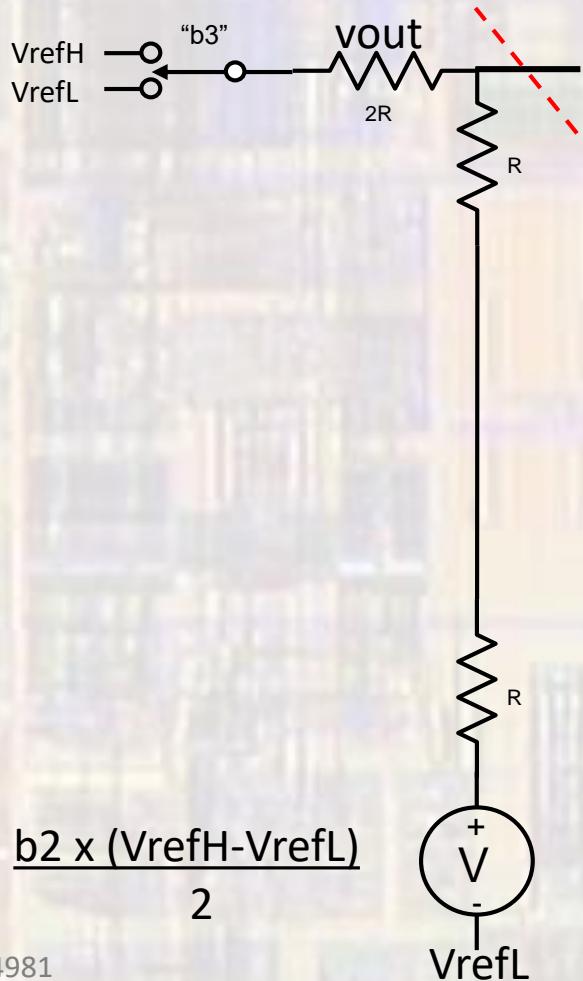

D/A



- R-2R DAC

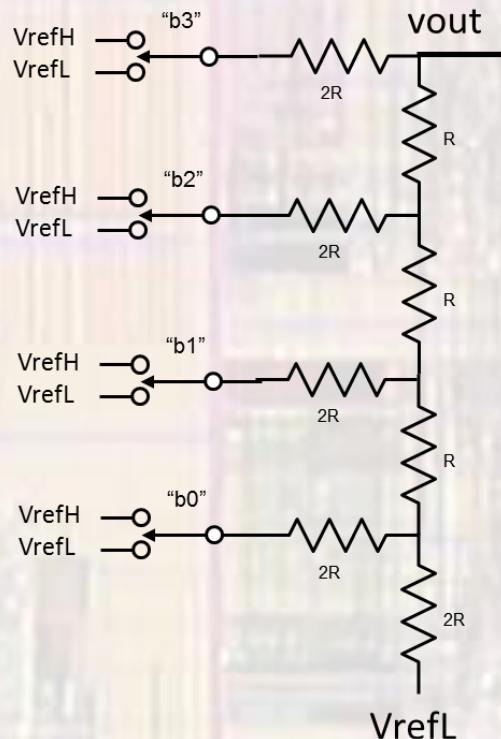- $V_{out} = ((b_0)/16 + (b_1)/8 + (b_2)/4 + (b_3)/2)(V_{refH}-V_{refL}) + V_{refL}$




D/A

- Current DAC

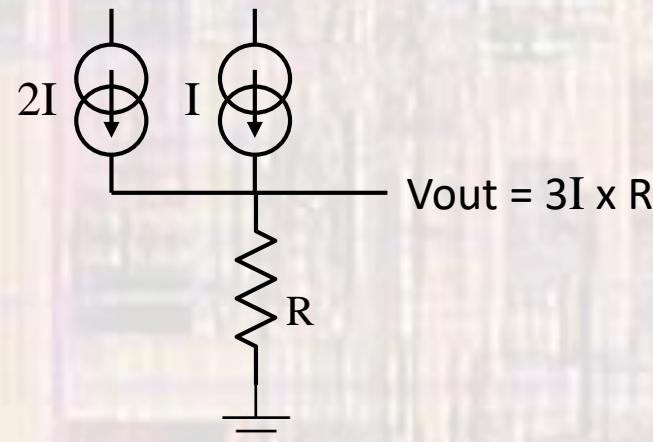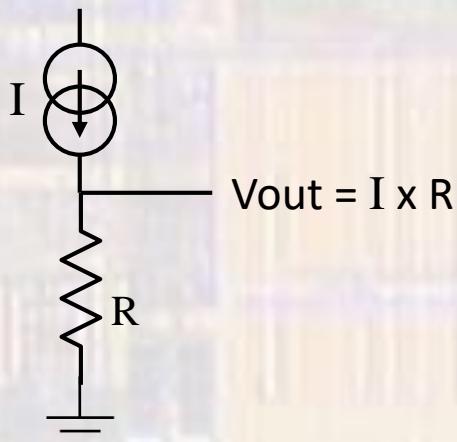


D/A

- Current DAC

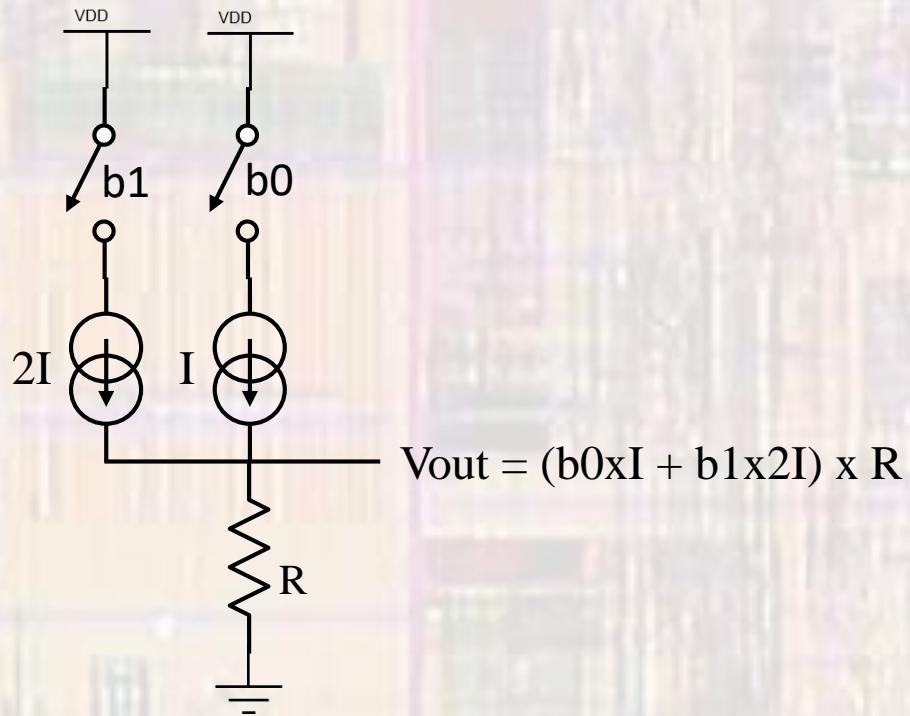

D/A


- Current DAC

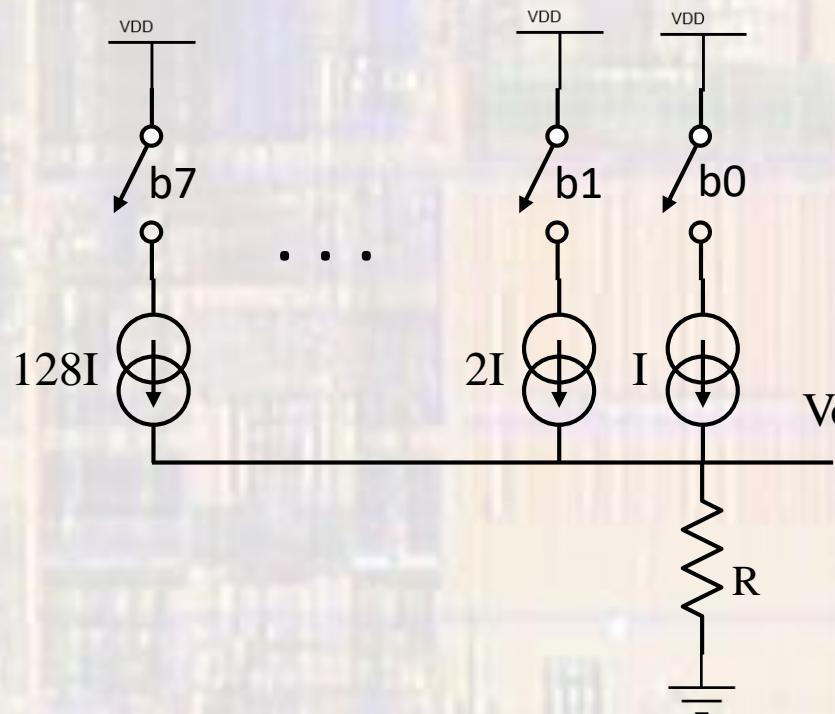

$$V_{out} = (b_0 \times I + b_1 \times 2I + b_2 \times 4I + b_3 \times 8I + b_4 \times 16I + b_5 \times 32I + b_6 \times 64I + b_7 \times 128I) \times R$$

D/A


- Current DAC
 - MOS implementation

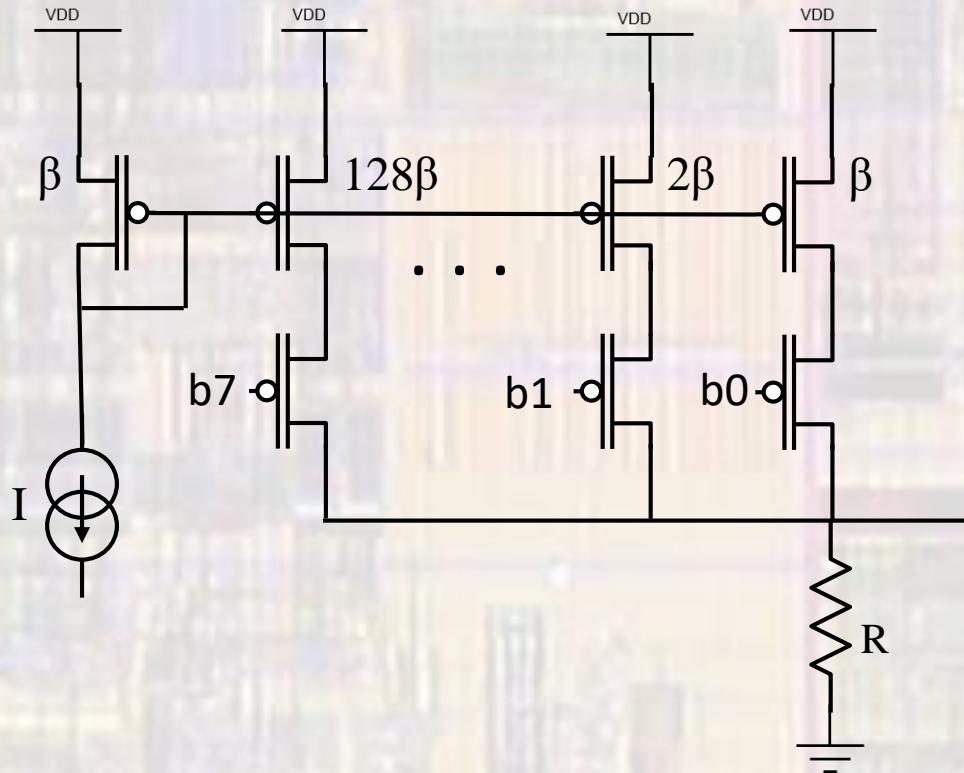

$$V_{out} = (b_0 \times I + b_1 \times 2I + b_2 \times 4I + b_3 \times 8I + b_4 \times 16I + b_5 \times 32I + b_6 \times 64I + b_7 \times 128I) \times R$$

D/A

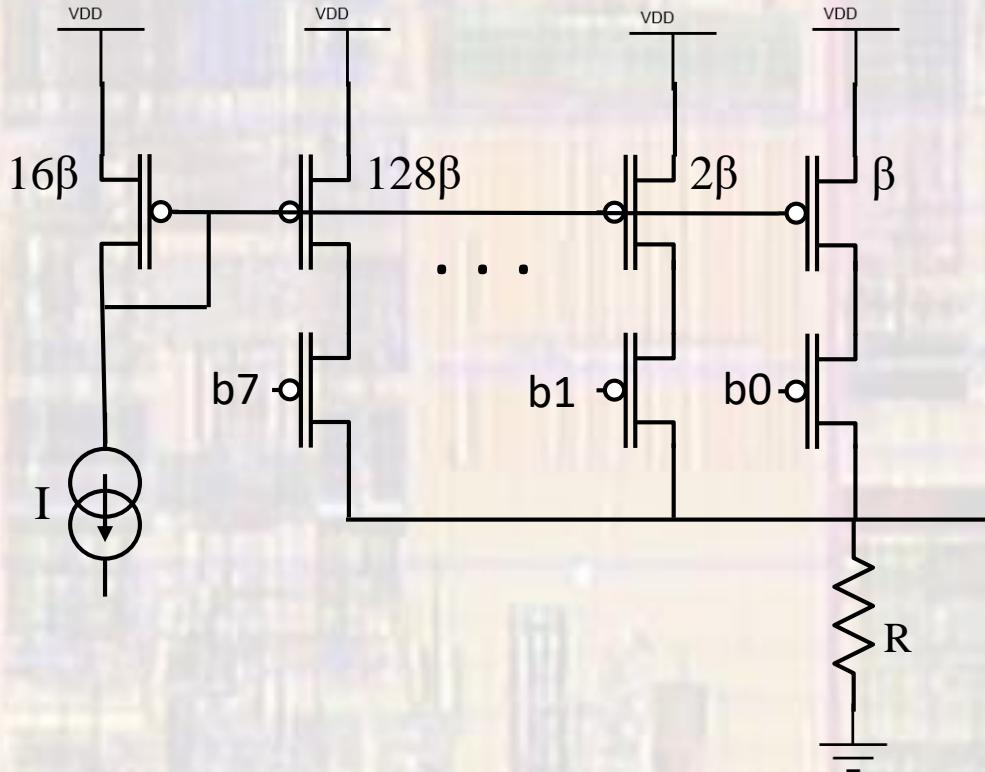
- Current DAC
 - Reduce the range relative to the current source



$$V_{out} = (b_0 \times I + b_1 \times 2I + b_2 \times 4I + b_3 \times 8I + b_4 \times 16I + b_5 \times 32I + b_6 \times 64I + b_7 \times 128I) \times R$$

D/A

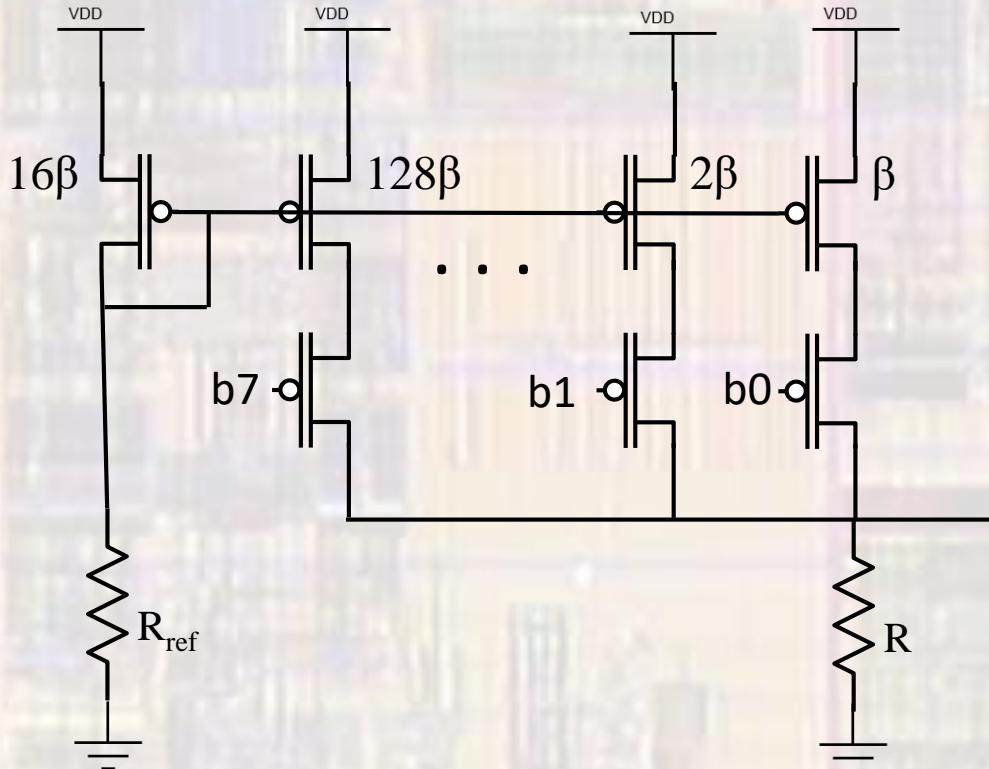- Current DAC
 - Reduce absolute resistor tolerance → ratio of R_s



$$V_{out} = (b_0 \times I + b_1 \times 2I + b_2 \times 4I + b_3 \times 8I + b_4 \times 16I + b_5 \times 32I + b_6 \times 64I + b_7 \times 128I) \times R$$

D/A

- Current DAC
 - Reduce absolute resistor tolerance → ratio of R_s

