

# Gain Stages

Last updated 4/7/19


# Gain Stages

- Threshold Voltage
  - Gate voltage  $V_{GS}$  that first allows conduction from source to drain
  - Function of Silicon processing



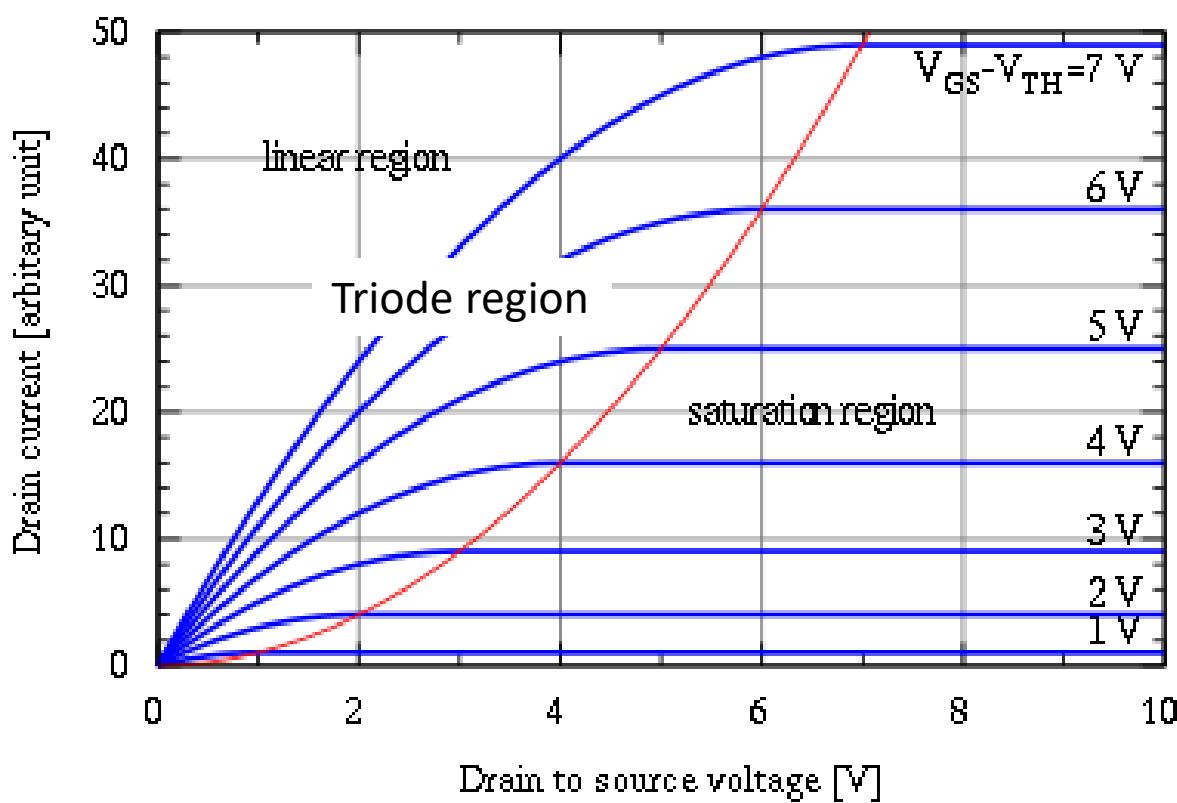
# Gain Stages

- Large Signal Analysis
  - $V_{GS} - V_{TH}$  : over voltage


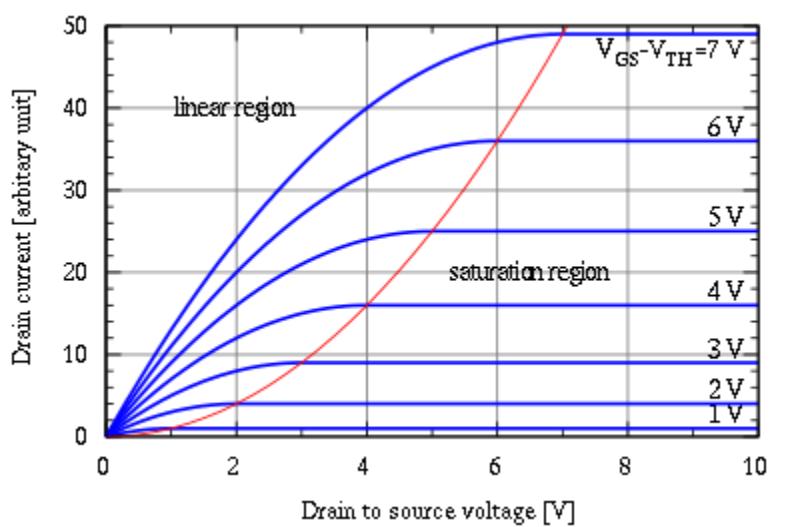
# Gain Stages


- Large Signal Analysis
  - Linear (Triode) Region
  - $V_{GS} > V_{TH}$
  - $V_{DS} < V_{GS} - V_{TH}$



$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$
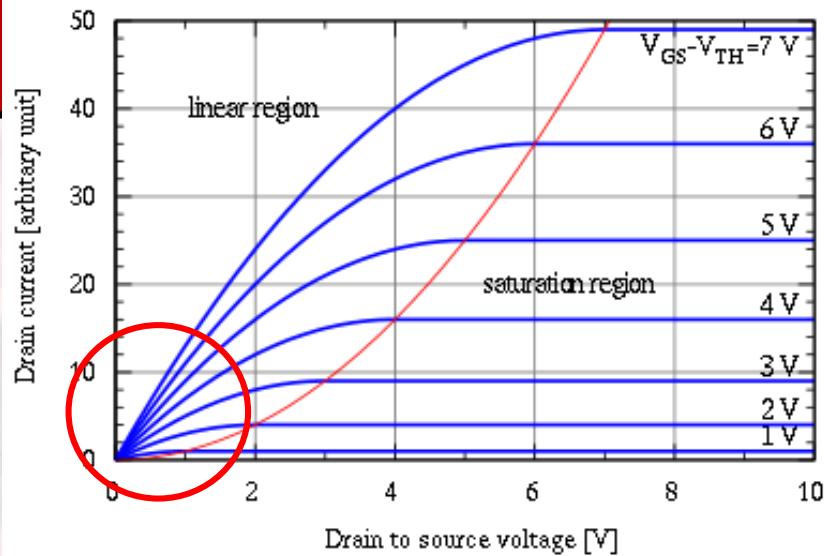
# Gain Stages

- Large Signal Analysis
  - Linear (Triode) Region
  - $V_{DS} \ll V_{GS} - V_{TH}$




$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{TH}) V_{DS} \right]$$

$$R_{EQ} = \frac{V_{DS}}{I_D} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$
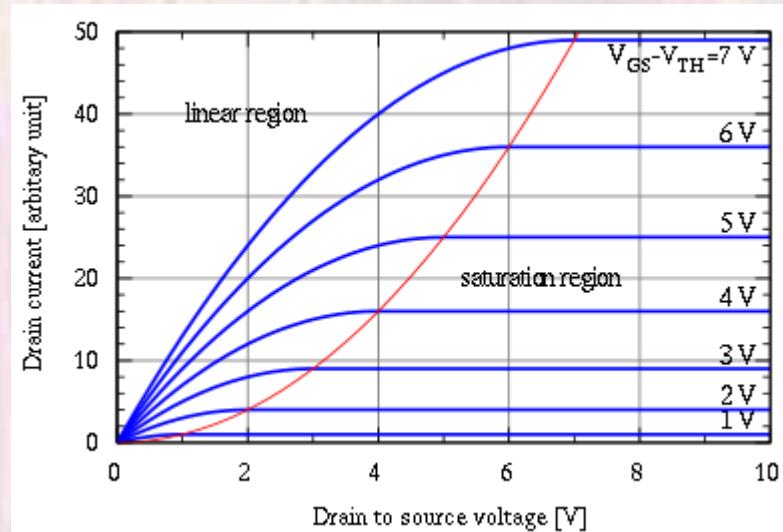
# Gain Stages

- Large Signal Analysis
  - Onset of Saturation
  - $V_{DS} = V_{GS} - V_{TH}$



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

# Gain Stages

- MOS Transconductance
  - Transconductance

$$\frac{\partial I}{\partial V}$$

- MOS Transconductance
  - In Saturation

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

units  
1/Ω

# Gain Stages

- MOS Transconductance

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

- with substitutions

$$50\text{uA/V}^2(5/0.1)(300\text{mV}) = 750 \times 10^{-6} / \Omega$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{GS} - V_{TH}}$$

$$(2 \times 112\text{uA})/300\text{mV} = 750 \times 10^{-6} / \Omega$$


# Gain Stages

- Non-Ideal Effects
  - Body Effect
    - Assuming the body/s/d junctions remain reverse biased the device will continue to operate – but with different threshold voltage characteristics
    - $V_{TH} = V_{TH0} + \gamma(\dots V_{BS} \dots)$


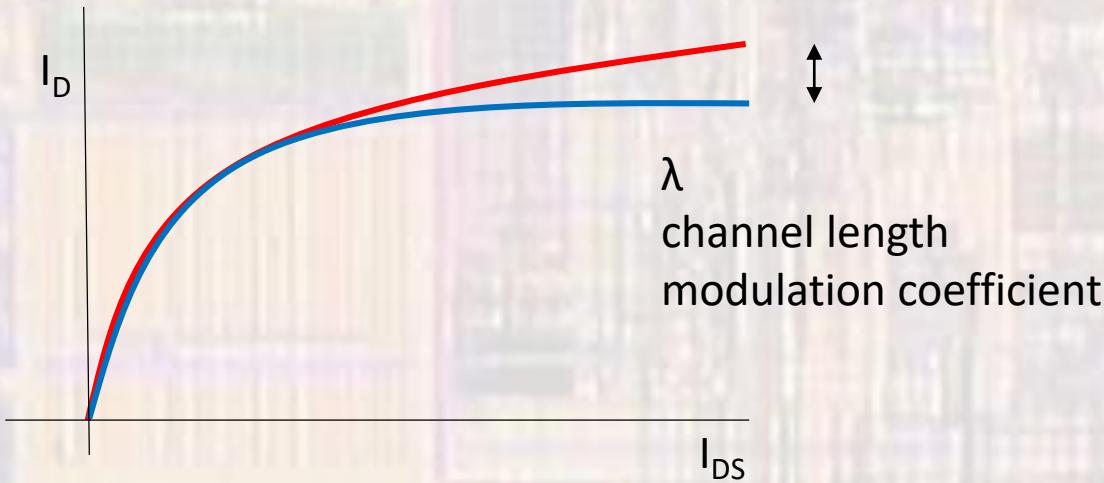
# Gain Stages

- Non-Ideal Effects
  - Channel Length Modulation



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

# Gain Stages

- Non-Ideal Effects
  - Subthreshold Conduction
    - Current conduction with  $V_{GS}$  below  $V_{TH}$
    - Called weak inversion

$$I_D = I_o \exp \frac{V_{GS}}{\xi V_T}$$

$$\xi > 1$$

# Gain Stages

- Small Signal Model

$$I_D = g_m V_{GS}$$

$$r_o = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{\frac{\partial I_D}{\partial V_{GS}}} = \frac{1}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \cdot \lambda} = \frac{1}{\lambda I_D}$$

$$1/(0.1 \times 112 \mu A) = 89 K\Omega$$


typically

$$\frac{1}{g_m} \ll r_o$$

$$1.3 K\Omega \ll 89 K\Omega$$


# Gain Stages

- Small Signal Model

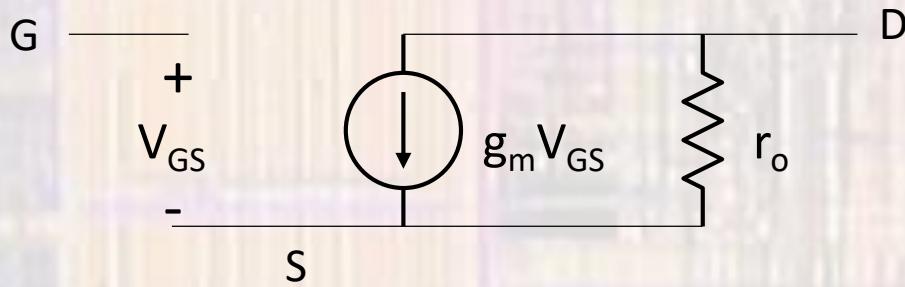


# Gain Stages

- Small Signal Model

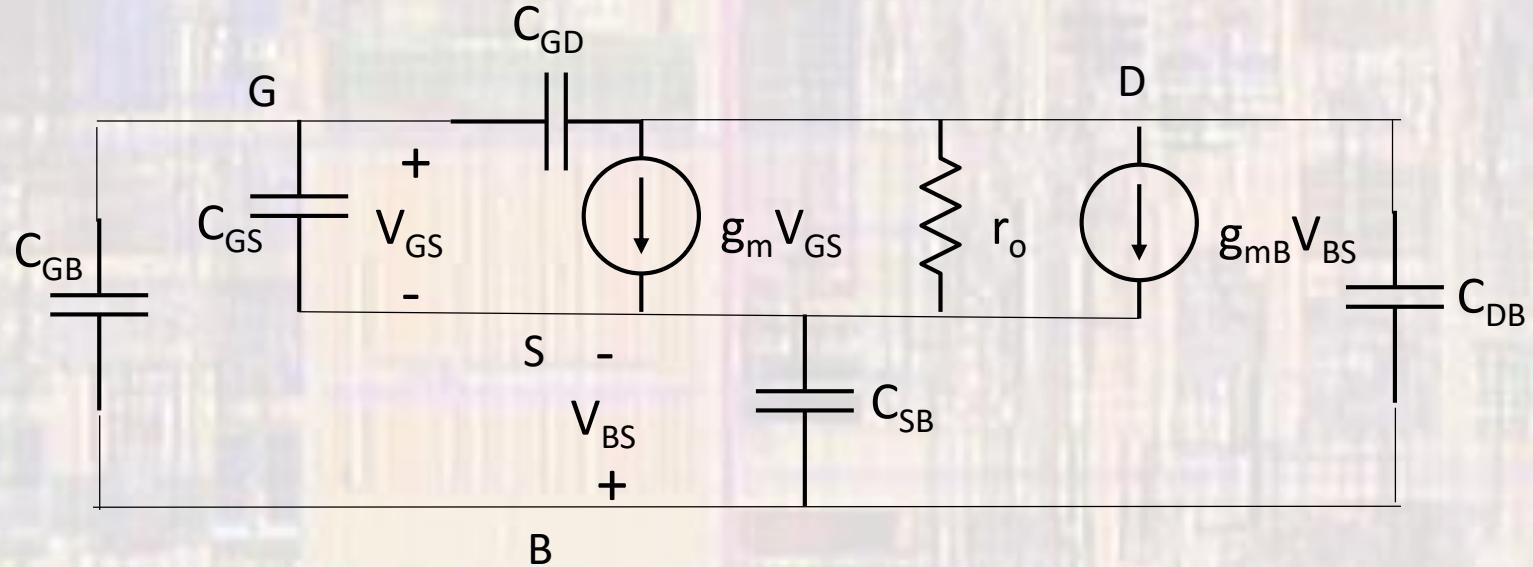

# Gain Stages

- Common Source – Resistive Load

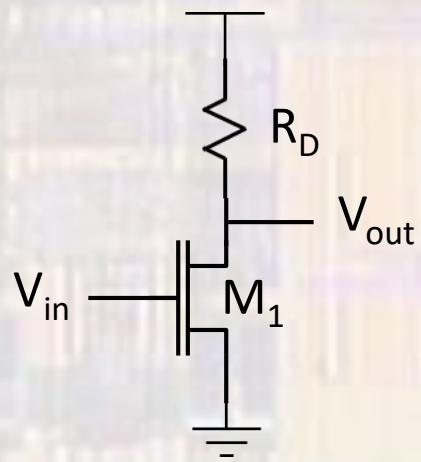

Linear Operation

$$M_1 \rightarrow R_{eq}$$

$$V_{out} = V_{DD} \frac{R_{eq}}{R_{eq} + R_D}$$

$$V_{out} = \frac{V_{DD}}{1 + R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})}$$


$$A_v = \frac{\partial V_{out}}{\partial V_{in}}$$

$$A_v = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})$$


$$A_v = -g_m R_D$$

# Gain Stages

- Common Source – Resistive Load

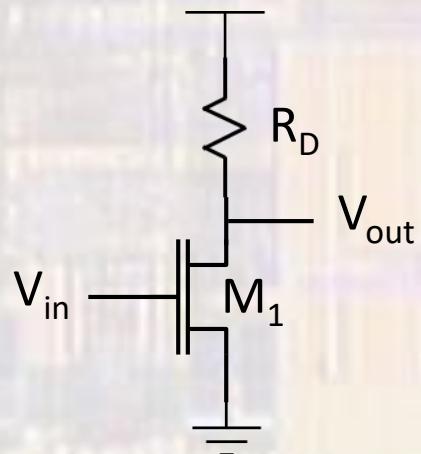

Saturation  
Small signal model

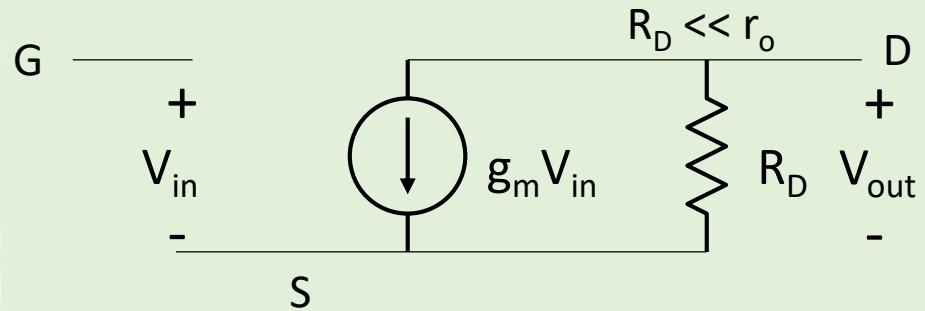


$$A_v = \frac{\partial V_{out}}{\partial V_{in}}$$

$$A_v = -g_m R_D$$


$$A_v = -(750 \times 10^{-6} / \Omega) \times 10 K\Omega = -7.5$$

# Gain Stages

- Common Source – Resistive Load

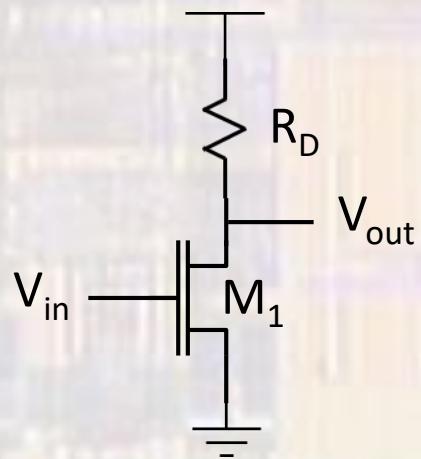

Saturation  
Small signal model

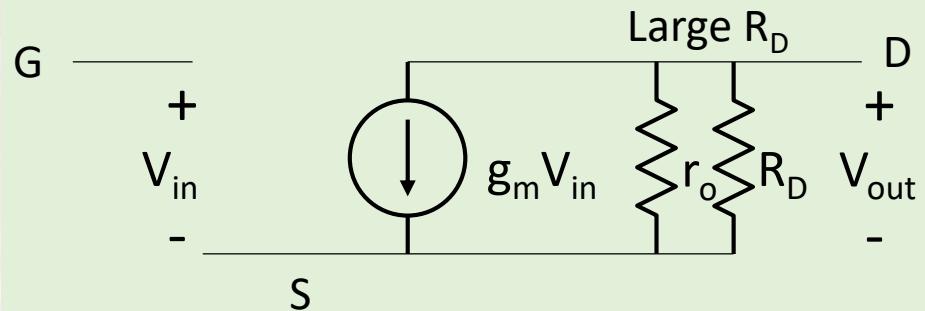


$$A_v = \frac{\partial V_{out}}{\partial V_{in}}$$

$$A_v = -g_m \frac{r_o R_D}{r_o + R_D}$$

$$A_v = -(750 \times 10^{-6} / \Omega) \times (10 \text{ k}\Omega || 90 \text{ k}\Omega) = -6.75$$
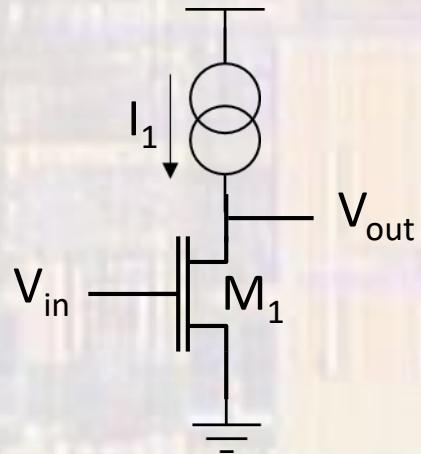
# Gain Stages

- Common Source – Current Source Load
  - Saturation



$$A_v = -g_m \frac{r_o R_D}{r_o + R_D}$$


$$R_D \rightarrow \infty$$

$$A_v = -g_m r_o$$

$$A_v = -(750 \times 10^{-6} / \Omega) \times 90 \text{ k}\Omega = -67.5$$

# Gain Stages

- Common Source – Diode Connected Load

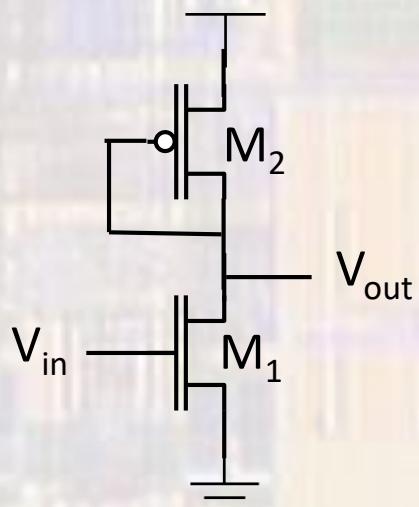


$$I_{D_{M1}} = \frac{1}{2} \mu_n C_{ox} \frac{W_n}{L_n} (V_{in} - V_{TH_n})^2 =$$
$$I_{D_{M2}} = -\frac{1}{2} \mu_p C_{ox} \frac{W_p}{L_p} (V_{out} - V_{DD} - V_{TH_p})^2$$

$$A_v = -\sqrt{\frac{\mu_n (W/L)_1}{\mu_p (W/L)_2}} = \frac{|V_{GS_2} - V_{TH_2}|}{V_{GS_1} - V_{TH_1}}$$

$$V_{dd} = 1.2V, v_{out} = V_{dd}/2, v_{in} = 0.5V$$
$$A_v = |-0.6 + 0.3| / (0.5 - 0.3) = -1.5$$

# Gain Stages

- Common Source – Diode Connected Load

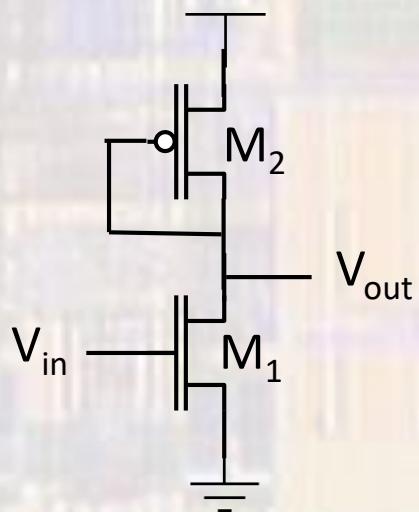

$$A_v = -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}} = \frac{|V_{GS_2} - V_{TH_2}|}{V_{GS_1} - V_{TH_1}}$$

for a gain of 5

$$\mu_n = 2 \mu_p$$



$$\rightarrow (W/L)_n = 12.5(W/L)_p$$

and

$$|V_{GS_2} - V_{TH_2}| = 5 \times (V_{GS_1} - V_{TH_1})$$

# Gain Stages

- Common Source – Current Source Load

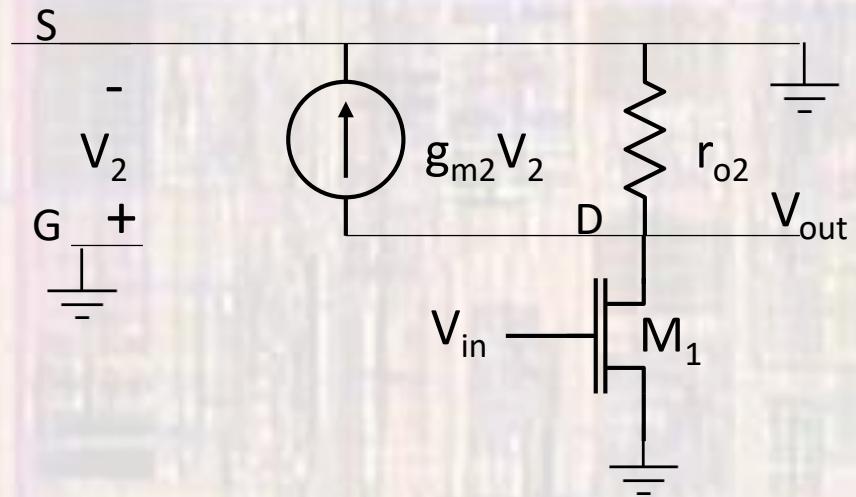
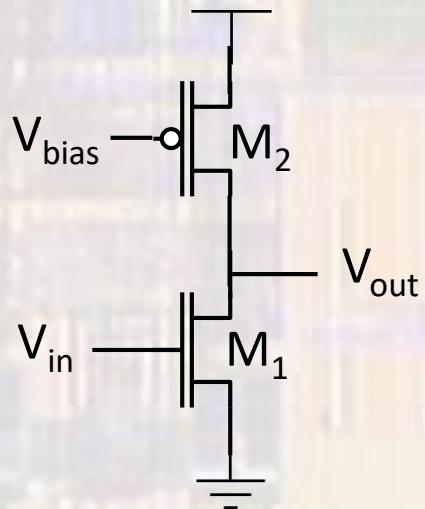


$$A_v = -g_{m1}(r_{o1} \parallel r_{o2})$$

$$Av = -(750 \times 10^{-6}/\Omega) \times (90\text{K}\Omega \parallel 90\text{K}\Omega) = -33.7$$

# Gain Stages

- Common Source – Active Load

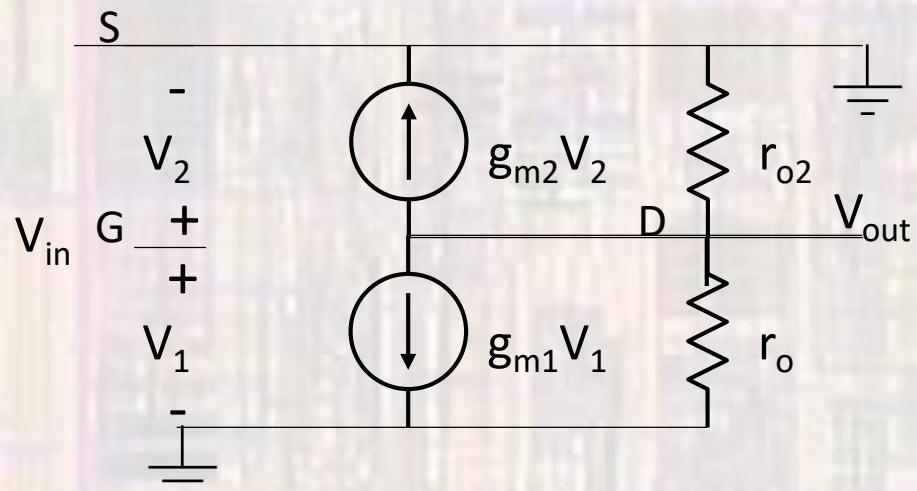
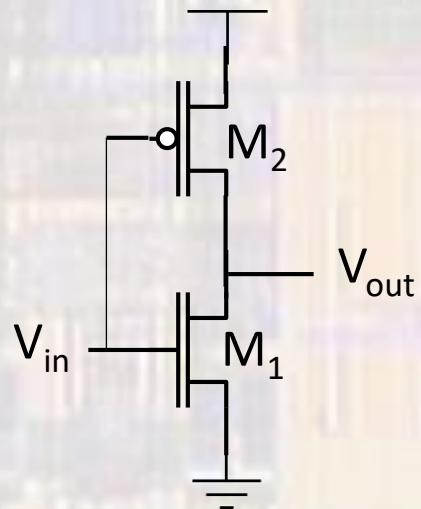


$$A_v = -(g_{m1} + g_{m2})(r_{o1} \parallel r_{o2})$$

$$Av = -(750 \times 10^{-6}/\Omega + 375 \times 10^{-6}/\Omega) \times (90K\Omega \parallel 90K\Omega) = -50.6$$

# Gain Stages

- Common Source – Source Degeneration

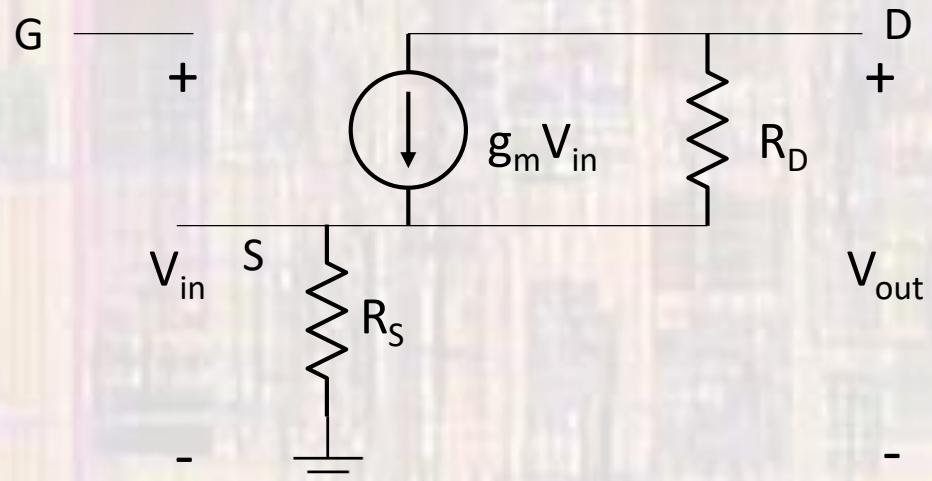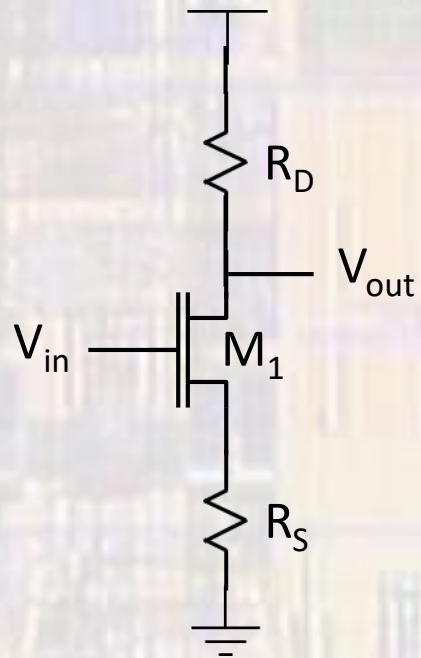


$$A_v = \frac{-g_m R_D}{1 + g_m R_S}$$

$$Av = -(750 \times 10^{-6} / \Omega) \times 10K\Omega / (1 + (750 \times 10^{-6} / \Omega) \times 500\Omega) = -5.4$$
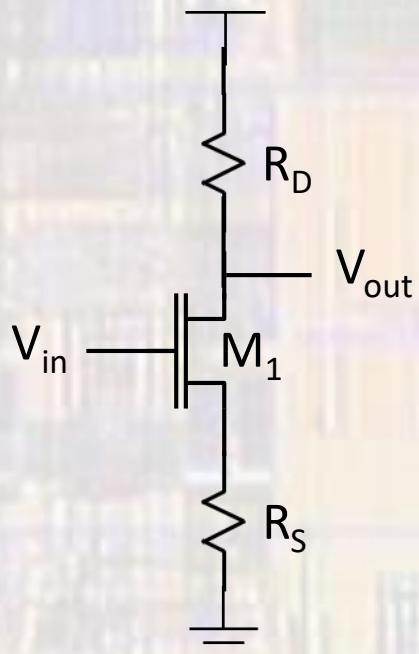
# Gain Stages

- Common Source – Source Degeneration
  - Increase in effective transistor output resistance
    - $R_S$  is seen through the transistor





$$r_{out} = [1 + g_m R_S] r_o$$

$$r_{out} = [1 + 750 \times 10^{-6}/\Omega \times 500\Omega] \times 90K\Omega = 124K\Omega$$

# Gain Stages

- Source Follower

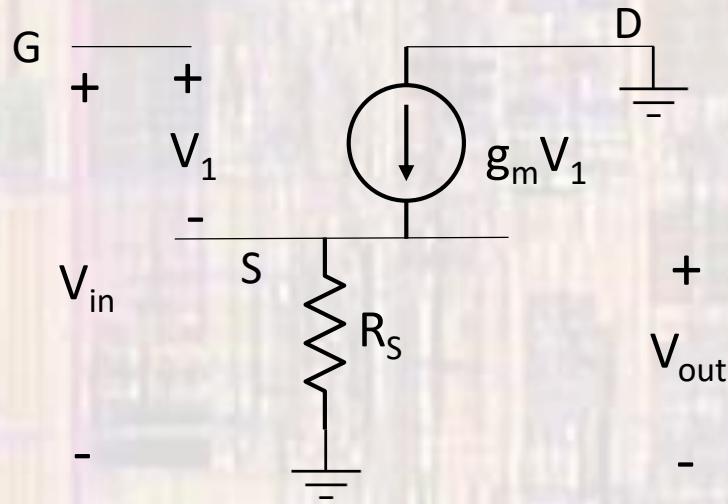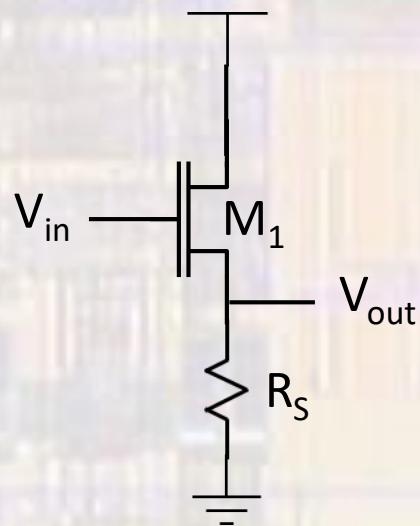


$$A_v = \frac{g_m R_S}{1 + g_m R_S}$$

$$Av = (750 \times 10^{-6} / \Omega) \times (10K\Omega) / (1 + (750 \times 10^{-6} / \Omega) \times (10K\Omega)) = 0.88$$

# Gain Stages



- Source Follower – active load

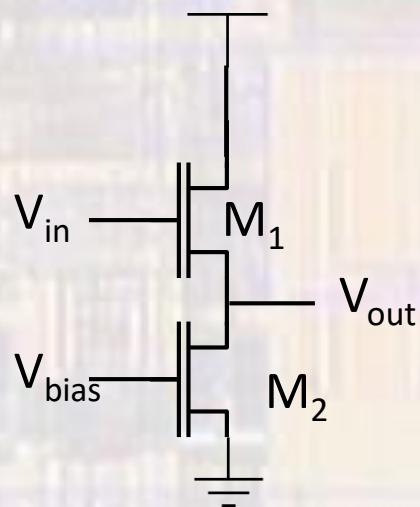

$$A_v = \frac{g_m R_{eq}}{1 + g_m R_{eq}}$$
$$R_{eq} = \frac{1}{g_{mB}} \parallel r_{o1} \parallel r_{o2}$$
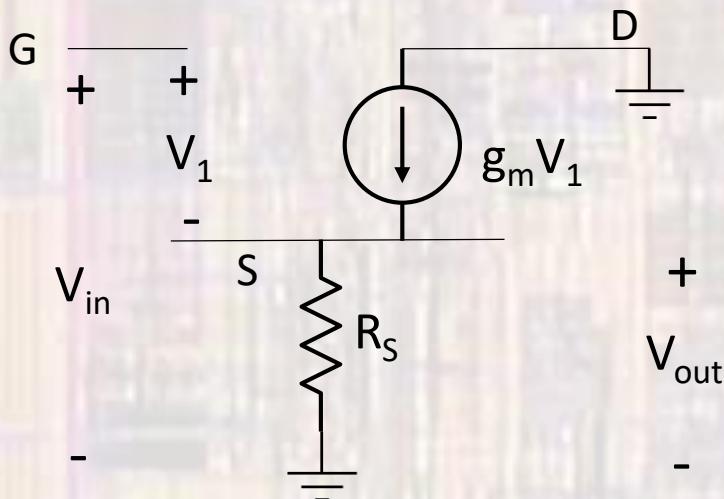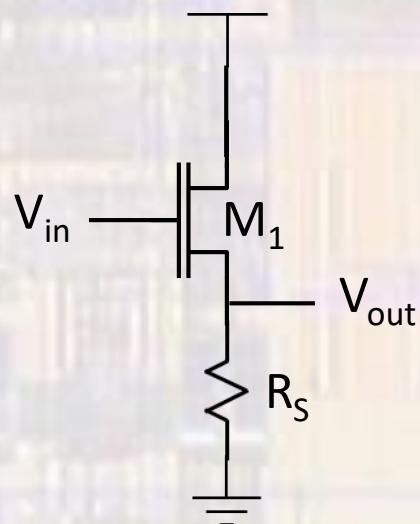
# Gain Stages

- Source Follower
  - Relatively low output impedance




$$r_o = 1/g_m$$

$$r_o = 1/(750 \times 10^{-6} / \Omega) = 1.33K \Omega$$

# Gain Stages

- Common Gate Stage

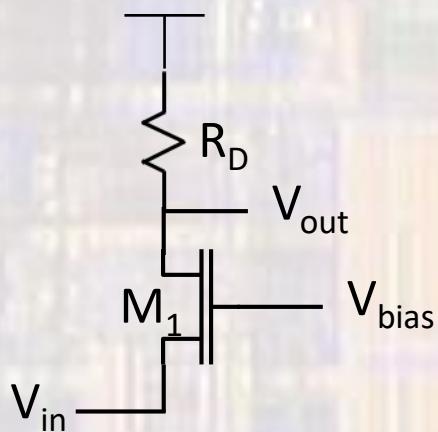

$$I_{D_{M1}} = \frac{1}{2} \mu_n C_{ox} \frac{W_n}{L_n} (V_{Bias} - V_{in} - V_{TH_n})^2$$

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W_n}{L_n} (V_{Bias} - V_{in} - V_{TH_n})^2 R_D$$


$$\frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W_n}{L_n} (V_{Bias} - V_{in} - V_{TH_n})^2 (-1 - \frac{\partial V_{TH}}{\partial V_{in}}) R_D$$

$$\frac{\partial V_{out}}{\partial V_{in}} = g_m (1 + \eta) R_D$$

positive

# Gain Stages

- Common Gate Stage

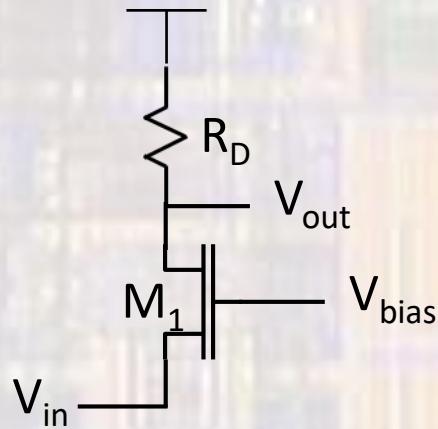


$$R_{in} = \frac{1}{\frac{1}{r_o} + g_m + g_{mb}}$$

$$R_{in} = 1/(750 \times 10^{-6}/\Omega + 400 \times 10^{-6}/\Omega + 1/90K\Omega) = 861\Omega$$

# Gain Stages

- Cascode Stage

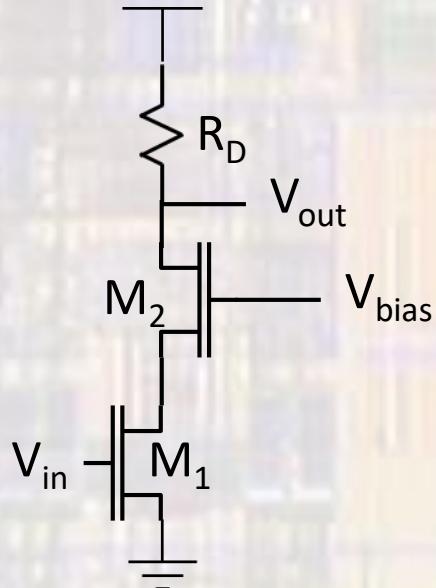

$$A_v = -g_m R_D$$



M<sub>2</sub> passes the current through

$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{o2}]r_{o1} + r_{o2}$$

looks like common source with r<sub>o2</sub> degeneration

# Gain Stages

- Cascode Stage

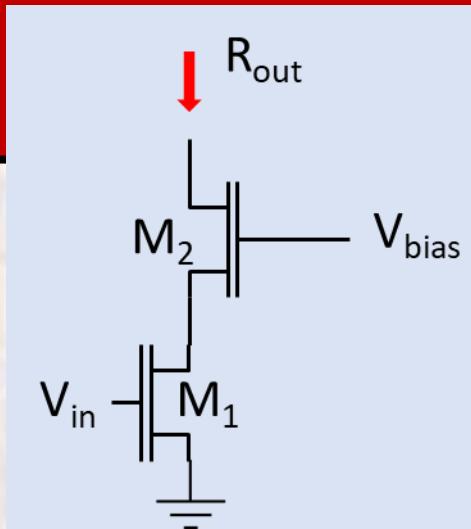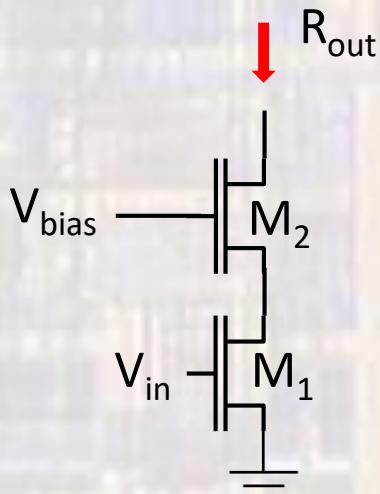


$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{o2}]r_{o1} + r_{o2}$$

looks like common source with r<sub>o2</sub> degeneration

$$R_{out} = [1 + (750 \times 10^{-6} / \Omega + 400 \times 10^{-6} / \Omega) 90 \text{ k}\Omega] 90 \text{ k}\Omega + 90 \text{ k}\Omega = 9.5 \text{ M}\Omega$$

# Gain Stages

- Cascode Load

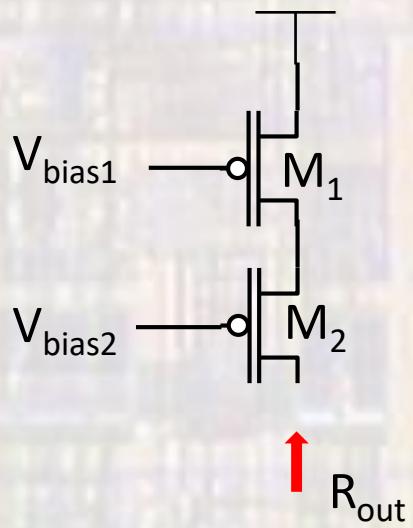


$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{o2}]r_{o1} + r_{o2}$$

looks like common source with r<sub>o2</sub> degeneration

# Gain Stages

- Cascode Amplifier



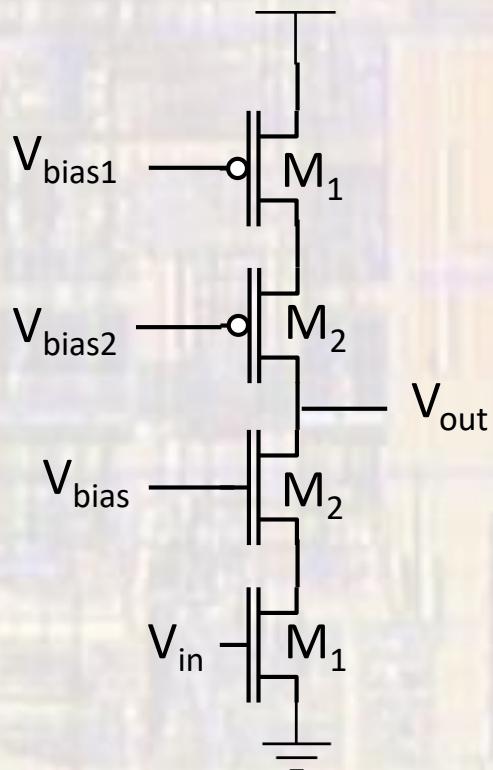


$$A_v = -g_{m1}[(g_{m2}r_{o2}r_{o1}) \parallel (g_{m3}r_{o3}r_{o4})]$$

$$A_v = -750 \times 10^{-6} / \Omega [(750 \times 10^{-6} / \Omega \times 90K\Omega \times 90K\Omega) \parallel (400 \times 10^{-6} / \Omega \times 90K\Omega \times 90K\Omega)] \\ = 1587$$



# Gain Stages

- Folded Cascode Amplifier

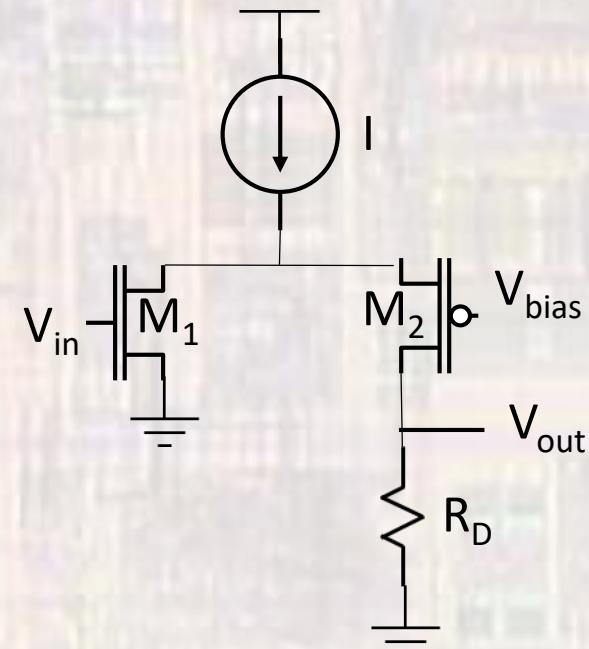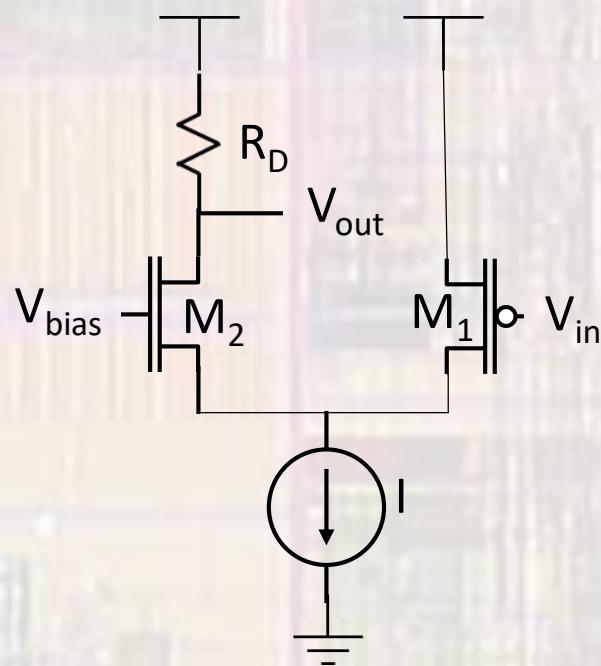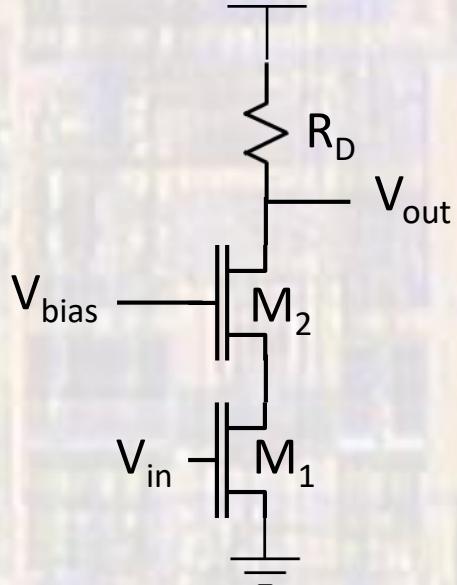

# Gain Stages


- Folded Cascode Amplifier

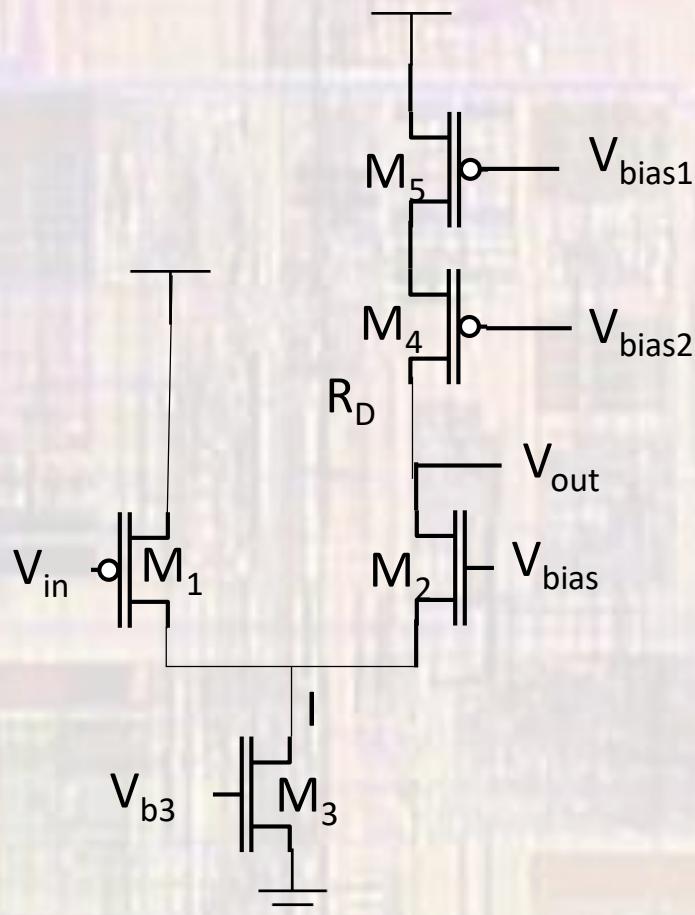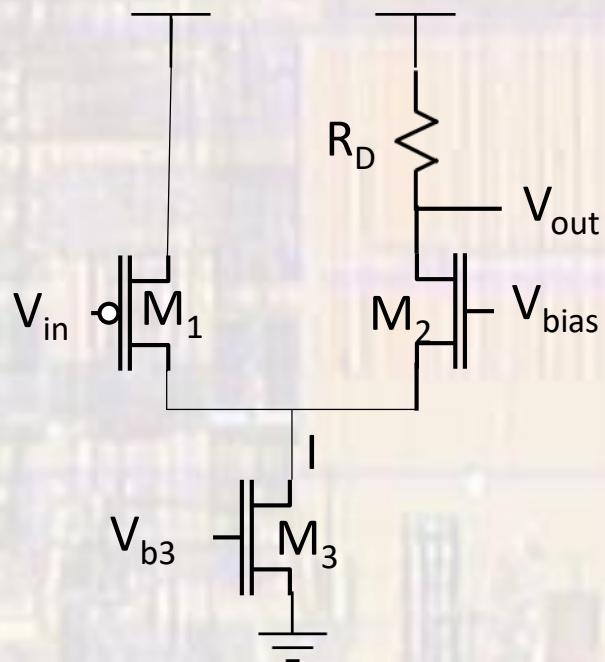


# Gain Stages

- Simulating  $g_m$


circuit for calculating  $g_m$

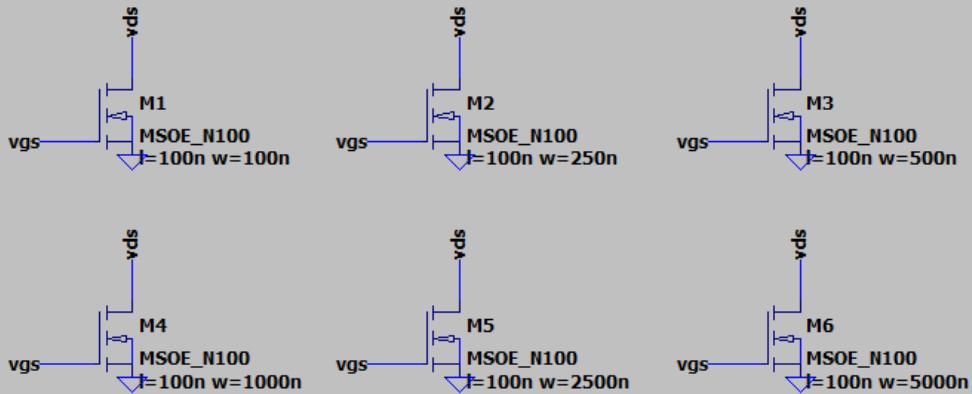

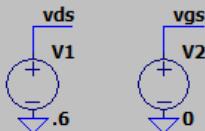plotting  $I_d$  vs  $V_{gs}$  for 7 values of  $V_{ds}$



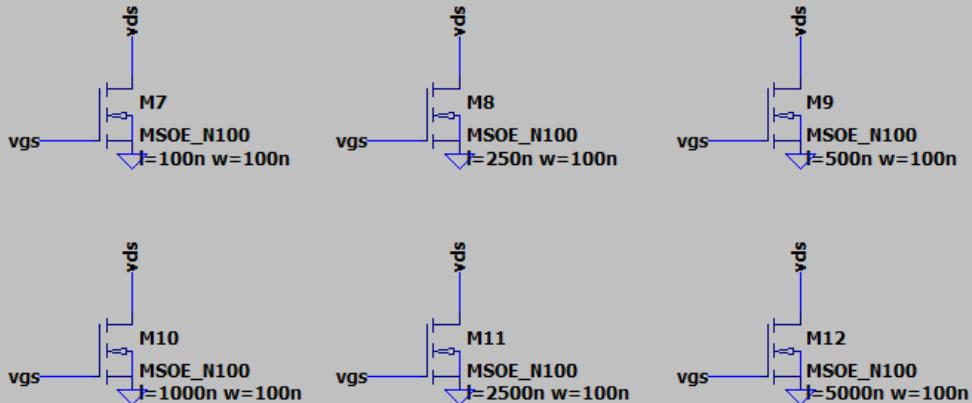
```
.inc D:\GDrive\MSOE\Common\Spice\Models\MSOE_100nm.txt  
.dc v2 0 1.2 .05 v1 .3 .9 .1
```




# Gain Stages

- Simulating  $g_m$

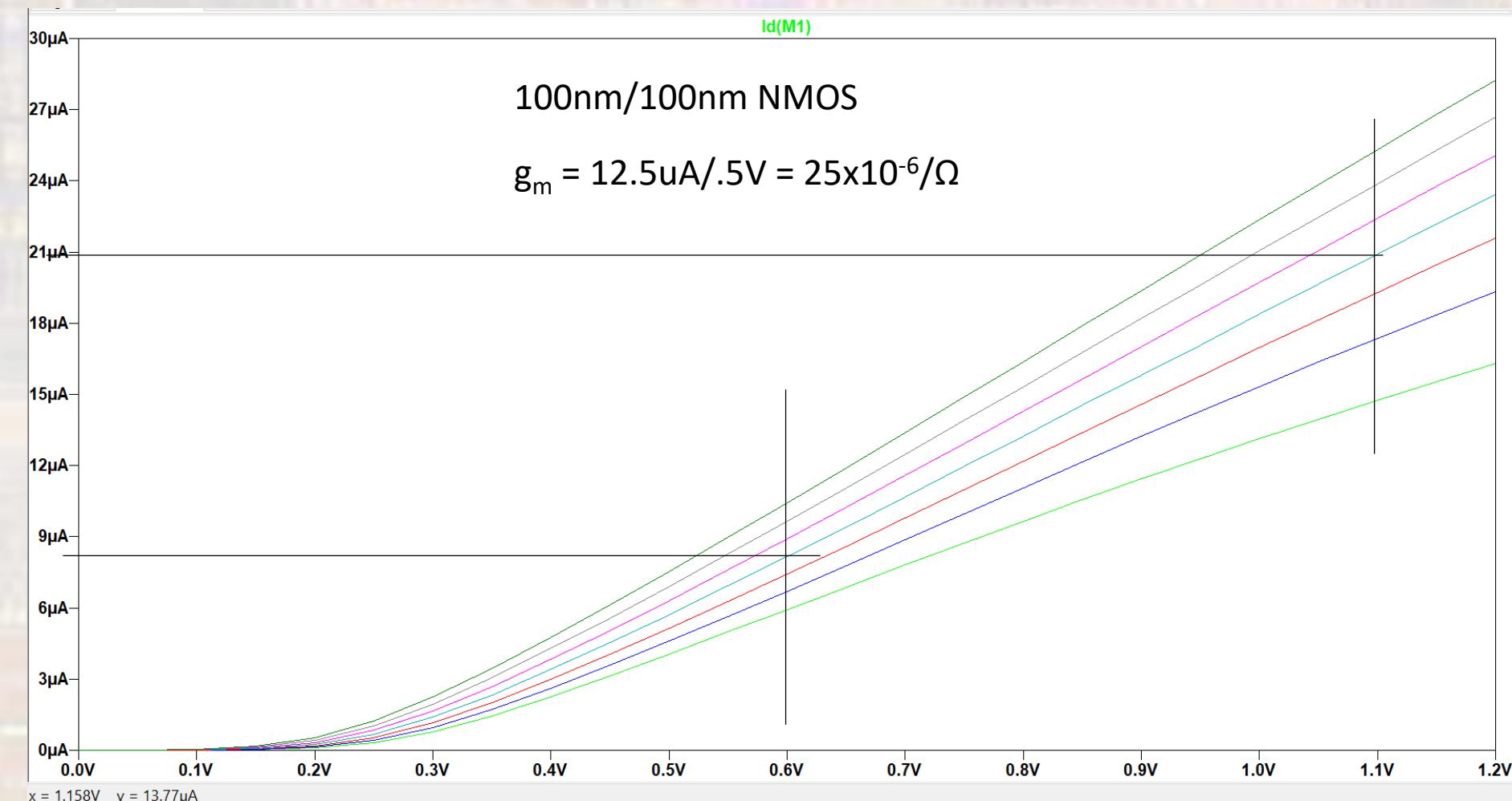

# Gain Stages

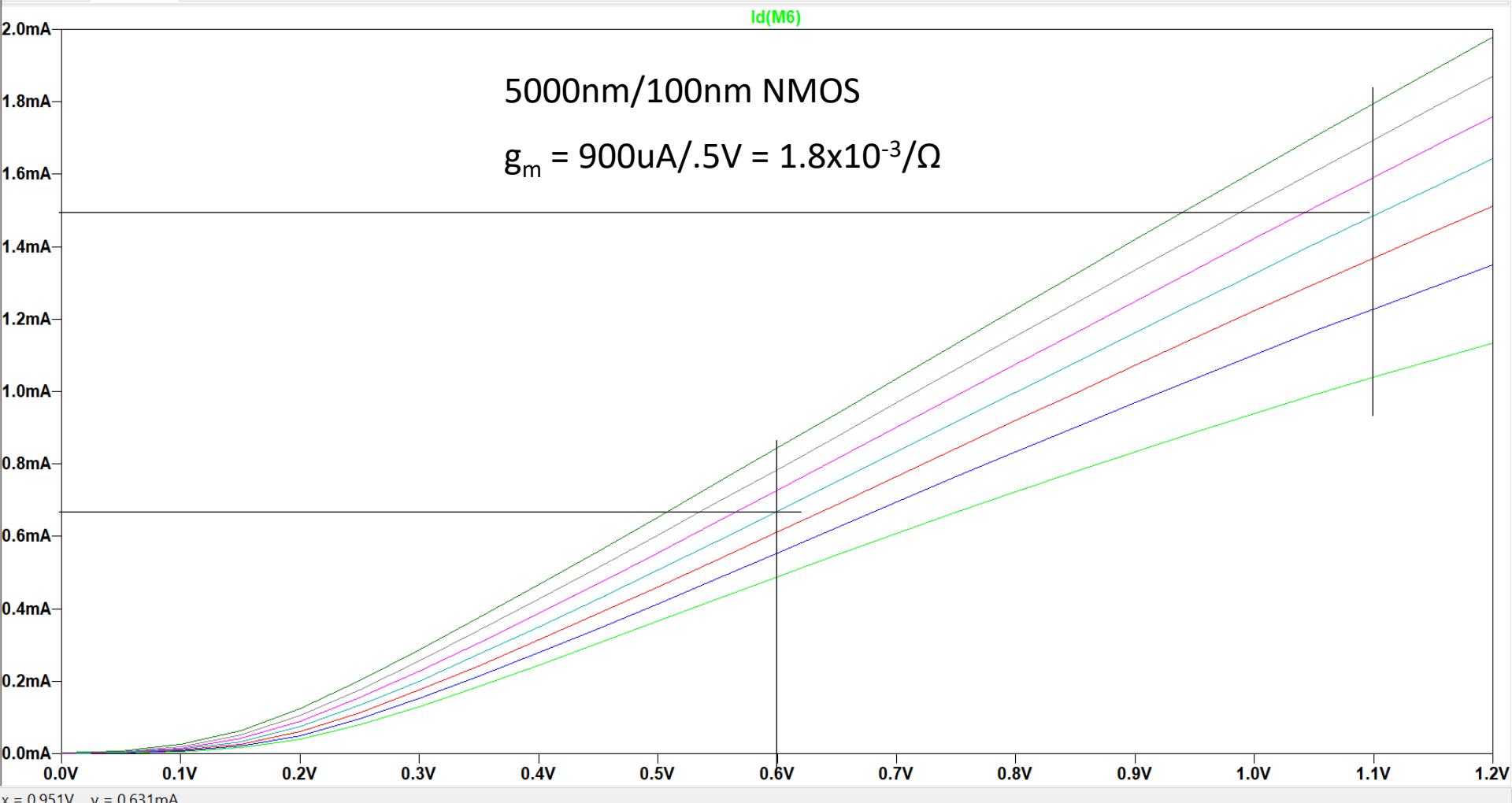

# Gain Stages

- Simulating  $g_m$

