

Adders / Subtractors

Last updated 8/23/24

Adders / Subtractors

- Addition and subtraction are common functions in digital designs
 - Long hand addition and subtraction is very tedious
 - VHDL synthesizers vendors have provided the ability to do addition and subtraction behaviorally
 - Makes no sense for SLV – just a collection of wires - not supported
 - Supported for signed and unsigned signals
 - signed + signed
 - unsigned + unsigned
 - signed – signed
 - unsigned – unsigned
 - No overflow/underflow detection
 - 4 bit unsigned : $12 + 12 \rightarrow 8$

Adders / Subtractors

- 4 bit unsigned adder


Explicit Type Conversions

```
--  
-- adder_unsigned_4.vhd1  
-- created 8/22/24  
-- tj  
-----  
-- Adder example for the notes  
-----  
-- inputs: 2 4 bit inputs  
-- outputs: 4 bit output, carry out  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity adder_unsigned_4 is  
  port (  
    i_a : in std_logic_vector(3 downto 0);  
    i_b : in std_logic_vector(3 downto 0);  
  
    o_sum : out std_logic_vector(3 downto 0)  
  );  
end entity;  
  
architecture behavioral of adder_unsigned_4 is  
  -- type conversions  
  signal a_sig : unsigned(3 downto 0);  
  signal b_sig : unsigned(3 downto 0);  
  signal sum_sig : unsigned(3 downto 0);  
  
begin  
  -- input conversion  
  a_sig <= unsigned(i_a);  
  b_sig <= unsigned(i_b);  
  
  add : process(a_sig, b_sig)  
  begin  
    sum_sig <= a_sig + b_sig;  
  end process;  
  
  -- output conversion  
  o_sum <= std_logic_vector(sum_sig);  
  
end architecture;
```

In-line Type Conversions

```
--  
-- adder_unsigned_4.vhd1  
-- created 8/22/24  
-- tj  
-----  
-- Adder example for the notes  
-----  
-- inputs: 2 4 bit inputs  
-- outputs: 4 bit output, carry out  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity adder_unsigned_4 is  
  port (  
    i_a : in std_logic_vector(3 downto 0);  
    i_b : in std_logic_vector(3 downto 0);  
  
    o_sum : out std_logic_vector(3 downto 0)  
  );  
end entity;  
  
architecture behavioral of adder_unsigned_4 is  
begin  
  o_sum <= std_logic_vector(unsigned(i_a) + unsigned(i_b));  
end architecture;
```


Identical Results

 

Adders / Subtractors

- 4 bit unsigned adder w/ carry out


```
--  
-- adder_unsigned_co_4.vhd1  
-- created 8/22/24  
-- tj  
--  
-----  
-- Adder example for the notes  
--  
-----  
-- inputs: 2 4 bit inputs  
-- outputs: 4 bit output, carry out  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity adder_unsigned_co_4 is  
  port (  
    i_a : in std_logic_vector(3 downto 0);  
    i_b : in std_logic_vector(3 downto 0);  
  
    o_sum : out std_logic_vector(3 downto 0);  
    o_carry_out : out std_logic  
  );  
end entity;  
  
architecture behavioral of adder_unsigned_co_4 is  
  -- type conversions  
  signal a_sig : unsigned(4 downto 0);  
  signal b_sig : unsigned(4 downto 0);  
  signal carry_sig : unsigned(4 downto 0);  
  
  -- temporary signal to overflow value  
  signal tmp_sig : unsigned(4 downto 0);  
  
begin  
  -- input conversion  
  a_sig <= unsigned('0' & i_a);  
  b_sig <= unsigned('0' & i_b);  
  
  add : process(a_sig, b_sig)  
  begin  
    tmp_sig <= a_sig + b_sig;  
  end process;  
  
  -- output conversion  
  o_sum <= std_logic_vector(tmp_sig(3 downto 0));  
  o_carry_out <= tmp_sig(4);  
  
end architecture;
```

 

Adders / Subtractors

- N bit unsigned adder

```
--  
-- adder_unsigned_n.vhdl  
-- created 8/22/24  
-- tj  
--  
-----  
-- Adder example for the notes  
--  
-----  
-- inputs: 2 N bit inputs  
-- outputs: N bit output  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity adder_unsigned_n is  
  generic(  
    N : natural := 8  
  );  
  port (  
    i_a : in std_logic_vector((N - 1) downto 0);  
    i_b : in std_logic_vector((N - 1) downto 0);  
  
    o_sum : out std_logic_vector((N - 1) downto 0)  
  );  
end entity;  
  
architecture behavioral of adder_unsigned_n is  
begin  
  o_sum <= std_logic_vector(unsigned(i_a) + unsigned(i_b));  
end architecture;
```

 

Adders / Subtractors

- N bit unsigned subtractor

```

--- subtractor_unsigned_n.vhd1
--- created 8/22/24
--- tj
-----
--- subtractor example for the notes
-----
--- inputs: 2 N bit inputs
--- outputs: N bit output
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity subtractor_unsigned_n is
    generic(
        N : natural := 8
    );
    port (
        i_minuend : in std_logic_vector((N - 1) downto 0);
        i_subtrahend : in std_logic_vector((N - 1) downto 0);
        o_diff : out std_logic_vector((N - 1) downto 0)
    );
end entity;

architecture behavioral of subtractor_unsigned_n is
begin
    o_diff <= std_logic_vector(unsigned(i_minuend) - unsigned(i_subtrahend));
end architecture;
    
```

