

Clock Dividers

Last updated 2/8/24

Clock Dividers

- Clock division
 - Normally a clock divider should **never** be used for internal circuits
 - Effectively a gated clock
 - Leads to timing issues
 - Use a PLL instead (we will cover this later)
 - A clock divider can be used for an external clock
 - Only if the external/internal relative clock edge is not critical
 - In order to see operation of designs on the DE10 we need to slow down the system clock (50MHz)
 - Run the entire system off of the slow clock
 - Removes timing issues
 - Typically dividing down to 1-30Hz
 - Approximately as fast as the human eye can see

Clock Dividers


- Clock Division Concept

- Reference Clock (Fclk)



- Divided Clock (Fclk/n)


- $n = 6$

 

- Need a way to cause the divided clock to go high and low

Clock Dividers

- Clock Division Concept

 

- Each $\frac{1}{2}$ clock period requires $n/2$ reference clock cycles
 - Toggle the divided clock after counting to $n/2$
- Odd divisions not allowed
 - Much more complex
 - Asymmetrical – no longer a square wave

Clock Dividers

- Clock Division Concept
 - 50MHz reference clock
 - 1Hz clock \rightarrow divide by 50,000,000 \rightarrow count 25,000,000 clocks
 - Toggle output
 - 10Hz clock \rightarrow divide by 5,000,000 \rightarrow count 2,500,000 clocks
 - Toggle output
 - Note: there may be overhead associated with the counter that modifies the count value

Clock Dividers

- Clock Divider – First try
 - 1Hz example

Counter sizing:

Count 25,000,000 clocks \rightarrow requires $\log_2 25,000,000 = 25$ bits

```
-----  
-- clock_1hz_first_try.vhdl  
-- created 7/15/23  
-- tj  
-- rev 0  
-----  
-- 1Hz clock divider  
-- Brute force 1st try  
-- assume a 50MHz external clock  
-----  
-- Inputs: rstb, clk_50MHz  
-- Outputs: clk_1Hz  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity clock_1hz_first_try is  
  port (  
    i_clk_50MHz : in std_logic;  
    I_rstb      : in std_logic;  
    o_clk_1Hz  : out std_logic  
  );  
end entity;
```

```
architecture behavioral of clock_1hz_first_try is  
  -- internal signals  
  --  
  signal cnt:      unsigned(24 downto 0);  
  signal clk_sig:  std_logic;  
begin  
  process(i_clk_50MHz, i_rstb)  
    begin  
      -- reset  
      --  
      if (i_rstb = '0') then  
        cnt <= (others => '0');  
        clk_sig <= '0';  
      elsif (rising_edge(i_clk_50MHz) ) then  
        cnt <= cnt + 1;  
        -- check if half way  
        --  
        if (cnt = 24999999) then  
          cnt <= (others => '0');  
          clk_sig <= not clk_sig;  
        end if;  
      end if;  
    end process;  
    --  
    -- output logic  
    --  
    o_clk_1Hz <= clk_sig;  
  end behavioral;
```

Remember 0 counts
as one of the count
values

Clock Dividers

- Clock Divider – Second try
 - 1Hz example

Clean up the code to make it easier to modify for different input/output frequencies

```
architecture behavioral of clock_1hz_second_try is
  -- constants and parameters
  constant INPUT_FREQUENCY: natural := 50_000_000;
  constant OUTPUT_FREQUENCY: natural := 1;
  constant CLKS_PER_HALF_PERIOD: unsigned(24 downto 0) := to_unsigned(((INPUT_FREQUENCY / 2) / OUTPUT_FREQUENCY), 25);
  -- internal signals
  signal cnt: unsigned(24 downto 0);
  signal clk_sig: std_logic;
begin
  process(i_clk_50MHz, i_rstb)
  begin
    -- reset
    if (i_rstb = '0') then
      cnt <= (others => '0');
      clk_sig <= '0';
    elsif (rising_edge(i_clk_50MHz) ) then
      cnt <= cnt + 1;
      -- check if half way
      if (cnt = (CLKS_PER_HALF_PERIOD - 1)) then
        cnt <= (others => '0');
        clk_sig <= not clk_sig;
      end if;
    end if;
  end process;

  -- output logic
  o_clk_1Hz <= clk_sig;
end behavioral;
```

Easy to find constants

Included output frequency in the calculation

Use _ instead of , for large numbers

Use the target value and account for 0 in counter

Using the constant

```
-----
-- clock_1hz_second_try.vhd1
-- created 7/15/23
-- tj
-- rev 0
-----
-- 1Hz clock divider
-- Better 2nd try
-- assume a 50MHz external clock
-----
-- Inputs: rstb, clk_50MHz
-- Outputs: clk_1Hz
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity clock_1hz_second_try is
  port (
    i_clk_50MHz : in std_logic;
    i_rstb : in std_logic;
    o_clk_1Hz : out std_logic
  );
end entity;
```

Clock Dividers

- Clock Divider – Third try
 - 1Hz example

Use 'best practices' and compare to <0 or ≥ 0

```
architecture behavioral of clock_1hz_third_try is
-- constants and parameters
constant INPUT_FREQUENCY: natural := 50_000_000;
constant OUTPUT_FREQUENCY: natural := 1;
constant CLKS_PER_HALF_PERIOD: signed(25 downto 0) := to_signed(((INPUT_FREQUENCY / 2) / OUTPUT_FREQUENCY), 26);
-- internal signals
--
signal cnt: signed(25 downto 0);
signal clk_sig: std_logic;
begin
process(i_clk_50MHz, i_rstb)
begin
-- reset
--
if (i_rstb = '0') then
cnt <= (CLKS_PER_HALF_PERIOD - 1);
clk_sig <= '0';
elsif (rising_edge(i_clk_50MHz) ) then
cnt <= cnt - 1;
-- check if half way
if (cnt < 0) then
cnt <= ((CLKS_PER_HALF_PERIOD - 1) - 1);
clk_sig <= not clk_sig;
end if;
end if;
end process;
-- output logic
--
o_clk_1Hz <= clk_sig;
end behavioral;
```

1 more bit required due to signed range < unsigned range

Comparing to <0

Why???

```
-----
-- clock_1hz_third_try.vhdl
-- created 7/15/23
-- tj
-- rev 0
-----
-- 1Hz clock divider
-- switching to signed to save gates
-- assume a 50MHz external clock
-----
-- Inputs: rstb, clk_50MHz
-- Outputs: clk_1Hz
-----
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity clock_1hz_third_try is
port (
i_clk_50MHz : in std_logic;
i_rstb : in std_logic;

o_clk_1Hz : out std_logic
);
end entity;
```


Clock Dividers

- Clock Divider – Comparison
 - 1Hz example

'best practices' saved 19 logic elements at the cost of 1 FF

Try 2

Flow Summary	
Search <<Filter>>	
Flow Status	Successful - Sat Jul 15 15:23:06 2023
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	Class_examples
Top-level Entity Name	clock_1hz_second_try
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	47 / 49,760 (< 1 %)
Total registers	26
Total pins	3 / 360 (< 1 %)
Total virtual pins	0
Total memory bits	0 / 1,677,312 (0 %)
Embedded Multiplier 9-bit elements	0 / 288 (0 %)
Total PLLs	0 / 4 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 2 (0 %)


Try 3

Flow Summary	
Search <<Filter>>	
Flow Status	Successful - Sat Jul 15 16:03:14 2023
Quartus Prime Version	18.1.0 Build 625 09/12/2018 SJ Lite Edition
Revision Name	Class_examples
Top-level Entity Name	clock_1hz_third_try
Family	MAX 10
Device	10M50DAF484C7G
Timing Models	Final
Total logic elements	28 / 49,760 (< 1 %)
Total registers	27
Total pins	3 / 360 (< 1 %)
Total virtual pins	0
Total memory bits	0 / 1,677,312 (0 %)
Embedded Multiplier 9-bit elements	0 / 288 (0 %)
Total PLLs	0 / 4 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 2 (0 %)

Clock Dividers

- Clock Divider – Third try
 - 1Hz example - Simulation

 Modified to do a divide by 10 (5MHz) to reduce simulation time



Clock Dividers

- Clock Divider – Fourth try
 - Further optimization – HW/Lab assignment